

Student's Name: \_\_\_\_\_

Student's Name: \_\_\_\_\_

Lab day &amp; time: \_\_\_\_\_

Date: \_\_\_\_\_

## Ohm's Law and Resistance (E3) - Data Sheets

*Write all results on the data sheets in ink. Complete all steps, prepare required graphs, and answer all questions on the data sheets before you leave.*

### Activity 1: Ohm's Law

(1 p.)

Before doing any calculations read the file "E3 – Theory and Procedure".

What is the function describing the dependence between voltage and current on the graph?

Is this the dependence you expect from Ohm's Law? \_\_\_\_\_

What are the values for the slope  $m$  and the y-intercept  $b$  in the equation of the line (i.e.,

$y = m \cdot x + b$ ) for the best-fit data?

$m =$  \_\_\_\_\_  $b =$  \_\_\_\_\_

The resistance  $R$  of the rheostat = \_\_\_\_\_ ( $\Omega$ )

**Print** this graph for the lab report.

Do not use the nominal resistance of the rheostat ( $45 \Omega$ ) - it is not accurate!

Now you need to compute the resistivity  $\rho$  for the rheostat coil. Use the following data for this calculation.

radius of the coil  $r = 0.0215$  ( m )

number of turns of the wire in the coil = 220

length of wire  $l =$  \_\_\_\_\_ ( )

diameter of the wire  $d = 0.86$  mm = \_\_\_\_\_ ( m )

cross-sectional area of the wire  $A =$  \_\_\_\_\_ ( )

Use the length and the cross-section of the wire to calculate the resistivity  $\rho$  of the wire.

$$\rho = \text{_____} ( \quad )$$

What material is your rheostat made of? (*Hint*: look at the table in the E3 - Theory and Procedure file)

---

**Lab Challenge 3.1. (Estimate the number of electrons)** (0.5 p.)

***Do not ask your TA for help with the lab challenge activity! You may consult with other students or use other available sources of information like textbook, online resources, etc.***

A relatively small current  $I = 1.00 \text{ mA}$  is running through a cross section of a copper wire. Calculate the number of electrons running through the wire cross section per second.

$$\text{Number of electrons per second} = \text{_____}$$

*Activity 2: Resistors in Series* (0.5 p.)

Before doing any calculations read the file “E3 – Theory and Procedure”. Pay special attention to the electrical circuit for this Activity.

What is the shape of your voltage vs. current graph? \_\_\_\_\_

What is the slope of this graph?  $m = \text{_____}$

From this information, what is the total resistance of your circuit?

$$R_{T1} = \text{_____} ( \quad )$$

Now calculate the resistance  $R_A$  of the unknown resistor “A”:

$$R_A = \text{_____} ( \quad )$$

*Activity 3: Resistors in Parallel* (0.5 p.)

What is the slope of the voltage vs. current graph?  $m = \text{_____}$

From this slope, determine the total resistance of your circuit.

$$R_{T2} = \text{_____} ( \quad )$$

Now calculate the resistance of the unknown resistor “B”.

$$R_B = \text{_____} ( \quad )$$

#### Activity 4: Resistance vs. Temperature for Metals

(1.5 p.)

What is the initial temperature (after 3-5 min. waiting to equalize the temperature of the coil and water)?

$$T_0 = \text{_____} ( \text{ }^\circ\text{C} ) \text{ (it should be close to the room temperature)}$$

Press the “Record” button. The computer will now plot the resistance and temperature points on the graph in front of you. This part of the experiment takes approximately 20-25 minutes to complete.

What is the shape of the graph you obtained?

What is the slope of this graph?  $m = \text{_____}$

What is the y-intercept of this graph?  $b = \text{_____}$

From Print/Printing preferences, select landscape orientation and **print a copy of your graph.**

Using the slope ( $m$ ) and the y-intercept ( $b$ ), determine the temperature coefficient of resistance  $\alpha$ . Note that the y-intercept  $b$  is not the same as  $R_0$ . The y-intercept on your graph is equal to the resistance at temperature equal to  $0^\circ\text{C}$ , whereas  $R_0$  is the resistance at the temperature  $T_0$  which is close to the room temperature  $\cong 20^\circ\text{C}$ . Therefore,

$$R(T) = R_0 + R_0\alpha(T - T_0) = R_0 + R_0\alpha T - R_0\alpha T_0 = R_0\alpha T + R_0(1 - \alpha T_0) = mT + b$$

$$m = R_0\alpha, \quad b = R_0(1 - \alpha T_0) \quad \Rightarrow \quad \frac{m}{b} = \frac{R_0\alpha}{R_0(1 - \alpha T_0)} = \frac{\alpha}{1 - \alpha T_0}$$

$$b\alpha = m - m\alpha T_0 \quad \Rightarrow \quad \alpha(b + mT_0) = m \quad \Rightarrow \quad \alpha = \frac{m}{b + mT_0}$$

$$\alpha = \text{_____} ( \quad )$$

What is the percent difference between your result above and the temperature coefficient of resistivity for copper given in the Table with  $\rho$  and  $\alpha$  values (in the *Theory and Procedure* file)?

$$\text{Percent difference} = \underline{\hspace{2cm}} \text{ ( \% )}$$

*Activity 5: Temperature of the Bulb's Filament*

(1 p.)

**5a.** The initial temperature of the bulb's filament is equal to the room temperature:

$$T_0 = \underline{\hspace{2cm}} \text{ ( }^\circ\text{C )}.$$

The initial resistance of the bulb's filament at temperature  $T_0$ :

$$R_0 = \underline{\hspace{2cm}} \text{ ( } \Omega \text{ )}$$

**5b.** Resistance of the **hot** bulb's filament:

$$R(T) = \underline{\hspace{2cm}} \text{ ( } \Omega \text{ )}.$$

NOTE: **The resistance changes with the applied current!** The hot bulb is an example of a **non-linear resistor**. Most of the semiconductor devices like diodes and transistors are also non-linear resistors. In this case the increase of current in the bulb increases the temperature of the filament. The warmer filament gets larger resistance resulting in a non-linear response to the current. **Print** this graph.

Use the thermal resistance equation,  $R(T) = R_0[1 + \alpha(T-T_0)]$ , and the resistance  $R_0$  at the room temperature  $T_0$ , to calculate the maximum temperature of the hot bulb filament. Remember that the bulb's filament is made from Tungsten with the temperature coefficient of resistivity  $\alpha = 0.0045/^\circ\text{C}$ .

The numerical value of the maximum temperature the filament reaches is equal to:

$$T = \underline{\hspace{2cm}} \text{ ( }^\circ\text{C )}.$$

Use the voltage versus current graph to calculate what is the electrical power dissipated in the bulb when it is brightest, i.e., when the maximum value of the voltage (= 5V ) is applied.

$$\text{Power } P = \underline{\hspace{2cm}} \text{ ( W )}$$

**Complete the Data Sheets and return the completed lab report to your TA.**