

- VI.G) 3) $\Rightarrow$
$$B = \frac{\mu \mu_0 N i}{\mu l + \mu_0 (2\pi r - l)}$$

-100-

for ferromagnetic materials $\mu l \gg 2\pi r$
 $(\mu = \mu(H))$

$$B \approx \frac{\mu_0 N i}{l} \gg \frac{\mu_0 N i}{2\pi r}$$


VII) Inductance:

A) Self inductance: Faraday's law $\mathcal{E}_L = - \frac{d\Phi_B}{dt}$

$$L = \frac{d\Phi_B}{di} = \frac{\Phi_B}{i} \text{ for linear media.}$$

1) SI unit of inductance = henry (H) $\equiv 1 \frac{\text{Volt} \cdot \text{sec.}}{\text{Ampere}}$

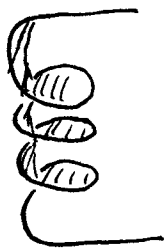2) Solenoid: a) flux linkages = total flux thru solenoid.



$$\begin{aligned} \Phi_B &= n l \Phi_{B_{\text{coil}}} = n l B \pi r^2 \\ &= \mu_0 n^2 l A i \end{aligned}$$

$$\Rightarrow L = \mu_0 n^2 l A$$

b) Voltage across each coil = $\mathcal{E}_{\text{coil}}$




$$\mathcal{E}_{\text{coil}} = - \frac{d\Phi_{B_{\text{coil}}}}{dt} = - \mu_0 n l \pi r^2 \frac{di}{dt}$$

But there are $n l$ -coils $\Rightarrow \mathcal{E}_L = n l \cdot \mathcal{E}_{\text{coil}}$

$$\Rightarrow L = \mu_0 n^2 l A$$

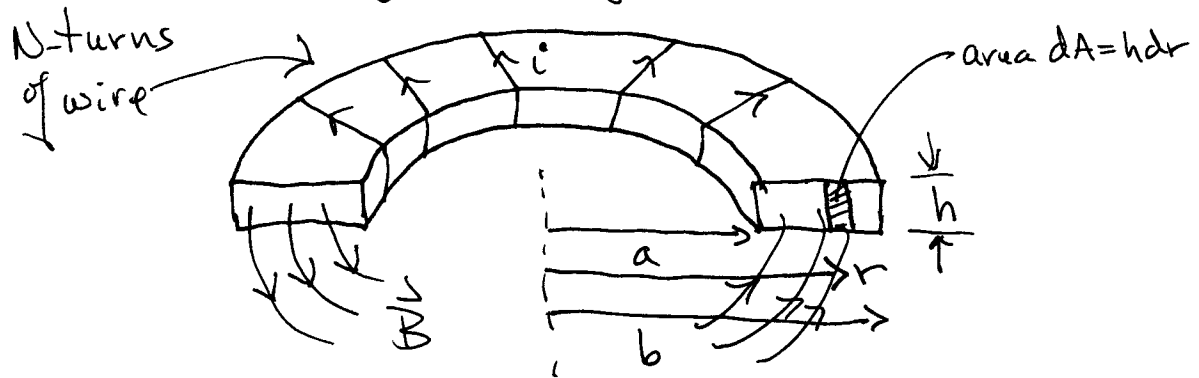- VII. A) 3) Toroid of rectangular cross section:



Total flux through coil of wire $\Phi_B = N \int_{\text{coil}} \vec{B} \cdot d\vec{A}$

$$\Phi_B = N \int_{r=a}^b \vec{B}(r) h dr$$

Use Ampere's law to find $B(r)$

$$\oint_C \vec{B} \cdot d\vec{s} = \mu_0 i_{\text{enclosed}} = \mu_0 N i$$

$$B(r) 2\pi r \Rightarrow B(r) = \frac{\mu_0 N i}{2\pi r}$$

$$\text{So } \Phi_B = \frac{\mu_0 N^2 i h}{2\pi} \ln\left(\frac{b}{a}\right) i$$


$$\Rightarrow \boxed{L = \frac{\mu_0 N^2 h}{2\pi} \ln\left(\frac{b}{a}\right)}$$

4) Fill inductors with magnetic material

$$\vec{B} = \frac{\mu}{\mu_0} \vec{B}_0 = (1 + \chi_m) \vec{B}_0 \leftarrow \vec{B} \text{ without magnetic material}$$

- VIII.A.4) $\Rightarrow$ Solenoid: $L = \mu n^2 A l$
 Toroid: $L = \frac{\mu N^2 h}{2\pi} \ln\left(\frac{b}{a}\right)$

B) Mutual Inductance: Wrap 2 independent coils of wire around solenoid

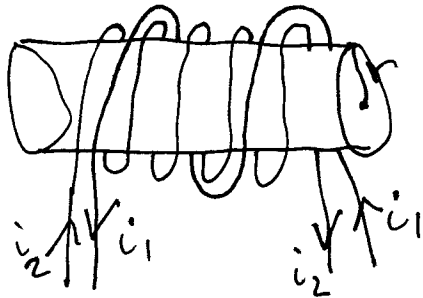

coil 1: $\phi_{B1} = \phi_{B11} + \phi_{B12}$

coil 2: $\phi_{B2} = \phi_{B21} + \phi_{B22}$

ϕ_{B21} = flux thru coil 2 due to B_1 = $\mu_0 n_1 n_2 l A i_1$

ϕ_{B12} = flux thru coil 1 due to B_2 = $\mu_0 n_1 n_2 l A i_2$

ϕ_{B11} = self-linkages coil 1 = $\mu_0 n_1^2 l A i_1$

ϕ_{B22} = self-linkages coil 2 = $\mu_0 n_2^2 l A i_2$

So Faraday's law $\Rightarrow$

$$\mathcal{E}_1 = -L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$\mathcal{E}_2 = -L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$M = \sqrt{L_1 L_2} \left\{ \begin{array}{l} L_1 = \text{self-inductance of coil 1} = \frac{\phi_{B11}}{i_1} = \mu_0 n_1^2 l A \\ L_2 = \text{self-inductance of coil 2} = \frac{\phi_{B22}}{i_2} = \mu_0 n_2^2 l A \\ M = \text{mutual inductance} = \frac{\phi_{B12}}{i_2} = \frac{\phi_{B21}}{i_1} = \mu_0 n_1 n_2 l A \end{array} \right.$

-103-

-III. c.) Magnetic Energy : Work required to move charge through inductor

$$dW = -\mathcal{E} dq = dq \frac{d\phi_B}{dt}$$

$$\text{But } dq = i dt \quad \& \quad \frac{d\phi_B}{dt} = \frac{d\phi_B}{di} \frac{di}{dt} = L \frac{di}{dt}$$

Hence $dW = i dt L \frac{di}{dt} = L i di$
 This is stored in the magnetic field of the inductor — it is the increase in Potential Energy stored in the magnetic field :

$$dU_B = dW = L i di$$

$$\Rightarrow \boxed{U_B = \frac{1}{2} L i^2 = \frac{1}{2} i \phi_B}$$

1) Applied to a solenoid : $L = \mu_0 n^2 A l \Rightarrow$
 $U_B = \frac{1}{2} \mu_0 n^2 i^2 (A l) \quad \text{but } B = \mu_0 n i$

$$\Rightarrow \boxed{U_B = \frac{1}{2\mu_0} B^2 (A l) = \frac{1}{2\mu_0} \int_{\text{All Space}} \vec{B} \cdot \vec{B} dV}$$

2) Energy density stored in magnetic field


$$\boxed{u_B = \frac{U_B}{A l} = \frac{1}{2\mu_0} \vec{B} \cdot \vec{B}} \quad ; \quad U_B = \int_{\text{All Space}} u_B dV$$

-VII.C) 3) If a magnetic material is present -104-

$$U_B = \frac{1}{2} \int_{\text{All Space}} \vec{B} \cdot \vec{H} dV$$

$$u_B = \frac{1}{2} \vec{B} \cdot \vec{H}$$

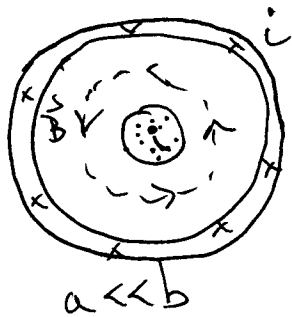4) Example: Coaxial Cable: What is the energy stored for a length l of cable.



inner conductor radius = a
outer conductor inner radius = b

Ampere's Law

$$\oint_C \vec{B} \cdot d\vec{s} = \mu_0 i_{\text{enclosed}}$$

$$B 2\pi r = \mu_0 i$$

$$B(r) = \frac{\mu_0 i}{2\pi r}$$

So energy stored in magnetic field ($a \leq r \leq b$)

$$u_B = \frac{1}{2\mu_0} B^2 = \frac{\mu_0 i^2}{8\pi^2 r^2}$$

Assume center conductor is small radius and outer conductor thin $\Rightarrow$



$$U_B = \frac{1}{2} \int_{r=a}^b \frac{1}{\mu_0} B^2 dV = \frac{\mu_0 i^2 l}{4\pi} \ln\left(\frac{b}{a}\right)$$

- VII.C.4) Recalling that $U_B = \frac{1}{2} Li^2$ we can determine the inductance of the cable from U_B above

$$L = \frac{\mu_0 l}{2\pi} \ln\left(\frac{b}{a}\right) \quad \text{which agrees with } L = \frac{\Phi_B}{i}$$

D) LR-Circuits

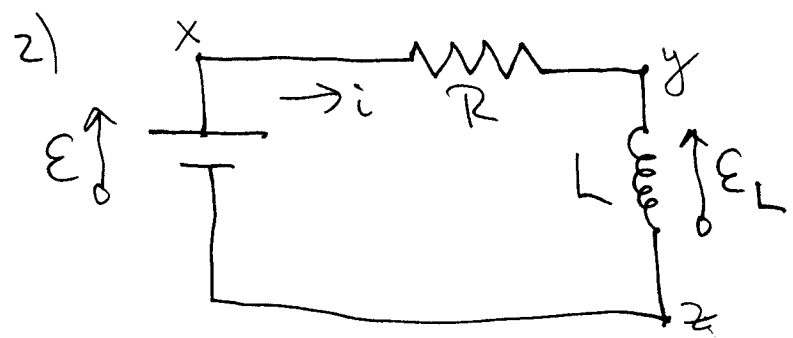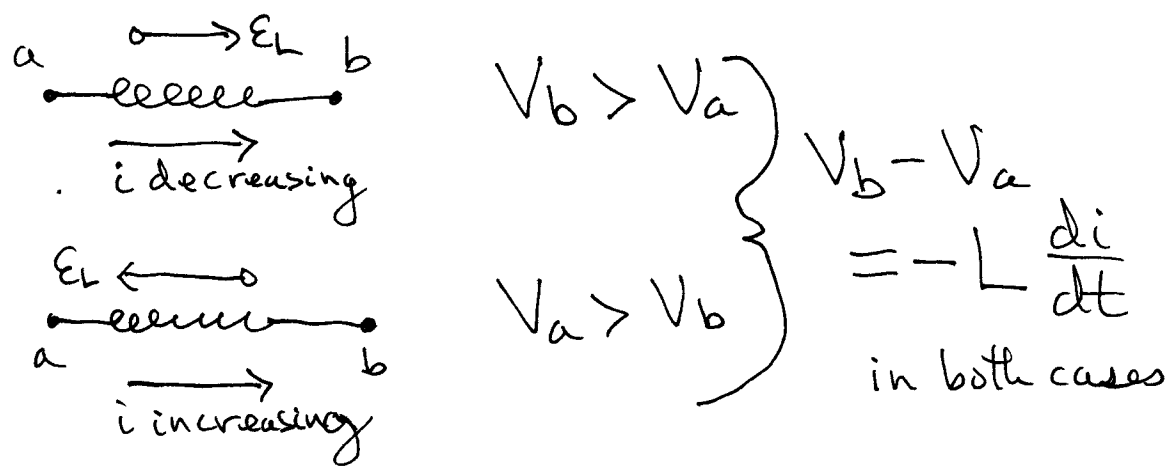1) Potential Difference across inductor (Lenz' Law)



Current Build Up



Loop Rule: $E = iR + L \frac{di}{dt}$

for i $\Rightarrow i(t) = \frac{E}{R} (1 - e^{-t/\tau})$


-VII.D) 2) with $\tau_L \equiv L/R = \text{inductive time constant}$

$$\text{So } V_R = V_x - V_y = iR = \mathcal{E}(1 - e^{-t/\tau_L})$$
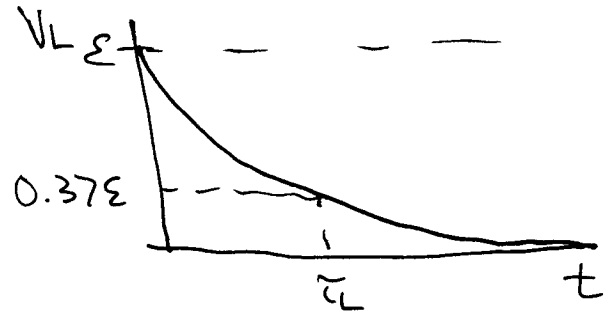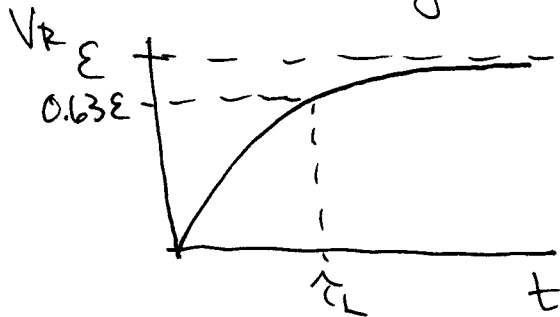
$$V_L = V_y - V_z = -\mathcal{E}_L = L \frac{di}{dt} = \mathcal{E} e^{-t/\tau_L}$$





3) Current Decay

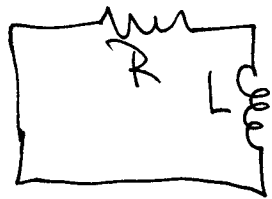


$$\text{Loop Rule: } L \frac{di}{dt} + iR = 0$$

$$\Rightarrow i(t) = i_0 e^{-t/\tau_L}$$

Let $i_0 = \mathcal{E}$

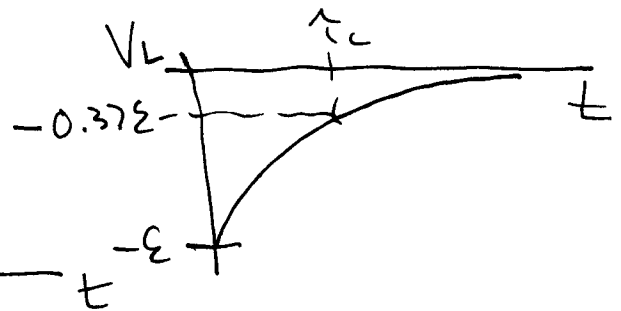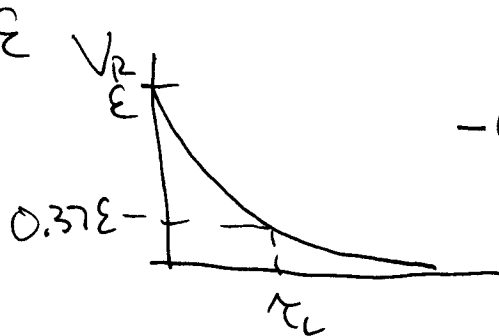

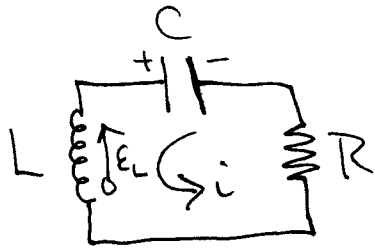vii. E.) LCR-Circuit : Initially charged capacitor




Loop Rule:

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

with initial conditions $q(0) = q_m$
 $\frac{dq(0)}{dt} = 0$.

(Mechanical Analog

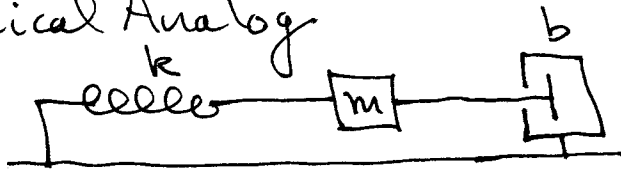

$$F = -kx - b\dot{x}$$

Newton's 2nd Law $\vec{F} = m\vec{a} \Rightarrow$
 with i.c. $x(0) = x_m$
 $\frac{dx(0)}{dt} = 0$

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + kx = 0$$


For $4\frac{L}{R^2} > R^2$ $q(t) = q_0 e^{-\frac{Rt}{2L}} \cos(\omega' t + \phi)$

i.c. $\Rightarrow \tan \phi = \frac{1}{\sqrt{\frac{4L}{R^2} - 1}}$; $q_0 = q_m \frac{1}{\sqrt{\frac{4L}{R^2} - 1}}$

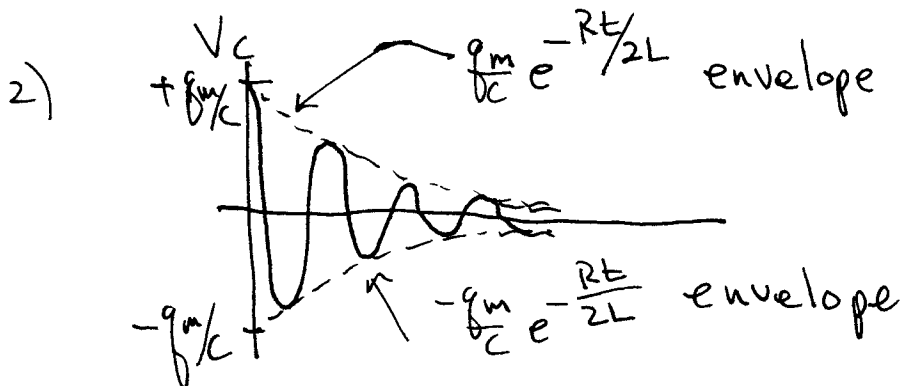
1) Energy Loss:

$$U = U_E + U_B = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} L i^2$$

$$\frac{dU}{dt} = -i^2 R \quad \text{Joule heating}$$



VII. E. 3) $R \rightarrow 0$

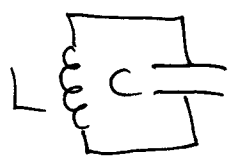


$$\frac{dU}{dt} = 0$$

$$U = \text{constant} = U_E + U_B \\ = \frac{1}{2} qm^2/c$$

energy oscillates between being stored in electric field and the magnetic field the current oscillates sinusoidally CW then CCW in circuit.

F.) Driven LCR-Circuit - Resonance

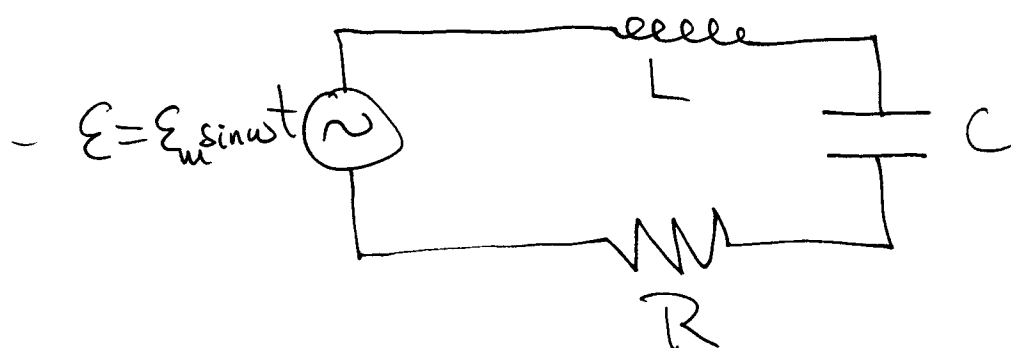

Loop Equation $\Rightarrow$
$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = \mathcal{E}_m \sin \omega t$$

(Mechanical Analog



$$q(t) = q_c(t) + q_p(t)$$

Complimentary
Solution = transient solution above

particular solution = steady state solution

- VII. F) Ansatz: $i_p(t) = \frac{i_m}{\omega} \sin(\omega t - \delta)$

Conventional $\delta \equiv \phi + \frac{\pi}{2}$ so

$$i = \dot{q}_p(t) = i_m \sin(\omega t - \phi)$$

Loop equation $\Rightarrow \tan \delta = \frac{\frac{R}{L} \omega}{\omega_0^2 - \omega^2}$


or 1) $\boxed{\tan \phi = \frac{\omega^2 - \omega_0^2}{\frac{R}{L} \omega}}$

where

$$\omega_0^2 \equiv \frac{1}{LC} \quad (\text{natural frequency of LC circuit})$$

$$2) i_m = \frac{\mathcal{E}_m}{R} \sec \phi$$
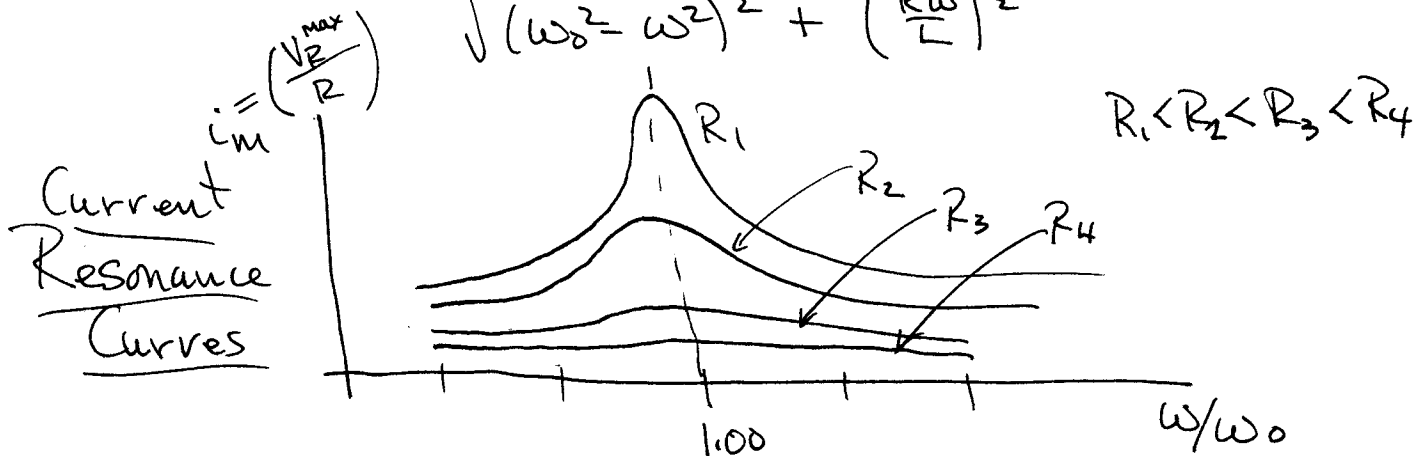
$$= \frac{\omega \cdot \mathcal{E}_m / L}{\sqrt{(\omega_0^2 - \omega^2)^2 + \left(\frac{R\omega}{L}\right)^2}}$$



$$\omega_R = \omega_0 = \frac{1}{\sqrt{LC}} \quad \left(\begin{array}{l} \text{Current } (V_R) \\ \text{Resonance} \end{array} \right)$$

VII. F.3) Voltage drop across capacitor = $V_C = \frac{q}{C}$


$V_{Cmax} = \frac{i_m}{\omega C}$ has resonance at charge frequency: $\omega_{GR} = \sqrt{\omega_0^2 - \frac{1}{2}(\frac{R}{L})^2} < \omega_0$ {P resonance at

4) Voltage drop across inductor = $V_L = L \frac{di}{dt}$


$V_{Lmax} = L \omega i_m$ has resonance at frequency: $\omega_{LR} = \frac{\omega_0}{\sqrt{1 - \frac{1}{2}(\frac{R^2 C}{L})}} > \omega_0$

G) Phasor Diagrams: $i(t) = i_m \sin(\omega t - \phi)$ through circuit element

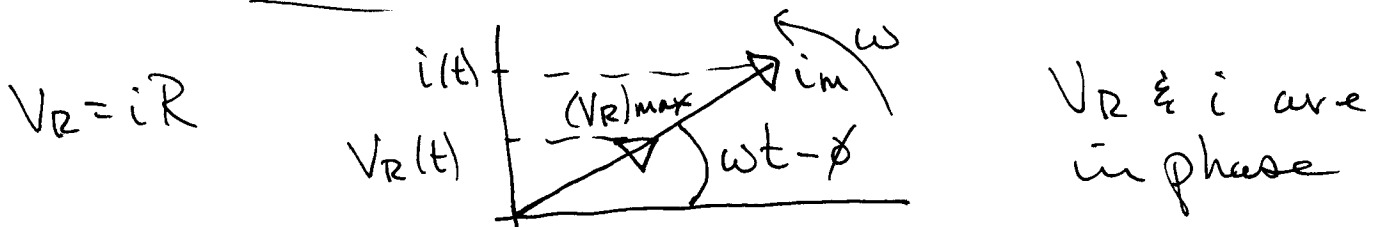1) Resistive Load: $V_R = i_m R \sin(\omega t - \phi)$



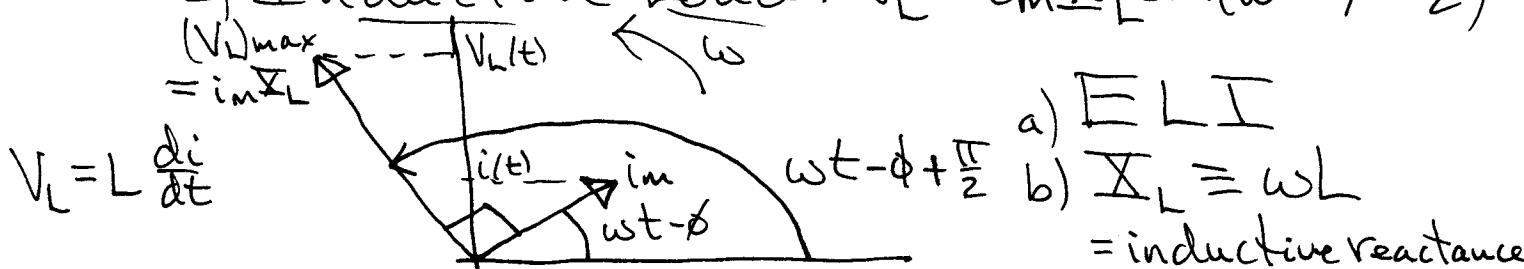
2) Inductive Load: $V_L = i_m X_L \sin(\omega t - \phi + \frac{\pi}{2})$



- VIII. Gr.) 3) Capacitive load: $V_c = i_m X_c \sin(\omega t - \phi - \frac{\pi}{2})$


$$V_c = \frac{q}{C}$$

$$= \frac{\int i dt}{C}$$

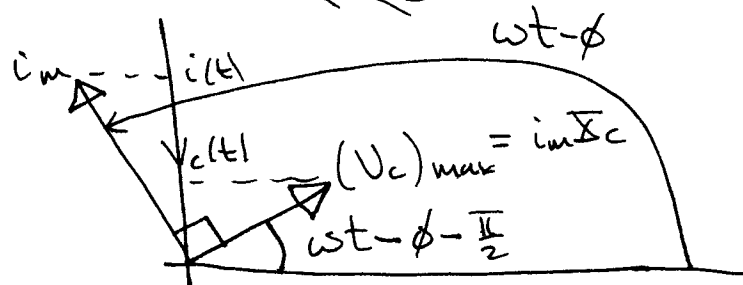


- a) $I C E$
 b) $X_c = \frac{1}{\omega C}$
 = capacitive reactance

4) LCR-Circuit:

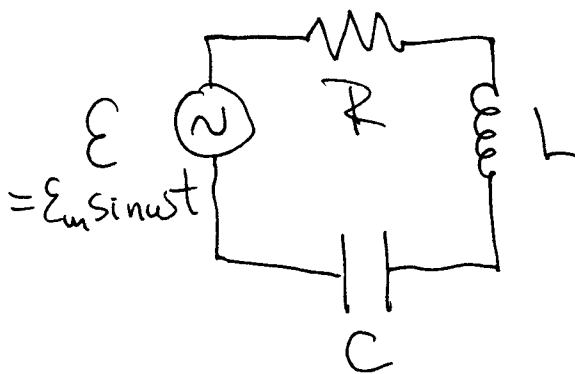

$$\varepsilon = \varepsilon_m \sin \omega t$$

Ansatz: $i = i_m \sin(\omega t - \phi)$

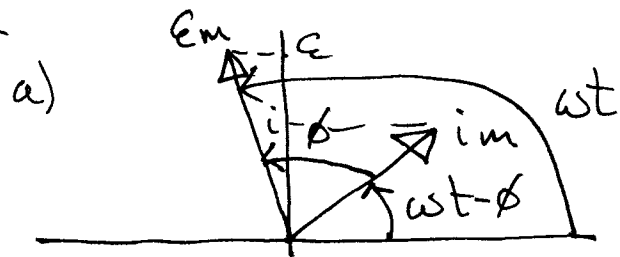


b) RLC Components:

loop rule:

$$\varepsilon = V_R + V_L + V_C$$


(scalar sum)

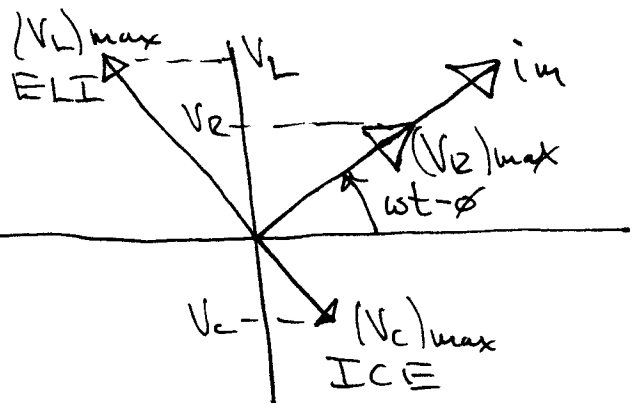

c) Vector sum of $(V_R)_{max}$, $(V_L)_{max}$, $(V_C)_{max}$ phasors
equals ε_m phasor

- VII. G4)c)

-112-

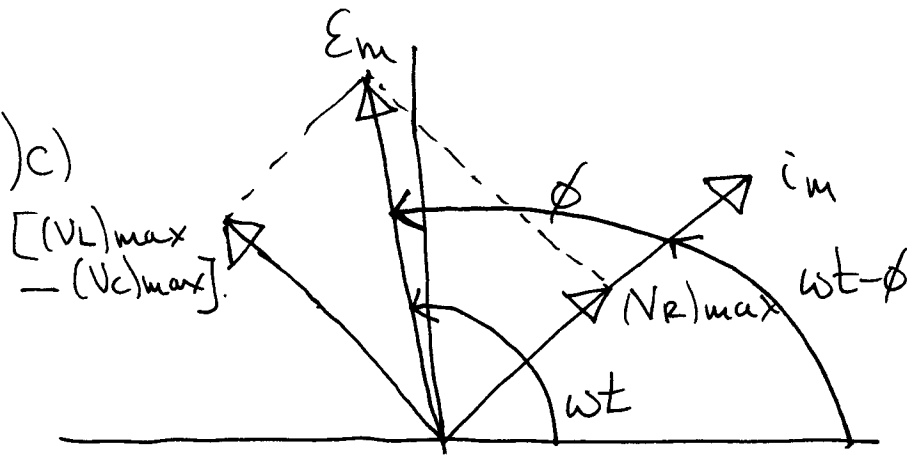

Since V_R, C, L phasors are at right angles $\Rightarrow$

$$\begin{aligned}\epsilon_m &= \sqrt{[(V_R)_{max}]^2 + [(V_L)_{max} - (V_C)_{max}]^2} \\ &= i_m \sqrt{R^2 + (X_L - X_C)^2}\end{aligned}$$

$$\Rightarrow i_m = \epsilon_m / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \text{impedance}$$

$$\tan \phi = \frac{(V_L)_{max} - (V_C)_{max}}{(V_R)_{max}} = \frac{X_L - X_C}{R} = \tan \phi$$

- 1) Resonance for the current occurs at $\phi = 0$
 $\Rightarrow X_L = X_C \Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{LC}}$,
 So $(V_L)_{max}$ and $(V_C)_{max}$ are equal and opposite to give i_m in phase with ϵ_m .

VII. H) Power in AC circuits:

1) Power dissipation in Resistor:

$$P = i^2 R = i_m^2 R \sin^2(\omega t - \phi)$$

Average power dissipation

$$\begin{aligned} \overline{P} &\equiv \frac{1}{N\pi} \int_0^{N\pi} P(t) dt \\ &= \frac{1}{2} i_m^2 R = i_{rms}^2 R \end{aligned}$$

with root mean square current

$$i_{rms} = \frac{i_m}{\sqrt{2}} \equiv \sqrt{\overline{(i)^2}}$$

2) Power supplied to circuit by source of emf

$$P = \frac{dW}{dt} = \mathcal{E}i = \mathcal{E}_m i_m \sin \omega t \sin(\omega t - \phi)$$

Average power supplied


$$\begin{aligned} \overline{P} &= \frac{1}{2} \mathcal{E}_m i_m \cos \phi \\ &= \mathcal{E}_{rms} i_{rms} \cos \phi \end{aligned}$$

VIII. H. 2) $\cos \phi \equiv \text{power factor}$

$$= \frac{R}{Z} = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

If resistive load $X_L = X_C \Rightarrow \cos \phi = 1$
 power delivered to circuit is maximum
 $P = E_{\text{rms}} i_{\text{rms}}$ ($Z = R$ resistive load)

I.) Transformer:

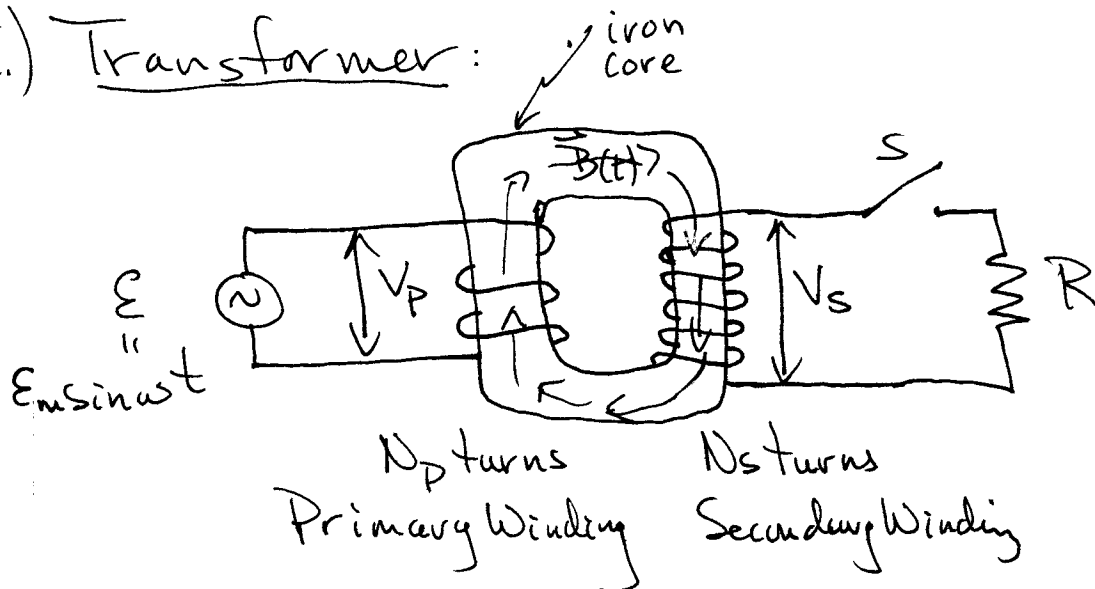

1) $\left(\frac{d\phi_B}{dt}\right)_{\text{primary per turn}} = \left(\frac{d\phi_B}{dt}\right)_{\text{secondary per turn}}$

$\Rightarrow \frac{V_p}{N_p} = \frac{V_s}{N_s}$

$\Rightarrow V_s = V_p \left(\frac{N_s}{N_p}\right)$

2) Energy Conservation: $i_p V_p = i_s V_s$ (Resistive load)

$\Rightarrow i_s = i_p \left(\frac{N_p}{N_s}\right)$