

Physics 21900

General Physics II

Electricity, Magnetism and Optics

Lecture 15 – Chapter 18.9-10

AC Voltage and Transformers

Fall 2015 Semester


Prof. Matthew Jones

Announcement

**Exam #2 will be on November 5th
in Phys 112 at 8:00 pm**

*Electric current, DC circuits, Kirchhoff's Rules
Magnetic Fields, Lorentz Force, Forces on Currents
Ampere's Law, Magnetic Induction, Lenz's Law
Induced EMF, AC Voltage, Transformers*

AC Voltage Generators

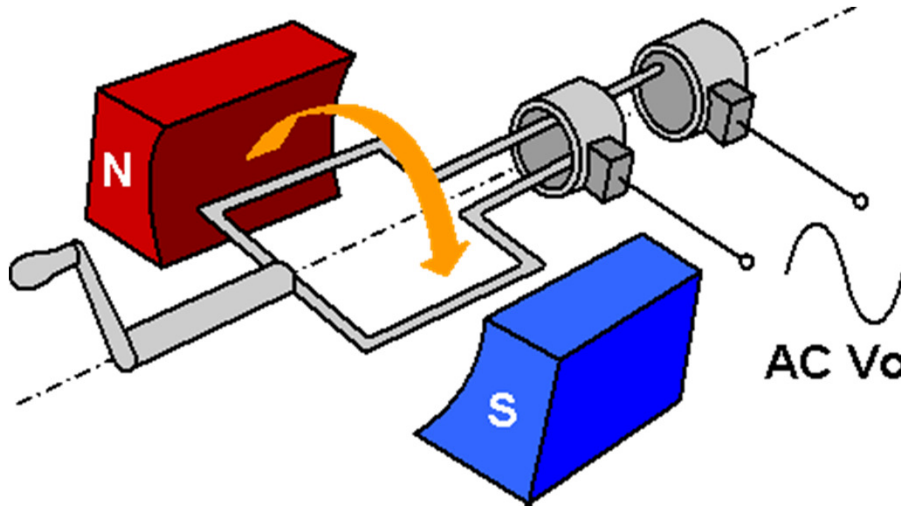


$$\text{Faraday's law: } \mathcal{E} = - \frac{\Delta \Phi_B}{\Delta t}$$

$$\Phi_B = NAB \cos \theta$$
$$= NAB \cos(\omega t)$$


$$\text{AC Voltage, } \mathcal{E} = V_{max} \sin(\omega t)$$

$$V_{max} = NAB\omega$$

$$\omega = 2\pi f$$

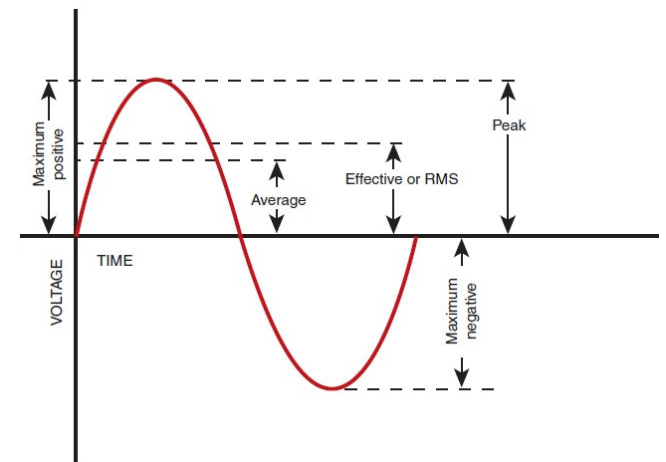

Alternating Current/Sine Waves

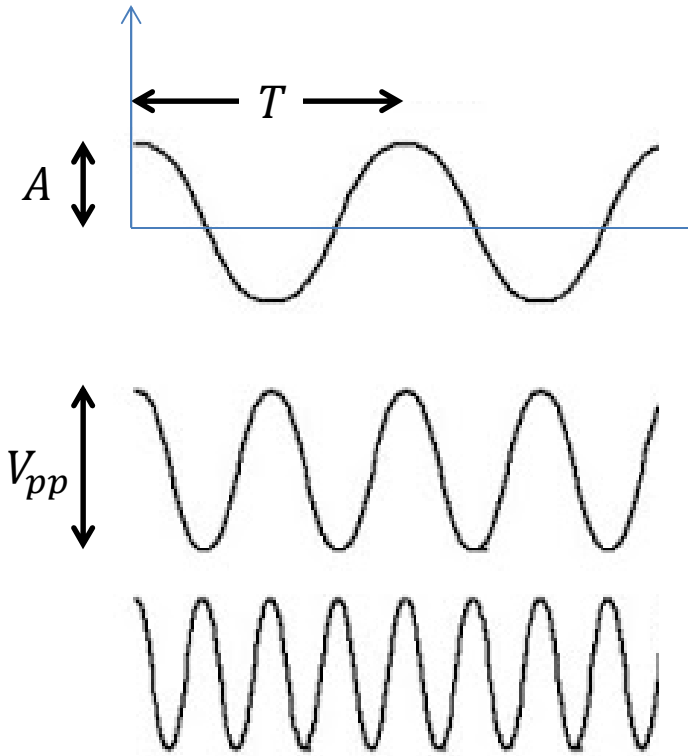

Period: T (seconds)

Frequency: $f = 1/T$ (Hertz, s^{-1})

Angular frequency: $\omega = 2\pi f$ (s^{-1})

Amplitude: $A = V_{max}$ or I_{max}

$$V(t) = V_{max} \sin \omega t$$

$$\text{or } V(t) = V_{max} \cos \omega t$$

Sometimes we refer to the peak-to-peak amplitude, V_{pp} .


The functions $\sin \omega t$ and $\cos \omega t$ look the same – just shifted in time by 90 degrees.

Alternating Current/Sine Waves

- Example:
 - In North America, the AC line voltage has a frequency of 60 Hz.
 - The angular frequency is

$$\begin{aligned}\omega &= 2\pi f \\ &= 2 \times 3.141592654 \times (60 \text{ s}^{-1}) \\ &= 377 \text{ radians/second}\end{aligned}$$

AC Voltage/AC Current

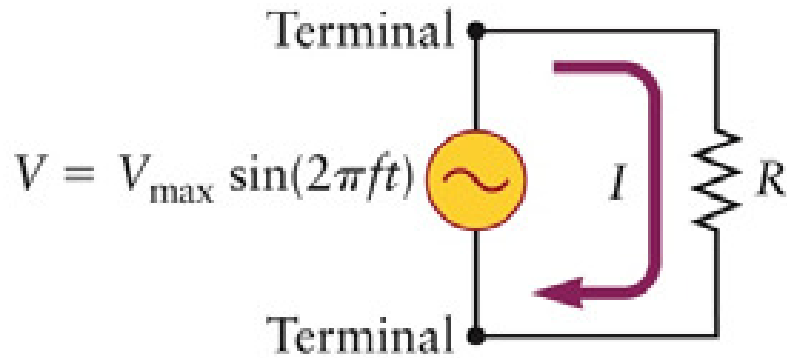


Ohm's Law: $I = V/R$

$$V(t) = V_{\max} \sin(2\pi ft)$$

$$I(t) = I_{\max} \sin(2\pi ft)$$


$$I_{\max} = V_{\max}/R$$

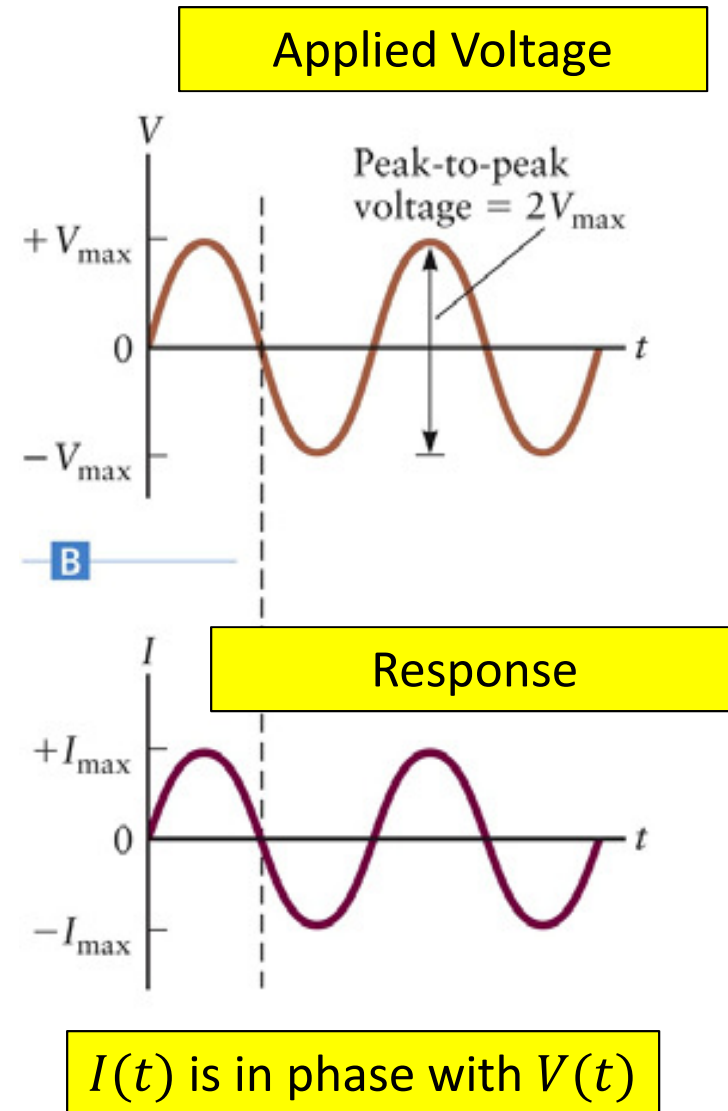

$I(t)$ is in phase with $V(t)$


Phasor Diagrams

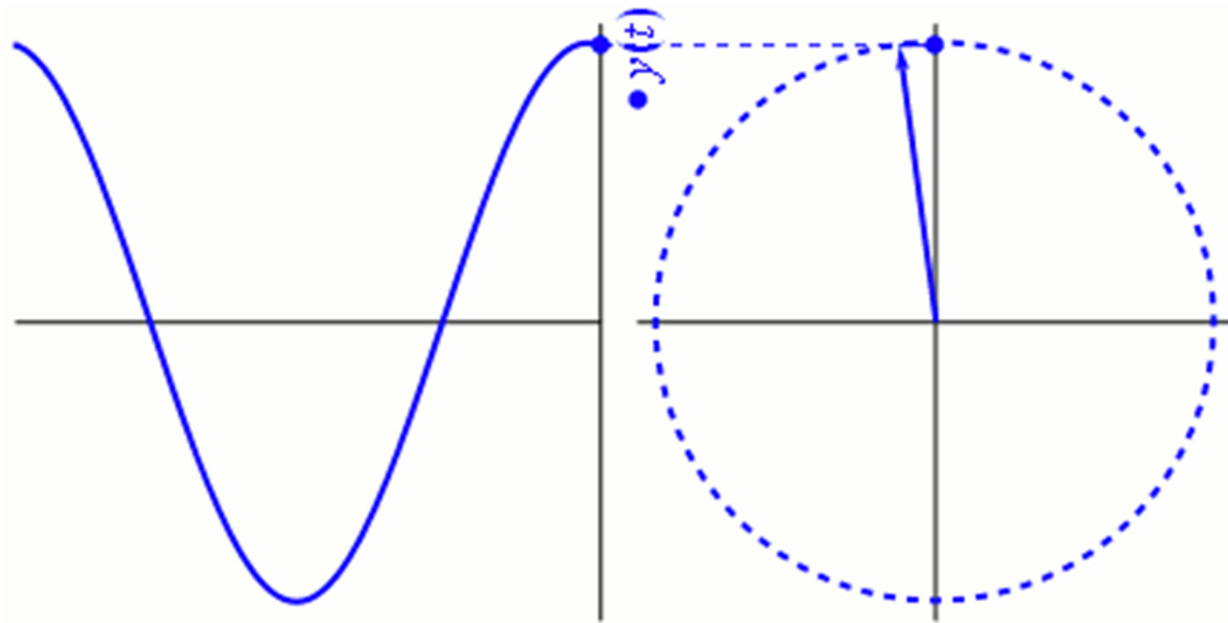- A rotating vector is one way to represent a sine wave.



Phasor Diagrams

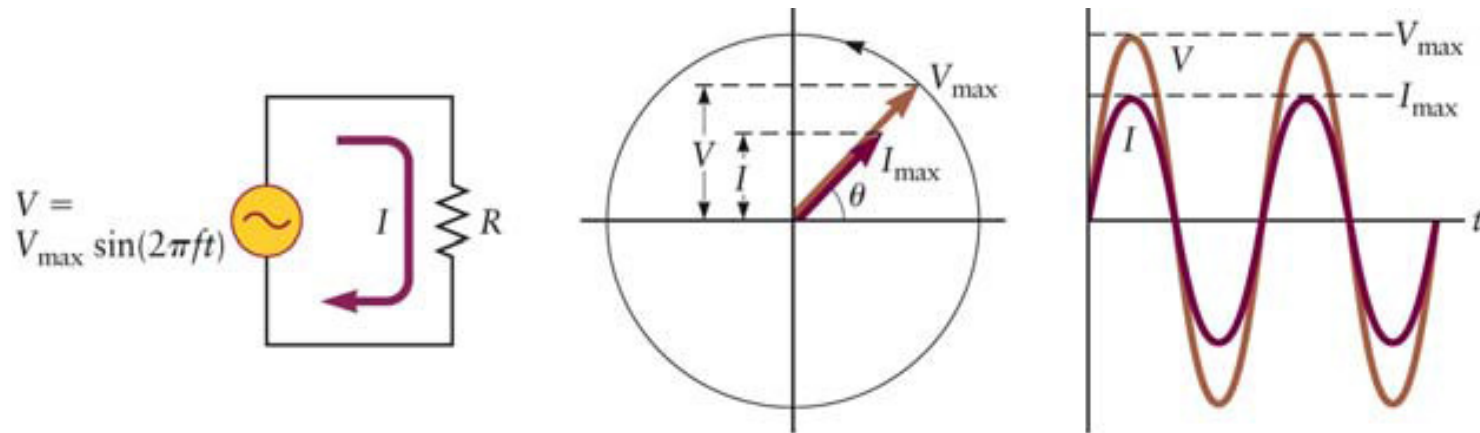- These diagrams show the relation between the phase of the current and the voltage:




- Both the voltage and current vectors rotate with constant angular velocity, $\omega = 2\pi f$.
- The vectors maintain their relative orientation.
- For a circuit with only resistors, the current and voltage have the same phase.

AC Power

- How much power is dissipated in the resistor?
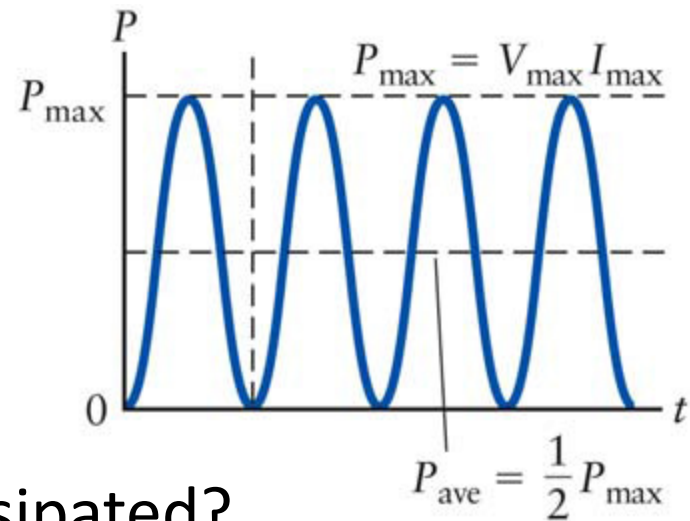
$$P = IV = I_{max}V_{max} \sin^2(2\pi ft)$$



- What is the average power dissipated?

$$\begin{aligned} P_{avg} &= \frac{1}{2} P_{max} \\ &= \left(\frac{I_{max}}{\sqrt{2}} \right) \left(\frac{V_{max}}{\sqrt{2}} \right) = I_{rms} V_{rms} \end{aligned}$$

AC Power


- For sine or cosine waves, the RMS voltage or current is just

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} \qquad V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

- Expressed using RMS voltage and current, Ohm's law can be used to express the average power:

$$P_{avg} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

Example: ac circuit analysis

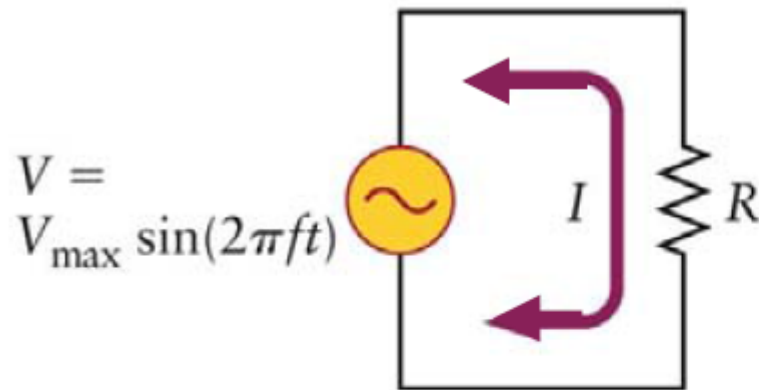

$$V_{\max} = 170 \text{ V}$$

$$f = 60 \text{ Hz}$$

$$R = 20 \Omega$$

What are V_{rms} , I_{rms} , and average power dissipated in load?

What are V_{\max} , I_{\max} , and maximum power dissipated in load?

Average values

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}} = \frac{170 \text{ V}}{1.414} = 120 \text{ V}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{120 \text{ V}}{20 \Omega} = 6 \text{ A}$$

$$P_{\text{ave}} = I_{\text{rms}} V_{\text{rms}} = (6 \text{ A})(120 \text{ V}) = 720 \text{ W}$$


Maximum values

$$V_{\max} = 170 \text{ V}$$

$$I_{\max} = \frac{V_{\max}}{R} = \frac{170 \text{ V}}{20 \Omega} = 8.5 \text{ A}$$


$$P_{\max} = I_{\max} V_{\max} = (8.5 \text{ A})(170 \text{ V}) = 1445 \text{ W}$$

An ac isolator

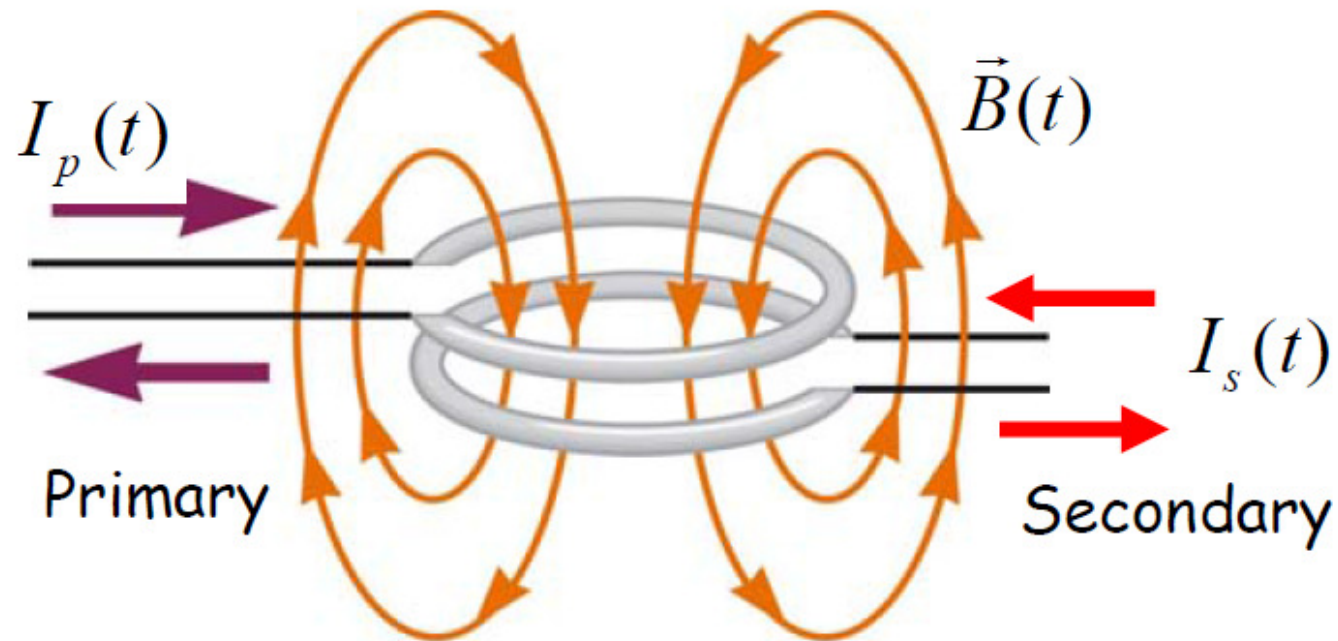


The Secondary is isolated from the Primary

Input: ac +dc signal

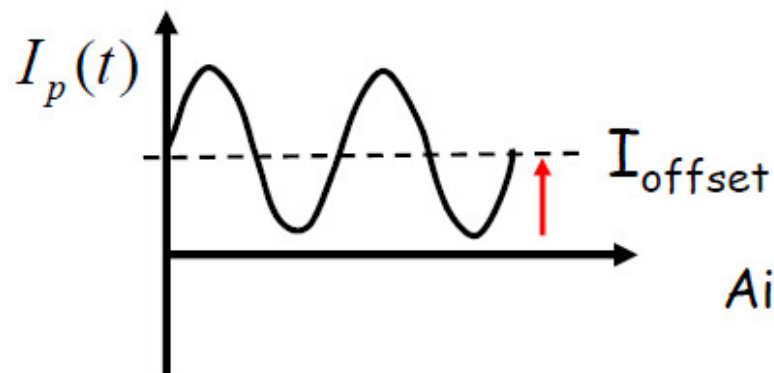

Output: ac signal ONLY

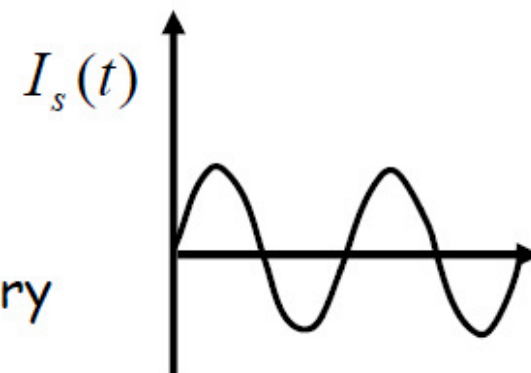


Air coupling not very efficient


A Practical Transformer

- Magnetic flux is trapped by an iron core.
- The magnetic flux through each coil is the same.
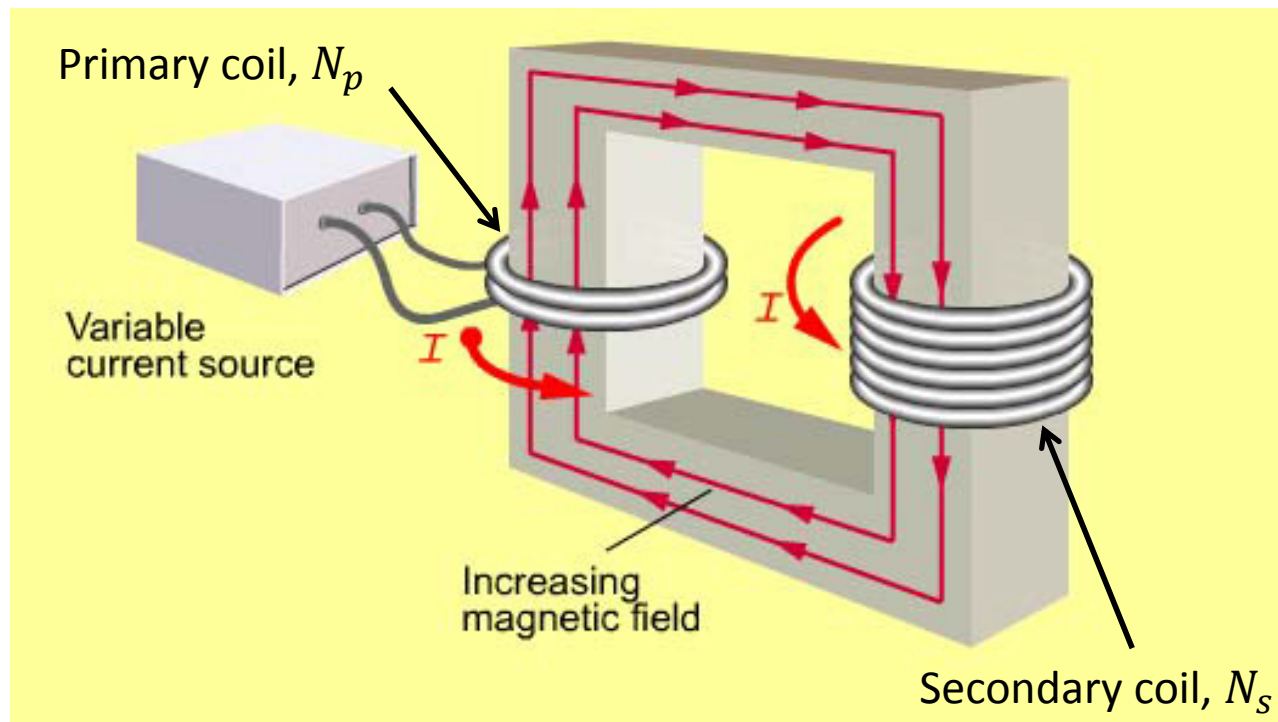
$$\Phi_B(t) \propto N_p I_p(t) = N_s I_s(t)$$





Transformers

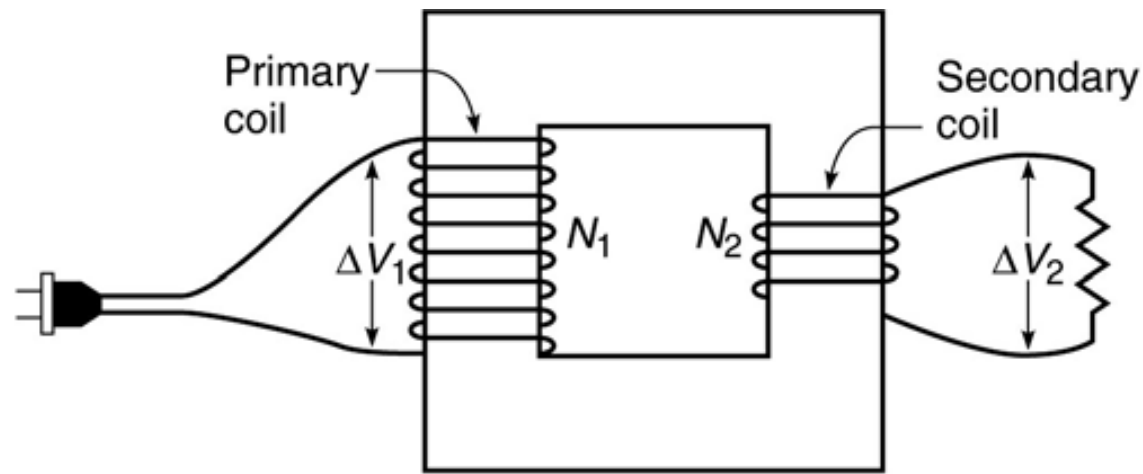

- The input voltage must vary with time so that $\Delta\Phi_B/\Delta t \neq 0$
- Energy must be conserved: $P_p = P_s$

$$I_p \Delta V_1 = I_s \Delta V_2$$
$$\frac{\Delta V_2}{\Delta V_1} = \frac{I_p}{I_s} = \frac{N_s}{N_p}$$

Examples

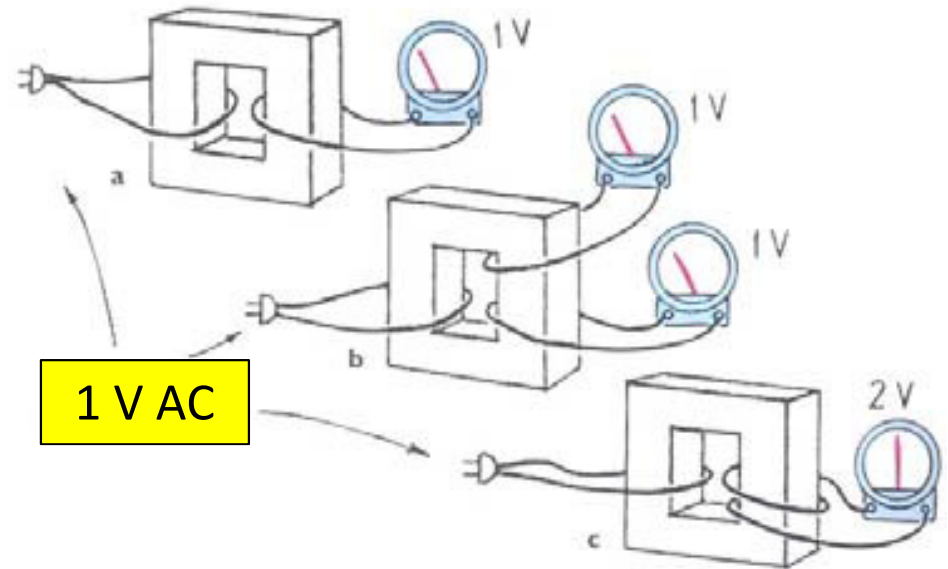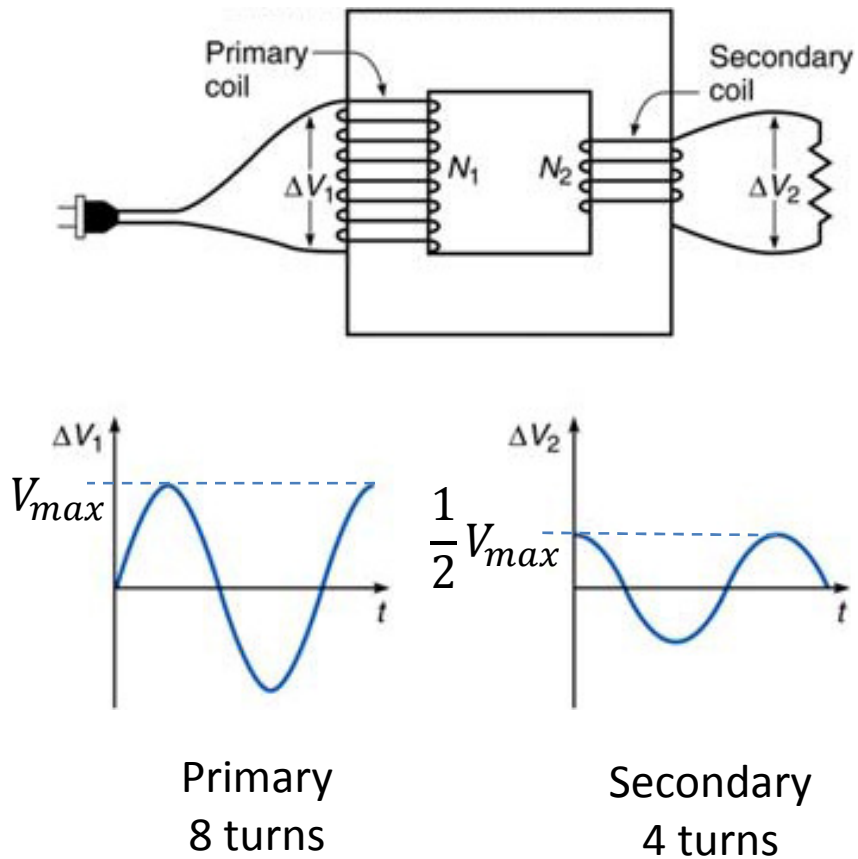

EXAMPLE

A transformer has 10 turns on the primary and 100 turns on the secondary. If 110V rms is applied to the primary, what is the peak-to-peak voltage across the secondary?


$$\frac{\Delta V_1}{\Delta V_2} = \frac{N_1}{N_2}$$

$$\frac{110V|_{\text{rms}}}{\Delta V_2|_{\text{rms}}} = \frac{10}{100}$$

$$\Delta V_2|_{\text{rms}} = 10(110V|_{\text{rms}}) = 1100V|_{\text{rms}}$$

$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} \Rightarrow V_{\text{max}} = 1555V$$
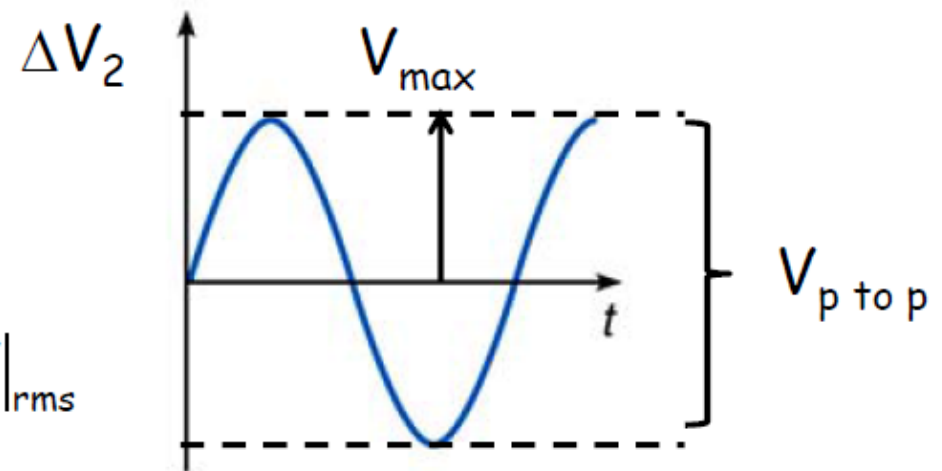
$$V_{\text{p to p}} = 2V_{\text{max}} = 3111V$$



If a $100\ \Omega$ load is connected to the secondary, what is the rms current in the primary?

$$\frac{\Delta V_1}{\Delta V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$


$$\frac{110V|_{rms}}{\Delta V_2|_{rms}} = \frac{10}{100}$$

$$\Delta V_2|_{rms} = 10(110V|_{rms}) = 1100V|_{rms}$$

$$I_2|_{rms} = \frac{\Delta V_2|_{rms}}{R_{load}} = \frac{1100V|_{rms}}{100\ \Omega} = 11A|_{rms}$$

$$\frac{N_1}{N_2} = \frac{I_2}{I_1} \Rightarrow \frac{10}{100} = \frac{11A}{I_1}$$

$$I_1|_{rms} = \left(\frac{100}{10}\right) 11A = 110A$$

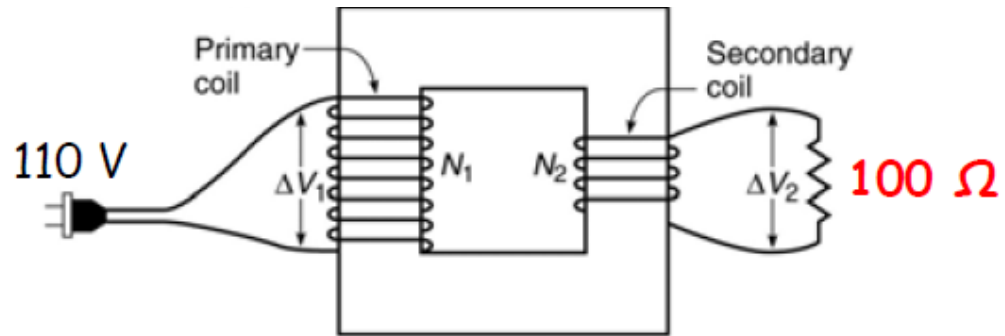


Primary
10 turns

Secondary
100 turns

APPENDIX: Transformers in the US Power Grid

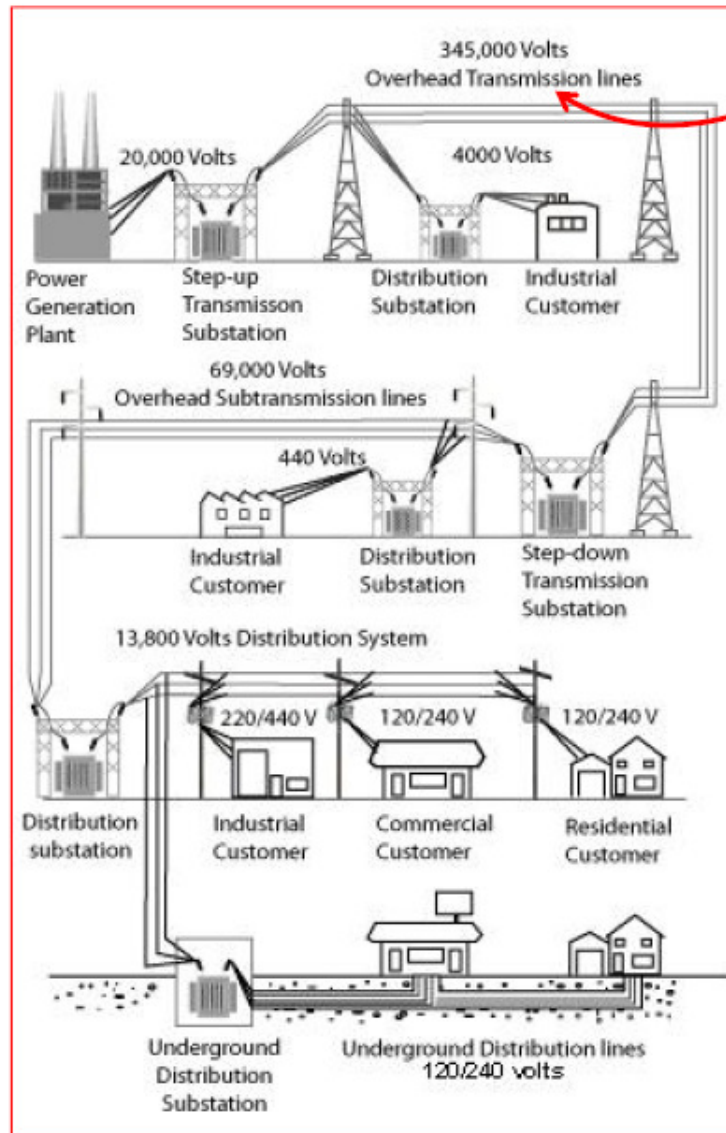Why is power transmitted at such high voltages?



$$\left. \begin{aligned} V_{rms} &= 345,000 \text{ V} \\ I_{rms} &= 1000 \text{ A} \end{aligned} \right\} \text{Typical values}$$

$$P_{\text{Transmitted}} = V_{rms} I_{rms} = (345,000 \text{ V})(1000 \text{ A}) = 345 \text{ MW}$$

SUPPOSE 10% of power is lost

$$P_{\text{Lost}} = 10\% P_{\text{Transmitted}} = 34.5 \text{ MW}$$

$$P_{\text{Lost}} = I_{rms}^2 R_{\text{line}}$$

$$R_{\text{line}} = 34.5 \Omega$$

Now suppose V_{rms} is decreased by 9/10 and I_{rms} is increased by 10/9, so the average power transmitted remains the same:

$$V_{rms} = \frac{9}{10} \times (345,000 \text{ V}) = 310,500 \text{ V}$$

$$I_{rms} = \frac{10}{9} \times (1000 \text{ A}) = 1111 \text{ A}$$

$$P_{\text{Transmitted}} = V_{rms} I_{rms} = (310,500 \text{ V})(1111 \text{ A}) = 345 \text{ MW} \text{ (same as before)}$$

How much power is now lost?

$$R_{\text{line}} = 34.5 \Omega \text{ (same as before)}$$

$$P_{\text{Lost}} = I_{rms}^2 R_{\text{line}} = (1111 \text{ A})^2 (34.5 \Omega) = 42.6 \text{ MW}$$

$$\frac{P_{\text{Lost}}}{P_{\text{Transmitted}}} = \frac{42.6 \text{ MW}}{345 \text{ MW}} = \text{power lost increases by 12.3\%}$$