

# ANNOUNCEMENT

- \***Exam 2:** Monday, November 5, 2012, 8 PM - 10 PM
- \***Location:** Elliot Hall of Music
- \*Covers all readings, lectures, homework from Chapters 25 through 28.
- \*The exam will be multiple choice (15-18 questions).

**Be sure to bring your student ID card and your own two-page (two-side) crib sheet, one from exam 1 and a new one.**

**NOTE THAT FEW EQUATIONS WILL BE GIVEN – YOU ARE REMINDED THAT IT IS YOUR RESPONSIBILITY TO CREATE WHATEVER TWO-SIDED CRIB SHEET YOU WANT TO BRING TO THIS EXAM.**

The equation sheet that will be given with the exam is posted on the course homepage. Click on the link on the left labeled “EquationSheet”

# **ANNOUNCEMENT**

No lecture on Tuesday, November 20  
(Week of Thanksgiving)

Physics 24100

# **Electricity & Optics**


Lecture 15 – Chapter 28 sec. 6-9

Fall 2012 Semester

Matthew Jones
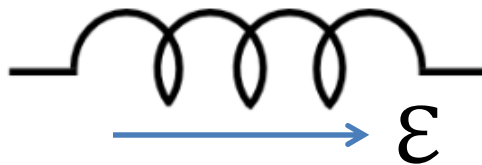
# Clicker Question

- An inductor in a circuit produces an induced EMF that is positive in the orientation shown:



- Which statement could describe the current?
  - (a) Increasing current to the right
  - (b) Decreasing current to the right
  - (c) Increasing current to the left
  - (d) Either (b) or (c)
  - (e) Either (a) or (c)

# Inductance

- Magnetic field inside the solenoid:

$$\vec{B} = \mu_0 n I$$


- Magnetic flux:

$$\begin{aligned}\phi_m &= N B A = (n \ell) B A \\ &= \mu_0 n^2 \ell A I\end{aligned}$$


- Flux is proportional to  $I$ .
- Inductance is

$$L = \mu_0 n^2 \ell A$$


$$\phi_m = L I$$

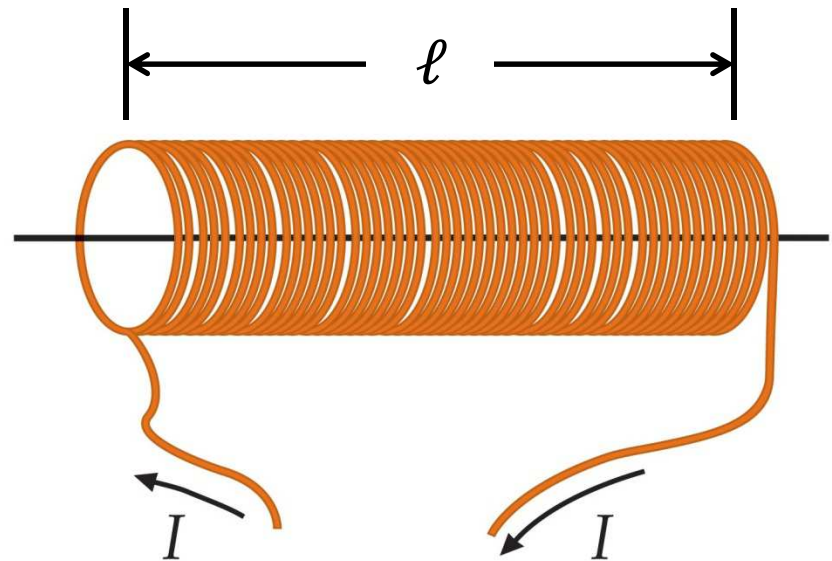

# Inductance vs Capacitance

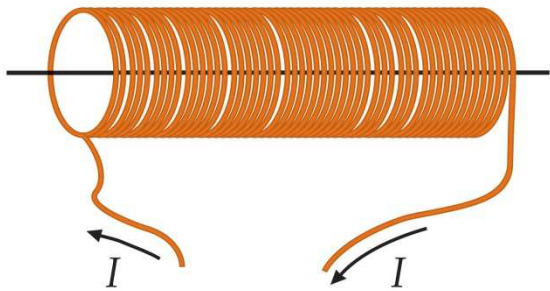

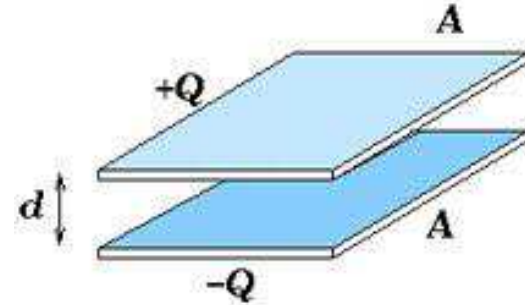- $L = \mu_0 n^2 \ell A$
- Assume  $r \ll \ell$
- $L$  only depends on geometry
- Add a core of magnetic material:  $\mu_0 \rightarrow \mu$
- Stores energy in the magnetic field



- $C = \epsilon_0 A / d$
- Assume  $d \ll \sqrt{A}$
- $C$  only depends on geometry
- Add a dielectric material:  $\epsilon_0 \rightarrow \epsilon$
- Stores energy in the electric field



# How Much Energy?

- Energy density of a magnetic field:

$$u_m = \frac{B^2}{2\mu_0}$$

- Integrate this over a volume to calculate the total energy stored in the magnetic field.
- Energy is conserved:
  - A change in the magnetic field changes the energy density
  - A changing magnetic field induces an electromotive force
  - The EMF does work on charge carriers
  - A reversible process

# How Much Energy?

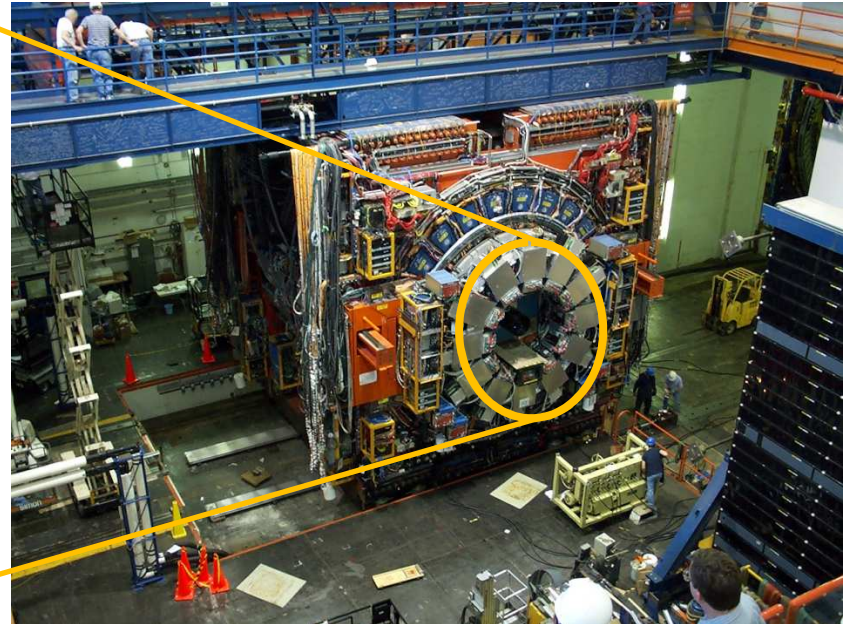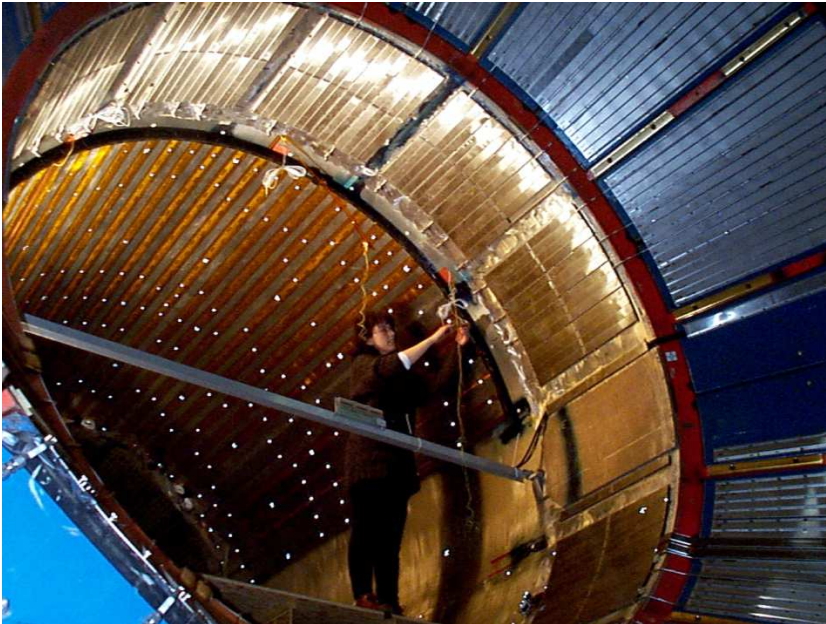

$$B = 1.4 \text{ T} \quad r = 1.5 \text{ m} \quad \ell = 5 \text{ m}$$

$$U_m = \frac{B^2}{2\mu_0} V = \frac{\pi r^2 B^2}{2\mu_0} \ell = 31 \text{ MJ}$$

( $10^5$  kg moving at 90 km/h)           






# Question

- Suppose we modify a solenoid in various ways:

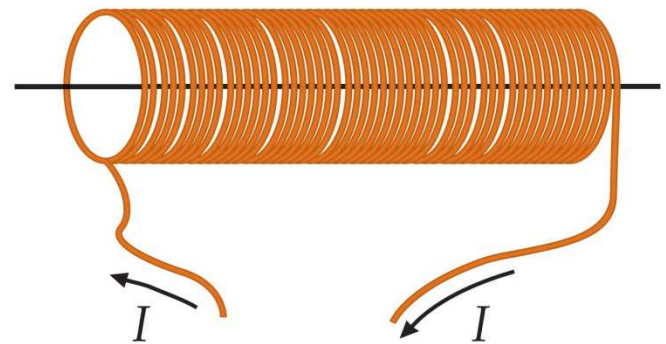1. Double the length,  $\ell$
2. Double the radius,  $r$
3. Double the current,  $I$



- Which statement about their inductances is true?
  - (a)  $L_1 > L_2 > L_3$
  - (b)  $L_3 > L_2 > L_1$
  - (c)  $L_2 > L_1 > L_3$
  - (d)  $L_2 > L_3 > L_1$


# Question

- For a solenoid,  $L = \mu_0 n^2 \ell A$
- Doubling  $\ell$  will double the inductance
- Doubling  $r$  will quadruple the inductance
- Doubling  $I$  does not change the inductance
  - It would double  $\phi_m$  but not  $L$

Which statement about their inductances is true?

- (a)  $L_1 > L_2 > L_3$
- (b)  $L_3 > L_2 > L_1$
- (c)  $L_2 > L_1 > L_3$**
- (d)  $L_2 > L_3 > L_1$

# Inductors in Circuits


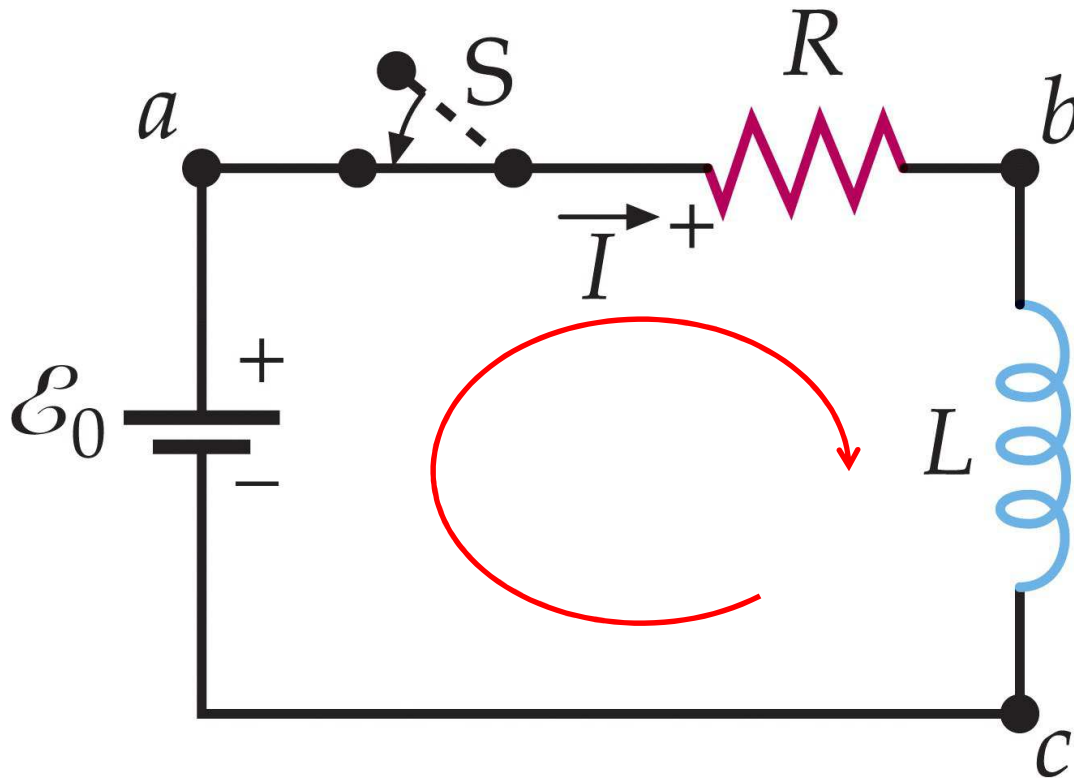


The voltage induced across the inductor opposes any change in current.

$$\mathcal{E}_0 - I R - L \frac{dI}{dt} = 0$$

Kirchhoff's Loop Rule!

# Inductors in Circuits

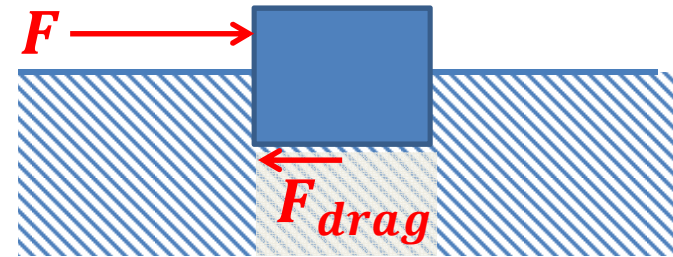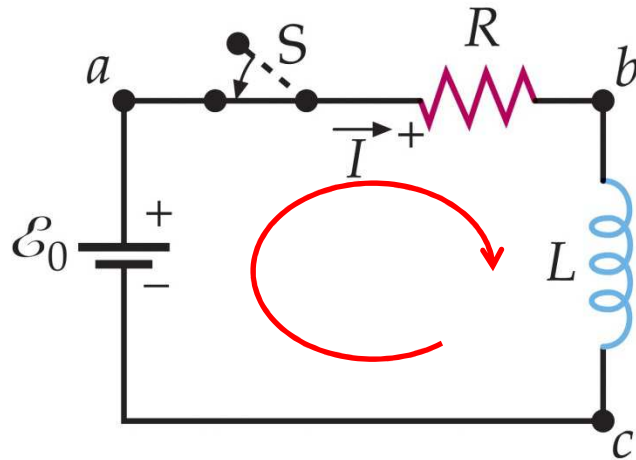

$$\mathcal{E}_0 - I R - L \frac{dI}{dt} = 0$$


$$\mathcal{E}_0 = I R + L \frac{dI}{dt}$$

$$F - F_{drag} = m \frac{dv}{dt}$$

$$F = \gamma v + m \frac{dv}{dt}$$


The mechanical analog of inductance is mass. The inertia associated with a mass resists changes in velocity. The inductance resists changes in current.

# Inductors in Circuits

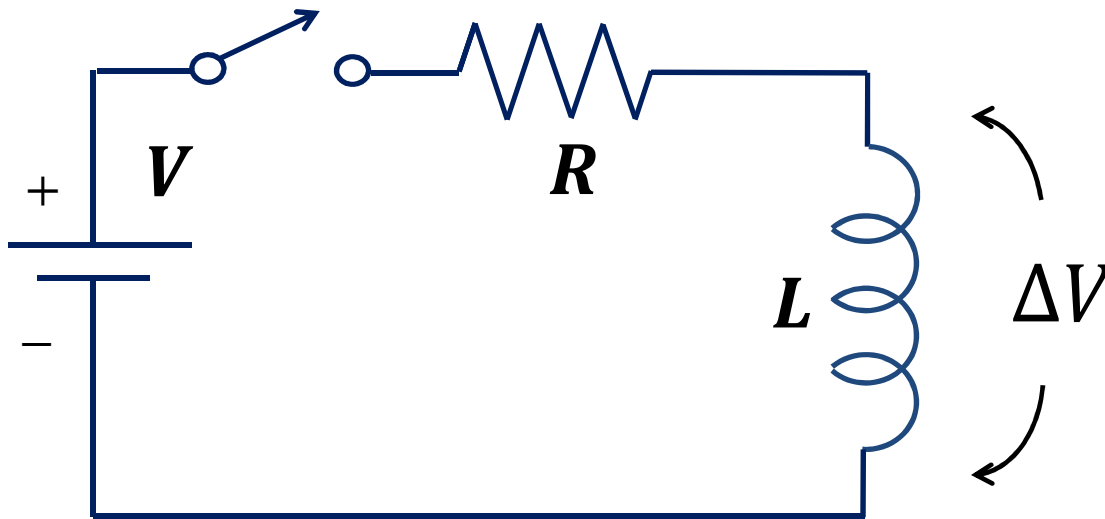

- At time  $t = 0$  the switch is closed and a current will start to flow.
- Initially, the inductor produces a potential difference equal to  $V$  which opposes the flow of current.
- When the current reaches the steady state  $I = V/R$ , the inductor acts like a wire, with no potential difference.

# Inductors in Circuits

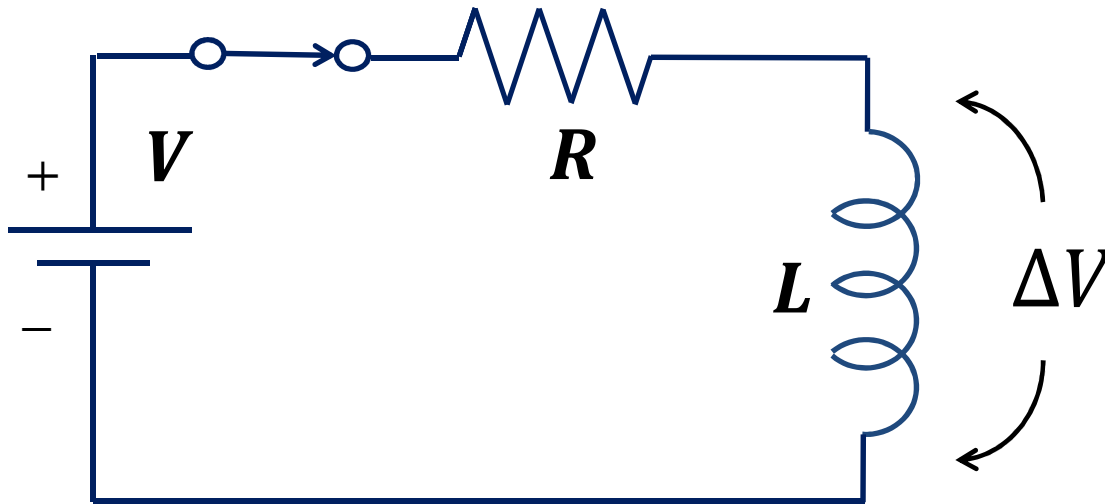


- Kirchhoff's loop rule:

$$V = I R + L \frac{dI}{dt}$$


- A solution is

$$I(t) = \frac{V}{R} (1 - e^{-t/\tau})$$

where  $\tau = L/R$

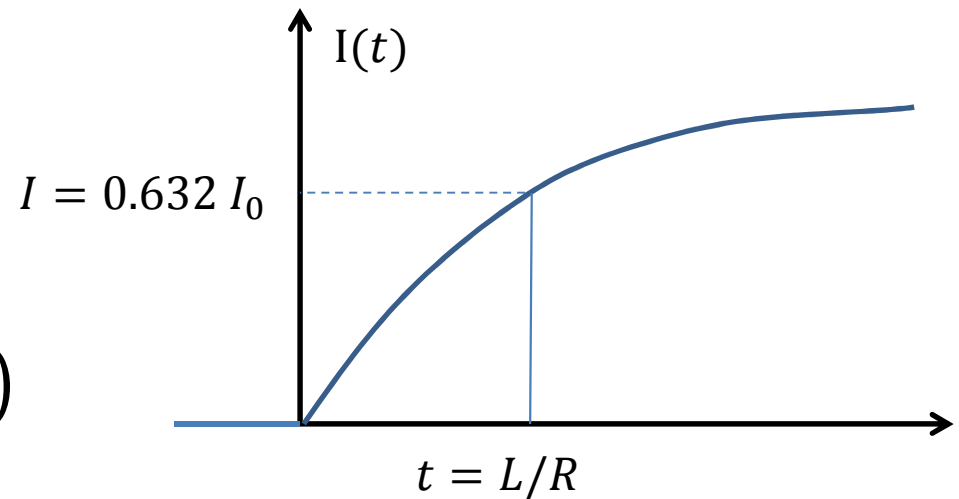

# Inductors in Circuits

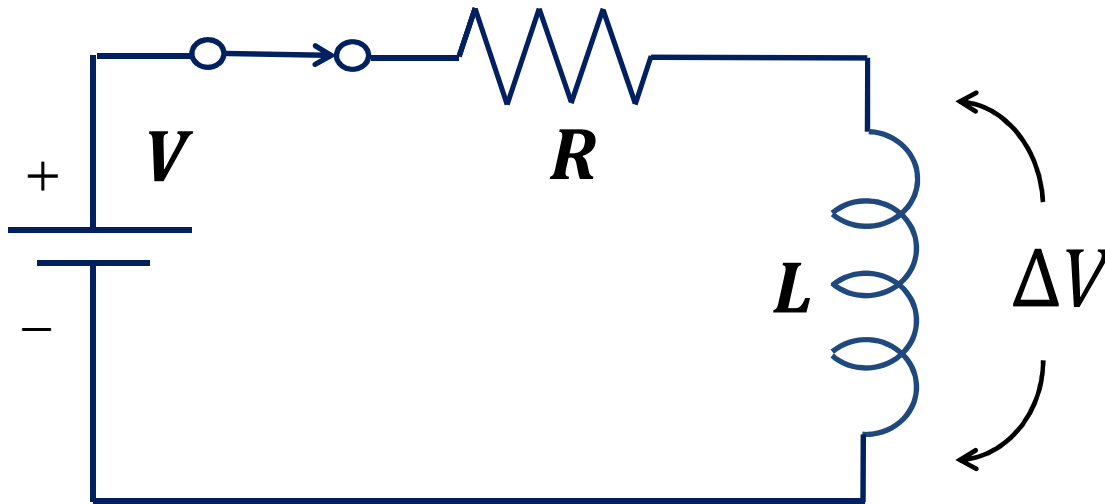


- What is the potential difference across the inductor?
- Kirchhoff's loop rule:


$$V - IR - \Delta V = 0$$

$$\Delta V = V e^{-t/\tau}$$

$$\Delta V = 0.368 V$$

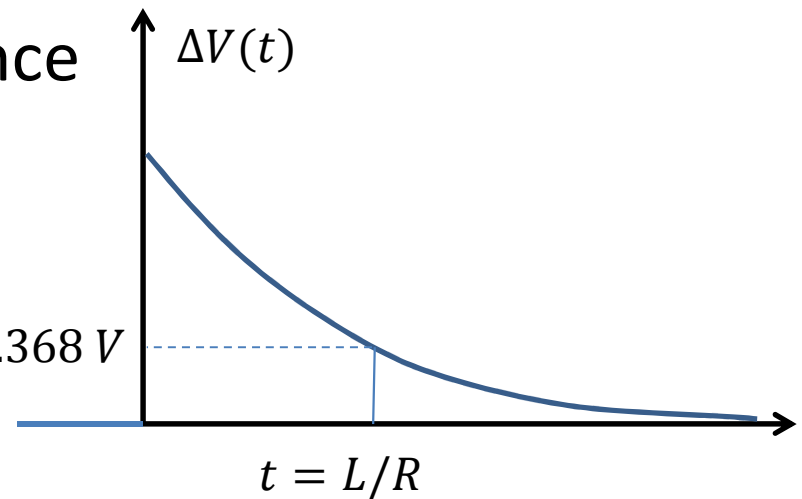

# Inductors in Circuits

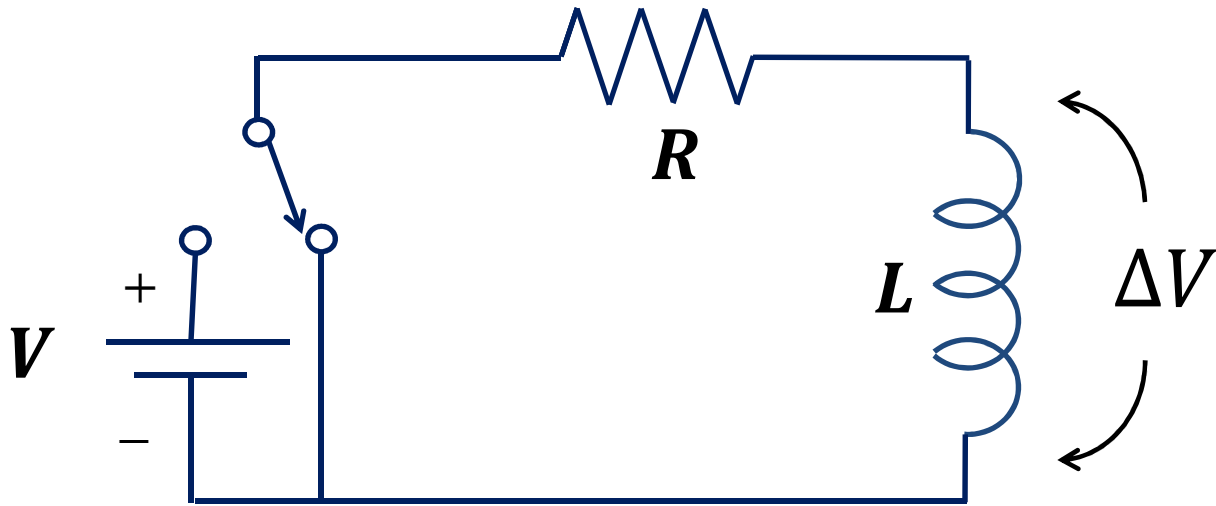


The current can still flow after the switch is flipped but now the voltage source isn't adding energy to the circuit.

- Initial current is  $I_0$
- Switched at  $t = 0$
- The inductor tries to keep the current flowing:


$$I(t) = I_0 e^{-t/\tau}$$

$$I = 0.368 I_0$$

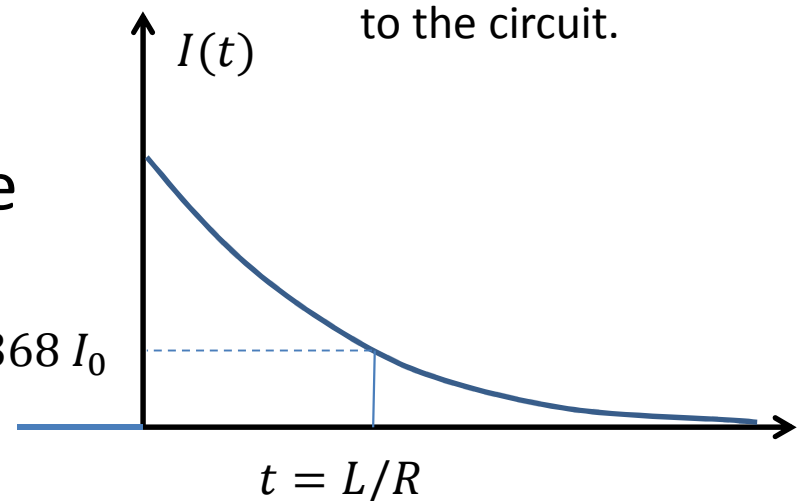




# Inductors in Circuits

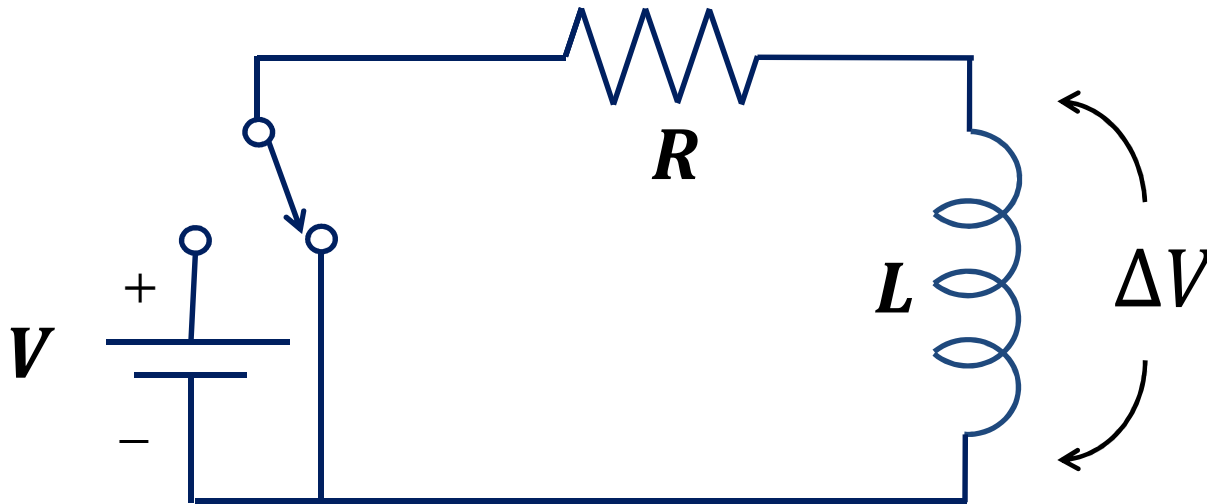

- What is the potential difference across the inductor after the switch is opened?

$$\Delta V(t) = V(1 - e^{-t/\tau})$$

$$\Delta V = 0.632 V$$

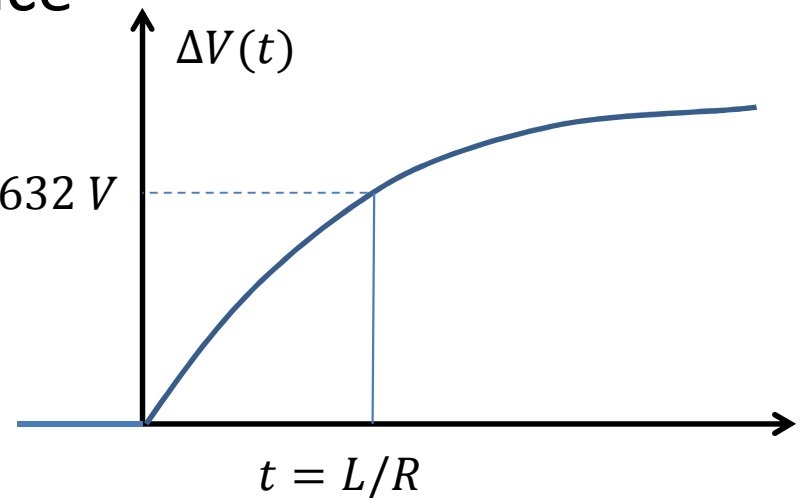

# Inductors in Series

- Putting two solenoids in series is like adding their lengths:  $L = \mu_0 n^2 \ell A$




$$L_{series} = L_1 + L_2 = \mu_0 n^2 A (\ell_1 + \ell_2)$$

Inductors in series add  
(just like resistors)

# Inductors in Parallel

- Use Kirchhoff's node rule:

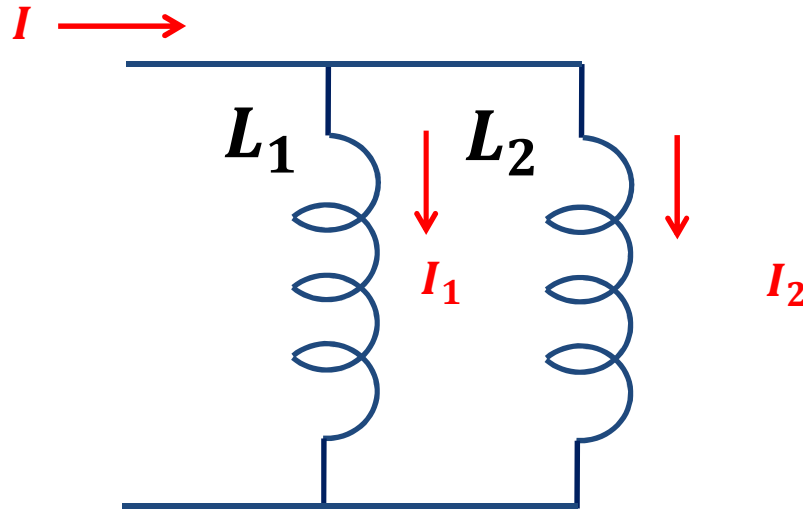

$$L_{\parallel} \frac{dI}{dt} = L_1 \frac{dI_1}{dt} = L_2 \frac{dI_2}{dt}$$


$$\frac{dI_1}{dt} = \frac{L_{\parallel}}{L_1} \frac{dI}{dt}$$

$$L_{\parallel} = \left( \frac{1}{L_1} + \frac{1}{L_2} \right)^{-1}$$

$$\frac{1}{L_{\parallel}} \frac{dI}{dt} = \frac{1}{L_{\parallel}} \left( \frac{dI_1}{dt} + \frac{dI_2}{dt} \right) = \left( \frac{1}{L_1} + \frac{1}{L_2} \right) \frac{dI}{dt}$$

# Mutual Inductance

- What if we had two loops?

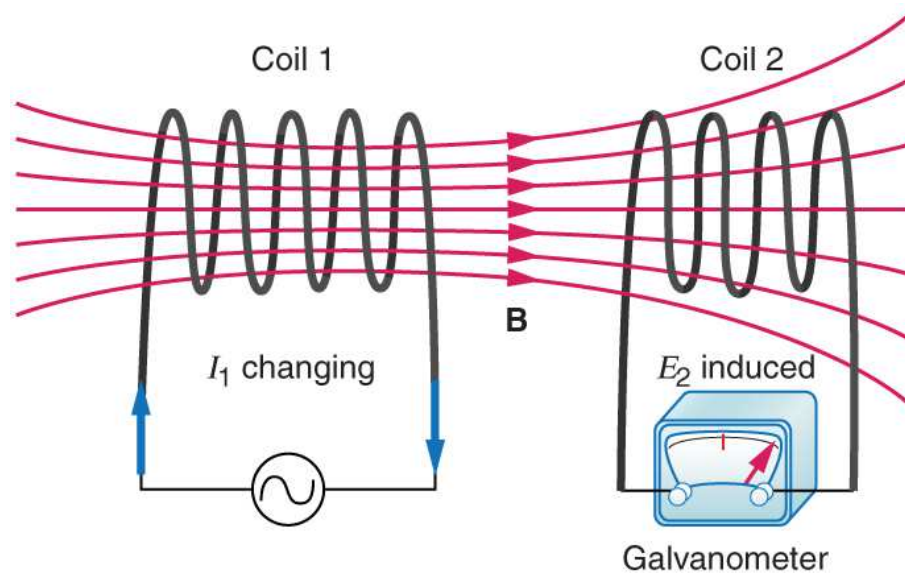


- In this case the flux through coil 2 is proportional to the current through coil 1.

$$\phi_2 \propto I_1 \quad \phi_2 = M_{12} I_1$$

- $M_{12}$  is called the “mutual inductance”

# Mutual Inductance

- Induced EMF from Faraday's Law...

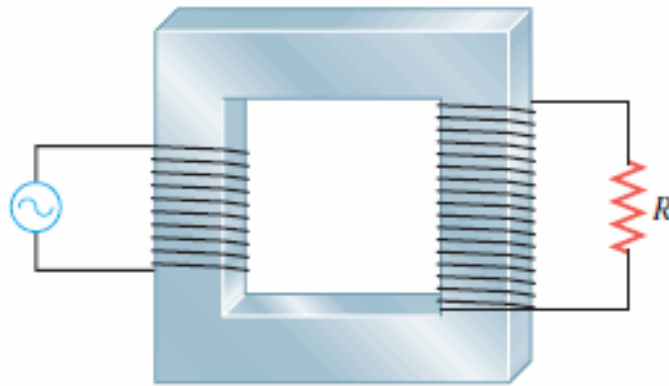

$$\mathcal{E}_2 = -\frac{d\phi_2}{dt} = -M_{12} \frac{dI_1}{dt}$$



- Important applications: Transformers
  - More on this later...


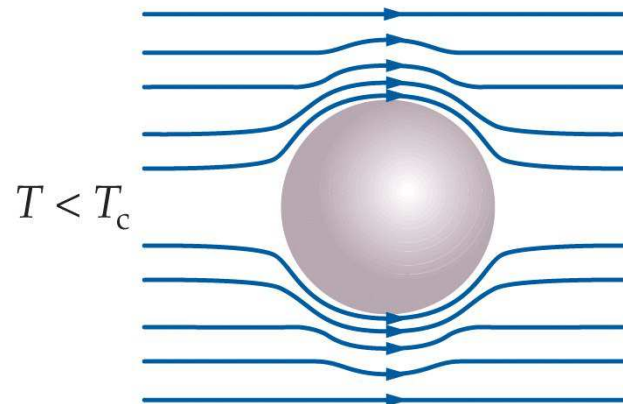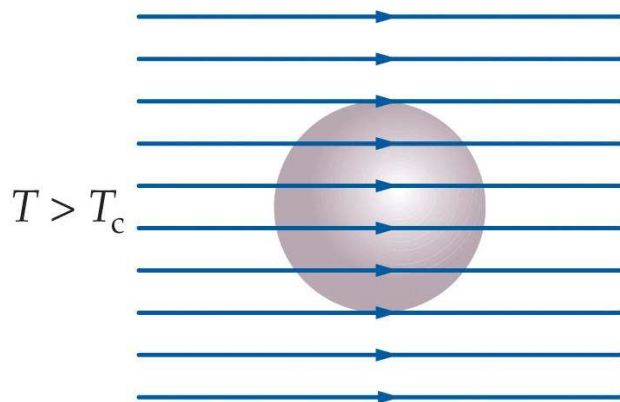
# Superconductors


- Below a critical temperature,  $T_c$ , a superconductor has zero resistance.
- A “Type I” superconductor is a perfect diamagnetic material:  $\chi_m = -1$
- When it is brought into a magnetic field, the induced current create an equal and opposite magnetic field

$$\vec{B} = \vec{B}_{app}(1 + \chi_m) = 0$$



# Superconductors

Magnet: NdFeB

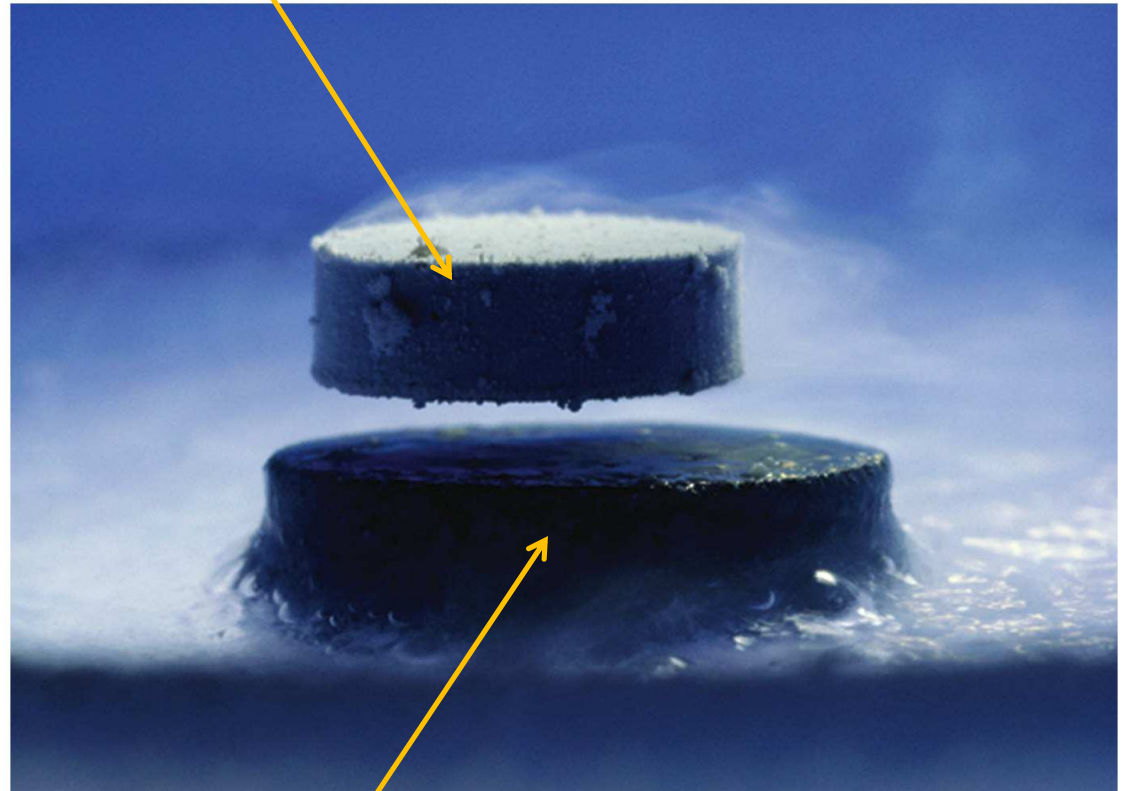

Superconductor: YBa<sub>2</sub>Cu<sub>3</sub>O<sub>7</sub>

# Question

- In which circuit will the light stay lit the longest when the circuit is switched at  $t = 0$ ?

