

Physics 42200


Waves & Oscillations

Lecture 17 – French, Chapter 6

Spring 2016 Semester

Other Continuous Systems



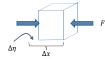


$$\frac{F}{A} = Y \frac{\Delta \eta}{\Delta x}$$

 $\frac{F}{A}=Y\;\frac{\Delta\eta}{\Delta x}$ Equal and opposite forces squish the cube of elastic material. Net force is zero so there is no acceleration.

$$F(x) = AY \frac{d\eta}{dx}$$

Other Continuous Systems



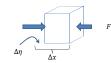


Suppose the force changes over distance Δx ...

$$F(x + \Delta x) = F(x) + \frac{dF}{dx} \Delta x$$

Net force is

$$F(x + \Delta x) - F(x) = \frac{dF}{dx} \Delta x = AY \frac{d^2 \eta}{dx^2} \Delta x$$


Other Continuous Systems

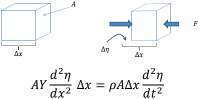

$$AY \frac{d^2\eta}{dx^2} \Delta x = \rho A \Delta x \frac{d^2\eta}{dt^2}$$
$$\frac{d^2\eta}{dx^2} = \frac{\rho}{Y} \frac{d^2\eta}{dt^2}$$


Electrical Circuits

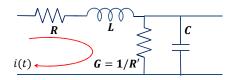• First, consider one "lump" of a circuit:



• It is convenient to describe the resistor that is in parallel with the capacitor in terms of its conductance, G=1/R'.

Electrical Circuits

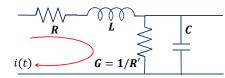

• Calculate the total impedance of the lump:

$$Z_R = R$$


$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$


$$\begin{aligned} X &= R + i\omega L & V(t) &= V_0 \, e^{i\omega t} \\ Y &= G + i\omega C & \Delta V(t) &= I(t) \, X \\ \Delta I(t) &= V(t) \, Y \end{aligned}$$

Electrical Circuits

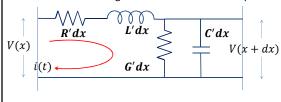- Suppose the resistance, inductance, capacitance and conductance were distributed uniformly with length:
 - Let R' be the resistance per unit length, L' be the inductance per unit length, etc...
- Consider the voltage on either side of the lump:



Electric Circuits

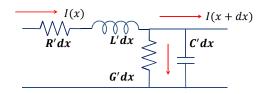


• Current flowing through G' and C' is
$$\Delta I = \frac{V(x)}{Z_{G+C'}} = V(x)Y$$

$$I(x+dx) = I(x) - V(x)Y$$

$$\frac{\partial I}{\partial x} = \frac{I(x+dx) - I(x)}{dx} = -V(x)Y$$

Electrical Circuits

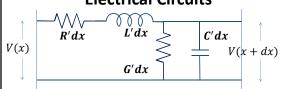

• Voltage drop across the lump:

e drop across the lump:

$$\frac{V(x + dx) = V(x) - I(x)X}{\partial x}$$

$$\frac{\partial V}{\partial x} = \frac{V(x + dx) - V(x)}{dx} = -I(x)X$$

$$\frac{\partial^2 V}{\partial x^2} = -\frac{\partial I}{\partial x}X = XYV(x)$$

Electrical Circuits

• When we assume that the voltage is of the form

$$V(x,t) = V(x)e^{i\omega t}$$

$$\frac{\partial^2 V}{\partial t^2} = -\omega^2 V(x)$$

• Using the previous result, $\frac{\partial^2 V}{\partial x^2} = XY \, V(x)$ we get: $\frac{\partial^2 V}{\partial x^2} + \frac{XY}{\omega^2} \frac{\partial^2 V}{\partial t^2} = 0$ • Does this recently $\frac{\partial^2 V}{\partial t^2} = 0$

$$\frac{\partial^2 V}{\partial x^2} + \frac{XY}{\omega^2} \frac{\partial^2 V}{\partial t^2} = 0$$

- Does this resemble the wave equation?
 - Expand out $XY = (R' + i\omega L')(G' + i\omega C')$
 - When R^\prime and G^\prime are small, which is frequently the case then $XY \approx -\omega^2 L'C'$

Electrical Circuits

• Wave equation:


$$\frac{\partial^2 V}{\partial x^2} = L'C' \frac{\partial^2 V}{\partial t^2} = \frac{1}{v^2} \frac{\partial^2 V}{\partial t^2}$$

• Speed of wave propagation is

$$v = \frac{1}{\sqrt{L'C'}}$$

Current in a Transmission Line

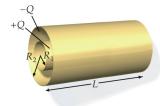- Speed of wave propagation depends on inductance per unit length and capacitance per unit length
- These depend on the geometry of the conductors
- Example:



Gauss's Law

Radius of Gaussian surface is \boldsymbol{r}





$$\oint_{S} \hat{n} \cdot \vec{E} \, dA = 2\pi r \ell E = \frac{Q_{inside}}{\epsilon_{0}}$$

ec E is uniform everywhere on the Gaussian surface E= Surface area is $A=2mr\ell$ Linear charge density: $\lambda=Q/\ell$

$$E = \frac{\lambda}{2\pi\epsilon_0 r}$$

Potential Difference and Capacitance

Work needed to move a charge between the conductors:

$$V = -\int_{R_2}^{R_1} \vec{E} \cdot d\vec{r} = -\frac{\lambda}{2\pi\epsilon_0} \int_{R_2}^{R_1} \frac{dr}{r}$$
$$= \frac{\lambda}{2\pi\epsilon_0} \log\left(\frac{R_2}{R_1}\right)$$

Capacitance is defined by C = Q/V

Charge inside is $Q = \lambda \ell$

Capacitance per unit length: $\mathcal{C}' = \frac{2\pi\epsilon_0}{\log\left(\frac{R_2}{R_1}\right)}$

Ampere's Law

Radius of Amperian surface is \boldsymbol{r}





Ampere's law: $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I$

 \vec{B} is uniform on the circular path of length $2\pi r$: $B = \frac{\mu_0 I}{2\pi r}$

$$B = \frac{\mu_0 I}{2\pi r}$$

Magnetic Flux and Inductance

Magnetic flux is defined:

$$\phi_m = \int_S \vec{B} \cdot d\vec{a} = \frac{\mu_0 I \ell}{2\pi} \int_{R_1}^{R_2} \frac{dr}{r} = \frac{\mu_0 I \ell}{2\pi} \log\left(\frac{R_2}{R_1}\right)$$

Inductance is defined: $\phi_m = LI$

Inductance per unit length: $L' = \frac{\mu_0}{2\pi} \log \left(\frac{R_2}{R_1}\right)$



Wave Propagation in a Coaxial Cable

- Capacitance per unit length: $C' = \frac{2\pi\epsilon_0}{\log(\frac{R_2}{R_*})}$
- Inductance per unit length: $L' = \frac{\mu_0}{2\pi} \log \left(\frac{R_2}{R_1}\right)$

- Speed of wave propagation:
$$v = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\epsilon_0\mu_0}} = c$$

• In practice, the conductors are separated by a dielectric with relative permittivity ϵ_r so the speed of wave propagation is $v=c/\sqrt{\epsilon_r}$

Transmission Lines

•	Coaxia	l:



$$\epsilon_r = 2.3, \qquad v = 0.66 c$$

Twisted pair:



$$\epsilon_r = 2.1, \qquad v = 0.69$$

• Microstrip:




v	≈	0.6 -	0.8 c

• Stripline:



Transmission Lines

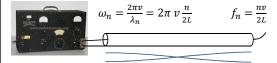- A transmission line can be driven by a voltage source at one end.
- Boundary conditions at the other end:
 - Open circuit: I(L) = 0
 - Short circuit: V(L) = 0




If $L=1\ m$ and $v=20\ cm/ns$...

n = 1

f = 100 MHz

Transmission Lines

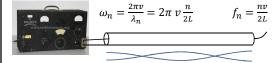- A transmission line can be driven by a voltage source at one end.
- Boundary conditions at the other end:
 - Open circuit: I(L) = 0
 - Short circuit: V(L) = 0




If $L=1\ m$ and $v=20\ cm/ns$...

n = 2

f = 200 MHz

Transmission Lines

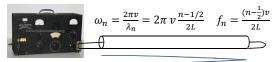- A transmission line can be driven by a voltage source at one end.
- Boundary conditions at the other end:
 - Open circuit: I(L) = 0
 - Short circuit: V(L) = 0




If $L=1\ m$ and $v=20\ cm/ns$...

n = 1

f = 50 MHz

Transmission Lines

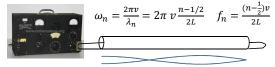- A transmission line can be driven by a voltage source at one end.
- Boundary conditions at the other end:
 - Open circuit: I(L) = 0
 - Short circuit: V(L) = 0



If $L=1\ m$ and $v=20\ cm/ns$...

$$n = 2$$
 $f = 150 \, MHz$

Fourier Analysis

- Wave equation: $\frac{\partial^2 y}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 y}{\partial t^2}$
- Normal modes:

$$f_n(x,t) = A_n \sin\left(\frac{n\pi x}{L}\right) \cos(\omega_n t - \delta_n)$$

(when $f_n(0,t) = f_n(L,t) = 0$)

- The general initial value problem specifies the initial displacement and velocity at $t=0\,$
- How can we represent the general solution as the sum of normal modes?

Fourier Analysis

• The general solution can be expressed

$$y(x,t) = \sum_{n=1}^{\infty} A_n \sin\left(\frac{n\pi x}{L}\right) \cos(\omega_n t - \delta_n)$$

• Initial conditions:

$$y(x,0) = u(x)$$
$$\dot{y}(x,0) = v(x)$$

- How do we determine the constants A_n and δ_n ?
- At t=0 the general solution looks like this:

$$y(x,t) = \sum_{n=1}^{\infty} B_n \sin\left(\frac{n\pi x}{L}\right)$$
 where $B_n = A_n \cos\delta_n$

Fourier Analysis

· Fourier transform:

$$B_k = \frac{2}{L} \int_0^L \sin\left(\frac{k\pi x}{L}\right) u(x) dx$$

- Really? Let's prove it by demonstration:
- At t=0, $u(x)=\sum_{n=1}^{\infty}B_{n}\sin\left(\frac{n\pi x}{L}\right)$ so we want to

$$\frac{2}{L} \int_{0}^{L} \sin\left(\frac{k\pi x}{L}\right) u(x) dx = \frac{2}{L} \sum_{n=1}^{\infty} B_{n} \int_{0}^{L} \sin\left(\frac{k\pi x}{L}\right) \sin\left(\frac{n\pi x}{L}\right) dx$$

Fourier Analysis

$$\sin \alpha \sin \beta = \frac{1}{2} (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\left(\frac{k\pi x}{L}\right) \sin\left(\frac{n\pi x}{L}\right) dx$$

$$1 \int_{-L}^{L} ((k - n)\pi x) \qquad 1 \int_{-L}^{L} ((k + n)\pi x)$$

Use the trigonometric identity:
$$\sin\alpha\sin\beta = \frac{1}{2}(\cos(\alpha-\beta)-\cos(\alpha+\beta))$$

$$\int_0^L \sin\left(\frac{k\pi x}{L}\right)\sin\left(\frac{n\pi x}{L}\right)dx$$

$$= \frac{1}{2}\int_0^L \cos\left(\frac{(k-n)\pi x}{L}\right)dx + \frac{1}{2}\int_0^L \cos\left(\frac{(k+n)\pi x}{L}\right)dx$$

$$= \frac{L}{2(k-n)\pi}\sin((k-n)\pi) + \frac{L}{2(k+n)\pi}\sin((k+n)\pi)$$
 This vanishes unless $k=n$ in which case,
$$\frac{1}{2}\int_0^L \cos\left(\frac{(k-n)\pi x}{L}\right)dx \to \frac{1}{2}\int_0^L dx = \frac{L}{2}$$
 So we write:

$$\frac{1}{2} \int_0^L \cos\left(\frac{(k-n)\pi x}{L}\right) dx \to \frac{1}{2} \int_0^L dx = \frac{L}{2}$$

$$\frac{2}{L} \int_{0}^{L} \sin\left(\frac{k\pi x}{L}\right) \sin\left(\frac{n\pi x}{L}\right) dx = \delta_{kn}$$

$$\delta_{kn} = \begin{cases} 0 \text{ if } k \neq n \\ 1 \text{ if } k = n \end{cases}$$

Fourier Analysis

With this result, we can write
$$\frac{2}{L} \int_0^L \sin\left(\frac{k\pi x}{L}\right) u(x) dx = \frac{2}{L} \sum_{n=1}^{\infty} B_n \int_0^L \sin\left(\frac{k\pi x}{L}\right) \sin\left(\frac{n\pi x}{L}\right) dx$$
$$= \sum_{n=1}^{\infty} B_n \, \delta_{kn} = B_k$$

Example

 How to describe a square wave in terms of normal modes:

lodds:


$$u(x) = \begin{cases} +1 \text{ when } 0 < x < \lambda/2 \\ -1 \text{ when } \lambda/2 < x < \lambda \end{cases}$$

$$B_n = \frac{2}{\lambda} \int_0^{\lambda/2} \sin(nkx) dx - \frac{2}{\lambda} \int_{\frac{\lambda}{2}}^{\lambda} \sin(nkx) dx$$

$$= \frac{2}{n\pi} [1 - \cos(n\pi)]$$

$$B_1 = \frac{4}{\pi}, B_3 = \frac{4}{3\pi}, B_5 = \frac{4}{5\pi}, \cdots$$

Example

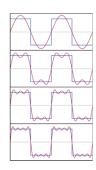

$$B_n = \frac{2}{n\pi} [1 - \cos(n\pi)]$$

$$B_1 = \frac{4}{\pi}, B_3 = \frac{4}{3\pi}, B_5 = \frac{4}{5\pi}, \cdots$$

$$B_2 = 0, B_4 = 0, B_6 = 0, \cdots$$