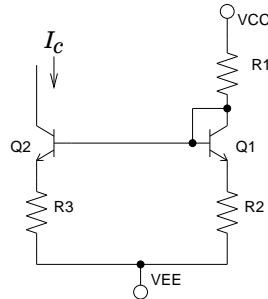



## Physics 536 - Assignment #7

1. Consider the current mirror circuit shown below:



Determine appropriate values for  $R_1$ ,  $R_2$  and  $R_3$  that will produce  $V_b = -5$  V and give  $I_c = 10$  mA when  $V_{CC} = +10$  V and  $V_{EE} = -10$  V. A reasonable choice for the current that will flow through  $Q_1$  is 1 mA. Assume that  $V_{be} = 0.7$  V.

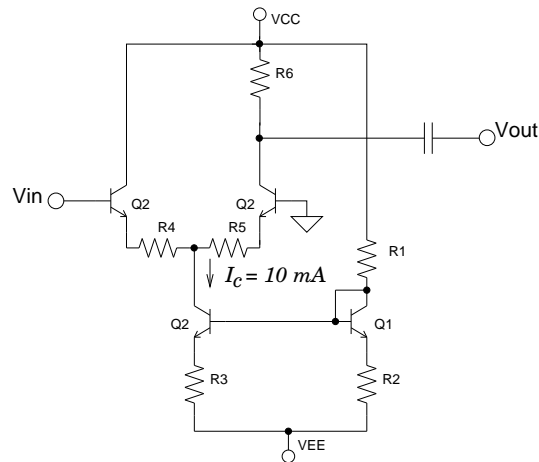
2. Suppose the current mirror described in question 1 was used as a current source in the differential pair amplifier shown below:



Suppose the component values were  $R_4 = R_5 = 50 \Omega$  and  $R_6 = 500 \Omega$  and that the capacitor is large enough that it does not change the shape of the output waveform.

- (a) Show that the small signal gain of this circuit is  $G = +5$ .
- (b) What is the output impedance of this circuit?
- (c) If the circuit were connected to a resistive load,  $R_L = 5 \text{ k}\Omega$ , what would be the amplitude of the voltage,  $v_L$ , measured across the load, in terms of  $v_{in}$ ?

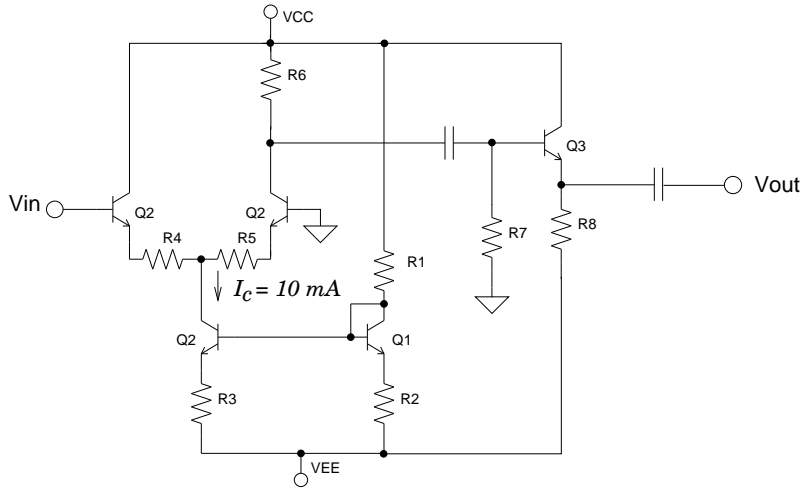3. Suppose the output of the previous circuit was connected to an emitter follower using a transistor with  $\beta = 100$  as shown below, in which  $R_7 = 100\text{ k}\Omega$  and  $R_8 = 1\text{ k}\Omega$ . The purpose of  $R_7$  is to keep the base of  $Q_3$  at a well defined DC voltage.



- (a) What is the output impedance of this amplifier circuit?
- (b) If a resistive load of  $R_L = 500\ \Omega$ , what would be the amplitude of the voltage,  $v_L$ , measured across the load?