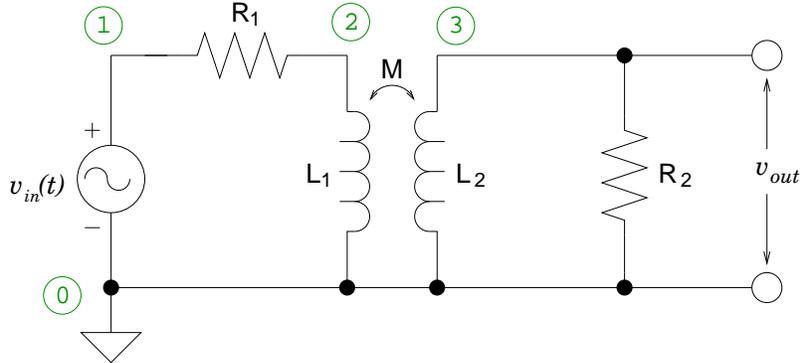


Physics 536 - Assignment #4 - Due February 15th

1. Consider the following transformer circuit:



(a) Show that the exact expression for the voltage gain is given by

$$A = \frac{|V_{out}|}{|V_{in}|} = \frac{n}{\sqrt{\left(1 + n^2 \frac{R_1}{R_2}\right)^2 + \left(\frac{R_1}{\omega L_1}\right)^2}} \quad (1)$$

where $n = n_2/n_1 = \sqrt{L_2/L_1}$ and where we assume perfect coupling between the two coils in the transformer, *ie.* $M = \sqrt{L_1 L_2}$.

(b) Describe the low-frequency and high-frequency behavior of this circuit and calculate the frequency, $\omega_{-3 \text{ db}}$, at which $A(\omega_{-3 \text{ db}}) = A_{\text{max}}/\sqrt{2}$.

(c) Suppose that $R_1 = 50 \Omega$, $R_2 = 100 \Omega$. What value of n will maximize the power dissipated in R_2 at high frequencies?

(d) In this case, what value of L_1 would be required to give $f_{-3 \text{ db}} = 1 \text{ MHz}$ where $\omega = 2\pi f$? What value of L_2 would then be required to give the desired value of n ?

(e) Use SPICE to perform an AC sweep analysis of the circuit using the component values determined in part (d). In SPICE, the transformer in this circuit is described using *coupled inductors* as follows:

```
L1  2  0  value
L2  3  0  value
K12 L1 L2  k
```

in which k is the constant in the expression $M = k\sqrt{L_1 L_2}$. For ideal coupling, as is the case in this problem, use $k = 1$.

Hand in the graph of the magnitude of the voltage across R_2 as a function of frequency, between 1 Hz and 10 MHz. Verify that $f_{-3 \text{ db}}$ occurs at the frequency calculated in part (d).