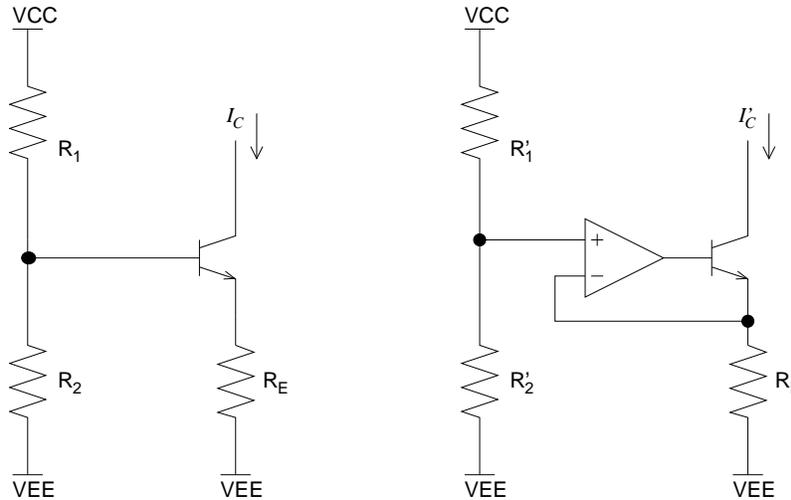


## Physics 536 - Assignment #8 - Due April 7<sup>th</sup>

1. Consider the following two current source circuits, in which  $V_{CC} = 10\text{ V}$  and  $V_{EE} = -10\text{ V}$ :




- (a) Derive the relationship between the values of  $R_1$ ,  $R_2$  and  $R_E$  that will produce a desired current  $I_C$  in the circuit on the left.
- (b) Derive the relationship between the values of  $R'_1$ ,  $R'_2$  and  $R'_E$  that will produce a desired current  $I'_C$  on the right.
- (c) What is the advantage of using the circuit on the left when a load applied to the current source changes at a high frequency?
- (d) What is the advantage of using the circuit on the right when the current  $I'_C$  is constant but the temperature of the circuit changes?

2. Determine the values of the resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  that will produce the linear relationship between the input and output voltages:

$$V_{out} = a + bV_{in} \tag{1}$$

in the following circuit:

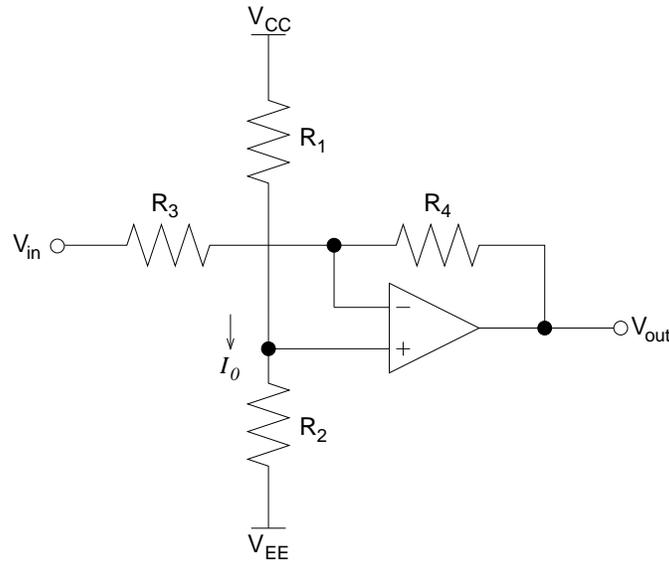


As a constraint, suppose that the current used by the voltage divider between  $V_{CC}$  and  $V_{EE}$  specified to be  $I_0$ .

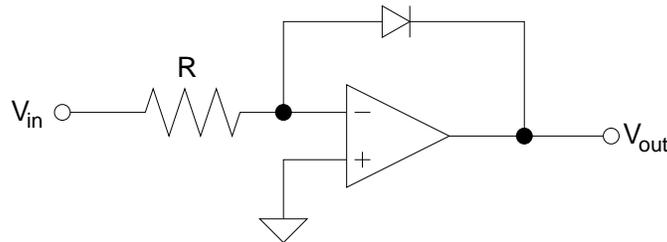
3. The relationship between the current,  $I$ , through the diode and the voltage drop,  $V$ , across it is

$$I = I_0 e^{V/kT} \quad (2)$$

when  $I \gg I_0$ . Determine the relation between  $V_{out}$  and  $V_{in}$  in the following *logarithmic amplifier* op-amp configuration:



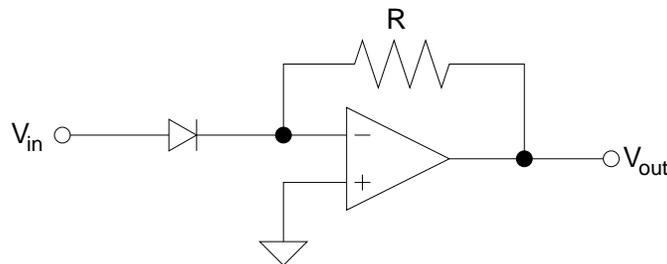4. Determine the relation between  $V_{out}$  and  $V_{in}$  in the following *exponential amplifier* op-amp configuration:



5. Describe qualitatively how to construct a circuit that produces an output voltage that is proportional to the *product* of two input voltages. Sketch the circuit configuration that would achieve this, but do not explicitly calculate any component values.