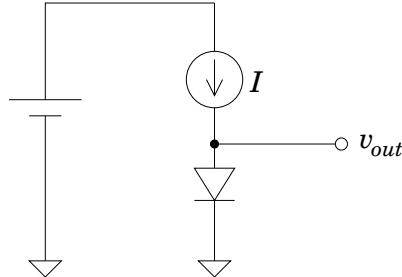



## Physics 536 - Assignment #5

1. Consider the following circuit consisting of a diode and a current source.




- (a) If the diode has a reverse saturation current of  $I_0 = 10^{-10}$  A, and the current source provides  $I = 10$  mA, calculate the voltage  $v_{out}$  as a function of temperature,  $T$ .
- (b) If the current through the diode provided by the current source fluctuates by a small amount,  $\delta I$ , what would the resulting fluctuation in  $v_{out}$  be?

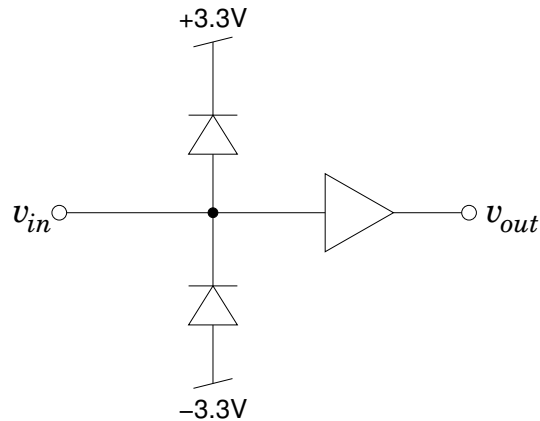2. A sensitive amplifier uses two diodes for input protection as shown:



Assuming  $V_D \approx 0.7$  V, what are the maximum and minimum input voltages that will be presented at the input to the amplifier?

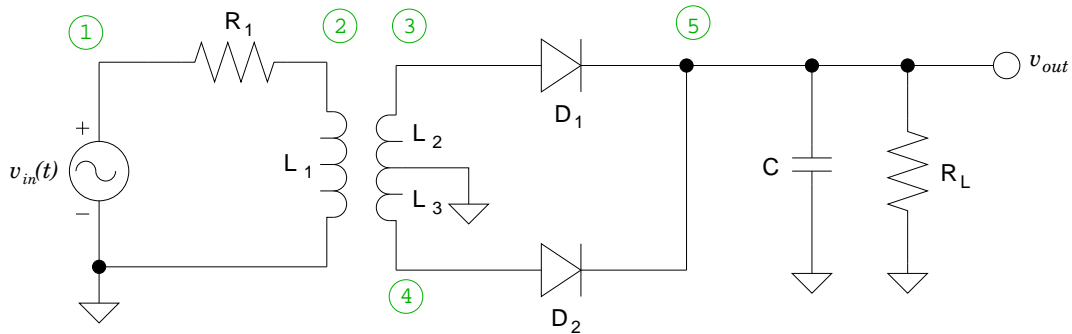3. Consider the following a power supply circuit:



This circuit can be modeled using SPICE in the following way:

- $v_{in}(t)$  represents a 60 Hz, 110 VAC (RMS) power source, modeled using:  
VIN 1 0 0 AC SIN(0 160V 60Hz 0 0)
- $R_1$  is a *small* resistance (eg,  $R_1 \sim 0.1 \Omega$ ), intended only to ensure numerical stability of the simulation. However, it could also represent a finite impedance of the voltage source.
- $L_1$ ,  $L_2$  and  $L_3$  represent a center-tapped transformer. Such a transformer with a 10:1 turns ratio can be represented in terms of coupled inductors using:

```
L1 2 0 1MH
L2 3 0 10UH
L3 0 4 10UH
K1 L1 L2 0.99
K2 L1 L3 0.99
K3 L2 L3 0.99
```

- Assume that  $D_1$  and  $D_2$  are 1N4001 rectifier diodes which have properties described by the SPICE model:

```
.MODEL D1N4001 D IS=29.5E-9 RS=73.5E-3 N=1.96 CJO=34.6P VJ=0.627
+M=0.461 BV=60 IBV=10U
```

and which can then be included in the netlist using the following statements:

```
D1 3 5 D1N4001
D2 4 5 D1N4001
```


- Suppose the capacitor has a capacitance of  $1000 \mu\text{F}$ .

(a) Perform a transient analysis of this circuit using


```
.TRAN 1MS 500MS 0 100US
```

for  $R_L = 1000 \Omega$ ,  $100 \Omega$  and  $10 \Omega$ . Provide the graphs of the output voltage,  $v_{out}$  as a function of time and tabulate the average voltage and amplitude of the ripple for each value of  $R_L$ .

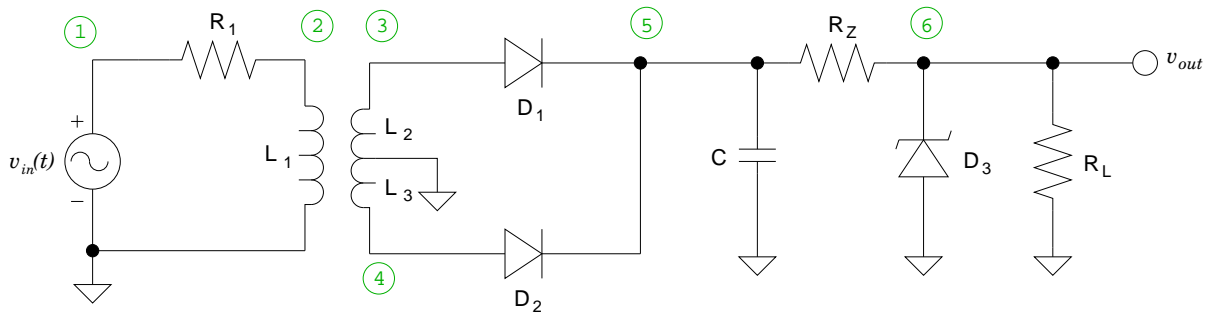(b) Next, consider the following circuit which uses a zener diode to provide a stable voltage reference:



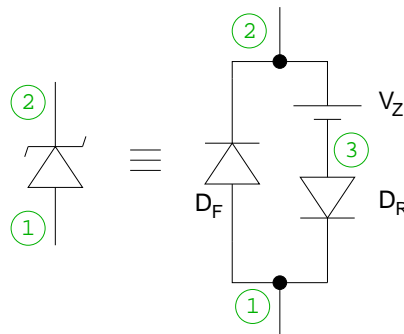Suppose the zener diode,  $D_3$ , is a 1N4740A device, which has a zener voltage of  $V_Z = 10 \text{ V}$  at  $I_Z = 25 \text{ mA}$ . If the load resistance is  $R_L = 1 \text{ k}\Omega$ , calculate the maximum value for  $R_Z$  that will allow the  $D_3$  to provide a stable voltage  $v_{out}$ . The zener diode can be modeled by the equivalent subcircuit:



in which  $D_F$  represents the behavior when the zener diode is forward biased and  $D_R$  in series with  $V_Z$  represent the behavior when the zener diode is reverse biased, as it would normally be operated. The SPICE subcircuit that describes the 1N4740A zener diode is

```
.SUBCKT DI_1N4740A 1 2
* Terminals A K (K is the pointy end)
D1 1 2 DF
DZ 3 1 DR
VZ 2 3 9.02
.MODEL DF D ( IS=41.2p RS=0.620 N=1.10 CJO=68.9p VJ=0.750 M=0.330 TT=50.1n )
.MODEL DR D ( IS=8.24f RS=0.403 N=1.30 )
.ENDS
```

which can then be included in the netlist for the power supply using

```
X1 0 6 DI_1N4740A
```

Simulate the circuit shown above using  $R_L = 1 \text{ k}\Omega$  and using the value for  $R_Z$  calculated above and provide a graph of the voltage  $v_{out}(t)$ .

(c) Calculate the current through the zener diode when  $R_L = 400 \Omega$  and  $200 \Omega$  and provide graphs to demonstrate that the zener diode fails to provide a stable voltage reference with these loads.