

Physics 536 - Assignment #6

1. The 2N5457 field effect transistor can be described in SPICE using the model


```
.MODEL 2N5457 NJF(IS=1N VT0=-1.5 BETA=1.125M LAMBDA=2.3M CGD=4PF CGS=5PF)
```

which can then be included in a circuit netlist using

```
J1 d g s 2N5457
```

in which *d*, *g* and *s* are the drain, gate and source nodes, respectively. Use the following circuit configuration to determine the parameters I_{DSS} and V_P in the formula


$$I_D = I_{DSS} \left(1 + \frac{V_{GS}}{|V_P|} \right)^2 \quad (1)$$

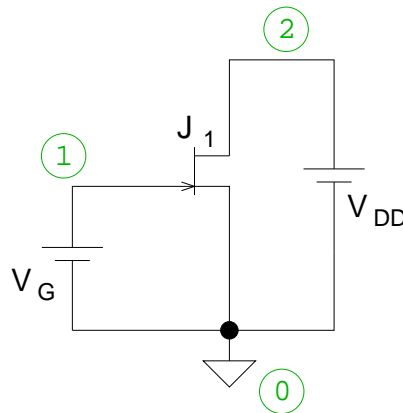

A graph of I_D as a function of V_G can be obtained using the SPICE statements

```
.DC VG <vstart> <vstop> <vstep>
.PRINT DC I(VDD)
```

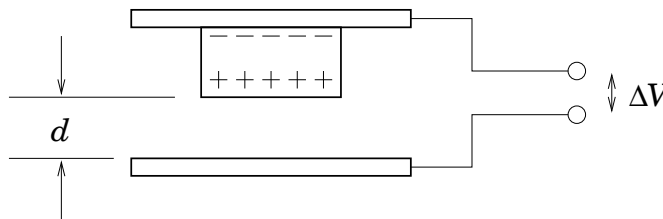2. An *electret* is like a magnet, except that instead of providing a permanent magnetic field, it sets up a permanent electric field by means of permanently polarizing its constituent molecules along a particular direction. An *electret microphone* is constructed by placing an electret between two parallel plates as shown:




This configuration is essentially a capacitor with but with a charge Q_0 permanently stored on its plates. As such, changes in the plate separation, d , due to sound pressure, change the voltage across the plates since

$$\Delta V = \frac{Q_0}{C} = \frac{Q_0 d}{\epsilon_0 A} \quad (2)$$

However, the output impedance of this device is very large – the capacitance is quite small and the time constant, RC , needs to be much larger than the period of pressure oscillations or else charge will redistribute and cancel any voltage across the plates. Therefore, an electret microphone requires a high-impedance preamplifier to produce a voltage source that can drive subsequent stages of a circuit.

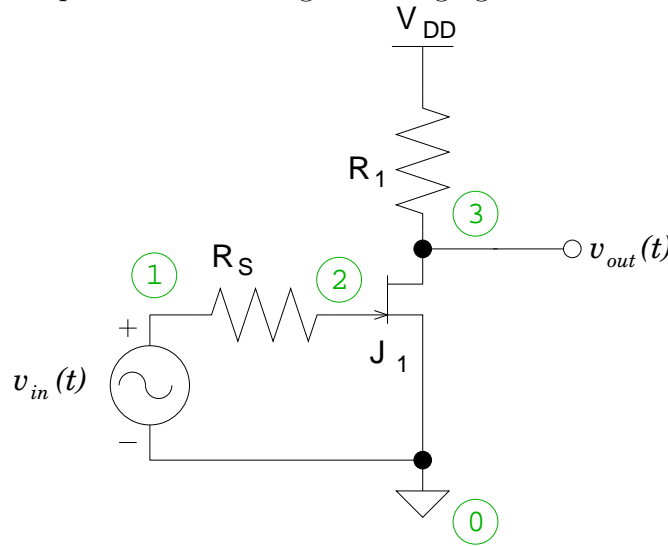(a) Model the electret microphone as an ideal AC voltage source with a frequency of 5 kHz and an amplitude of 1 mV in series with an impedance of $R_S = 100 \text{ k}\Omega$. In the following circuit, calculate the value of R_1 that should provide a small signal voltage gain of -10 at v_{out} .



(b) What voltage, V_{DD} , will be required to ensure that the field effect transistor is in the active region?


(c) Perform a small signal transfer function analysis using the SPICE statement

```
.TF V(3) VIN
```

to calculate the voltage gain and output impedance.


(d) Adjust the value of R_1 and V_{DD} to obtain a voltage gain that is close to the desired value of $A = -10$.

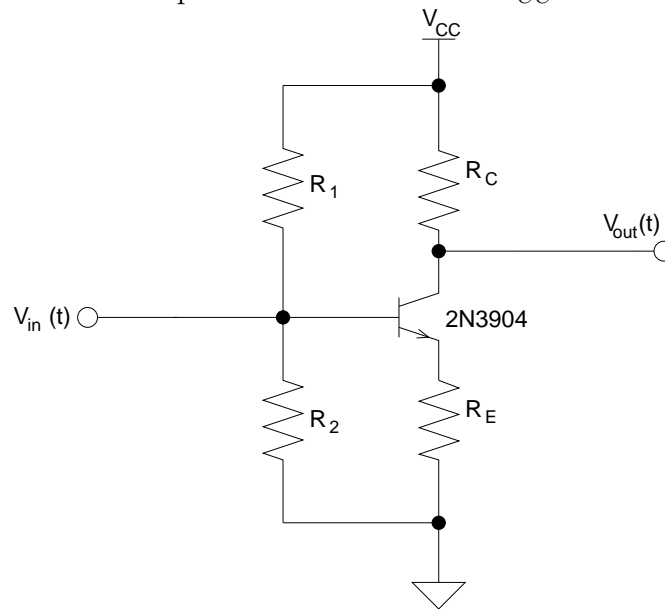3. Consider the common emitter amplifier circuit for which $V_{CC} = 10\text{ V}$:



- (a) Calculate the values of R_1 and R_2 that will bias the base of the transistor at a voltage of $V_B = 2\text{ V}$ and provide an input impedance of $3\text{ k}\Omega$. Ignore any current that flows into the base.
- (b) Assuming $V_{be} \approx 0.7\text{ V}$, calculate the value of R_E that will produce a quiescent current of 5 mA through the transistor.
- (c) Calculate the value of R_C will produce a small signal voltage gain of $A = -5$. What is the largest value of R_C and consequently, the largest small signal voltage gain, that can be obtained at this operating point?
- (d) If the output of the amplifier design in question 2 were capacitively coupled to the input of the common emitter amplifier designed above, what would the overall voltage gain of the two-stage amplifier be? Explain your reasoning.

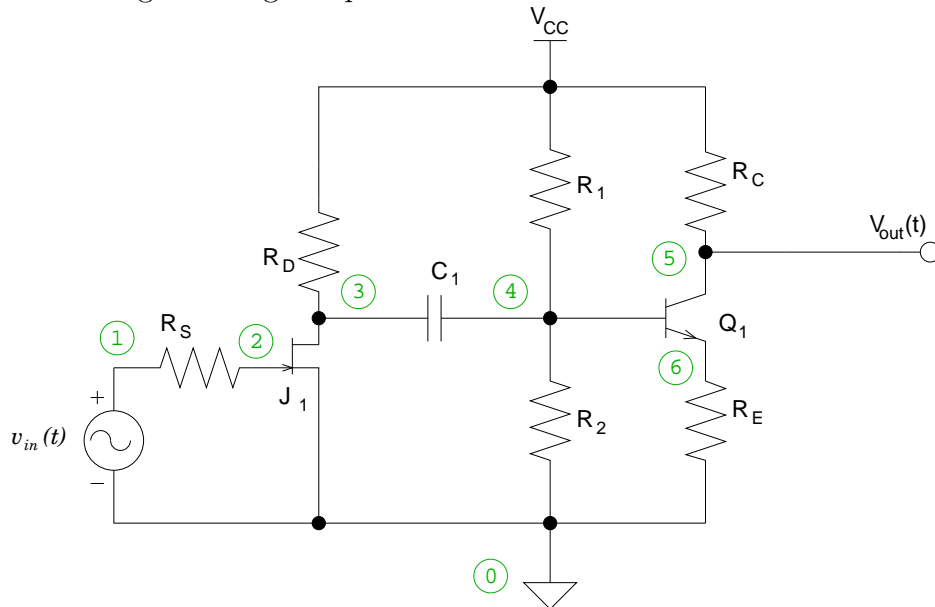4. Consider the following two-stage amplifier circuit:



for which $V_{CC} = 10 \text{ V}$, $R_D = 3 \text{ k}\Omega$, $R_1 = 15 \text{ k}\Omega$, $R_2 = 3.75 \text{ k}\Omega$, $R_E = 220 \Omega$, $R_C = 1200 \text{ k}\Omega$ and $C_1 = 1 \mu\text{F}$.

(a) Perform an small signal AC analysis of this circuit using SPICE, plotting the voltage gain measured at $v_{out}(t)$ over the frequency range 1 Hz to 1 MHz. Use the model for the 2N5457 field effect transistor from question 1 for J_1 and the following 2N3904 model for Q_1 :

```
*
* SPICE model for 2N3904/MMBT3904 transistor
*
.MODEL 2N3904 NPN(IS=4.639E-15 NF=0.9995 ISE=2.091E-14 NE=1.6 BF=160.1 IKF=0.12
+ VAF=98.69 NR=1.001 ISC=3.257E-12 NC=1.394 BR=5.944 IKR=0.06
+ VAR=19.29 RB=1 IRB=1E-6 RBM=1 RE=0.3614 RC=1.755 XTB=0
+ EG=1.11 XTI=3 CJE=5.631E-12 VJE=0.7002 MJE=0.3385
+ TF=3.001E-10 XTF=27 VTF=1.461 ITF=0.2723 PTF=0 CJC=4.949E-12
+ VJC=0.5969 MJC=0.1928 XCJC=0.864 TR=9.4E-8 CJS=0 VJS=0.75
+ MJS=0.333 FC=0.5582)
```

which can be included in the netlist using

```
Q1 c b e 2N3904
```

in which c, b and e are the collector, base and emitter nodes, respectively. For your convenience, you can download the text for this model from

http://www.physics.purdue.edu/~mjones/phys536/2N3904_model.txt

(b) At what frequencies is the gain reduced by a factor of $1/\sqrt{2}$ compared to the maximum gain? What component values influence the low-frequency cutoff? Compare this with the calculated low-frequency -3 dB frequency. What effects limit the high-frequency cutoff?