Physics 536 - Summary of ODE's for RLC circuits.

The RLC circuit discussed in class led to the integral-differential equation

$$L\frac{di}{dt} + Ri(t) + \frac{1}{C}\left(Q_0 + \int_0^t i(t)dt\right) = V \tag{1}$$

but by differentiating once we obtained

$$L\frac{d^{2}i}{dt^{2}} + R\frac{di}{dt} + \frac{1}{C}i(t) = 0$$
(2)

which is a *linear*, second-order, homogeneous differential equation with constant coefficients. One can hypothesize that a solution to this differential equation might be of the form $i(t) = e^{\alpha t}$ which can be substituted into the equation to discover what conditions the constant α must satisfy. Thus,

$$\frac{di}{dt} = \alpha i(t) \tag{3}$$

$$\frac{d^2i}{dt^2} = \alpha^2 i(t) \tag{4}$$

and therefore, $(L\alpha^2 + R\alpha + 1/C)i(t) = 0$. Since $i(t) \neq 0$, α must be a root of the polynomial

$$L\alpha^2 + R\alpha + 1/C = 0. \tag{5}$$

These roots are

$$\alpha_{+} = \frac{-R}{2L} + \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$
(6)

$$\alpha_{-} = \frac{-R}{2L} - \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}.$$
(7)

and a general solution to the differential equation is

$$i(t) = Ae^{\alpha_+ t} + Be^{\alpha_- t} \tag{8}$$

where A and B are constants of integration.

The algebraic sign of the expression $R^2/4L^2 - 1/LC$ determins whether the roots are purely real or whether they are complex numbers.

If $R^2/4L^2 \ll 1/LC$, then $\alpha_{\pm} \approx -\gamma \pm i\omega_0$ where

$$\gamma = \frac{R}{2L} \tag{9}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}.$$
 (10)

and the general solution can be expressed in the form

$$i(t) = Ae^{-\gamma t} \cos \omega_0 t + Be^{-\gamma t} \sin \omega_0 t \tag{11}$$

The constants of integration can be determined by substituting this form of the solution into the original equation and solving for A and B so as to satisfy the initial conditions. In the case where the current is initially zero and $Q_0 = 0$, we have

$$LB\omega_0 = V \tag{12}$$

from which we obtain $B = V/L\omega_0 = V\sqrt{C/L}$. Thus, the complete solution is

$$i(t) = \begin{cases} 0 & \text{for } t < 0\\ V\sqrt{\frac{C}{L}}e^{-\gamma t}\sin\omega_0 t & \text{for } t > 0. \end{cases}$$
(13)