

Physics 536 - Formula Sheet - v1.0

Kramer's rule:

$$\begin{pmatrix} a & b \\ c & d \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} v_1 \\ v_2 \end{pmatrix} \quad (1)$$


$$i_1 = \frac{\begin{vmatrix} v_1 & b \\ v_2 & d \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}} = \frac{dv_1 - bv_2}{ad - bc} \quad (2)$$

$$i_2 = \frac{\begin{vmatrix} a & v_1 \\ c & v_2 \end{vmatrix}}{\begin{vmatrix} a & b \\ c & d \end{vmatrix}} = \frac{av_2 - cv_1}{ad - bc} \quad (3)$$

Definitions:

$$\text{Voltage gain in dB: } G = 20 \log_{10}(A) \quad (4)$$


Resistors:

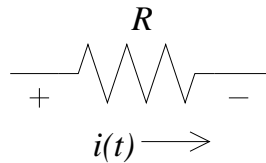

$$\Delta v(t) = i(t)R \quad (5)$$

$$\Delta V = IR \quad (6)$$


Capacitors:

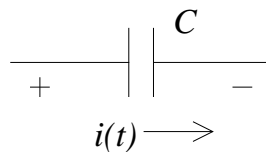

$$\Delta v(t) = \frac{1}{C} \left(Q_0 + \int_0^t i(t) dt \right) \quad (7)$$

$$\Delta V = \frac{I}{i\omega C} \quad (8)$$


Inductors:

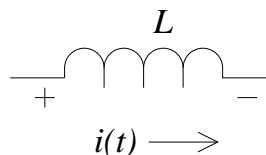

$$\Delta v(t) = L \frac{di}{dt} \quad (9)$$

$$\Delta V = i\omega LI \quad (10)$$

Transformers:

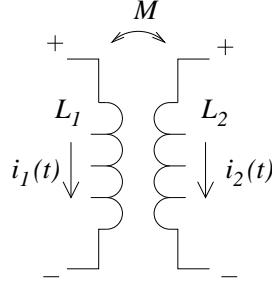

$$\Delta v_1(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad (11)$$

$$\Delta v_2(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \quad (12)$$

$$\Delta V_1 = i\omega L_1 I_1 + i\omega M I_2 \quad (13)$$

$$\Delta V_2 = i\omega L_2 I_2 + i\omega M I_1 \quad (14)$$

$$M = k\sqrt{L_1 L_2} \quad (15)$$

Transmission lines:

$$\frac{\partial^2 V}{\partial x^2} + \gamma^2 V(x, t) = 0 \quad (16)$$

$$\frac{\partial^2 I}{\partial x^2} + \gamma^2 I(x, t) = 0 \quad (17)$$

$$I(x, t) = Ae^{\gamma x + i\omega t} + Be^{-\gamma x + i\omega t} \quad (18)$$

$$V(x, t) = -Z_0(Ae^{\gamma x + i\omega t} - Be^{-\gamma x + i\omega t}) \quad (19)$$

$$\gamma = \sqrt{(R' + i\omega L')(G' + i\omega C')} = \alpha + i\beta \quad (20)$$

$$v = \frac{\omega}{\beta} \approx \frac{c}{\sqrt{\epsilon_r}} \quad (21)$$

$$Z_0 = \sqrt{\frac{R' + i\omega L'}{G' + i\omega C'}} \quad (22)$$

$$I_+(x, t) = \frac{V_0}{Z_S + Z_0} \frac{e^{-\gamma x}}{1 - \Gamma_S \Gamma_L e^{-2\gamma \ell}} \quad (23)$$

$$I_-(x, t) = \frac{V_0 \Gamma_L e^{-2\gamma \ell}}{Z_S + Z_0} \frac{e^{\gamma x}}{1 - \Gamma_S \Gamma_L e^{-2\gamma \ell}} \quad (24)$$

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} \quad (25)$$

$$(26)$$