

Student's Name:

Student's Name:

Lab day & time: _____

Date: _____

Alternating Current Circuits (E6B) - Data Sheets

Write all results on the data sheets in ink.

Activity 1: Time Constant for RL Circuits

(1.5 p.)

- 1.2. Read the exact value of the DC voltage V (should be close to 4.50 V) and the maximum value of the current I_{max} .

$$V = \text{_____} (\quad) \quad I_{max} = \text{_____} (\quad)$$

Use Ohm's law to calculate the resistance (R) of the coil and the 10.0 Ω resistor connected in series.

$$R = R_{total} = R_{resistor} + R_{coil} = \text{_____} (\quad) \quad R_{resistor} = 10.0 (\Omega)$$

The resistance of the coil attached to the “RLC Circuit” board.

$$R_{coil} = \text{_____} (\quad)$$

- 1.4. To select points that computer needs for the fit click anywhere on the “Current in the Coil” graph to make it active and use the “Highlight range of points” tool . The fitting parameter “ B ” for the coil and 10.0 Ω resistor connected in series.

$$"B" = \text{_____} (\quad) \quad I(t) = A * \exp(-Bt)$$

What is the unit for the fitting parameter “ B ”?

Print the graph for 10.0 Ω resistor and label it “Time constant #1”.

The time constant τ for the RL circuit $\tau = \text{_____} (\quad) = L_1/R_{total}$

- 1.5. The inductance of the coil attached to the RLC board $L_1 = \text{_____} (\quad)$

- 1.6. Calculate the potential energy PE_{ind} stored in the coil's magnetic field when the current is running through the coil and 10.0 Ω resistor (before the external voltage is turned off). Use

equation (5) and the average value of the coil inductance L_{AV} . The current I_{max} was measured in step 1.2.

$$PE_{ind} = \text{_____} (\quad)$$

- 1.7. Calculate the resistance R in the RL circuit.

$$R_{resistor} = 33.0 (\Omega) \quad R = R_{total} = R_{resistor} + R_{coil} = \text{_____} (\quad)$$

- 1.8. The fitting parameter "B" = _____ (\quad)

The time constant τ for the RL circuit $\tau = \text{_____} (\quad) = L_2/R_{total}$

The inductance of the coil attached to the RLC board $L_2 = \text{_____} (\quad)$

Should the value of inductance L_2 be similar to the inductance measured using the RL circuit with 10.0 Ω resistor (L_1)? _____

- 1.9. Calculate the average value of the coil inductance L_{AV} .

$$L_{AV} = (L_1 + L_2)/2 = \text{_____} (\quad)$$

- 1.10. Calculate the potential energy PE_{ind} stored in the coil's magnetic field when the current is running through the coil and 33.0 Ω resistor (before the external voltage is turned off). Use equation (5) and the average value of the coil inductance L_{AV} . The current I_{max} was measured in step 1.2.

$$PE_{ind} = \frac{1}{2} L_{AV} I_{max}^2 = \text{_____} (\text{J})$$

Activity 2: Impedance as a Function of Frequency for RL Circuits (1 p.)

The RL circuit includes now:

- $R_{resistor} = 10.0 \Omega$;
- a coil with inductance L_{AV} and resistance R_{coil} (measured in the previous Activity);
- no capacitors.

- 2.1. Calculate the resistance R in the RL circuit. Use the value of the coil resistance R_{coil} from Activity 1.

$$R_{resistor} = 10.0 (\Omega) \quad R = R_{resistor} + R_{coil} = \text{_____} (\quad)$$

- 2.3. Use equation (10) to describe what would be the expected change in the impedance Z when the frequency f increases. You need to analyze parts of the equation and explain how they contribute to the conclusion, which could be: an *increase of the impedance* or a *decrease of the impedance*.

- 2.4. Read and record the amplitude of current - “Maximum Current” and the amplitude of voltage - “Maximum Voltage” (this should be very close to 4.5 V). Calculate the measured value of the impedance Z using Eq. (8).

| Frequency f (Hz) | Voltage Amplitude V_{max} (V) | Current Amplitude I_{max} (A) | Measured Impedance Z (Ω) |
|-------------------------|---|---|---|
| 100 | | | |
| 200 | | | |
| 300 | | | |
| 400 | | | |
| 500 | | | |
| 600 | | | |
| 800 | | | |
| 1000 | | | |

- 2.5. Change the frequency f to the next value in the table and repeat measurements.

Activity 3: Impedance as a Function of Frequency for RC Circuits

(1 p.)

The RC circuit includes now:

- $R_{resistor} = 33.0 \Omega$;
- no coil; Inductance: $L = 0 \text{ (H)}$
- $C = 100 \mu\text{F}$ capacitor.

3.1. Calculate the resistance R in the RC circuit.

$$R = R_{resistor} = 33.0 \text{ (}\Omega\text{)} \text{ (no coil in the circuit)}$$

$$\text{Capacitance: } C = 100 \text{ (}\mu\text{F)}$$

$$\text{Inductance: } L = 0 \text{ (H)} - \text{the coil is bypassed with a jumper cable}$$

3.3. Use equation (13) to describe what would be the expected change in the impedance Z when the frequency f increases. You need to analyze parts of the equation and explain how they contribute to the conclusion, which could be: an *increase of the impedance* or a *decrease of the impedance*.

3.4. Read and record the amplitude of current - “Maximum Current” and the amplitude of voltage - “Maximum Voltage” (this should be very close to 5.0 V). Calculate the measured value of the impedance Z using Eq. (8).

| Frequency f (Hz) | Voltage Amplitude V_{max} (V) | Current Amplitude I_{max} (A) | Measured Impedance Z (Ω) |
|-----------------------|---------------------------------------|---------------------------------------|---|
| 10 | | | |
| 20 | | | |
| 30 | | | |
| 40 | | | |
| 50 | | | |
| 60 | | | |
| 80 | | | |

| | | | |
|-----|--|--|--|
| 100 | | | |
| 150 | | | |
| 200 | | | |

Activity 4: Resonance in RLC Circuits

(1 p.)

This time the RLC circuit includes:

- no external resistors;
- a coil with inductance L_{AV} and resistance R_{coil} ;
- $C = 100 \mu\text{F}$ capacitor.

- 4.1. **Remove** the "bypass" wire connecting terminals **A** and **B**. Calculate the resistance R in the single-loop RLC circuit. Move the wire from terminal **D** to terminal **A** on the board.

$R_{resistor} = 0 (\Omega)$ $R = R_{coil} = \underline{\hspace{2cm}}$ () (no external resistors) R_{coil} was measured in Activity 1.

Capacitance: $C = 100 (\mu\text{F})$ Inductance: $L = L_{AV} = \underline{\hspace{2cm}}$ ()

- 4.3. Read and record the amplitude of current - "Maximum Current" and the amplitude of voltage - "Maximum Voltage" (this should be very close to 1.50 V). Calculate the measured value of the impedance Z using Eq. (8).

| Frequency f (Hz) | Voltage Amplitude V_{max} (V) | Current Amplitude I_{max} (A) | Measured Impedance Z (Ω) |
|-----------------------|---------------------------------------|---------------------------------------|---|
| 100 | | | |
| 120 | | | |
| 140 | | | |
| 160 | | | |
| 170 | | | |
| 180 | | | |

| | | | |
|-----|--|--|--|
| 190 | | | |
| 200 | | | |
| 220 | | | |
| 240 | | | |
| 260 | | | |
| 280 | | | |

- 4.4. Change the frequency f to the next value (120 Hz) and repeat measurements and calculations listed in step 4.3.
- 4.5. Prepare a graph of the measured impedance Z versus the frequency f . **Print** the graph and attach it to your lab report. Find the frequency that corresponds to the minimum impedance, i.e., find the resonance frequency f_{res} .

$$f_{res} = \text{_____} (\quad)$$

- 4.6. Calculate the theoretical value of the resonance frequency f_0 according to Eq. (17).

$$f_0 = \text{_____} (\quad)$$

Calculate the percent difference between the measured resonance frequency f_{res} and the theoretical resonance frequency f_0 .

$$\frac{|f_{res} - f_0|}{f_0} \times 100\% = \text{_____} (\quad \%)$$

- 4.7. Disconnect all wires from the “RLC Circuit” board.

Complete the lab report and return it to the lab TA.