

II.) Currents


A) Electric current, i , is the rate at which charge is transported through a given surface

$$i = \frac{dq}{dt}$$

1) SI units: $[i] = 1 \text{ Ampere} = 1 \frac{\text{Coulomb}}{\text{Second}}$

2) Convention: Current is in the direction of positive charge flow.


3) Current obeys scalar addition

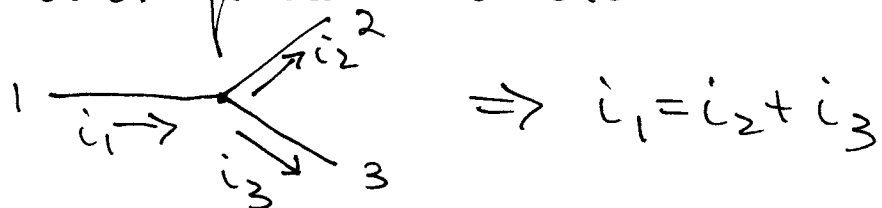

B) Conducting medium: free electron gas model electrons move at constant drift velocity $\vec{v}_d$ when an $\vec{E}$ -field is established in conducting wire

1) Suppose conducting medium has one type of charge carrier q with $N = \frac{\text{\# of charge carriers}}{\text{Volume}}$ each has drift velocity $\vec{v}_d$ in an $\vec{E}$ -field

- II B) 1)

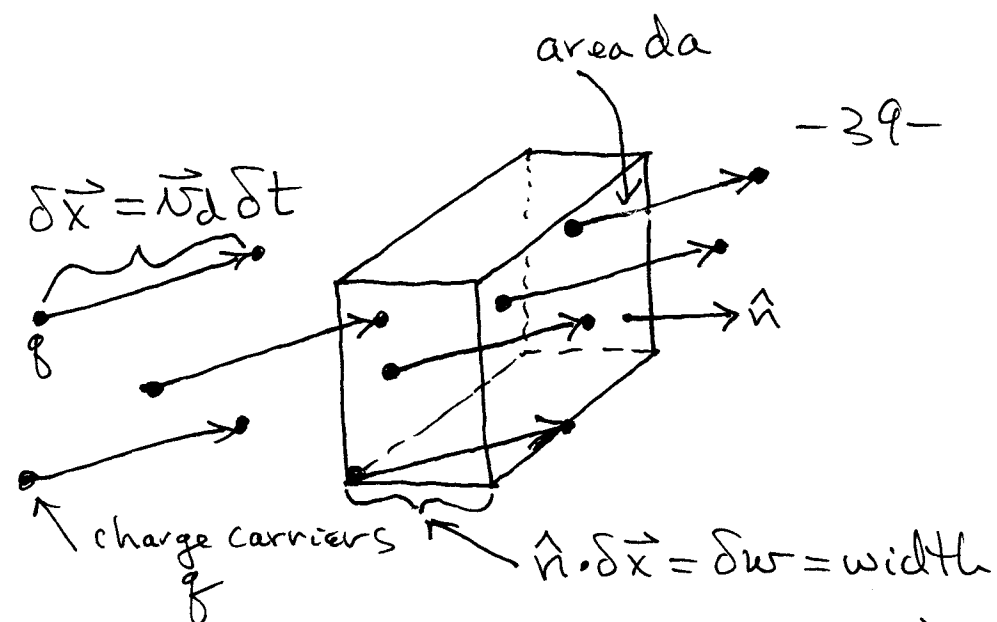

In time δt , each charge carrier moves $\delta \vec{x} = \vec{v}_d \delta t$.
 Charge δQ passes through area da in time δt

$$\delta Q = (qN)(\delta \vec{x} \cdot \hat{n} da)$$

$$= qN \vec{v}_d \cdot d\vec{A} \delta t \quad \text{where } d\vec{A} = da \hat{n}$$

Hence, di = current transported through da

$$di = \frac{\delta Q}{\delta t} = Nq \vec{v}_d \cdot d\vec{A}$$


$$\boxed{di = \vec{j} \cdot d\vec{A}}$$

With the current density $\vec{j} \equiv Nq \vec{v}_d$

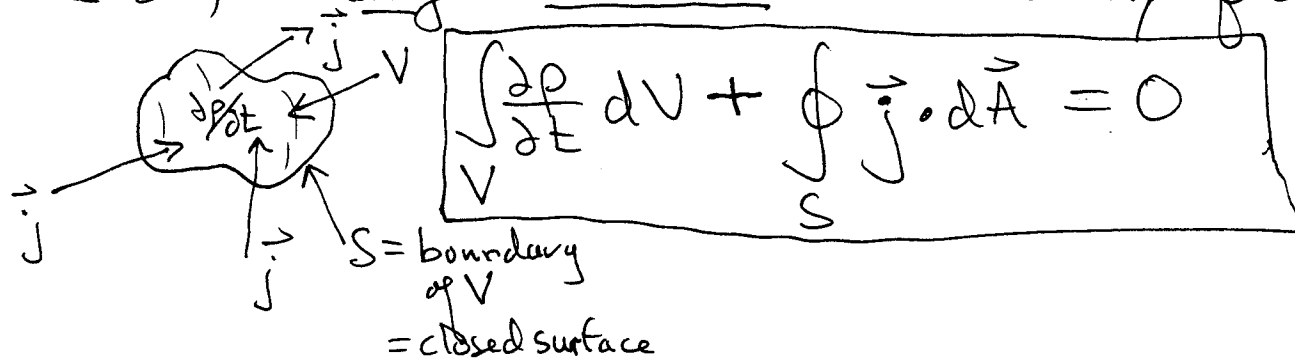2) Current flowing through an arbitrarily shaped surface S of macroscopic size

$$i = \int_S \vec{j} \cdot d\vec{A}$$

II B3) Charge Conservation = Continuity Equation



$$\int_V \frac{\partial \rho}{\partial t} dV + \oint_S \vec{j} \cdot d\vec{A} = 0$$

$S = \text{boundary of } V$
 $= \text{closed surface}$

C) Ohm's Law: Linear, isotropic conducting medium


$$\vec{j} = \sigma \vec{E}$$

$\sigma = \text{conductivity of material}$

1) SI units: $1 \text{ ohm } (\Omega) \equiv 1 \frac{\text{Volt}}{\text{Ampere}}$

$$[\sigma] = \Omega^{-1} \text{m}^{-1}$$

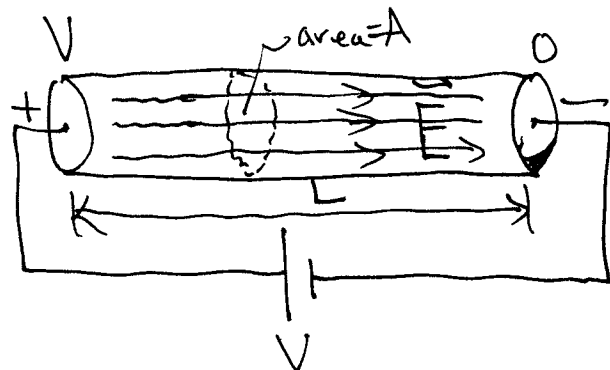2) Wire of conductivity σ , length L , cross sectional area A



$$\begin{aligned} V &= + \int_0^L \vec{E} \cdot d\vec{s} \\ &= EL \\ \Rightarrow E &= \frac{V}{L} \end{aligned}$$

II.C.) 2) $i = \int_A \vec{j} \cdot d\vec{A} = jA = \sigma EA = \left(\sigma \frac{A}{L} \right) V$ -41-
 $\Rightarrow$ $V = iR$ Macroscopic Ohm's Law $\underbrace{\left(\sigma \frac{A}{L} \right)}_{\equiv R^{-1}}$

a) SI units of R : $[R] = \text{ohm}$

b) $\rho \equiv \frac{1}{\sigma} = \text{resistivity of material}$
 $R = \frac{\rho L}{A}$ $[\rho] = \Omega \cdot \text{m}$

c) Circuit Symbol for Resistor 

D) Work done by $\vec{E}$ -field in moving dQ through potential difference V

$$dW = dQ V = i dt V$$

Rate of energy transfer = Power P

$P = \frac{dW}{dt} = iV$


(Units:
1 Amp·Volt
= 1 watt)

i) For Ohmic Device $V = iR$
 $\Rightarrow P = iV = i^2 R = \frac{V^2}{R}$

II.E.) Electromotive Force (emf) $\mathcal{E}$

$$\mathcal{E} = \frac{dW}{dq}$$

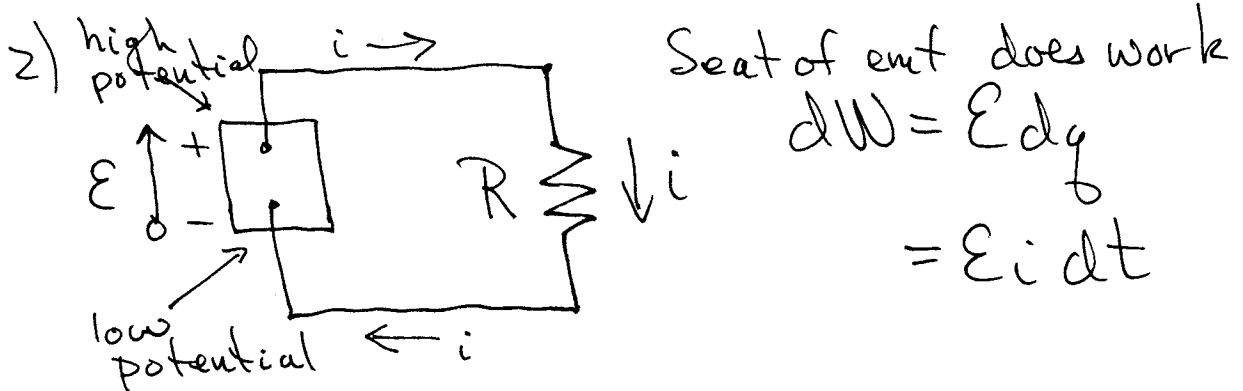1) SI units: $[\mathcal{E}] = 1 \frac{\text{Joule}}{\text{Coulomb}} = 1 \text{ Volt.}$




Conservation of energy: $\mathcal{E} i dt = i^2 R dt$
 $\Rightarrow i = \mathcal{E} / R$

3) Kirchhoff's ~~Second~~ Rule (Loop Rule):
 (Conservation of energy)

The algebraic sum of the changes in potential encountered in a complete traversal of any closed circuit is zero.

4) Internal resistance of seat of emf

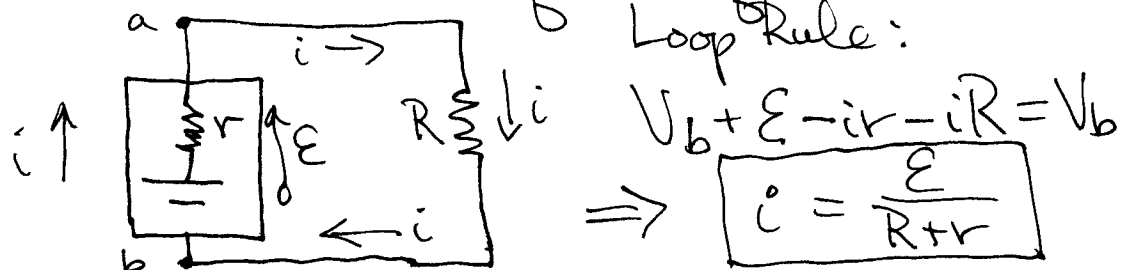


II E.4.) Potential Difference V_{ab} : traverse part of circuit by any path that includes the two points a & b

$$\begin{aligned} \left. \begin{array}{l} \text{a) Start at b} \\ \text{and go CCW} \\ \text{to a} \end{array} \right\} & V_b + iR = V_a \\ & \Rightarrow V_a - V_b \equiv V_{ab} = iR \\ & = \mathcal{E} \frac{R}{R+r} \end{aligned}$$

$$\begin{aligned} \left. \begin{array}{l} \text{b) Start at a} \\ \text{and go CCW} \\ \text{to b} \end{array} \right\} & V_a + ir - \mathcal{E} = V_b \\ & \Rightarrow V_{ab} = \mathcal{E} - ir = \mathcal{E} \frac{R}{R+r} \end{aligned}$$

the same as above.

5.) Example

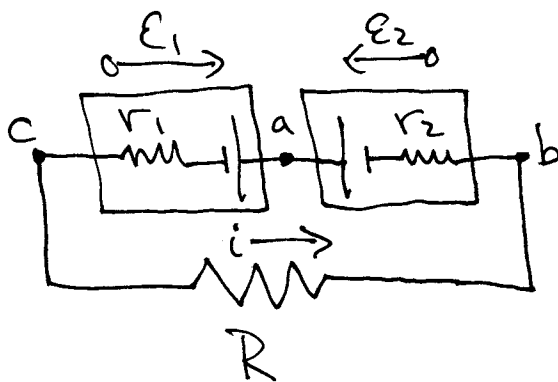

a) $i = ?$ Loop Rule: Start at "a" go CW back to "a"

$$-\mathcal{E}_2 + ir_2 + iR + ir_1 + \mathcal{E}_1 = 0$$

$$\Rightarrow \boxed{i = \frac{\mathcal{E}_2 - \mathcal{E}_1}{R + r_1 + r_2}}$$

II E5) a) The sign of i tells its direction of flow

b) $V_{ab} = ?$ Start at "b" go CCW to "a"

$$V_b - ir_2 + \mathcal{E}_2 = V_a$$

$$\Rightarrow \boxed{\begin{aligned} V_{ab} &= -ir_2 + \mathcal{E}_2 \\ &= \frac{\mathcal{E}_1 r_2 + \mathcal{E}_2 (R + r_1)}{R + r_1 + r_2} \end{aligned}}$$


c) $V_{ac} = ?$ Start at "c" go CW to "a"

$$V_c + ir_1 + \mathcal{E}_1 = V_a$$

$$\Rightarrow \boxed{\begin{aligned} V_{ac} &= \mathcal{E}_1 + ir_1 \\ &= \frac{\mathcal{E}_1 (R + r_2) + \mathcal{E}_2 r_1}{R + r_1 + r_2} \end{aligned}}$$


F) Equivalent Resistance

1) Resistors in Parallel

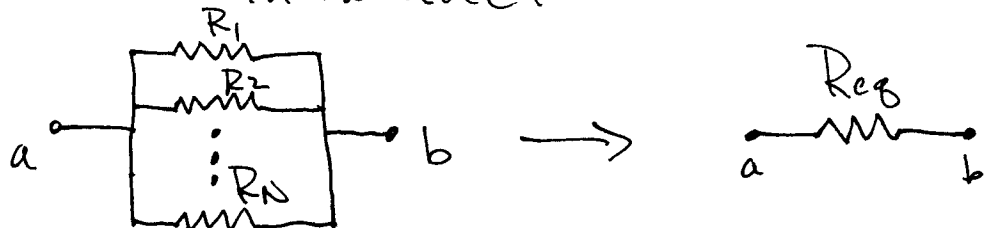



II F1)
$$\frac{1}{R_{eq}} = \sum_{i=1}^N \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

2) Resistors in Series

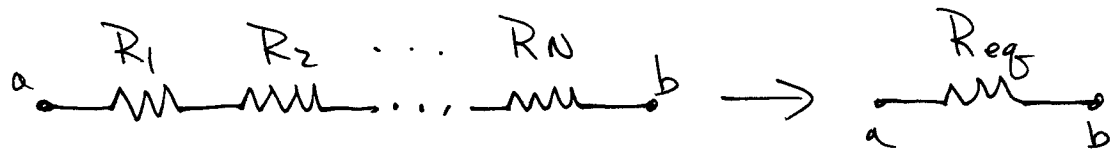


$$R_{eq} = \sum_{i=1}^N R_i = R_1 + R_2 + \dots + R_N$$

3) Example

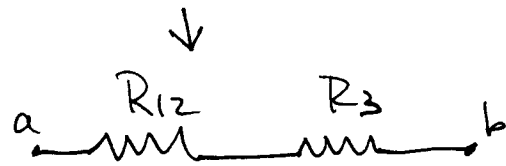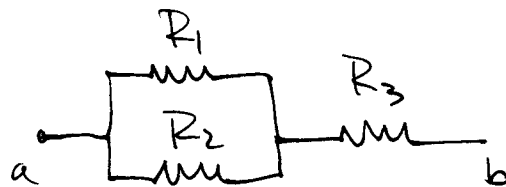


$$R_{12} = \frac{R_1 R_2}{R_1 + R_2}$$

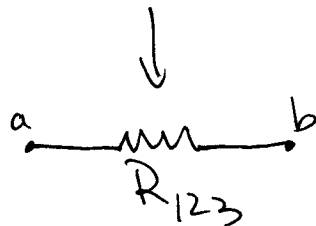


$$R_{123} = R_{12} + R_3 = \frac{R_1 R_2}{R_1 + R_2} + R_3$$

$i_1 = ?$

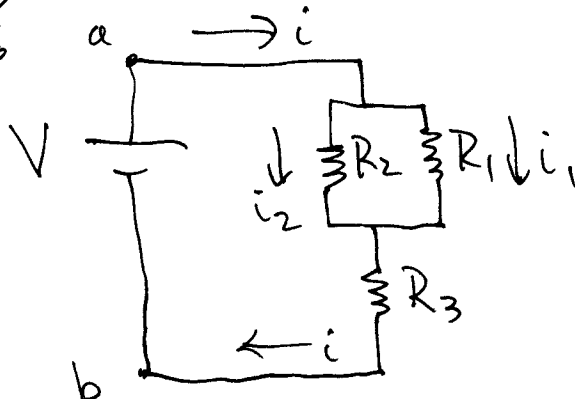


Steps:

a)
$$i = \frac{V}{R_{123}}$$

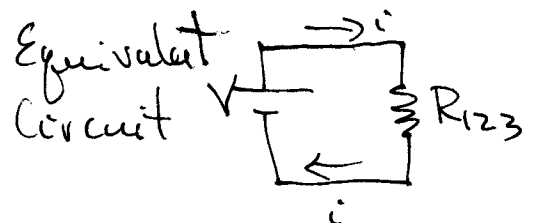

II F3) b) Equivalent Circuit

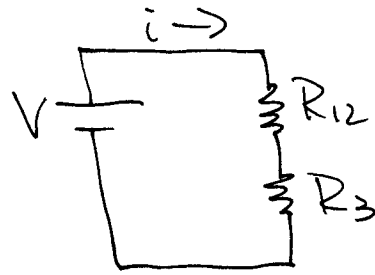

$$V_{12} = i R_{12}$$

c) Since R_1 & R_2 are in $\parallel$, V_{12} is the voltage that appears across both — so
 $(V_1 = V_2 = V_{12})$

$$\begin{aligned} i_1 &= \frac{V_{12}}{R_1} \\ &= \frac{V R_{12}}{R_1 R_{123}} \end{aligned}$$


G) Multiloop Circuits: Made up of junctions and branches

Junction = 3 or more wire segments meet
 Branch = Circuit path that starts at one junction and ends at another.

1) Kirchhoff's First Rule (Junction Rule)
 (Conservation of Charge)

At any junction, the sum of the currents leaving the junction equals the sum of the currents entering the junction.

- II G2) Example:

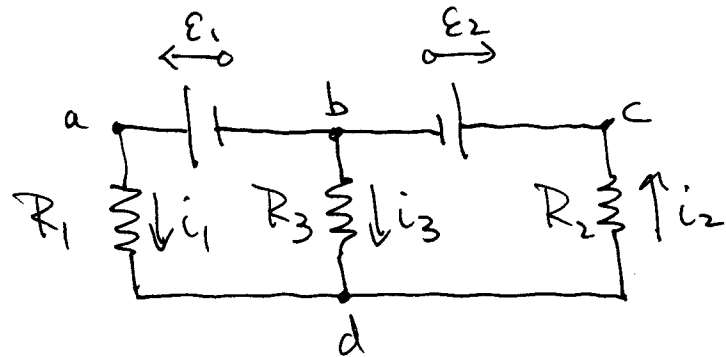

a) 2 Junctions b & d

b) 3 Branches: Left Branch bad
Central Branch bd
Right Branch bcd

Find i_1, i_2, i_3 :

1) Apply Junction Rule to d $\Rightarrow$

$$i_1 + i_3 = i_2$$

2) Apply Loop Rule: CCW b-a-d-b

$$\mathcal{E}_1 - i_1 R_1 + i_3 R_3 = 0$$

3) Apply Loop Rule: CCW b-d-c-b

$$-i_3 R_3 - i_2 R_2 - \mathcal{E}_2 = 0$$

$\Rightarrow$ 3 equations for 3 unknowns i_1, i_2, i_3
(Use either junction to apply junction rule, get same equation, use any 2 independent loops, get same information)

- II G2) Solve 3 simultaneous equations


$$i_3 = - \frac{R_2 \mathcal{E}_1 + R_1 \mathcal{E}_2}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

(negative result
 $\Rightarrow i_3$ flows from
 $d \rightarrow b$ opposite
 how we drew)

$$i_2 = \frac{\mathcal{E}_1 R_3 - \mathcal{E}_2 (R_1 + R_3)}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

$$i_1 = \frac{\mathcal{E}_1 (R_2 + R_3) - \mathcal{E}_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

3) Example:

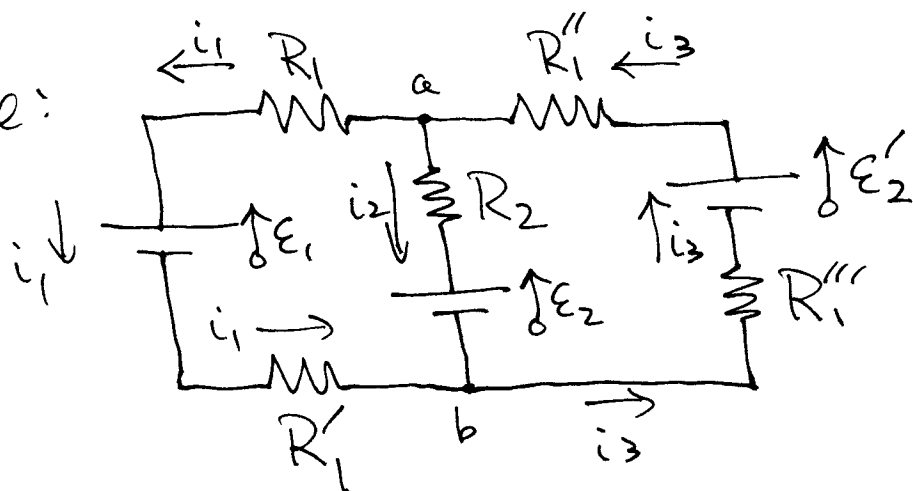

1) Apply Junction Rule at b

$$i_1 + i_2 = i_3$$

2) Apply Loop Rule: CCW a-b-a (Left Loop)

$$-i_1 R_1 - \mathcal{E}_1 - i_1 R_1' + \mathcal{E}_2 + i_2 R_2 = 0$$

$$(if R_1' = R_1 \Rightarrow 2i_1 R_1 - i_2 R_2 = \mathcal{E}_2 - \mathcal{E}_1)$$

II G3) 3) Apply Loop Rule: CW a-b-a (Right Loop)


$$i_3 R_1'' - \mathcal{E}_2' + i_3 R_1''' + \mathcal{E}_2 + i_2 R_2 = 0$$

$$(if R_1'' = R_1''' = R_1 \text{ and } \mathcal{E}_2' = \mathcal{E}_2 \Rightarrow i_2 R_2 + 2 i_3 R_1 = 0)$$

Hence we have 3 equations for the 3 unknowns i_1, i_2, i_3 — solve simultaneously:
(See class notes for solution and $V_a - i_2 R_2 - \mathcal{E}_2 = V_b \Rightarrow V_{ab} = \mathcal{E}_2 + i_2 R_2$)

H) Measuring Instruments:

i) Ammeter measures current

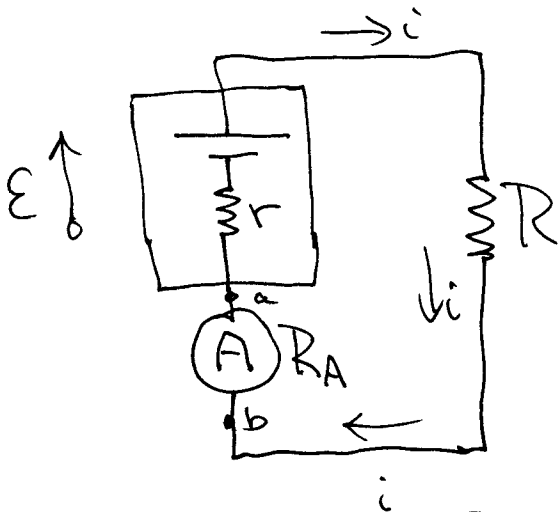


Loop Rule

$$0 = \mathcal{E} - iR - iR_A - ir$$

$$\Rightarrow i = \frac{\mathcal{E}}{r + R + R_A}$$

Ideal Ammeter $R_A = 0$
Realistic Ammeter $R_A \ll r + R$
to give small error

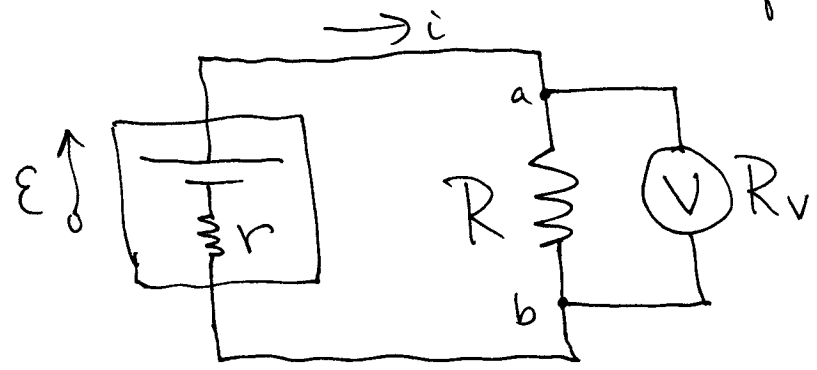- II H 2) Voltmeter measure potential difference



Loop Rule

$$\mathcal{E} - iR_{eq} - ir = 0$$

$$i = \frac{\mathcal{E}}{r + R_{eq}}$$

$$R_{eq} = \frac{RR_v}{R + R_v}$$

Potential Difference measured

$$V_a - iR_{eq} = V_b$$

$$\Rightarrow V_{ab} = iR_{eq} = \mathcal{E} \frac{R_{eq}}{R_{eq} + r}$$


Without Voltmeter this would be $V_{ab}^0 = \mathcal{E} \frac{R}{R + r}$

So ideal Voltmeter $R_v = \infty$ (Then $R_{eq} = R$)

Realistic Voltmeter $R_v \gg R$

to give small error

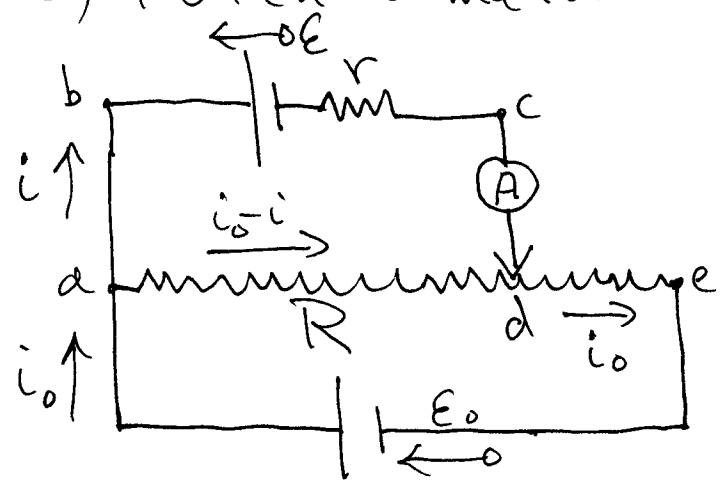3) Potentiometer: Measures unknown emf $\mathcal{E}_x$ by comparing to standard emf $\mathcal{E}_s$



R = resistance between a-d

- IIH3) Step 1: Place $\mathcal{E}_s$ where $\mathcal{E}$ is and adjust R until $i=0$ - potentiometer is "balanced" call this value of $R = R_s$ at balance

Loop Rule CW a-b-c-d-a

$$-\mathcal{E}_s - ir + (i_0 - i)R_s = 0$$

But $i=0$ in balance $\Rightarrow$

$$\mathcal{E}_s = i_0 R_s.$$


Step 2: Substitute $\mathcal{E}_x$ for $\mathcal{E}_s$ and adjust R to R_x for balance $i=0$ again

Now loop Rule gives $\mathcal{E}_x = i_0 R_x$
(same i_0)

$$\Rightarrow \boxed{\mathcal{E}_x = \mathcal{E}_s \frac{R_x}{R_s}}$$

(independent)
of $\mathcal{E}_0 - i=0$
"null instrument"

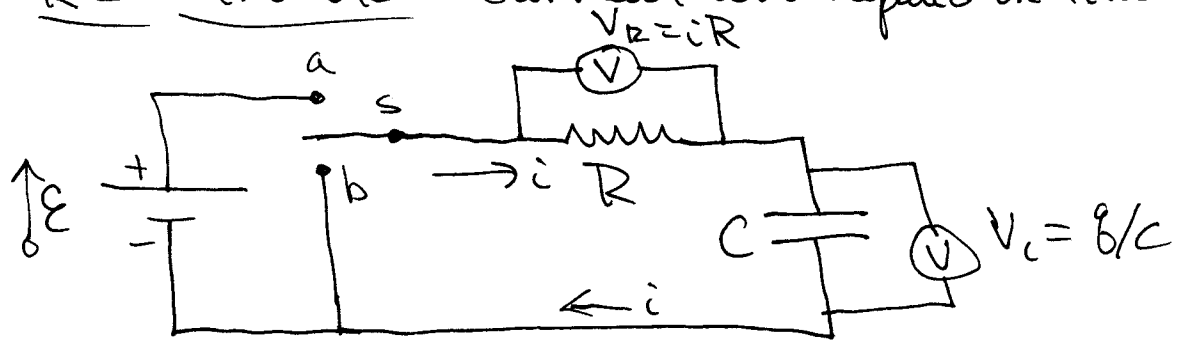- II). I) RC-circuits: Current will depend on time -52-



a) Throw switch to a — charge capacitor
 Loop Rule: CW start at a end at a
 with $V_R = iR$ and $V_C = q/C$

$$\mathcal{E} = iR + q/C$$

$$= R \frac{dq}{dt} + q/C$$

This is DE for $q = q(t)$:

$$\int_0^{q(t)} \frac{dq}{\mathcal{E}C - q} = \frac{1}{RC} \int_0^t dt$$

$$- \ln[\mathcal{E}C - q] \Big|_0^{q(t)} = \frac{1}{RC} t$$

$$\Rightarrow \ln \left[\frac{\mathcal{E}C - q(t)}{\mathcal{E}C} \right] = - \frac{t}{RC}$$



$$\Rightarrow \frac{\mathcal{E}C - q(t)}{\mathcal{E}C} = e^{-t/RC}$$

- IIIa) $\Rightarrow$

$$q(t) = \epsilon C [1 - e^{-t/\tau_c}]$$

with $\tau_c \equiv RC = \text{Capacitive Time Constant}$

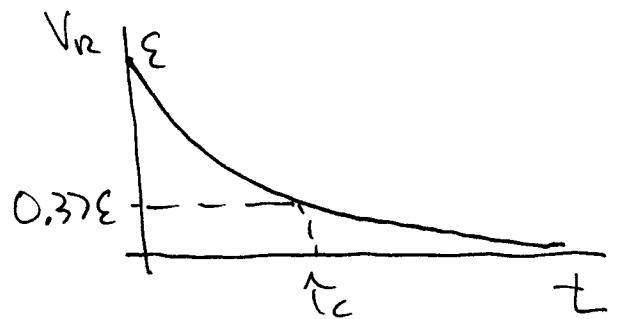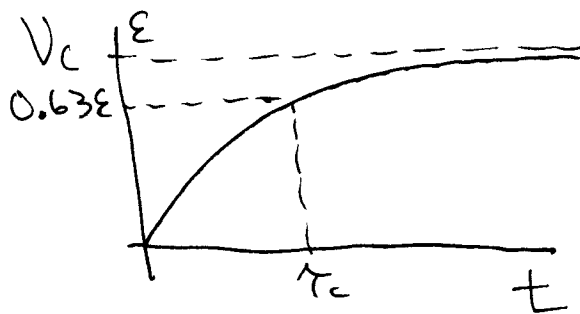Hence $i = i(t) = \frac{dq(t)}{dt} = \frac{\epsilon}{R} e^{-t/\tau_c}$



b) Throw switch from a to b: Discharge Capacitor

Loop Rule:

$$iR + q/c = 0$$

$$\Rightarrow R \frac{dq}{dt} + \frac{1}{C} q = 0$$

$$\Rightarrow \int_{q_0}^{q(t)} \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$

$$\Rightarrow \boxed{q(t) = q_0 e^{-t/\tau_c}}$$

II.I.b) $q_0 =$ initial charge on capacitor
for $t \gg \tau_c$ in part a $q_0 \approx \epsilon C$.

$$q(t) = \epsilon C e^{-t/\tau_c}$$

and

$$i(t) = \frac{dq(t)}{dt} = -\frac{\epsilon}{\tau_c} e^{-t/\tau_c}$$

