

Physics 24100

Electricity & Optics

Lecture 11 – Chapter 25 sec. 4-5

Fall 2012 Semester

Matthew Jones

Thursday's Clicker Question

- The resistance across the human body is approximately $2\text{ k}\Omega$
- If it takes only 50 mA of current to kill a human, what voltage could be lethal?

(a) 0.1 Volts

(b) 1 Volt

(c) 10 Volts

(d) 100 Volts

(e) 1000 Volts

Ohm's law: $V = I R = (50\text{ mA}) \times (2\text{ k}\Omega) = 100\text{ V}$



Kirchhoff's Rules


- General problem:
 - Calculate the currents that flow in an electric circuit composed of voltage sources and resistors connected by wires.
 - Recall that work done to move a charge q from point a to point b is $W = -q \int_a^b \vec{E} \cdot d\vec{\ell}$
 - If a and b are the same point then $W = 0$

$$\oint \vec{E} \cdot d\vec{\ell} = 0$$

Kirchhoff's Loop Rule


$$\oint \vec{E} \cdot d\vec{\ell} = 0$$

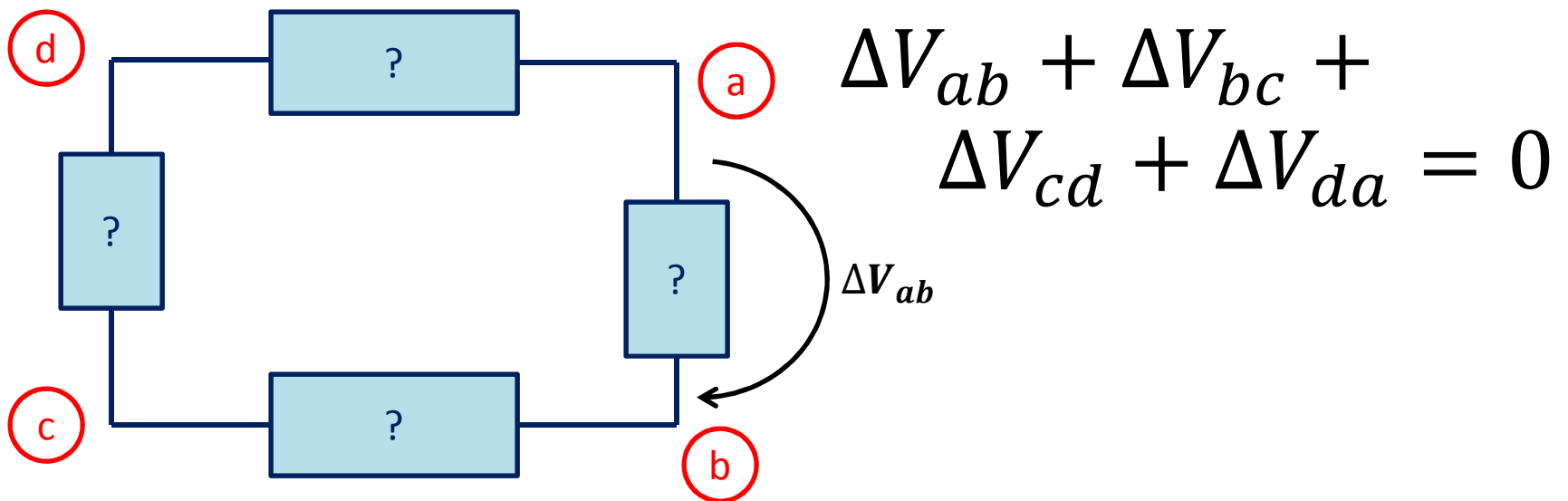“The sum of the potential differences around a closed loop is zero.”



Circuit Elements


- Voltage sources (like batteries):

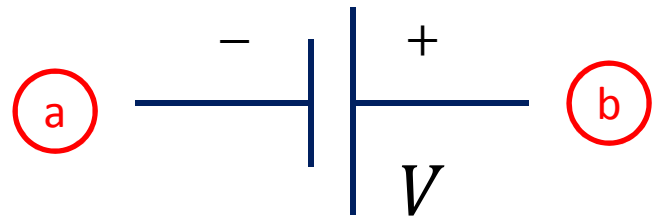

A circuit diagram showing a voltage source between two nodes, 'a' and 'b'. Node 'a' is on the left and node 'b' is on the right. The voltage source is represented by two vertical lines of unequal height. The shorter line is on the left, connected to node 'a', and has a minus sign (-) above it. The taller line is on the right, connected to node 'b', and has a plus sign (+) above it. The voltage 'V' is written below the taller line.

$$V_b = V_a + V$$

- Make sure you get the sign right!

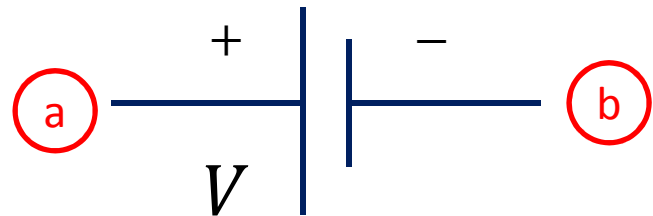


A circuit diagram showing a voltage source between two nodes, 'a' and 'b'. Node 'a' is on the left and node 'b' is on the right. The voltage source is represented by two vertical lines of unequal height. The taller line is on the left, connected to node 'a', and has a plus sign (+) above it. The shorter line is on the right, connected to node 'b', and has a minus sign (-) above it. The voltage 'V' is written below the taller line.

$$V_b = V_a - V$$

Circuit Elements


- Resistors:

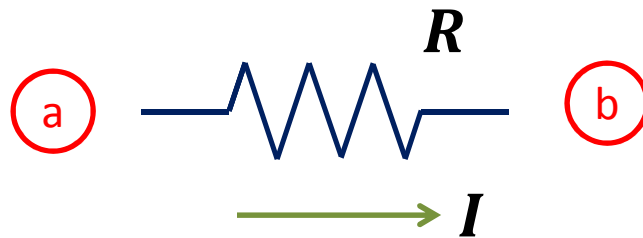The charges lose energy as they are pushed through the resistor.



$$V_b = V_a - IR$$


- Make sure you get the sign right!

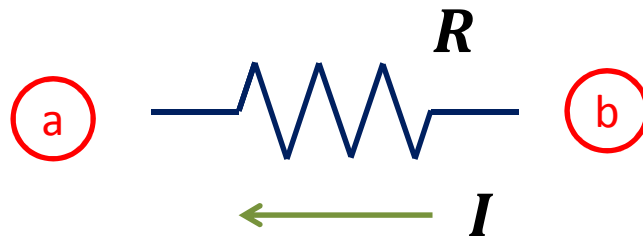

$$V_b = V_a + IR$$


Circuit Analysis

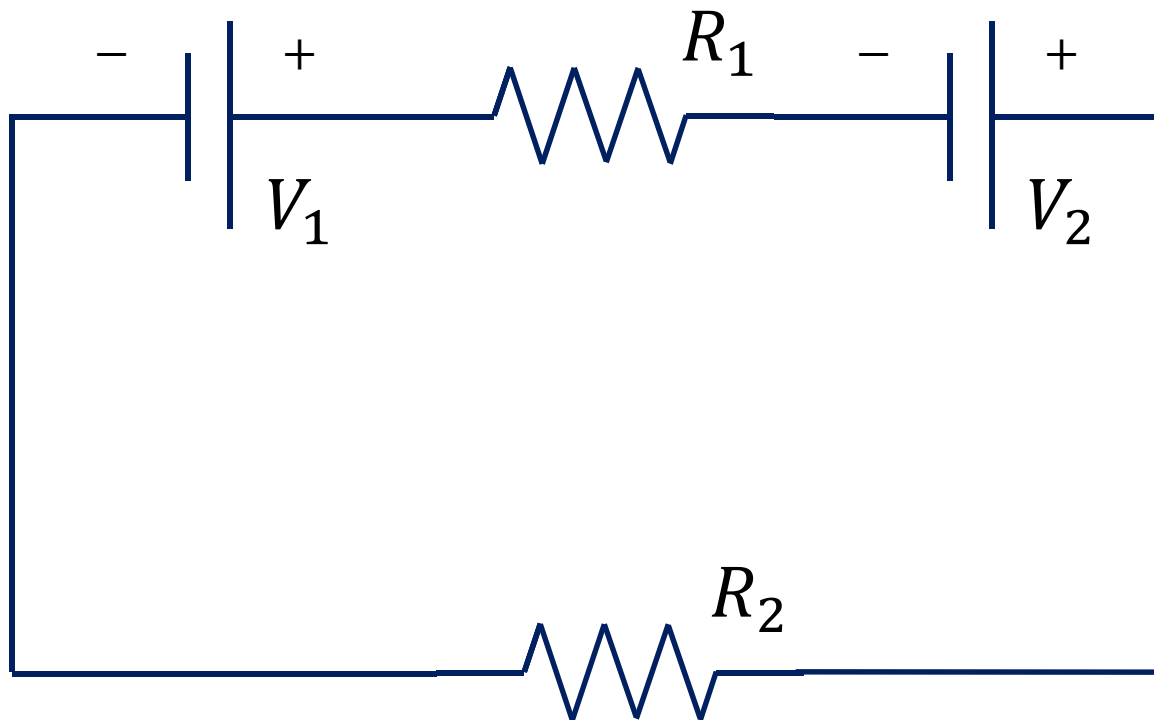- Find the current in the following circuit:



Circuit Analysis

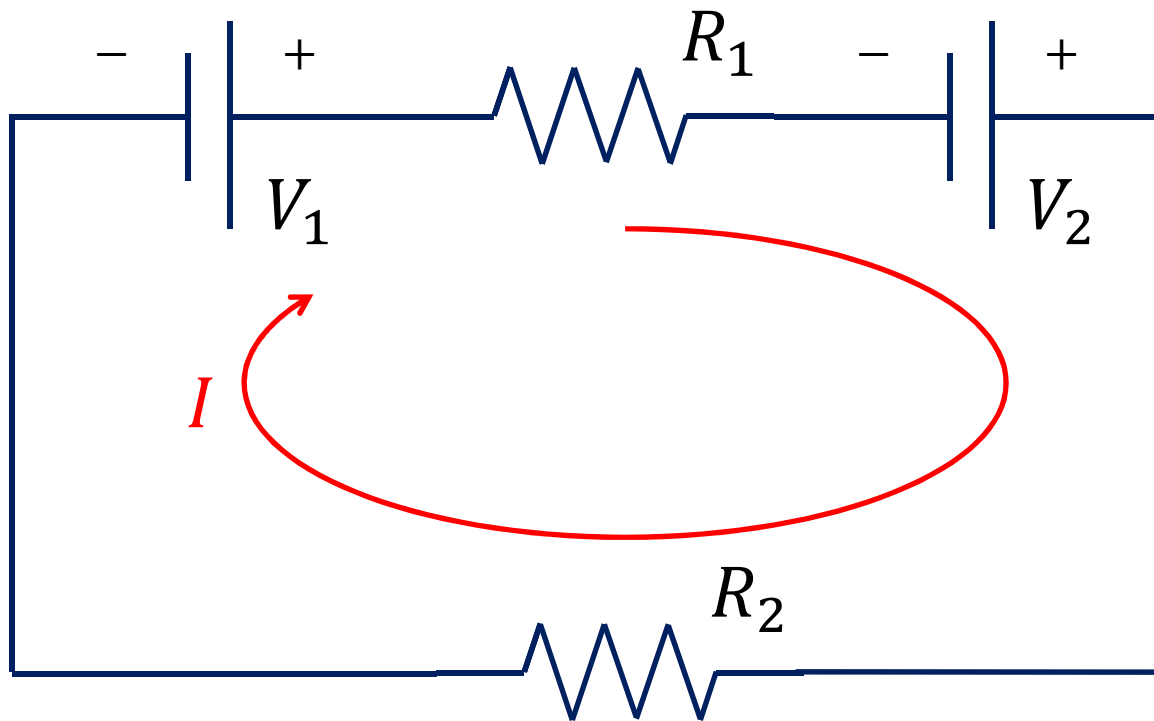
- Step 1: Draw a loop to represent the current.



Which direction? It doesn't matter, but let's ALWAYS pick clockwise to avoid confusion.

Circuit Analysis


- Step 2: Apply Kirchhoff's Loop Rule...

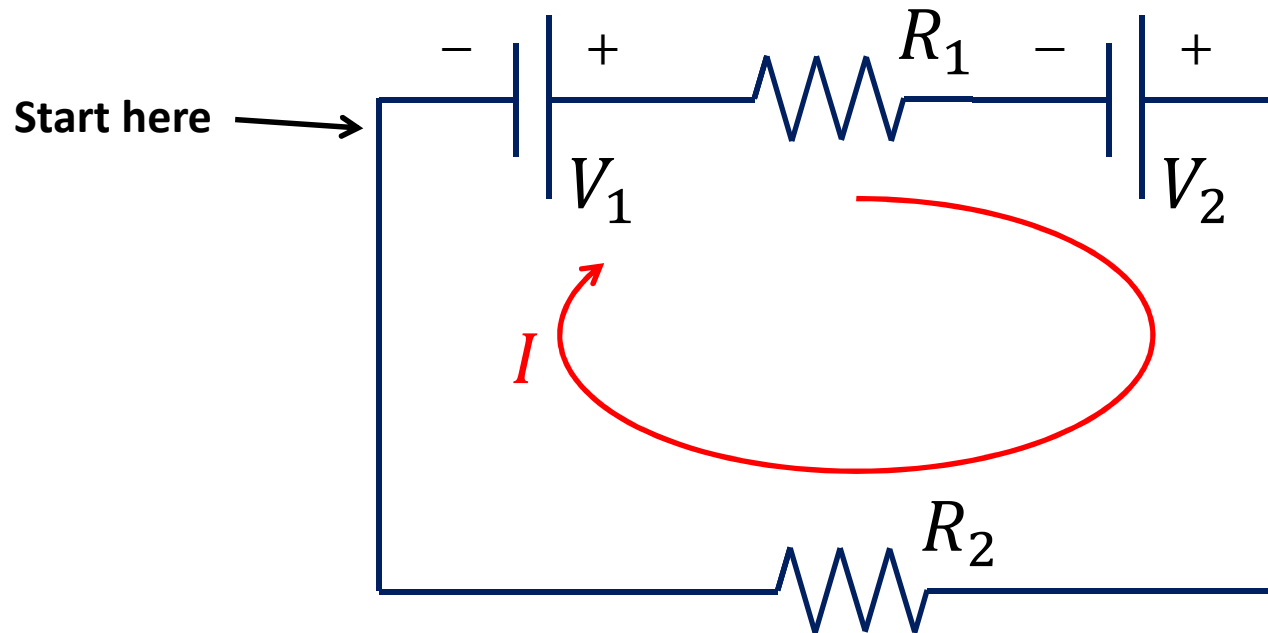

V_1

Circuit Analysis

- Step 3: Solve for I ...

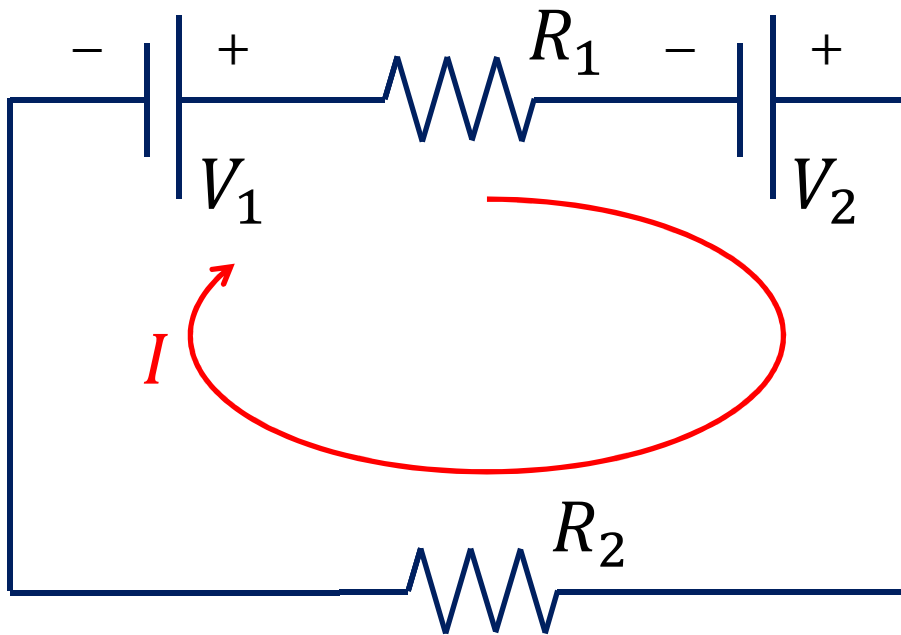


$$I = \frac{V_1 + V_2}{R_1 + R_2}$$

What if I is negative? Then it means the current flows in the opposite direction.

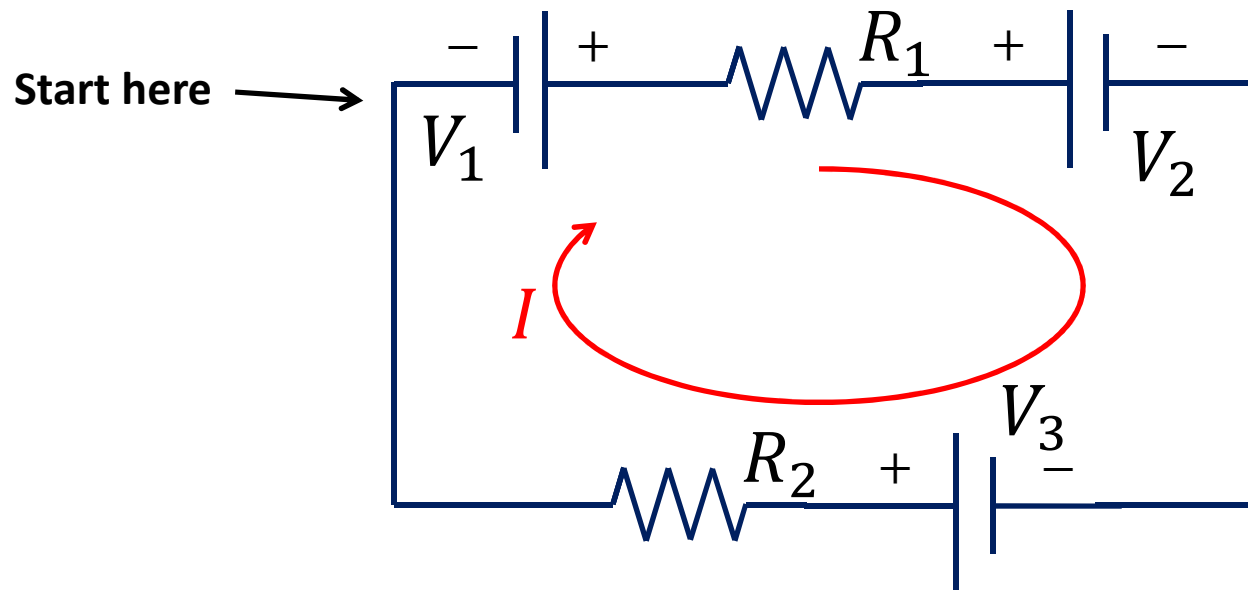Question


- Which formula shows the correct application of Kirchhoff's Loop rule to the following circuit:



- (a) $V_1 - I R_1 + V_2 + V_3 - I R_2 = 0$
- (b) $-V_1 - I R_1 - V_2 + V_3 - I R_2 = 0$
- (c) $V_1 - I R_1 - V_2 + V_3 - I R_2 = 0$
- (d) $V_1 + I R_1 + V_2 + V_3 + I R_2 = 0$


Two Loops

- Step 1: Assign currents to each loop

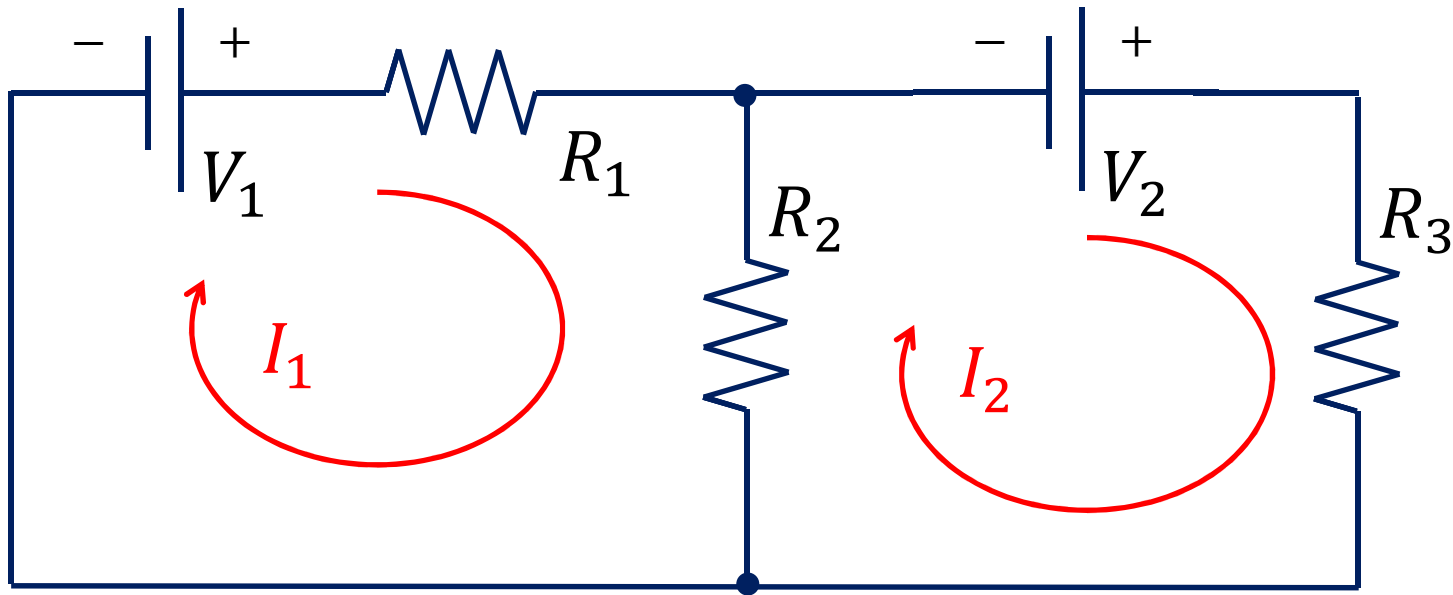

Two Loops

- Step 2: Apply Kirchhoff's Loop rule

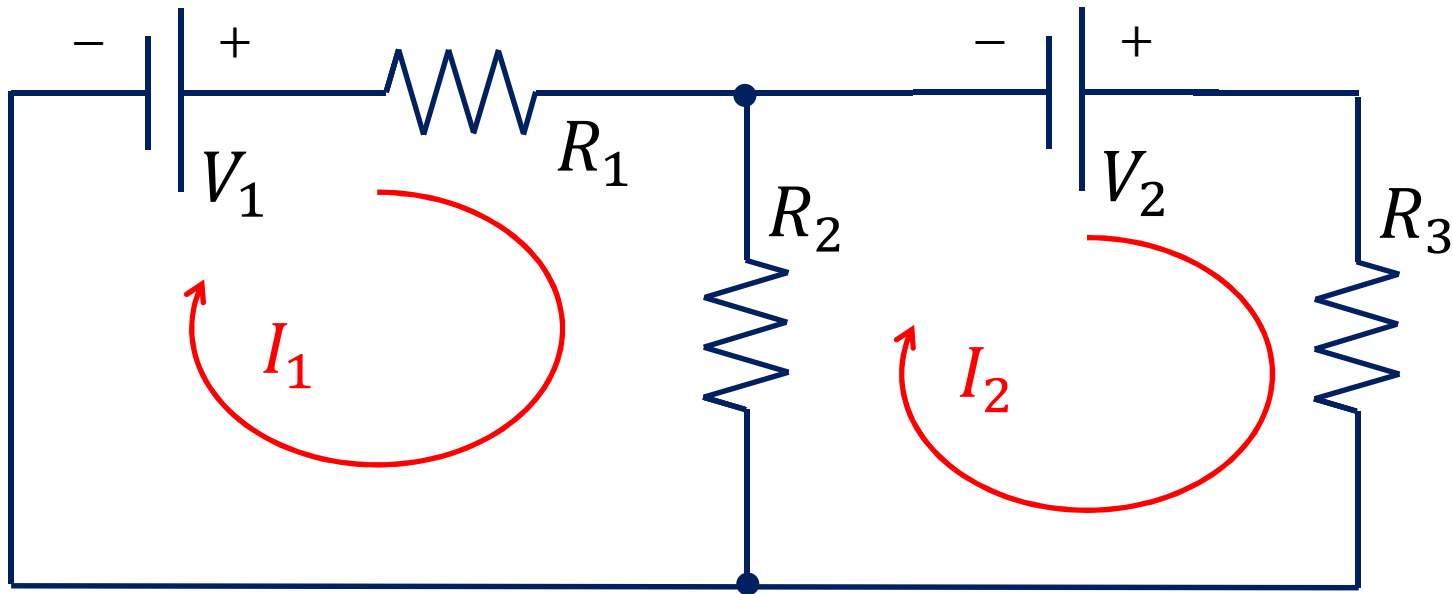

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$V_2 - I_2 R_3 - (I_2 - I_1) R_2 = 0$$

Two Loops

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$V_2 - I_2 R_3 - (I_2 - I_1) R_2 = 0$$

This is a system of linear equations... write them as a matrix equation:

$$\begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

This should *always* be a symmetric matrix.

Kramer's Rule

- This is the “formula” that gives you the solution to a system of linear equations:

$$\begin{aligned}a_1x + b_1y &= c_1 \\ a_2x + b_2y &= c_2\end{aligned}$$

$$x = \frac{\begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}} = \frac{c_1b_2 - c_2b_1}{a_1b_2 - a_2b_1}$$

$$y = \frac{\begin{vmatrix} a_1 & c_1 \\ a_2 & c_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}} = \frac{a_1c_2 - a_2c_1}{a_1b_2 - a_2b_1}$$

Two Loops


$$\begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & -R_2 \\ V_2 & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}} = \frac{V_1(R_2 + R_3) + V_2 R_2}{(R_1 + R_2)(R_2 + R_3) - (R_2)^2}$$


$$I_2 = \frac{\begin{vmatrix} R_1 + R_2 & V_1 \\ -R_2 & V_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}} = \frac{V_2(R_1 + R_2) + V_1 R_2}{(R_1 + R_2)(R_2 + R_3) - (R_2)^2}$$

Kirchhoff's Node Rule

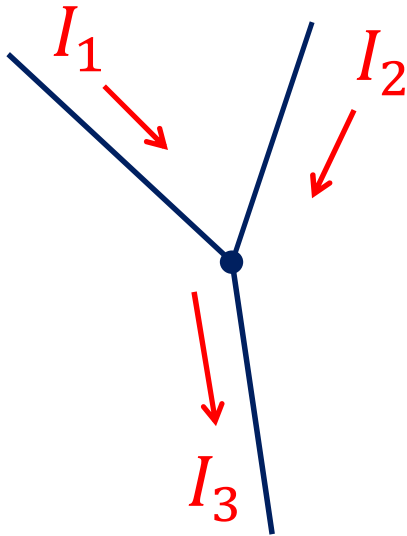- The sum of the currents entering a node must equal the sum of the currents leaving.



$$I_1 + I_2 = I_3$$

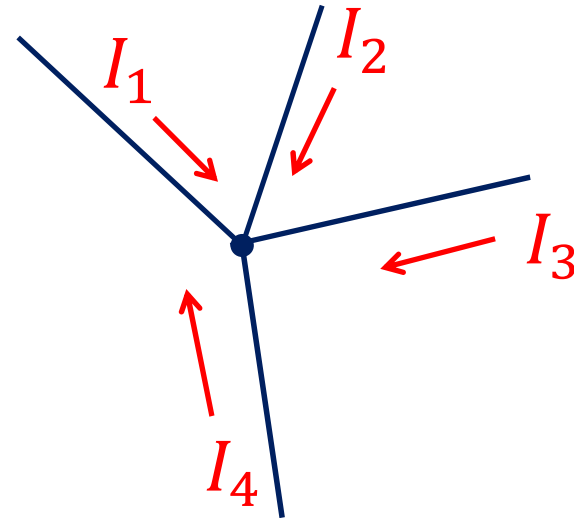


$$I_1 + I_2 + I_3 + I_4 = 0$$

(at least one of these must be negative)


Equivalent Series Resistors

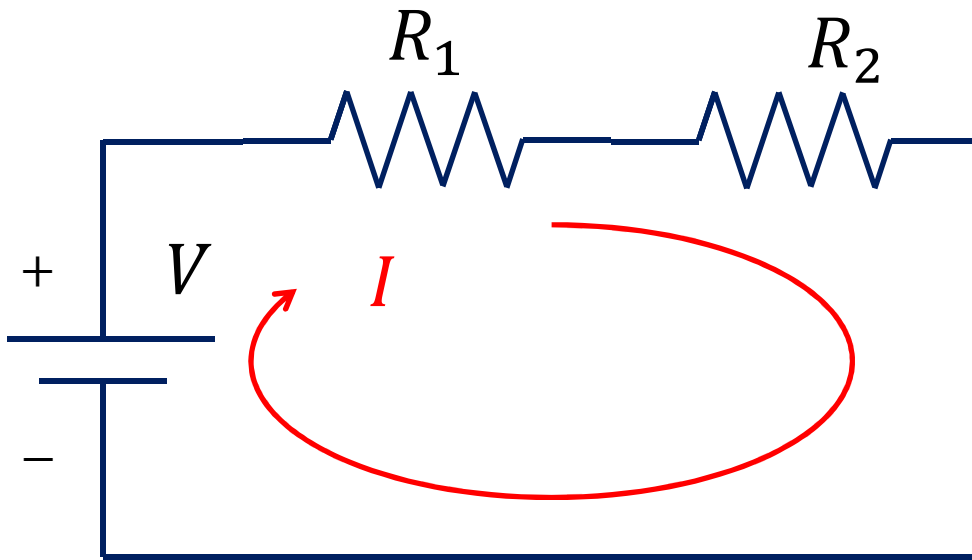- What resistance R would produce the same current as the series combination of R_1 and R_2 ?



$$V - I R_1 - I R_2 = 0$$


$$I = \frac{V}{R_1 + R_2}$$

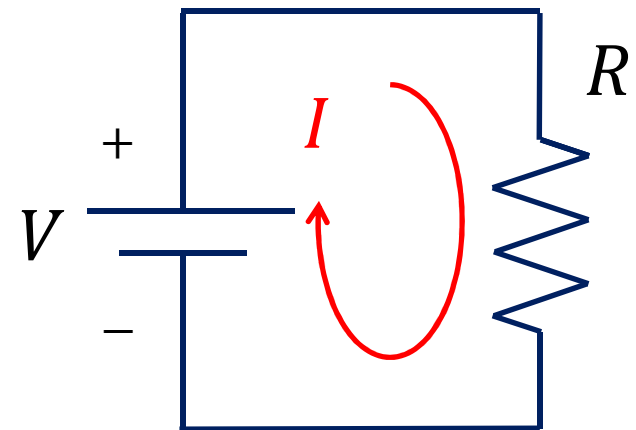

$$\mathbf{R = R_1 + R_2}$$

Equivalent Parallel Resistance

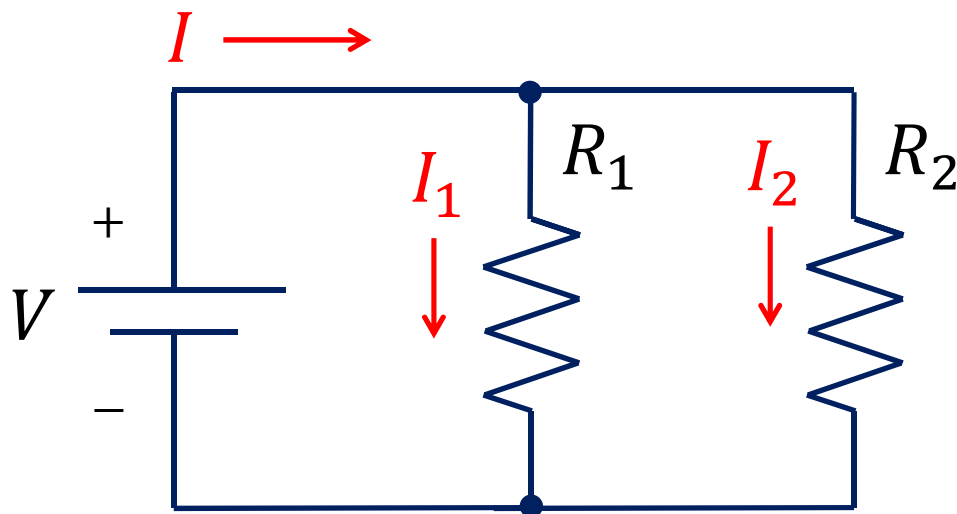- What resistance R would produce the same current as the parallel combination of R_1 and R_2 ?




The voltage across each resistor is equal.

$$V = I_1 R_1$$

$$V = I_2 R_2$$
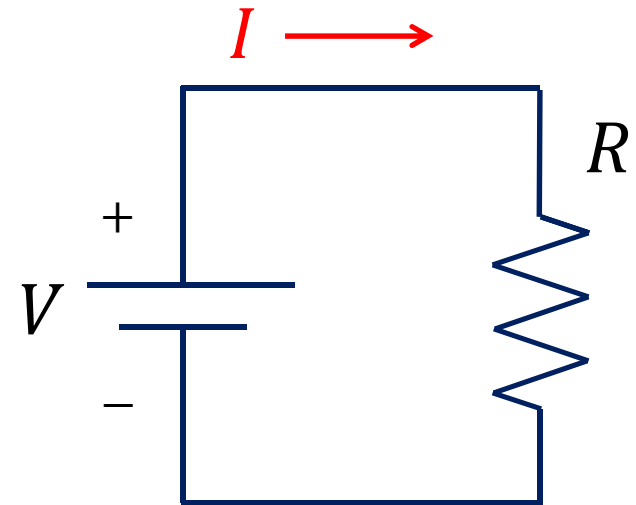
$$I = I_1 + I_2 = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$




$$I = \frac{V}{R}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


Series and Parallel




$$R = R_1 + R_2$$

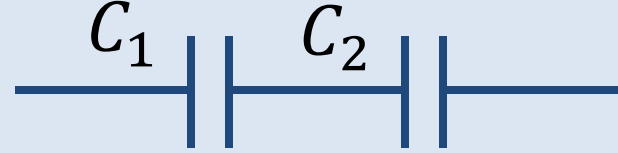
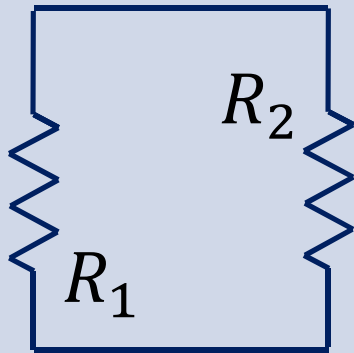
$$C = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$




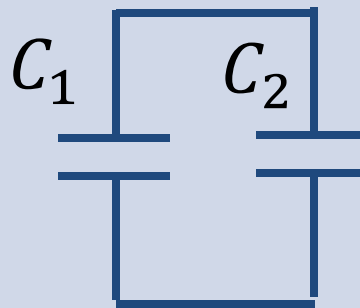
$$R = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$



$$C = C_1 + C_2$$


Internal Resistance

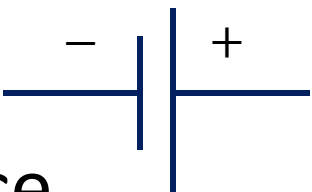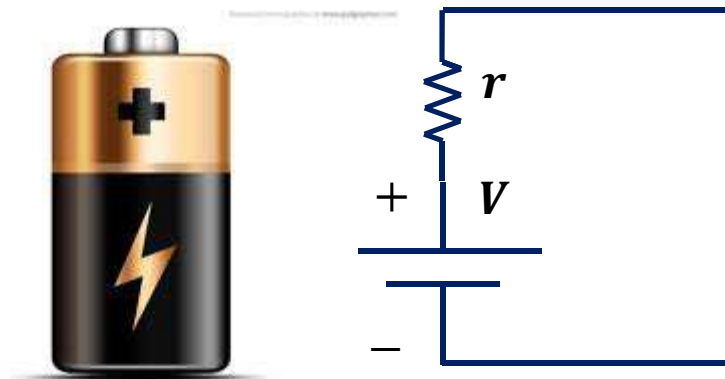- The symbol  represents an *ideal* voltage source.
 - The voltage is the same no matter how much current flows through it.
- A real voltage source is equivalent to an ideal voltage source in series with a resistor.
 - The resistor is called the “internal resistance”
 - It is usually small.



Internal Resistance

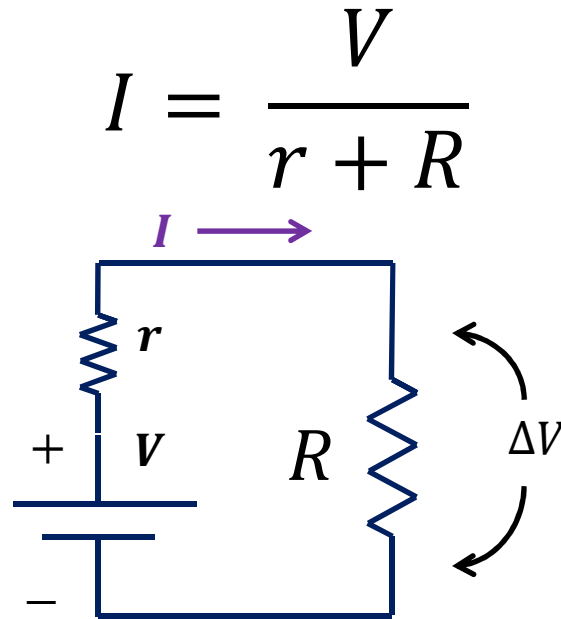- The voltage across a load depends on the current.




$$V - Ir - \Delta V = 0 \quad \text{so} \quad \Delta V = V - Ir$$

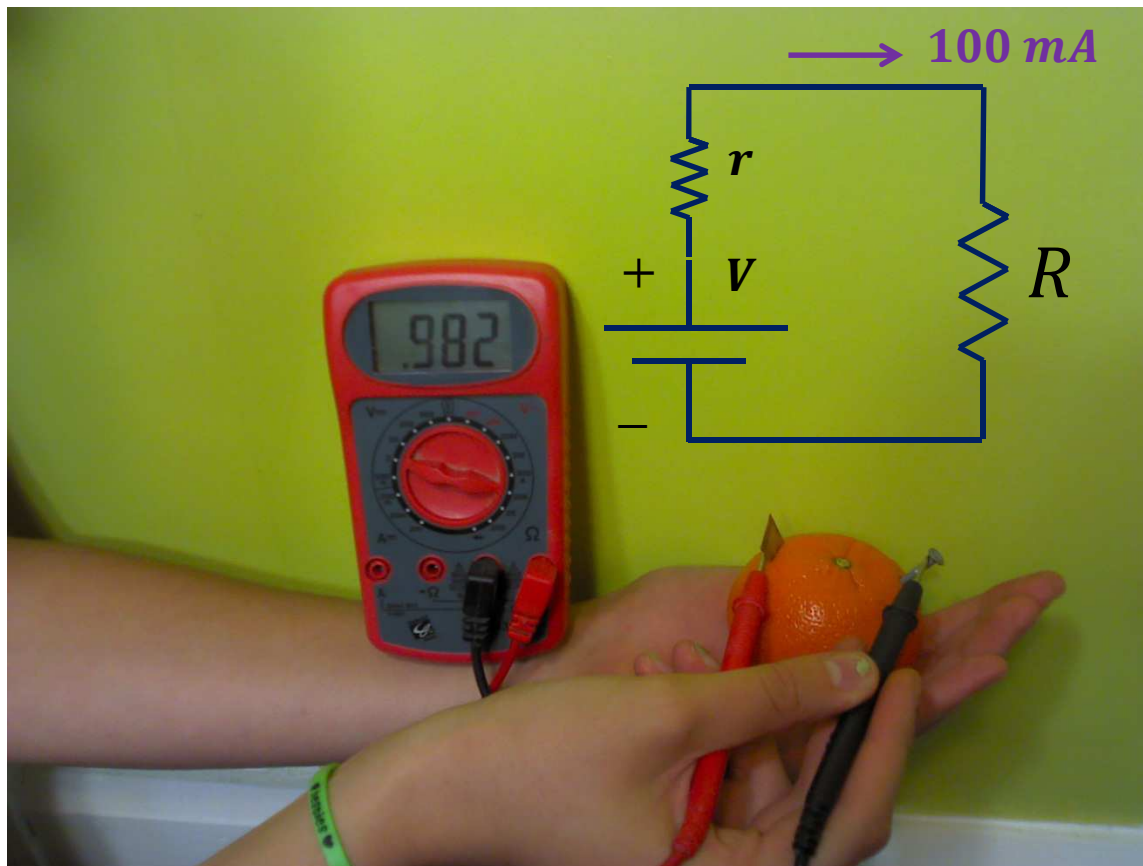Question

When there is no load, the orange provides 0.982 Volts.

What is the internal resistance of the orange if the voltage drops to 0.082 volts when the current is 100 mA?



- (a) 9Ω
- (b) 90Ω
- (c) 0.9Ω
- (d) 10Ω
- (e) not enough information

