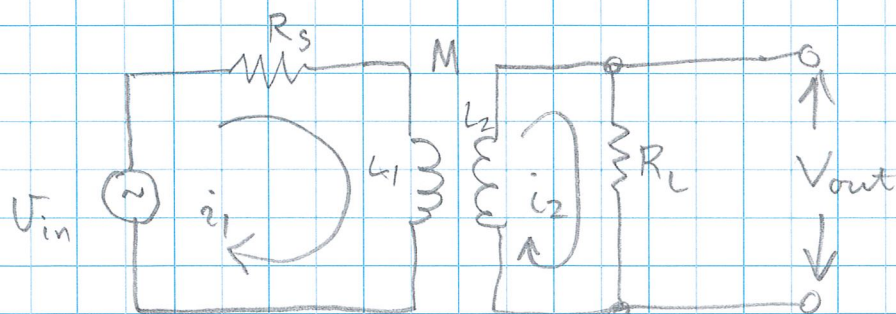


Assignment # 2



Kirchoff's rules:

$$V_{in} - i_1 R_s - Z_{L_1} i_1 + Z_m i_2 = 0$$

$$-i_2 R_L - Z_{L_2} i_2 + Z_m i_1 = 0$$

$$\begin{pmatrix} R_s + Z_{L_1} & -Z_m \\ -Z_m & R_L + Z_{L_2} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} V_{in} \\ 0 \end{pmatrix}$$

$$i_2 = \frac{V_{in} Z_m}{(R_s + Z_{L_1})(R_L + Z_{L_2}) - Z_m^2}$$

$$V_{out} = \frac{V_{in} R_L Z_m}{R_s R_L + R_s Z_{L_2} + R_L Z_{L_1} + Z_{L_1} Z_{L_2} - Z_m^2}$$

(a) With perfect coupling, $Z_m^2 = Z_{L_1} Z_{L_2}$

$$\begin{aligned} \text{So } V_{out} &= \frac{V_{in} R_L Z_m}{R_s R_L + R_s Z_{L_2} + R_L Z_{L_1}} \\ &= \frac{j\omega M V_{in} R_L}{R_s R_L + j\omega (L_1 R_L + L_2 R_s)} \end{aligned}$$

(b) Assuming that $L_1 \propto n_1^2$ and $L_2 \propto n_2^2$ and in the limit where $R_s R_L \ll \omega(L_1 R_L + L_2 R_s)$,

$$V_{out} = \frac{\sqrt{L_1 L_2} V_{in} R_L}{L_1 R_L + L_2 R_s}$$

$$= \frac{n_1 n_2 V_{in} R_L}{R_L n_1^2 + R_s n_2^2}$$

If $R_s \ll R_L$ then

$$V_{out} = V_{in} \frac{n_2}{n_1}$$

(c) The power dissipated in the load is

$$P = I_2 V_2 = I_2^2 R_L = V_{in}^2 R_L \left(\frac{n_1 n_2}{n_1^2 R_L + n_2^2 R_s} \right)^2$$

$$= V_{in}^2 R_L \left(\frac{n_2/n_1}{R_L + R_s n_2^2/n_1^2} \right)^2$$


If we write $r = n_2/n_1$, then P is maximized when

$$\frac{dP}{dr} = \left(\frac{2V_{in}^2 R_L r}{R_L + r^2 R_s} \right) \left(\frac{1}{R_s r^2 + R_L} - \frac{2R_s r^2}{(R_s r^2 + R_L)^2} \right) = 0$$

$$\Rightarrow R_s r^2 + R_L - 2R_s r^2 = 0$$

$$r^2 = \frac{R_L}{R_s} \Rightarrow r = \frac{n_2}{n_1} = \sqrt{\frac{R_L}{R_s}}$$

2.

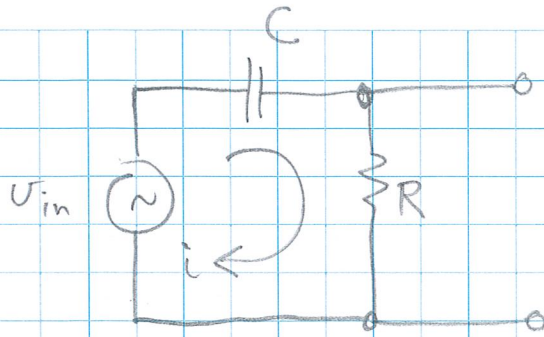

Kirchoff's rules:

$$V_{in} - iZ_c - iR = 0$$

$$i = \frac{V_{in}}{R + Z_c}$$

$$V_{out} = iR = \frac{R V_{in}}{R + Z_c}$$

$$= \frac{R V_{in}}{R - j/\omega C} = \frac{V_{in}}{1 - j/\omega RC}$$

$$= \frac{j\omega RC V_{in}}{j\omega RC + 1}$$


(a) In the high frequency limit, $\omega \gg 1/RC$,

$$\frac{1}{\omega RC} \ll 1 \quad \text{and} \quad V_{out} \rightarrow V_{in}.$$

In the low frequency limit, $\omega \ll 1/RC$

$$V_{out} \rightarrow 0.$$

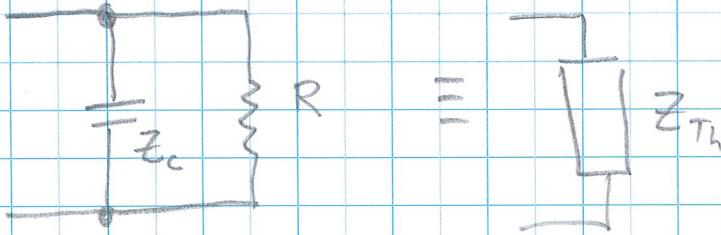- (b) The Thevenin equivalent impedance is calculated by considering the R and C in parallel:




$$Z_{Th} = \left(\frac{1}{R} + \frac{1}{Z_c} \right)^{-1} = \left(\frac{1}{R} + j\omega C \right)^{-1}$$
$$= \frac{R}{1 + j\omega RC}$$

In the low frequency limit, $\omega \ll 1/RC$,

$$Z_{Th} \rightarrow R$$

In the high frequency limit, $\omega \gg 1/RC$
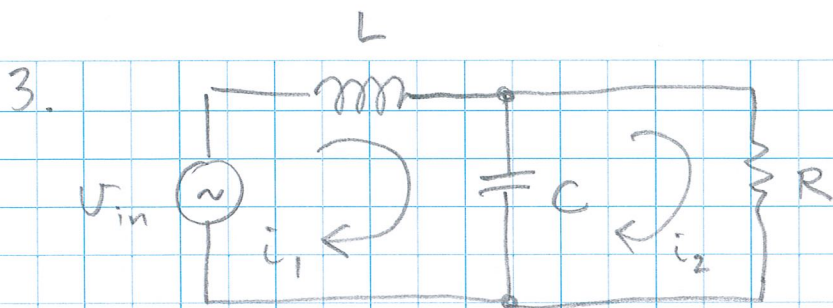
$$Z_{Th} \rightarrow \frac{1}{j\omega C}$$



$$(a) \quad V_{in} - I_1 Z_L - (I_1 - I_2) Z_C = 0$$

$$- I_2 R - (I_2 - I_1) Z_C = 0$$

$$\begin{pmatrix} Z_L + Z_C & -Z_C \\ -Z_C & R + Z_C \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_{in} \\ 0 \end{pmatrix}$$

$$I_2 = \frac{\begin{vmatrix} Z_L + Z_C & V_{in} \\ -Z_C & 0 \end{vmatrix}}{\begin{vmatrix} Z_L + Z_C & -Z_C \\ -Z_C & R + Z_C \end{vmatrix}}$$

$$= \frac{V_{in} Z_C}{(Z_L + Z_C)(R + Z_C) - Z_C^2}$$

$$= \frac{V_{in} Z_C}{R Z_C + Z_C(R + Z_C)}$$

$$V_{out} = I_2 R = \frac{V_{in} R Z_C}{R(Z_C + Z_C) + Z_C Z_C}$$

$$= \frac{V_{in} R (-j/\omega C)}{R(j\omega L - j/\omega C) + L/C}$$

$$= \frac{-V_{in} R}{R\omega^2 LC - R - j\omega L}$$

$$= \frac{-V_{in}}{(1 - \omega^2 LC) - j\omega L/R}$$

(6)

The magnitude of V_{out} is

$$|V_{out}| = \frac{|V_{in}|}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 L^2 / R^2}}$$

(b) When R is large, the resonant frequency is ω_0 , given by

$$1 - \omega_0^2 LC = 0$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

(c) When $\omega = \omega_0$ the amplitude of V_{out} will be

$$|V_{out}| = \frac{|V_{in}|}{\sqrt{L^2 / R^2 LC}}$$

$$= R |V_{in}| \sqrt{\frac{C}{L}}$$

When the gain is -3 db,

$$\frac{|V_{out}|}{|V_{in}|} = R \sqrt{\frac{C}{L}} = \frac{1}{\sqrt{2}}$$

$$\text{Hence, } R = \sqrt{\frac{L}{2C}}$$

(d) At high frequencies, the gain approaches the following form:

$$A \rightarrow \frac{1}{\omega^2 LC}$$

If ω increases by a factor of 10 then A will decrease by a factor of 100.

$$\begin{aligned} \text{Thus, } G &= 20 \log_{10} 10^{-2} \\ &= -40 \text{ db per decade.} \end{aligned}$$

For a first-order low-pass filter the high frequency response is -20 db/decade.

(e) Component values that give $f_0 = \frac{\omega_0}{2\pi} = 1 \text{ MHz}$ must satisfy

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


If we pick C then L is given by

$$L = \left(\frac{1}{2\pi f_0} \right)^2 \cdot \frac{1}{C}$$

$$\text{With } C = 1 \mu\text{F}, \quad L = 25.33 \text{ nH}$$

$$\begin{aligned} \text{Then we could pick } R &= \sqrt{\frac{L}{2C}} = \sqrt{\frac{25.33 \text{ nH}}{2 \cdot 1 \mu\text{F}}} \\ &= 0.1125 \Omega \end{aligned}$$

8

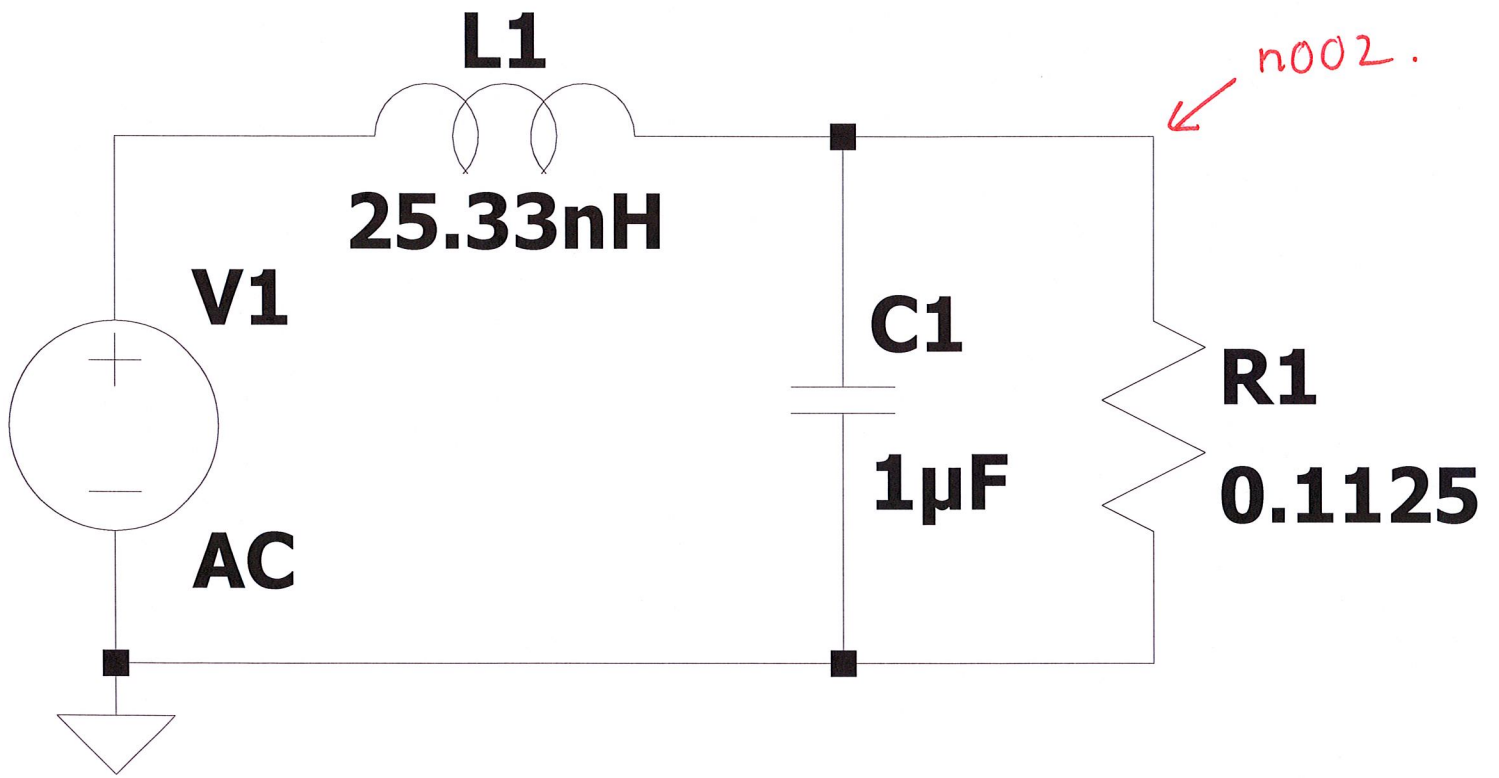

.ac dec 10 1 1E8

