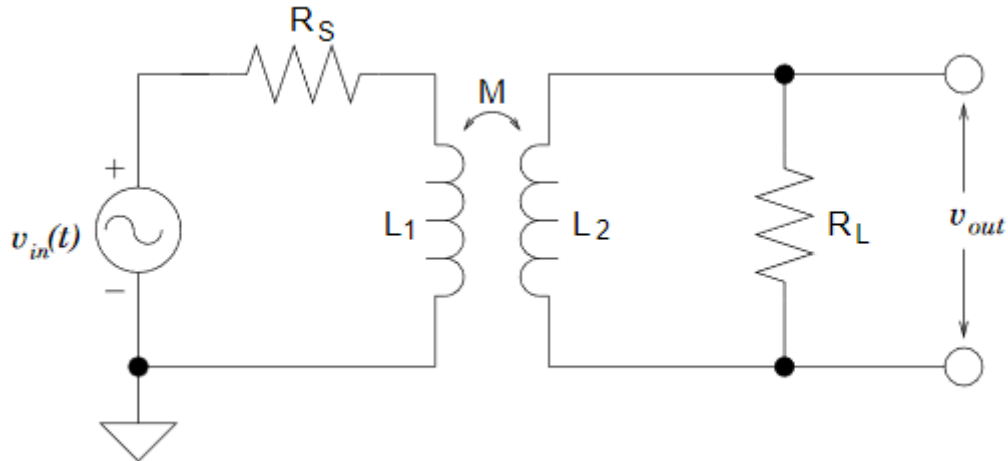


## Physics 53600 – Assignment #2 – Due February 11, 2020

1. Consider the following transformer circuit:



- (a) Show that when perfect coupling is assumed, so that  $M = \sqrt{L_1 L_2}$  the output voltage is given by

$$V_{out} = \frac{j\omega M V_{in} R_L}{R_S R_L + j\omega(L_1 R_L + L_2 R_S)}$$

- (b) Assuming that  $L_1 \propto n_1^2$  and  $L_2 \propto n_2^2$  and in the limit  $R_S R_L \ll \omega(L_1 R_L + L_2 R_S)$ , show that


$$V_{out} = V \frac{n_2}{n_1}$$

where  $n_2/n_1$  is the turns-ratio of the transformer.

- (c) Show that the turns-ratio that maximizes the power dissipated by  $R_L$  is

$$\frac{n_2}{n_1} = \sqrt{\frac{R_L}{R_S}}$$

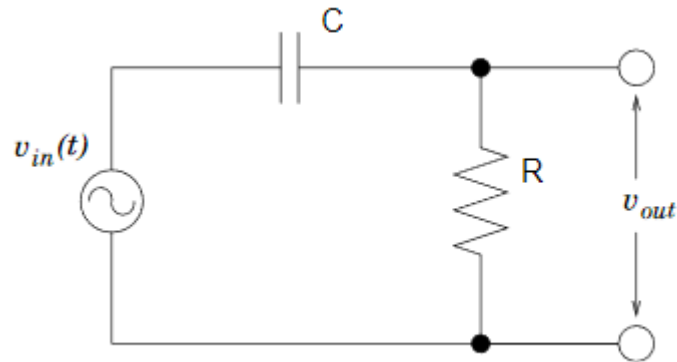
2. Consider the high-pass RC filter circuit:



When  $v_{in}(t) = V_{in}e^{j\omega t}$ , the Thevenin equivalent circuit would consist of an ideal voltage source  $V_{Th}$  in series with an impedance  $Z_{Th}$ , both of which depend on the frequency,  $\omega$ .

- (a) With no additional load across the resistor, calculate  $V_{out}$ . How does  $V_{out}$  behave in the low-frequency ( $\omega \ll 1/RC$ ) and high-frequency ( $\omega \gg 1/RC$ ) limits?
- (b) Calculate the Thevenin equivalent impedance  $Z_{Th}$  for the circuit where the impedance of the resistor is  $R$  and the impedance of the capacitor is  $j/\omega C$ . How does  $Z_{Th}$  behave in the low-frequency and high-frequency limits?

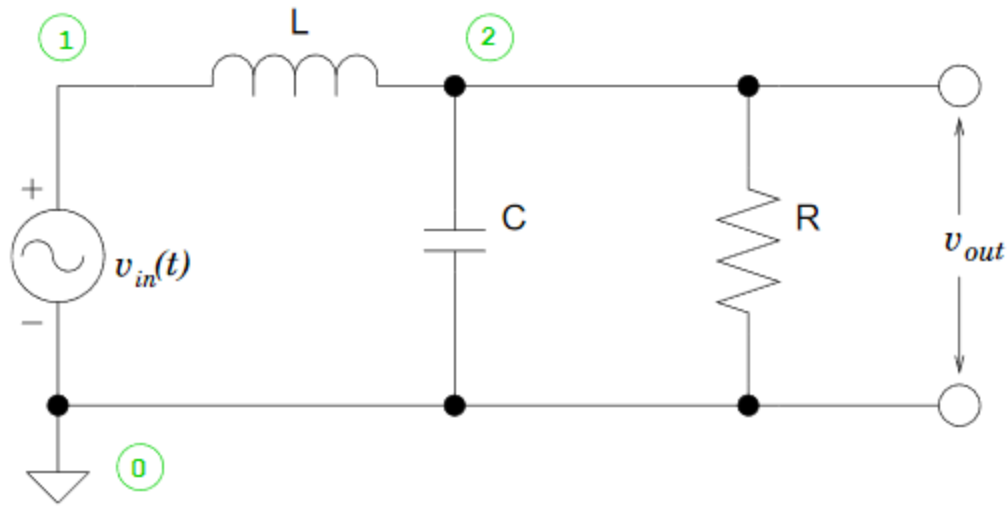3. Consider the following low-pass filter circuit:



- (a) Assuming  $v_{in}(t) = V_{in}e^{j\omega t}$  and  $v_{out}(t) = V_{out}e^{j\omega t}$ , solve for the magnitude of  $V_{out}$  in terms of  $V_{in}$ ,  $R$ ,  $L$ , and  $C$ .
- (b) In principle, this circuit could have a resonance if  $R$  is too large. Assuming that  $R$  is large enough that it can be ignored, estimate the resonant frequency,  $\omega_0$ .
- (c) If this circuit is intended to form a low-pass filter, what value of  $R$  would be needed to provide a gain of -3 db at the frequency calculated in part (b)?
- (d) At high frequencies, how many db per decade of frequency does this circuit attenuate? Compare this with the result for a first-order RC or RL low-pass filter.
- (e) Select component values such that  $f_0 = 2\pi\omega_0 = 1 \text{ MHz}$  and simulate the circuit using LtSPICE, plotting the gain as a function of frequency up to at least 100 MHz.