

Physics 53600 – Assignment #4 Solutions

1. The 2N3819 JFET has a pinch-off voltage of $V_P = -3\text{ V}$ and a drain-source saturation current of $I_{DSS} = 11.7\text{ mA}$. When biased in the active region, the drain current is then given by

$$I_D = I_{DSS} \left(1 + \frac{V_G}{|V_P|} \right)^2$$

- (a) What value of V_G will produce a constant drain current of 5 mA?

This is just straight-forward algebra where we solve for V_G :

$$V_G = |V_P| \left(\sqrt{\frac{I_D}{I_{DSS}}} - 1 \right) = -1.039\text{ V}$$

- (b) Determine the values of R_1 and R_2 that will result in a voltage divider between $V_{DD} = +5\text{ V}$ and $V_{SS} = -5\text{ V}$ that produces the gate voltage determined in part (a) and has an impedance of $100\text{ k}\Omega$. Consult the solutions to the midterm exam for an example.

From the solutions given to the midterm, we can use the formulas:

$$V_{out} = \frac{V_{CC}R_2 + V_{EE}R_1}{R_1 + R_2}$$

$$Z = \frac{R_1R_2}{R_1 + R_2}$$

from which we can get

$$R_1 = Z \left(\frac{V_{CC} - V_{EE}}{V_{out} - V_{EE}} \right)$$


$$R_2 = Z \left(\frac{V_{CC} - V_{EE}}{V_{CC} - V_{out}} \right)$$

Here, it is assumed that R_1 is connected to V_{CC} and R_2 is connected to V_{EE} . Using these equations, you can calculate:

$$R_1 = 252\text{ k}\Omega$$

$$R_2 = 166\text{ k}\Omega$$

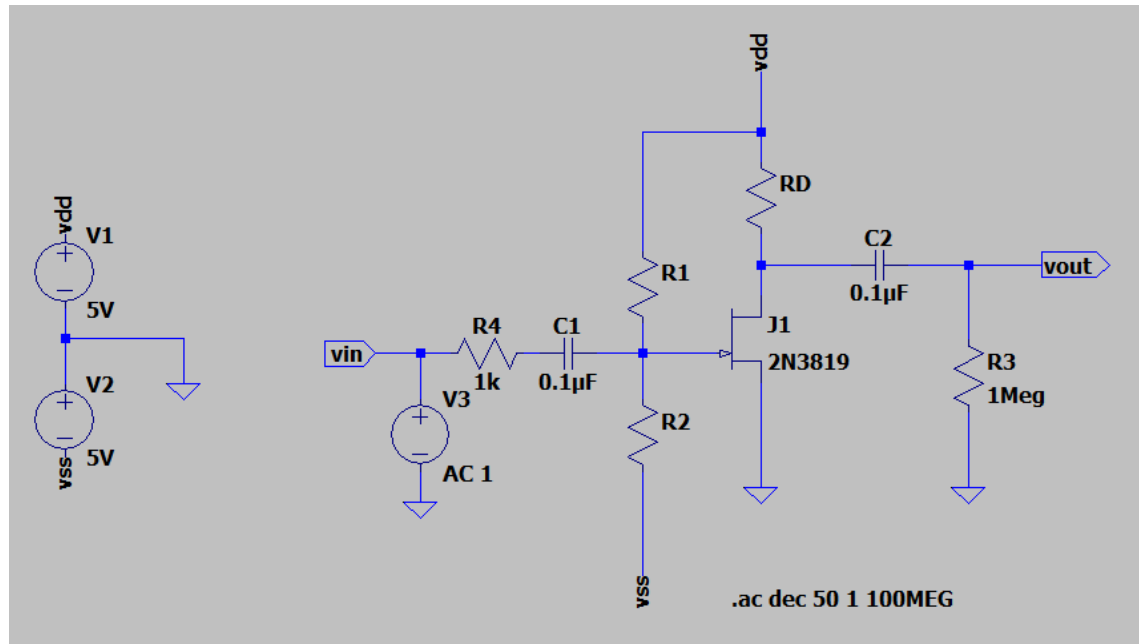- (c) Consider the following circuit, in which R_4 represents the finite output impedance of a signal to be amplified.



what value of R_D will produce a small-signal voltage gain of $A = 3$?

Well technically the question should have been asking for a gain of $A = -3$ because this is an inverting amplifier configuration. Since the current into the drain is

$$I_D = I_{DSS} \left(1 + \frac{V_G}{|V_P|} \right)^2$$

a small change in V_G results in a corresponding small change in I_D which is given by

$$\delta I_D = 2 \frac{I_{DSS}}{|V_P|} \left(1 + \frac{V_G}{|V_P|} \right) \delta V_G$$

and the small variation in the output voltage will be

$$\delta V_{out} = -R_D \delta I_D.$$

Thus,

$$\begin{aligned} R_D &= -\frac{\delta V_{out}}{\delta I_D} = -\frac{\delta V_{out}}{\delta V_G} \left(2 \frac{I_{DSS}}{|V_P|} \left(1 + \frac{V_G}{|V_P|} \right) \right)^{-1} \\ &= -A \left(2 \frac{I_{DSS}}{|V_P|} \left(1 + \frac{V_G}{|V_P|} \right) \right)^{-1} \\ &= 588 \, \Omega \end{aligned}$$


- (d) Simulate the circuit using both a DC operating point and an AC frequency sweep analysis. Identify in the simulation output the quiescent drain current, the gate voltage, and the voltage gain at moderate frequencies of ~10 kHz.

Here are the results of the DC operating point analysis:

--- Operating Point ---		
V(n001) :	2.01724	voltage
V(n003) :	-1.02871	voltage
V(vss) :	-5	voltage
V(vdd) :	5	voltage
V(n002) :	-1.02871e-015	voltage
V(vin) :	0	voltage
V(vout) :	2.01724e-012	voltage
I(C2) :	-2.01724e-018	device_current
I(C1) :	-1.02871e-018	device_current
Id(J1) :	0.0050641	device_current
Ig(J1) :	-5.09349e-012	device_current
Is(J1) :	-0.0050641	device_current
I(R4) :	-1.02871e-018	device_current
I(R3) :	2.01724e-018	device_current
I(R2) :	2.39234e-005	device_current
I(R1) :	2.39234e-005	device_current
I(Rd) :	0.0050641	device_current
I(V3) :	-1.02871e-018	device_current
I(V1) :	-0.00508802	device_current
I(V2) :	-2.39234e-005	device_current

Gate voltage

Drain current

 


This shows that at moderate frequencies (eg. 10 kHz) the voltage gain is 9.45 dB. Using the definition. Using the definition

$$G = 20 \log_{10} A$$


this confirms that

$$A = 10^{G/20} = 2.97 \approx 3$$

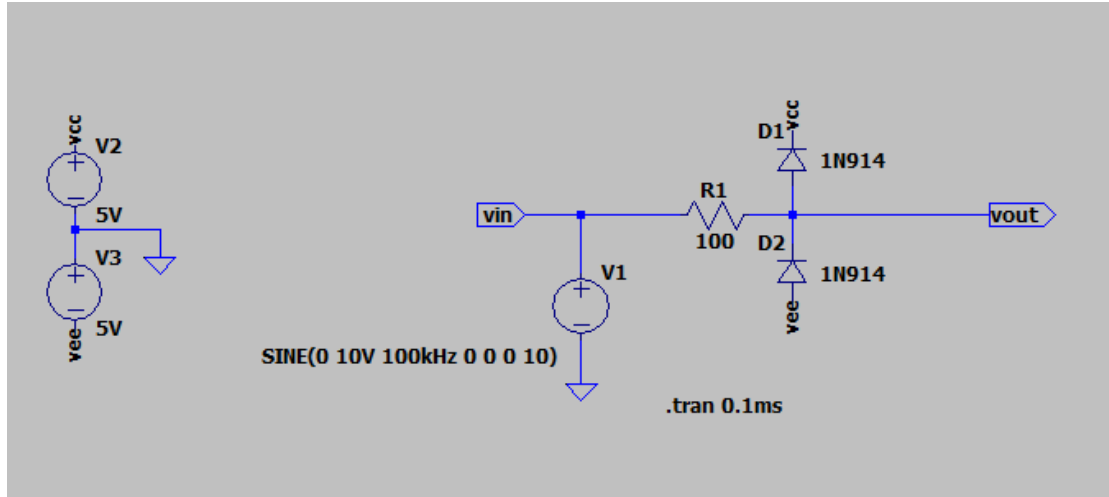2. A diode clamp circuit can be used to limit the range of input voltages to a sensitive circuit. Using 1N914 silicon diodes, simulate the following circuit and demonstrate that the voltage at the node V_{out} has been limited and identify what the limiting voltage range is.




Here is the output of the simulation:

 

which shows that the voltage has been limited to about ± 5.7 V.

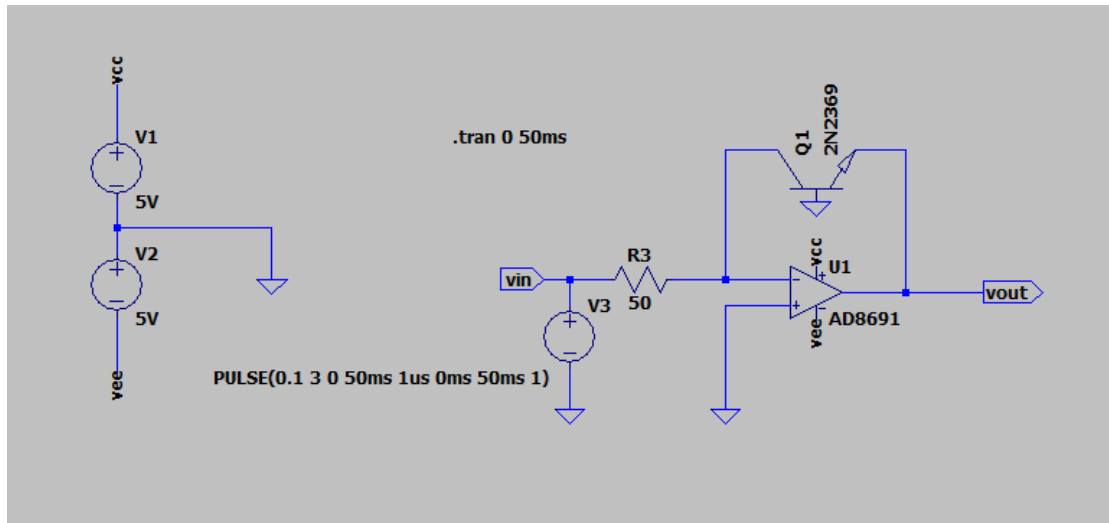3. The following circuit is a logarithmic amplifier:



(a) What is the output voltage when the input voltage is 0.1 V?

From the DC operating point simulation of this circuit, it can be determined that the output voltage is $v_{out} = -0.635 \text{ V}$ when the input voltage is $v_{in} = 0.1 \text{ V}$.

(b) What is the output voltage when the input voltage is 3 V?

Again, the DC operating point simulation determines that $v_{out} = -0.736 \text{ V}$ when $v_{in} = 3 \text{ V}$.

(c) Design a second state operational amplifier circuit, configured as an inverting summing amplifier that produces an output of 0V when the input voltage is 0.1 V and an output voltage of 1 V when the input voltage is 3 V.

An inverting, summing amplifier, like the one shown on page 6 of Lecture 14, provides an output voltage that is related to the input voltages as follows:

$$v_{out} = -R_F \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} \right)$$

In this case, we can select $R_1 = R_2$ to obtain


$$v_{out} = -\frac{R_F}{R_1} (v_1 + v_2)$$

where v_1 is the output of the logarithmic amplifier and v_2 is a constant voltage source that will satisfy the specified requirements. In this case, $v_2 = +0.635 \text{ V}$ so that $v_{out} = 0 \text{ V}$ when $v_{in} = 0.1 \text{ V}$. Next, when $v_{in} = 3 \text{ V}$, the output of the logarithmic amplifier would be $v_1 = -0.736 \text{ V}$ and

$$v_{out} = -\frac{R_F}{R_1} ((-0.736 \text{ V}) + (0.635 \text{ V})) = -\frac{R_F}{R_1} (-0.101 \text{ V}) = 3 \text{ V}$$

Thus, the ratio of resistances must be 10. A reasonable choice would be to use $R_F = 10\text{ k}\Omega$ and $R_1 = 1\text{ k}\Omega$.

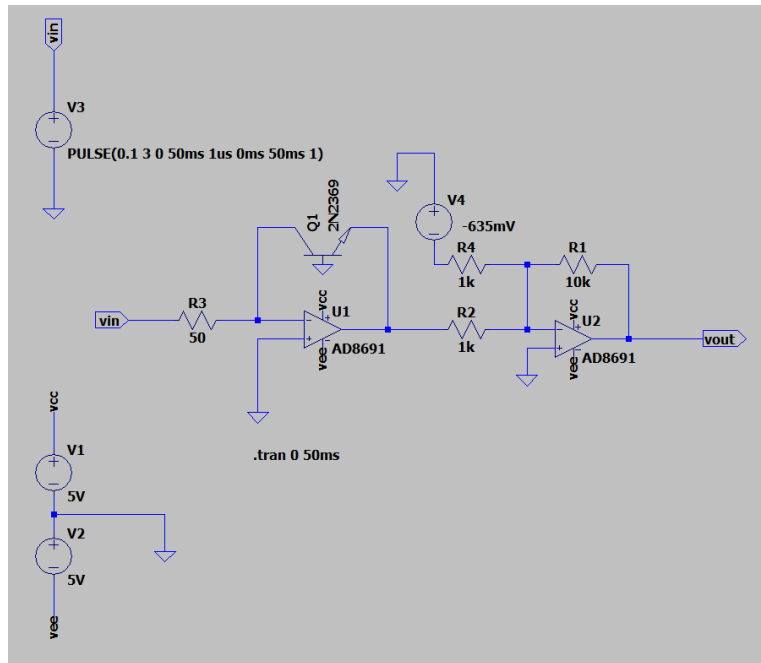The required circuit is shown below, although some of the resistor labels are different from what has been described previously.



with the following simulation output:

