

# Physics 53600

# Electronics Techniques for Research

*Now in PowerPoint!*

Spring 2020 Semester

Prof. Matthew Jones

# Midterm Exam – February 25

1. Resistor divider as a non-ideal voltage source
2. Initial value problem – transient response
3. AC circuit analysis/filter circuit
4. Transmission line question

If you are interested, Dawith Lim will give a review session at 4:30 pm on Friday, probably in the lab (Phys 349?)

# Bipolar Junction Transistors


- Simplified design rules:
  1. Assume  $V_{be} \approx 0.7\text{ V}$
  2. NPN:  $V_e = V_b - V_{be}$ , PNP:  $V_e = V_b + V_{be}$
  3. Collector current:  $I_c = I_e$
- Example:
  - Design a current 10 mA current source
  - A typical problem with electronics design is that this is not enough information to constrain the design.

# Bipolar Junction Transistors

- Additional constraints:
  - Let's use an NPN transistor
  - What is the voltage source?
  - What is the maximum acceptable collector voltage?
    - $V_b < V_c$  to reverse bias an NPN transistor.
    - $V_b > V_c$  to reverse bias an PNP transistor.
  - What is a convenient way to generate the required base voltage?
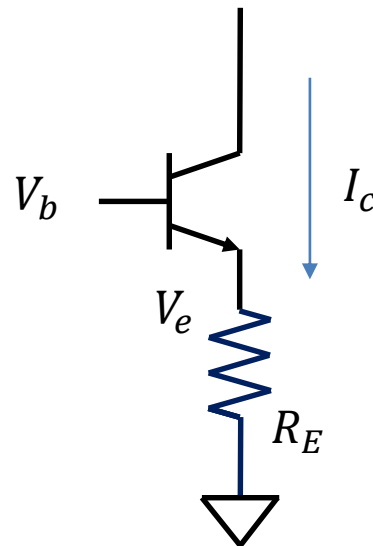
# Bipolar Junction Transistors


- Assume, in this example, that  $V_{CC} = 5\text{ V}$ .
- Furthermore, assume that  $V_C > 2.5\text{ V}$ .
  - This constrains the base voltage:  $V_b \approx 2.4\text{ V}$ .
  - If  $V_{be} = 0.7\text{ V}$ , then  $V_e = V_b - V_{be} = 1.7\text{ V}$ .



$$\begin{aligned} R_E &= \frac{V_e}{I_e} \\ &= \frac{1.7\text{ V}}{10\text{ mA}} \\ &= 170\ \Omega \end{aligned}$$
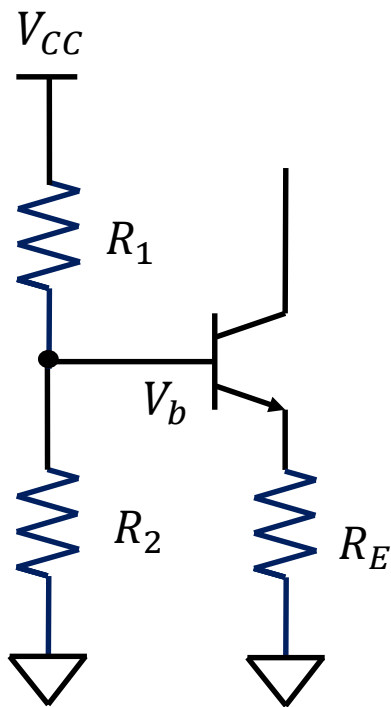
# Bipolar Junction Transistors

- A convenient way to generate the base voltage is with a voltage divider:



$$V_b = V_{CC} \frac{R_2}{R_1 + R_2}$$


But this is not enough information to constrain  $R_1$  and  $R_2$ .

*The impedance of the voltage source should be small compared with the input impedance of the base.*

$$R_b \sim \beta R_E \approx 17 \text{ k}\Omega$$
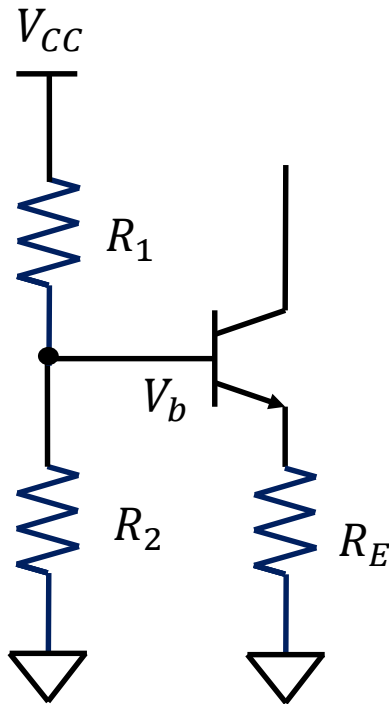
# Bipolar Junction Transistors

- Suppose we want the impedance of the voltage source to be about  $R_{th} = 10 \text{ k}\Omega$ .



$$V_b = V_{CC} \frac{R_2}{R_1 + R_2}$$


$$R_{th} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$R_1 = \frac{V_{CC}}{V_b} R_{th} = \left( \frac{5 \text{ V}}{2.4 \text{ V}} \right) (10 \text{ k}\Omega) = 21 \text{ k}\Omega$$

$$R_2 = R_1 \frac{V_b}{V_{CC} - V_b} = (21 \text{ k}\Omega) \left( \frac{2.4 \text{ V}}{2.6 \text{ V}} \right) = 19 \text{ k}\Omega$$
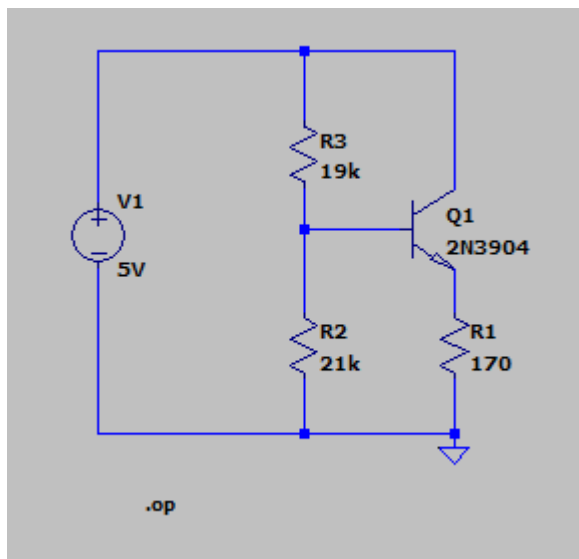
# Bipolar Junction Transistors

- These estimates provide a good starting point for simulating the circuit:



```
--- Operating Point ---
V(n001) :      5      voltage
V(n002) :      2.31434 voltage
V(n003) :      1.59986 voltage
Ic(Q1) :      0.00937979 device_current
Ib(Q1) :      3.11436e-005 device_current
Ie(Q1) :      -0.00941094 device_current
I(R3) :      0.00014135 device_current
I(R2) :      0.000110207 device_current
I(R1) :      0.00941094 device_current
I(V1) :      -0.00952115 device_current
```

This is close... maybe raise the base voltage a little bit by increasing R2.

$$R_2 = 24 \text{ k}\Omega \text{ gives } I_c = 10.075 \text{ mA.}$$



# Temperature Dependence



- Recall that the potential across the PN junction is temperature dependent:

$$I = I_0 \left( e^{eV/kT} - 1 \right)$$

$$V_{be} = \frac{kT}{e} \log \left( \frac{I}{I_0} \right)$$

- The current source should vary linearly with temperature.


# Temperature Dependence

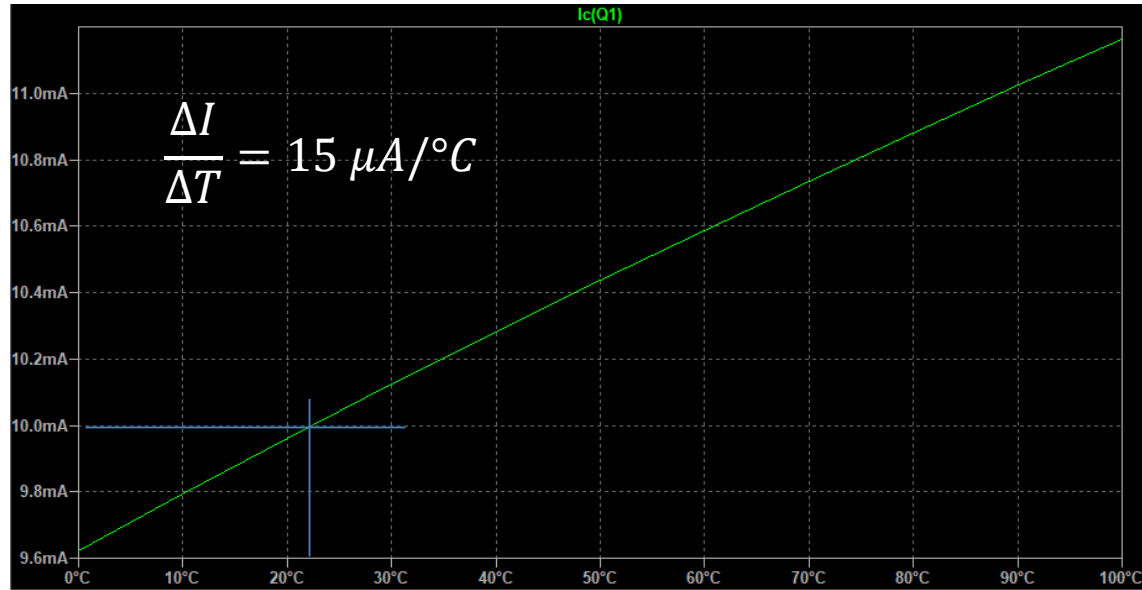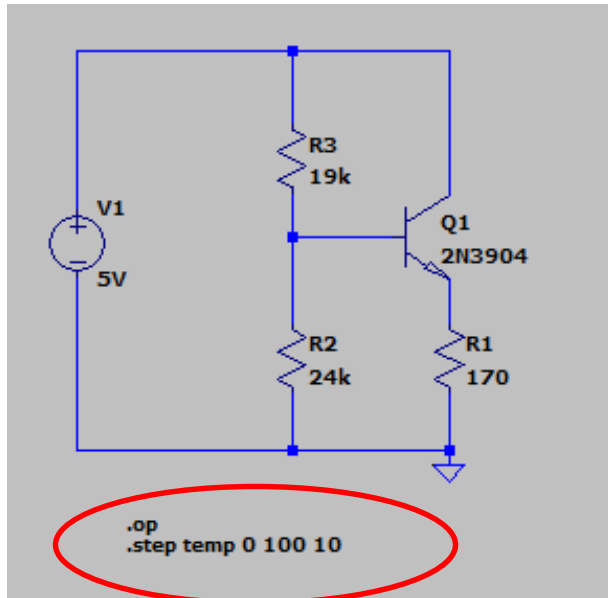

- Sometimes this is perfect: it provides an ideal way to measure temperature.
- This is usually not ideal... the current depends linearly on temperature.
- Thermal runaway: more current dissipates more power and heats up the junction even more...
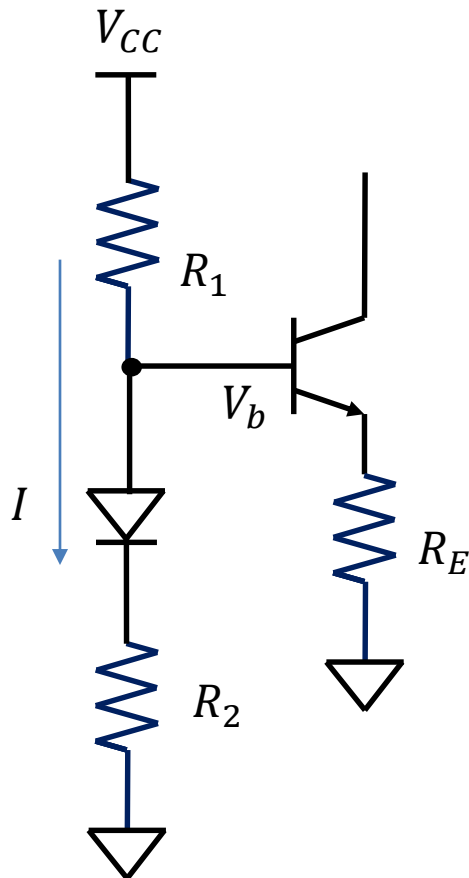
# Temperature Compensation

- What if we added another PN junction in the voltage divider?




- Now the base voltage is

$$V_b = I R_2 + V_D$$

$$I = \frac{V_{CC} - V_D}{R_1 + R_2}$$

$$V_b = \frac{V_{CC} R_2 + R_1 V_D}{R_1 + R_2}$$

# Temperature Compensation

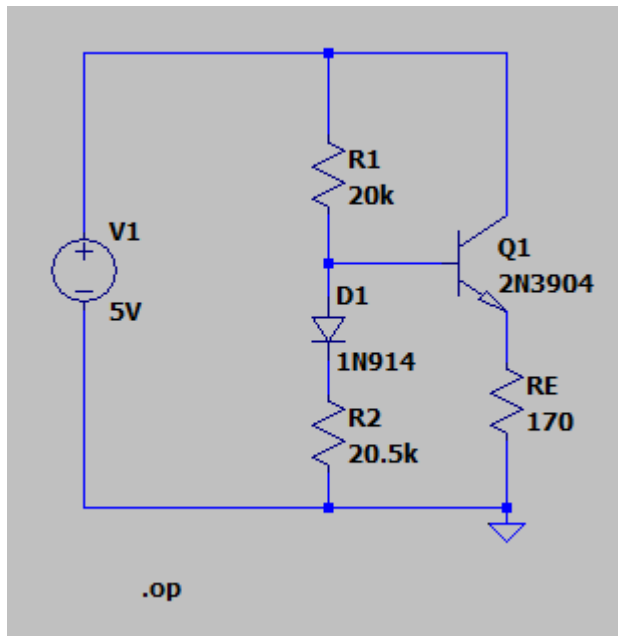


```

--- Operating Point ---
V(n001) :      5          voltage
V(n002) :      2.42848    voltage
V(n003) :      1.71207    voltage
V(n004) :      1.95074    voltage
Ic(Q1) :      0.0100376   device_current
Ib(Q1) :      3.34179e-005 device_current
Ie(Q1) :      -0.010071   device_current
I(D1) :      9.5158e-005  device_current
I(R1) :      0.000128576  device_current
I(R2) :      9.5158e-005  device_current
I(Re) :      0.010071     device_current
I(V1) :      -0.0101661   device_current
    
```

- $R_1$  and  $R_2$  are adjusted to achieve 10 mA
- This results in only partial temperature

compensation:  $V_b \propto \frac{R_1 V_D}{R_1 + R_2}$


# Temperature Dependence

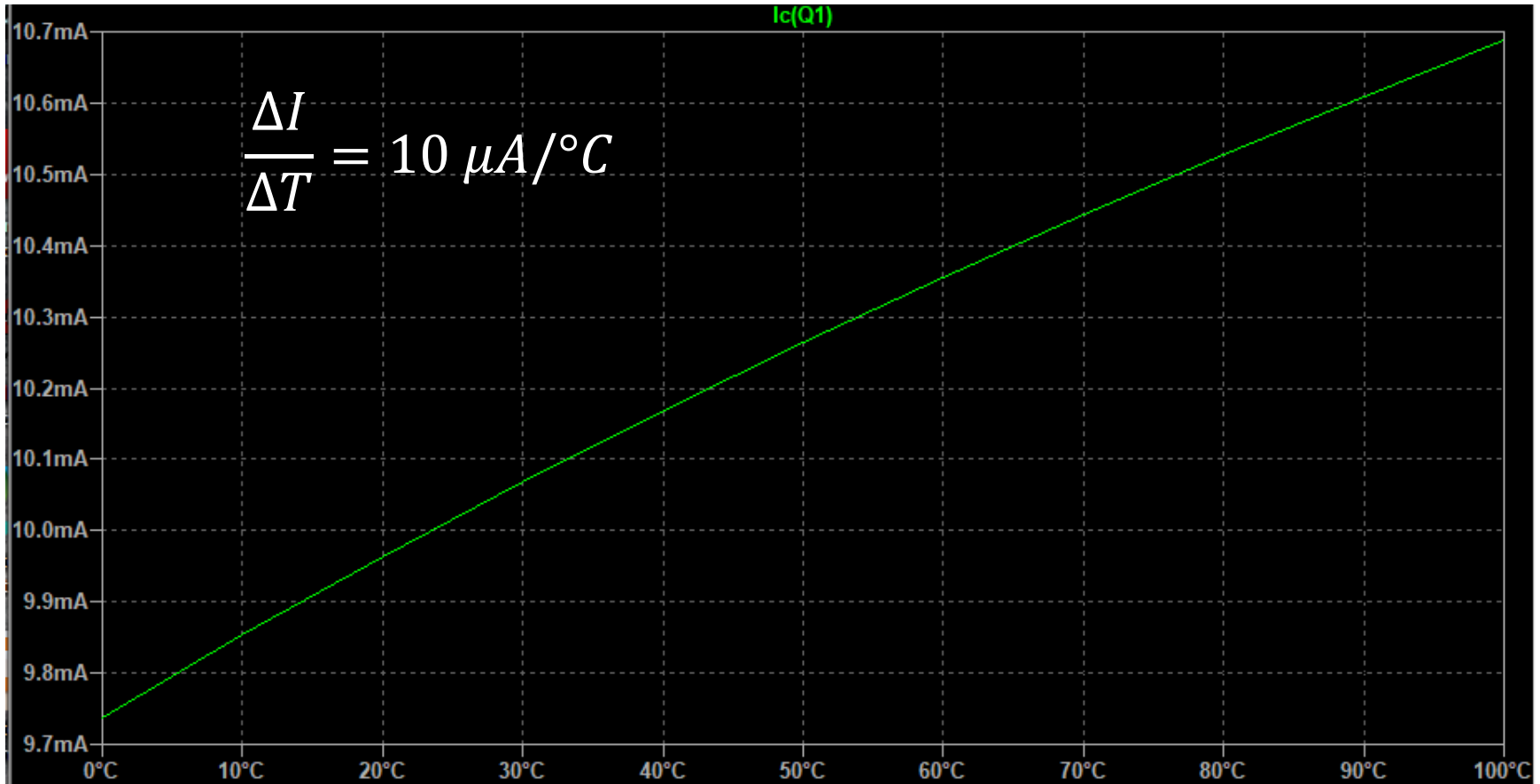

The base voltage still depends on the current through the resistor divider.

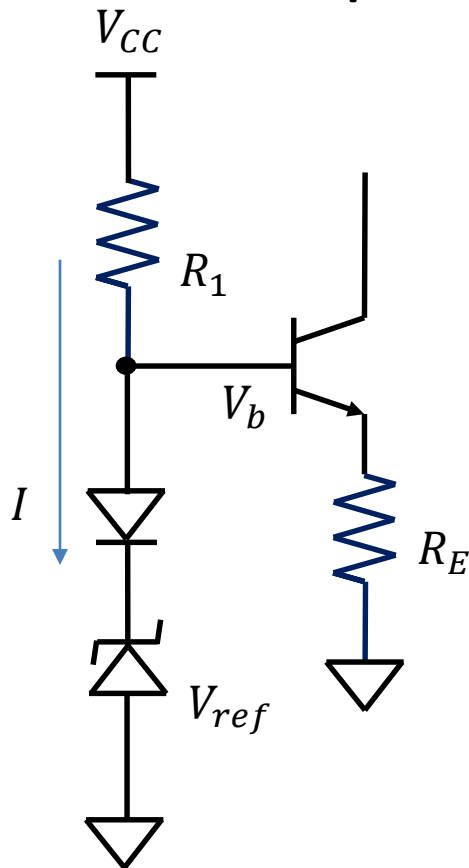
# Temperature Dependence

- A voltage reference can provide a voltage that is independent of the current




- They typically have a high output impedance


- Example:

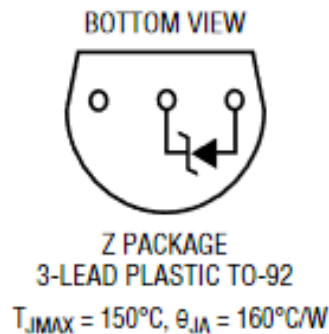

LT1004  
Micropower Voltage  
Reference

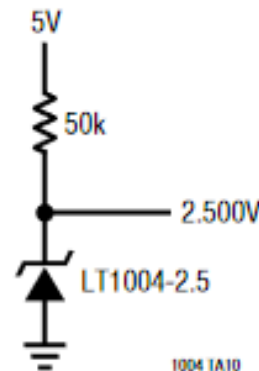

# Temperature Compensation

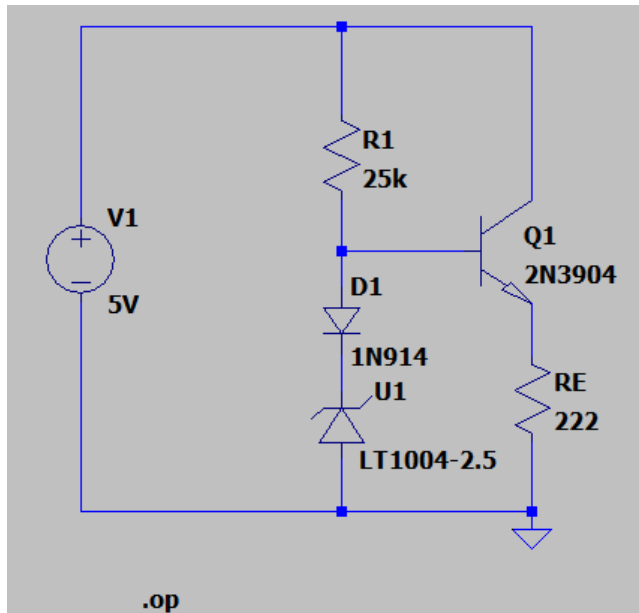

```

--- Operating Point ---


V(n001) :      5      voltage
V(n002) :      2.94711 voltage
V(n003) :      2.23062 voltage
V(n004) :      2.49994 voltage
Ic(Q1) :      0.0100143 device_current
Ib(Q1) :      3.35122e-005 device_current
Ie(Q1) :      -0.0100478 device_current
I(D1) :      4.86034e-005 device_current
I(R1) :      8.21156e-005 device_current
I(Re) :      0.0100478 device_current
I(V1) :      -0.0100964 device_current
Ix(u1:1) :      4.86034e-005 subckt_current
Ix(u1:2) :      -4.86034e-005 subckt_current
    
```



$$\frac{\Delta I}{\Delta T} = 3 \mu A/^{\circ}C$$

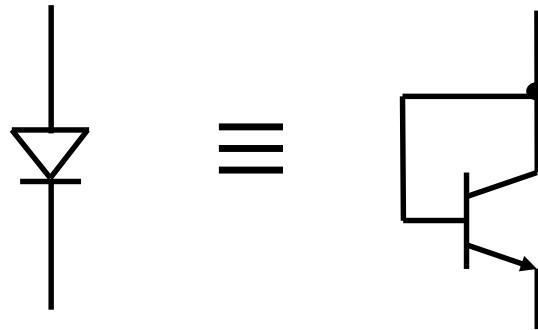
# Temperature Compensation

- Better temperature compensation can be achieved by using exactly the same type of PN junction in the voltage reference circuit





# Temperature Compensation

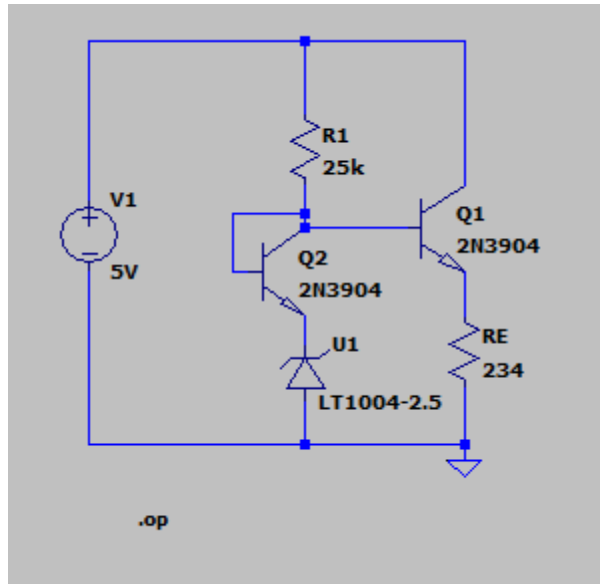


```

--- Operating Point ---
V(n001):      5          voltage
V(n002):      3.07384    voltage
V(n003):      2.35724    voltage
V(n004):      2.49994    voltage
Ic(Q2):       4.32593e-005 device_current
Ib(Q2):       1.44214e-007 device_current
Ie(Q2):       -4.34035e-005 device_current
Ic(Q1):       0.01004    device_current
Ib(Q1):       3.3643e-005 device_current
Ie(Q1):       -0.0100737 device_current
I(R1):        7.70465e-005 device_current
I(RE):        0.0100737  device_current
I(V1):        -0.0101171 device_current
Ix(u1:1):     4.34035e-005 subckt_current
Ix(u1:2):     -4.34035e-005 subckt_current
    
```




$$\frac{\Delta I}{\Delta T} = 0.68 \mu A/^{\circ}C$$


# Current Mirror

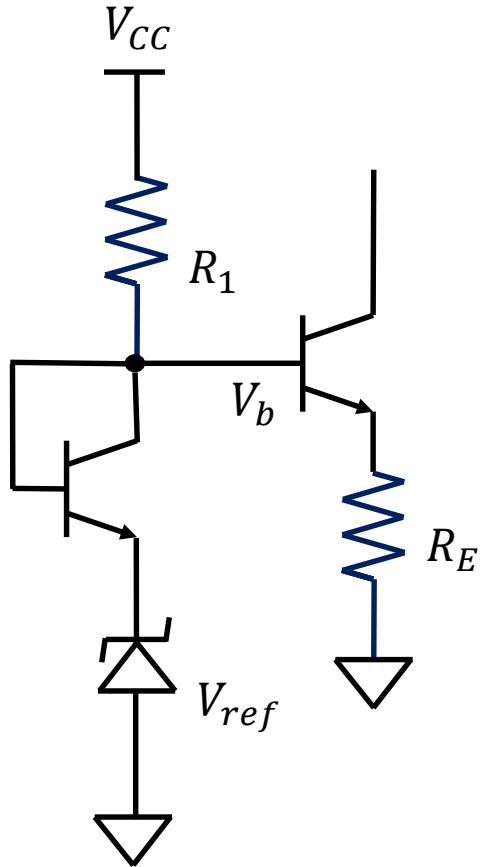

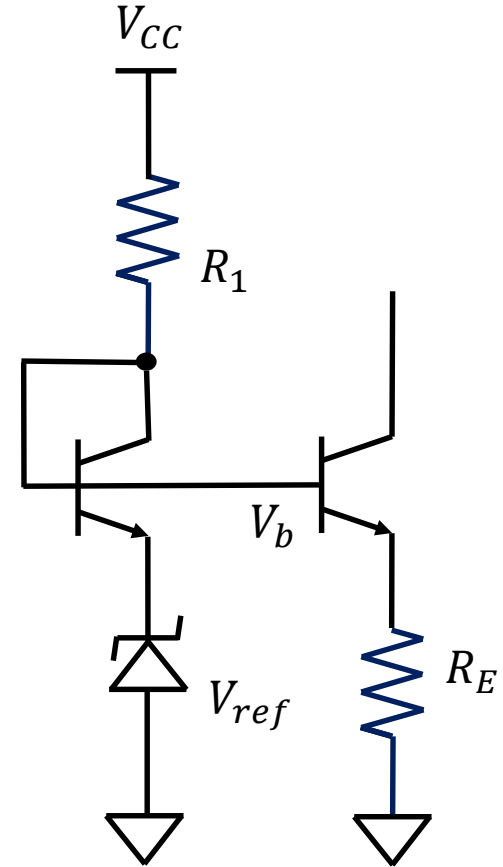This is frequently also drawn this way, particularly in IC designs...





# Current Mirror

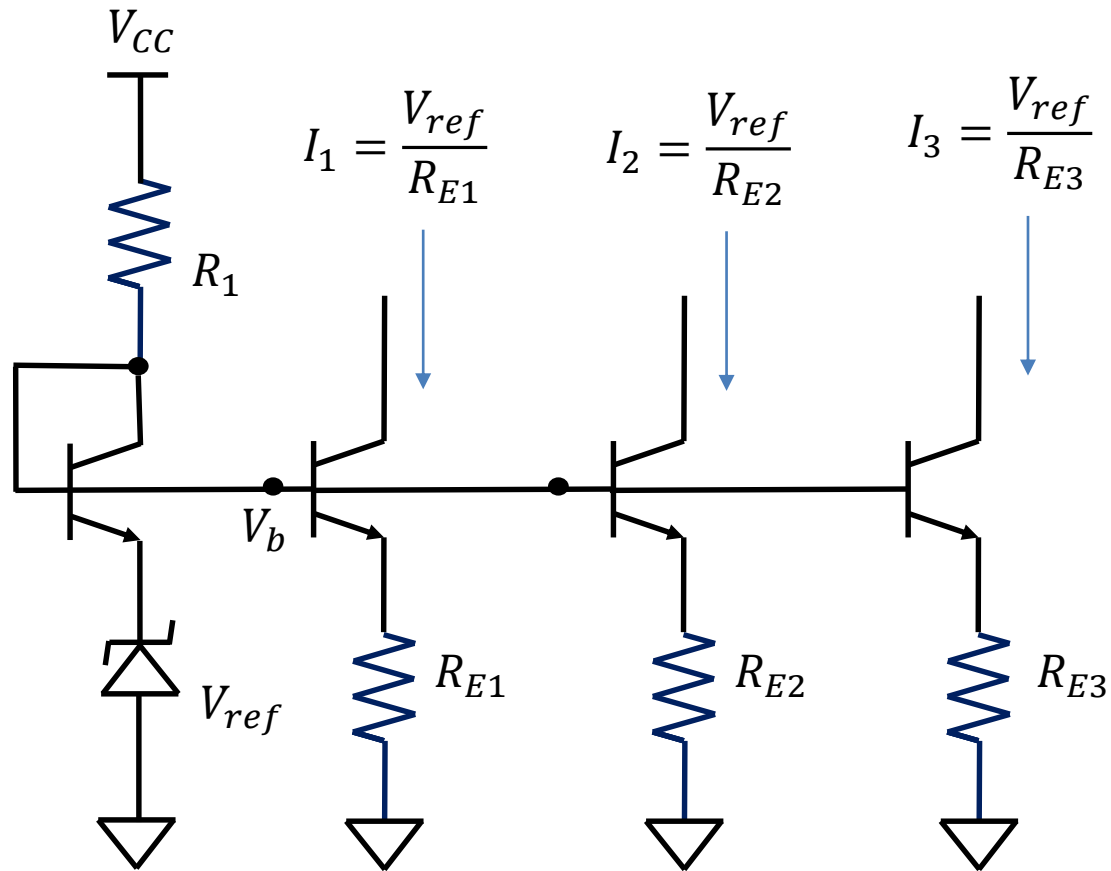

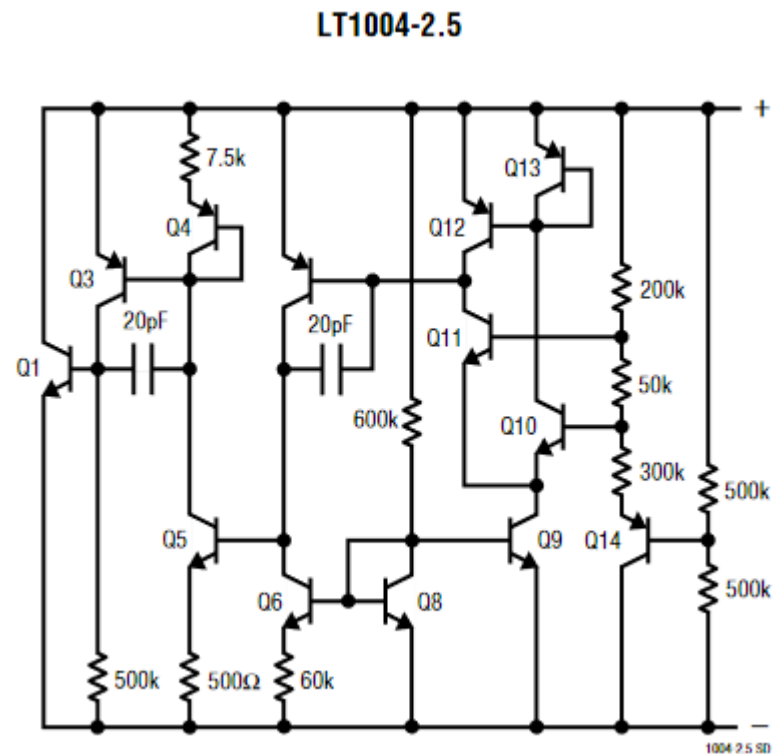
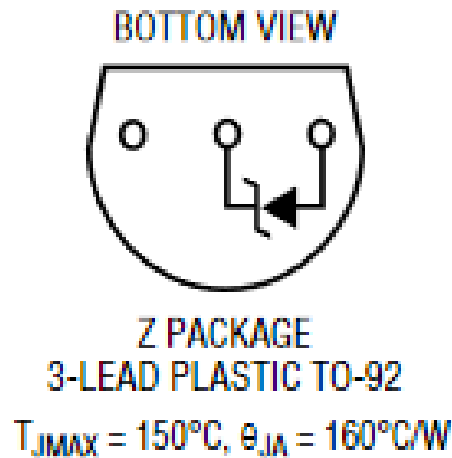
# Current Mirror

- Now you can recognize the purpose of some of the transistors in complicated circuits:


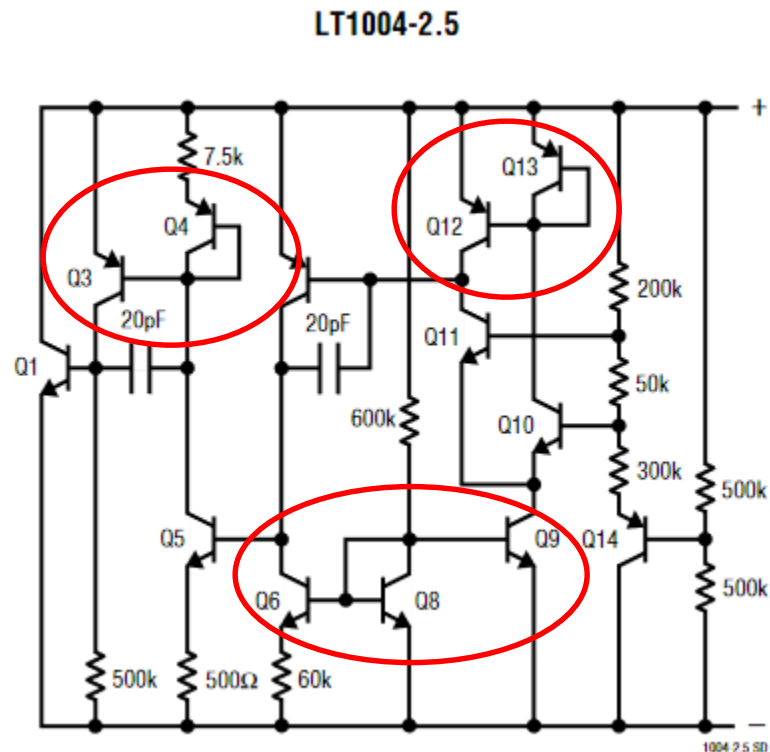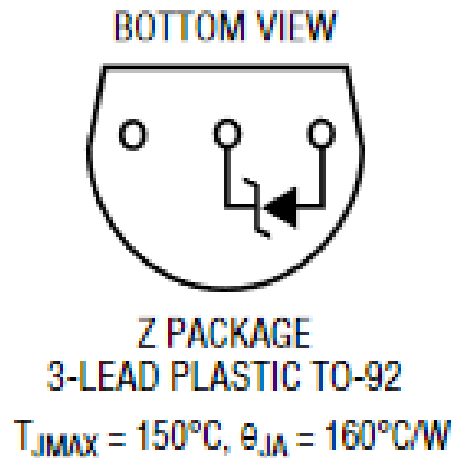
# Current Mirror

- Now you can recognize the purpose of some of the transistors in complicated circuits:



# Current Mirror


- Transistors have maximum current ratings:

**MAXIMUM RATINGS**

Rating	Symbol	Value	Unit
Collector – Emitter Voltage	$V_{CEO}$	40	Vdc
Collector – Base Voltage	$V_{CBO}$	60	Vdc
Emitter – Base Voltage	$V_{EBO}$	6.0	Vdc
Collector Current – Continuous	$I_C$	200	mA <sub>dc</sub>
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	625 5.0	mW mW/ $^\circ\text{C}$
Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above $25^\circ\text{C}$	$P_D$	1.5 12	W mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	$T_J, T_{stg}$	-55 to +150	$^\circ\text{C}$

- This may not matter much for discrete components, but it can be limiting in integrated circuits.

# Output Characteristics

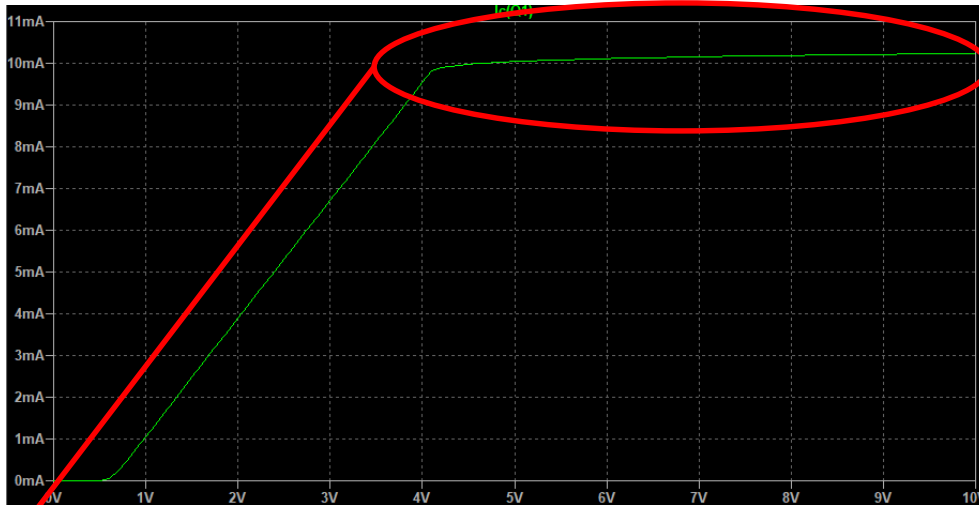


This is still not a perfect current source. The output impedance is about 20 k $\Omega$ .



Sensitivity to the exact power supply voltage could be a problem.

# Wilson Current Mirror

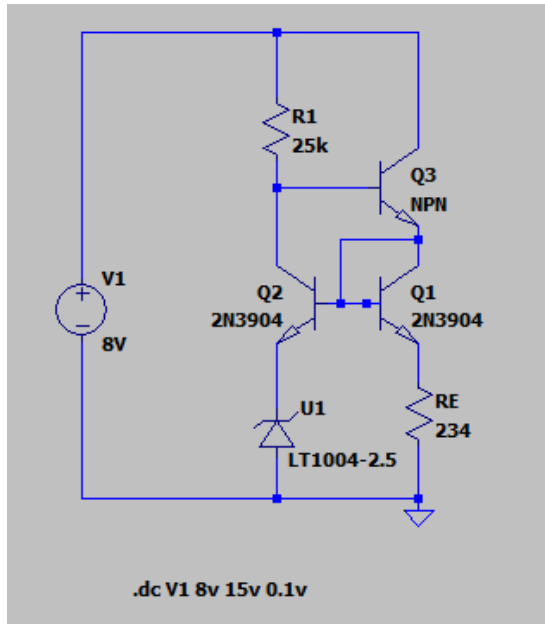

Now the output impedance is 35 k $\Omega$  but the collector of Q3 is at a higher potential with respect to ground.