


Physics 53600
**Electronics Techniques for
Research**

Now in PowerPoint!

Spring 2020 Semester

Prof. Matthew Jones

Current Mirror

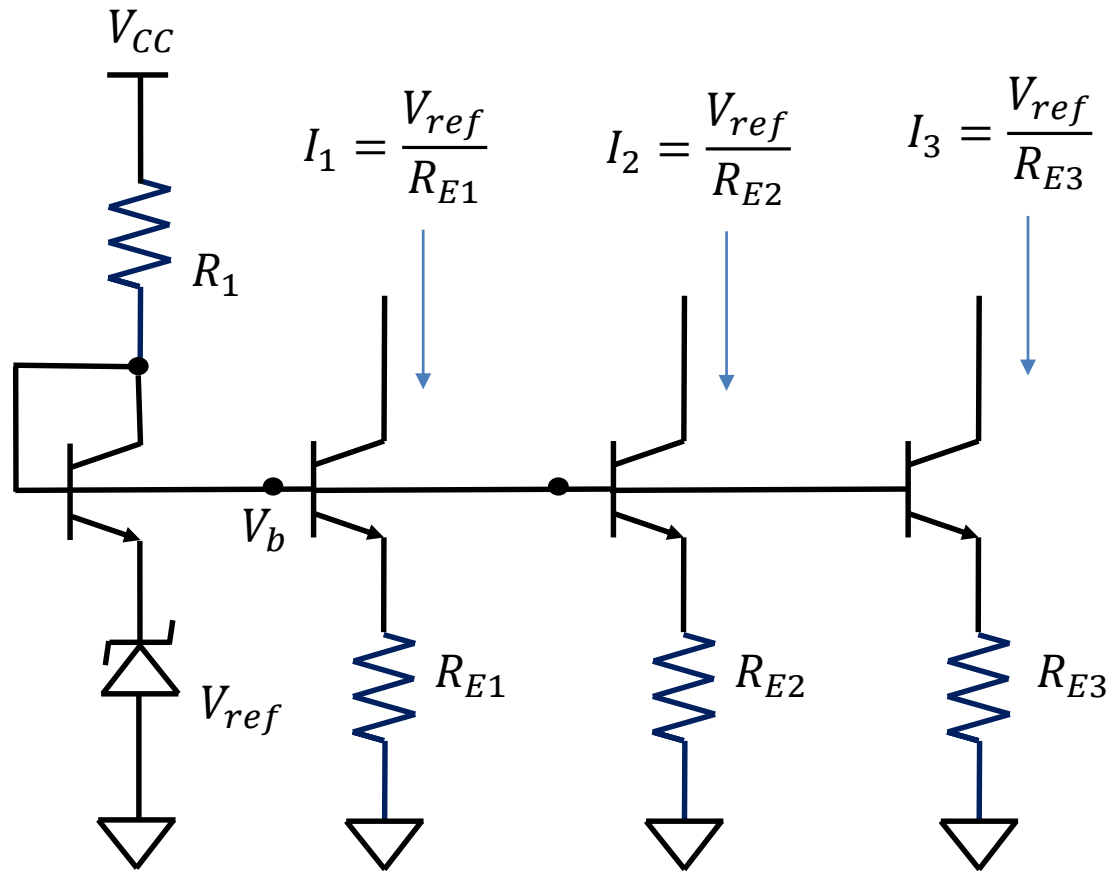


Current Mirror

- What good are all these current sources?
- They can provide the quiescent current through other transistors
- This is the default current when no other signal is present

Differential Pair

- Consider this circuit:

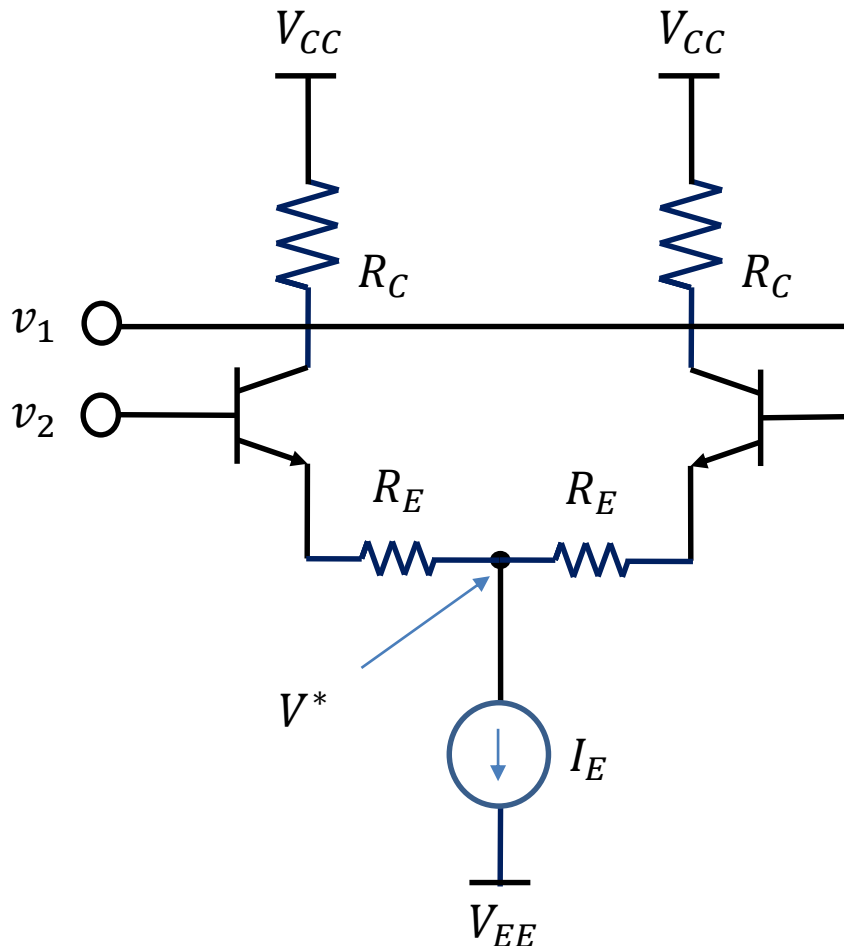

1. Ignore currents flowing into bases

2. $I_1 + I_2 = I_E$ (always!)

3. $V_{E1} = v_1 - V_{be}$
 $V_{E2} = v_2 - V_{be}$

4. $I_1 = \frac{V_{E1} - V^*}{R_E}$
 $I_2 = \frac{V_{E2} - V^*}{R_E} = I_E - I_1$

$\Rightarrow I_1 = \frac{1}{2} \left(I_E - \frac{v_2 - v_1}{R_E} \right)$

$\Rightarrow I_2 = \frac{1}{2} \left(I_E + \frac{v_2 - v_1}{R_E} \right)$

Differential Pair

- The output can be taken from the collector of one of the resistors

$$\begin{aligned}v_{out} &= V_{CC} - I_1 R_C \\ \delta v_{out} &= -\delta I_1 R_C \\ &= -\delta(v_1 - v_2) \frac{R_C}{2R_E}\end{aligned}$$

- v_{out} does not depend on V_{be}
 - No temperature dependence
- v_{out} depends only on Δv , not on v_1 or v_2 explicitly


Differential Pair

- v_{out} measures the differential voltage between v_1 and v_2
- The common mode voltage is cancelled


$$\Delta v = v_1 - v_2$$
$$v_{cm} = \frac{1}{2}(v_1 + v_2)$$

- Any electronic noise picked up on both v_1 and v_2 will be cancelled.
- The total current draw is constant; it is just switched between the two transistors.


Differential Pair

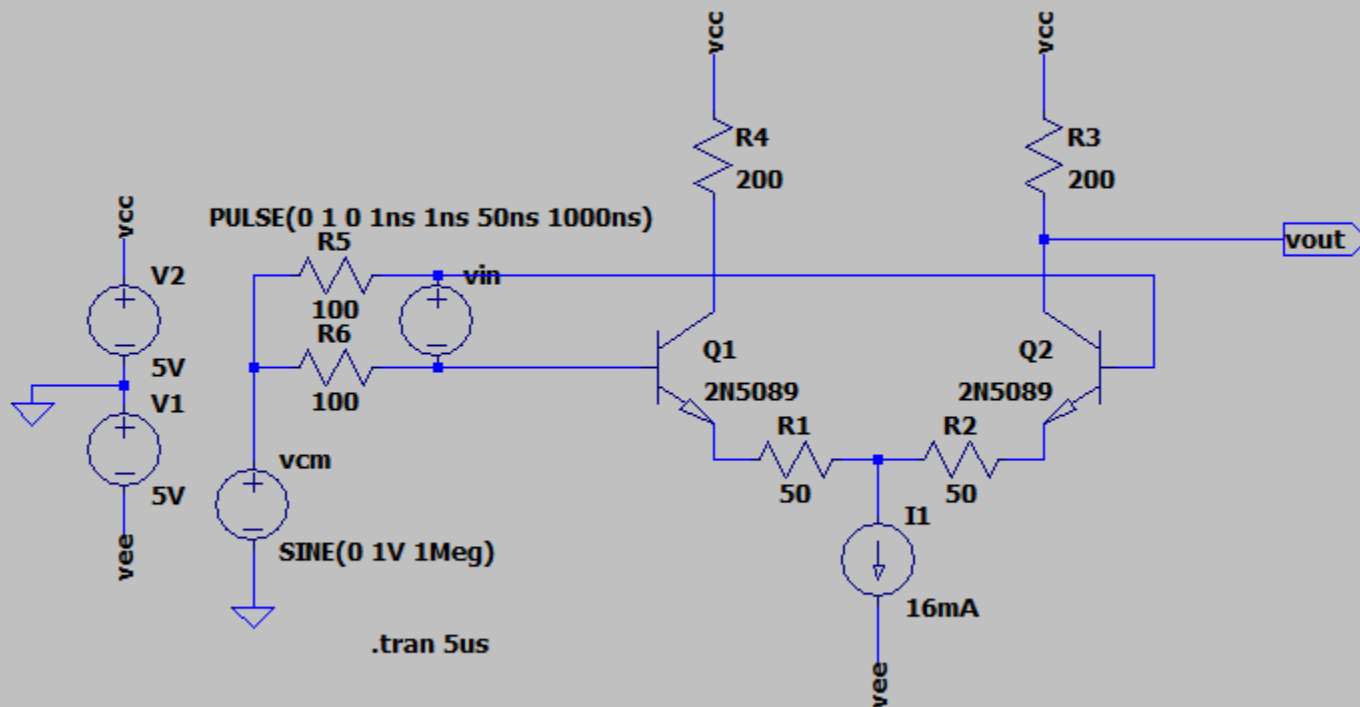

Differential Pair

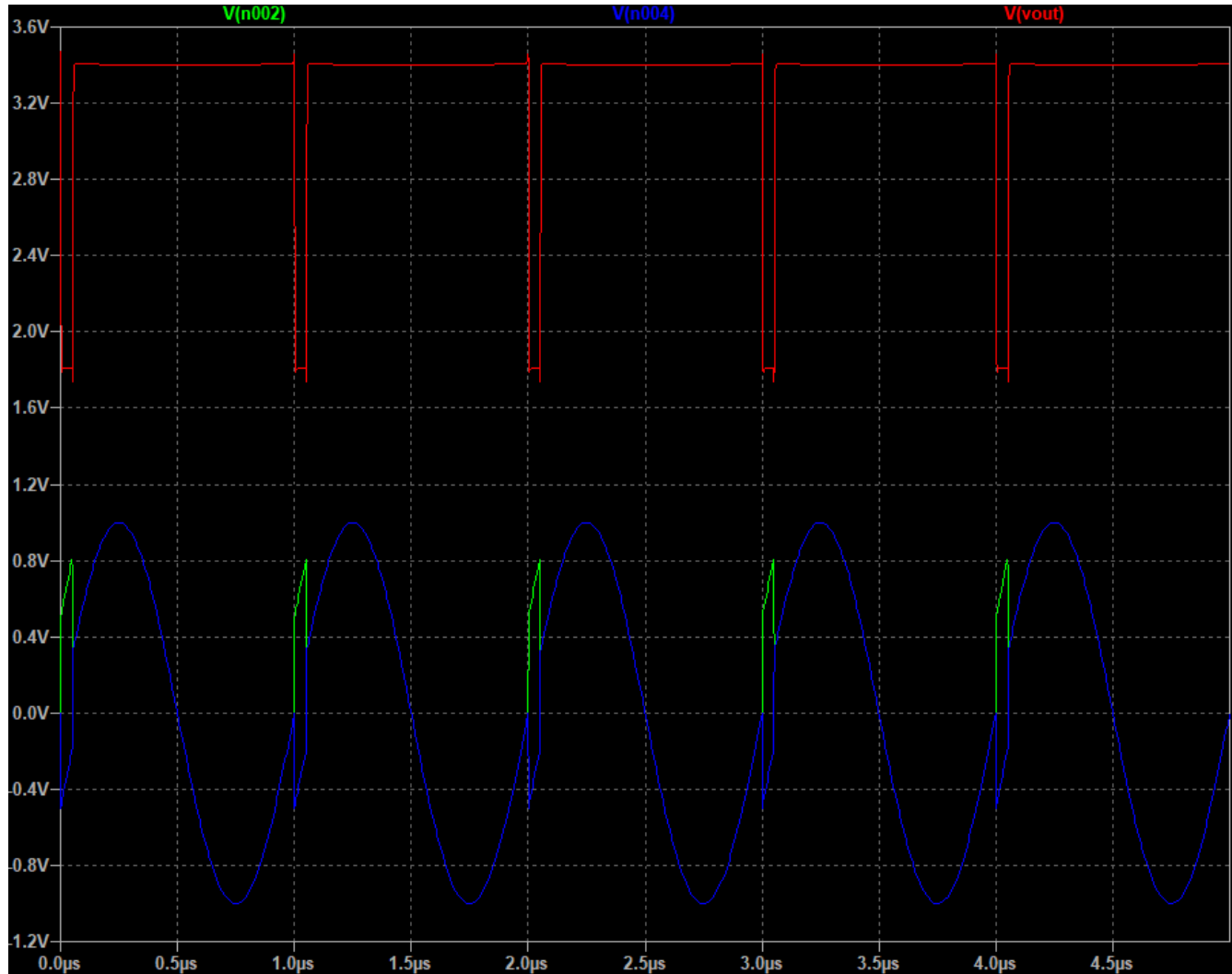

Differential Pair

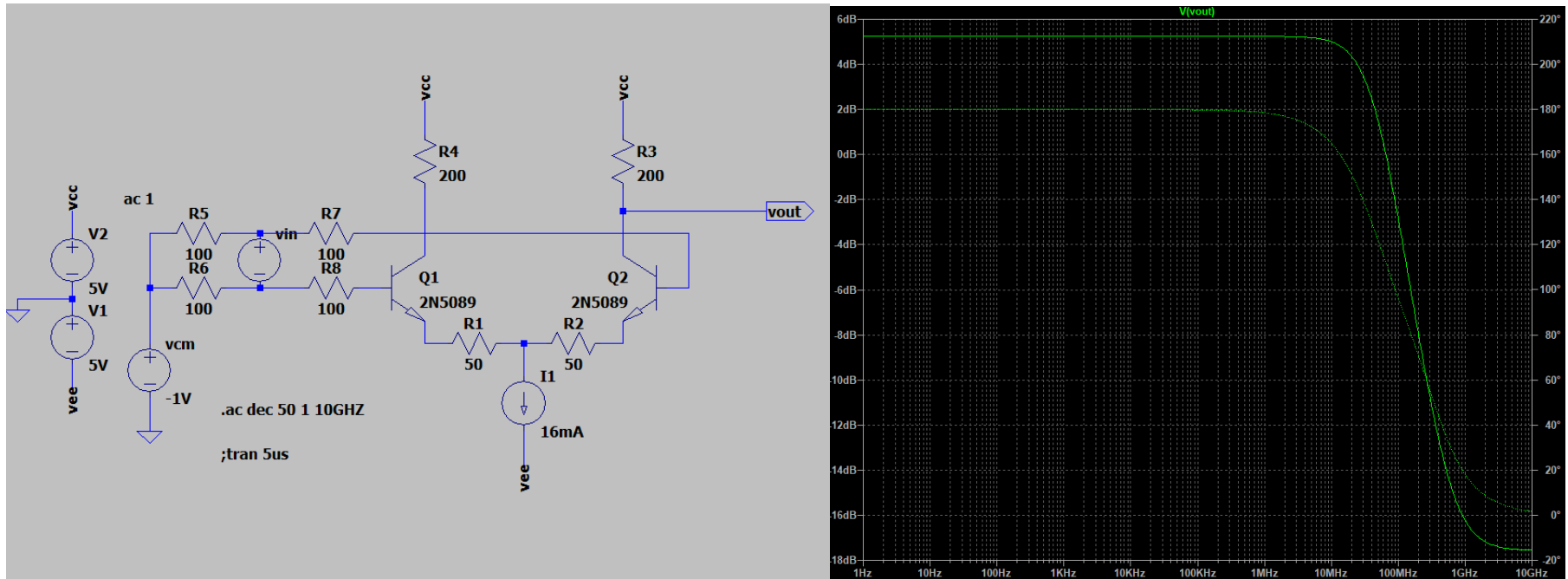


Gain reduced by -3 dB at about 40 MHz

What limits the frequency response?


- Parasitic capacitance within the transistors between the collector and the base
- What if we could shield the base by keeping the collector at a constant potential?

Cascode Configuration

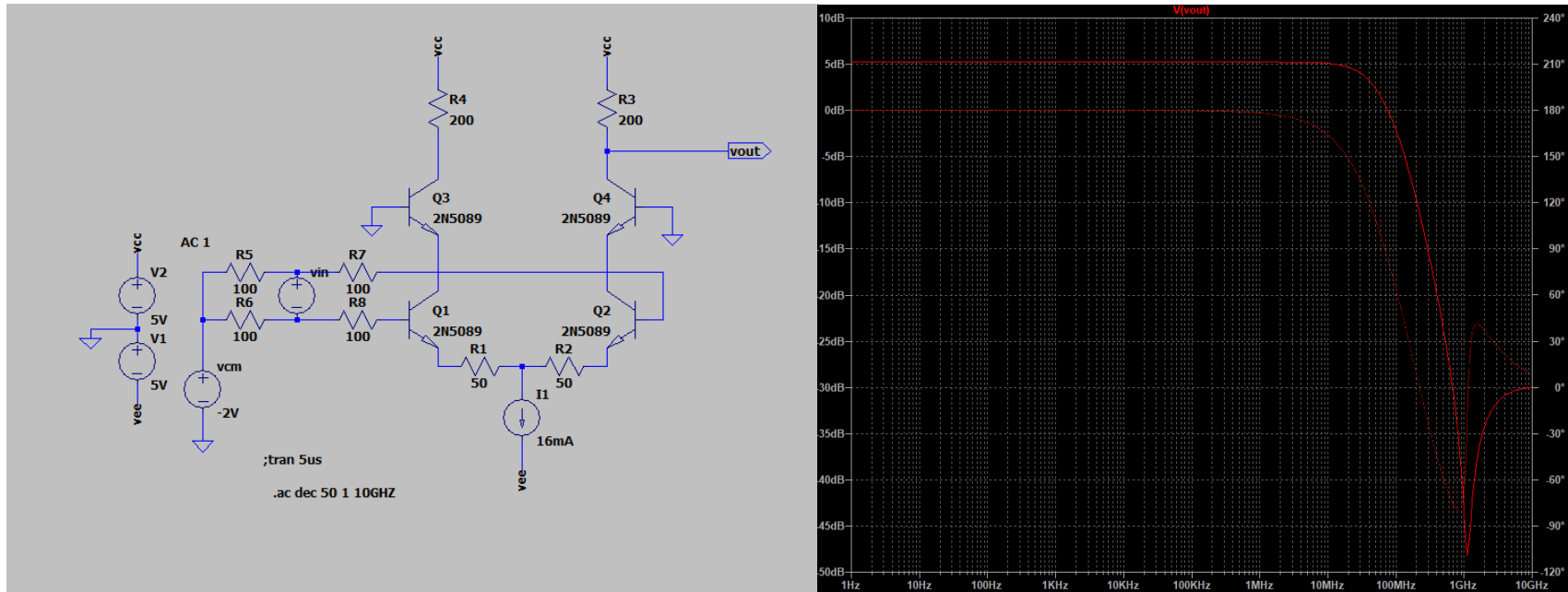

- Now the gain is reduced by -3 dB at about 60 MHz
 - More important for higher speed transistors
- (it's a good design practice but your mileage may vary)

Transistor Configurations

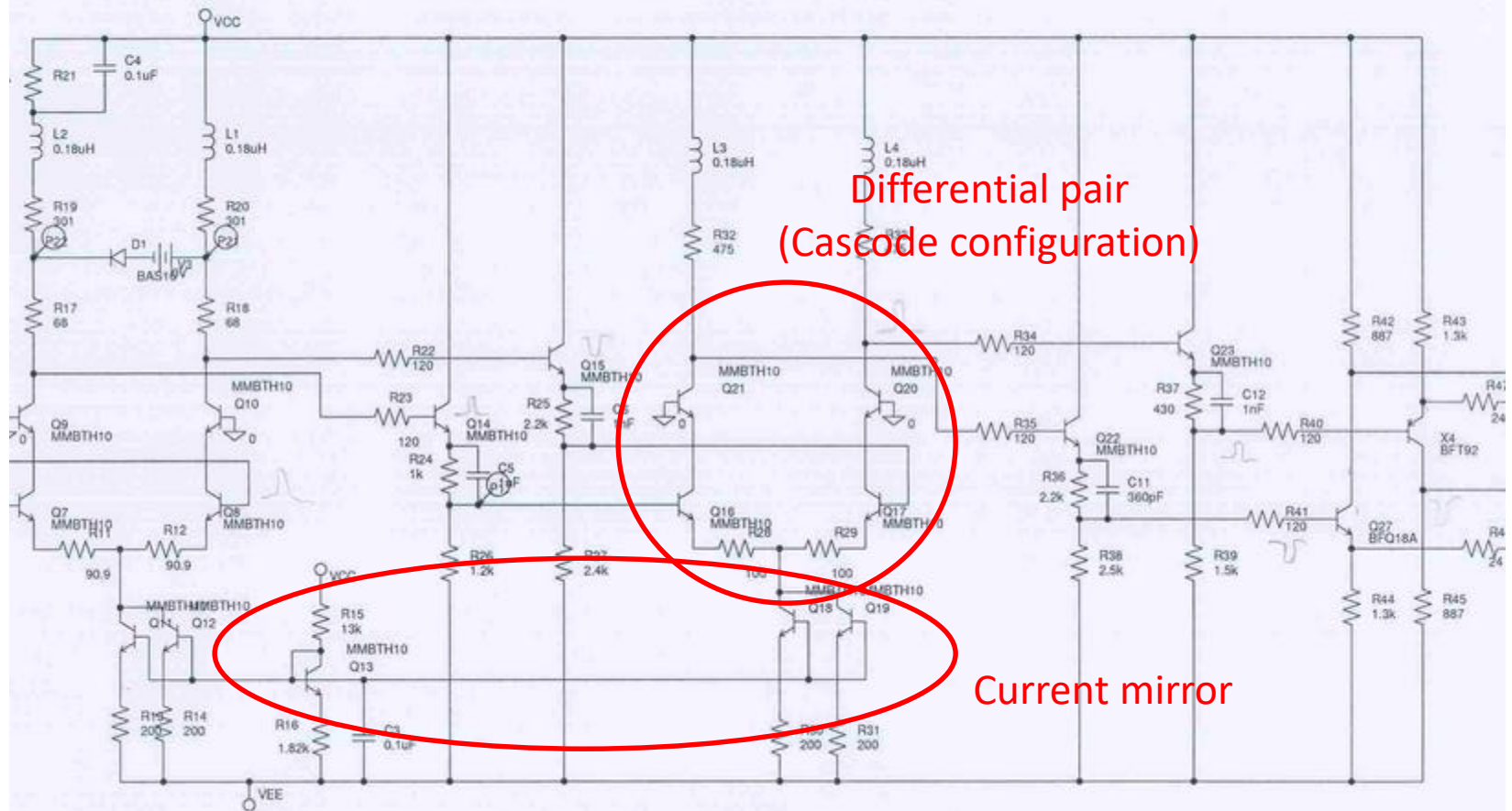


Discrete Component Amplifiers

- Advantages:
 - Relatively simple
 - Specific to a given application
 - Can be quite fast / high frequency
- Disadvantages:
 - Limited dynamic range
 - Possibly non-linear
 - Complexity of design needed to counteract non-ideal characteristics

Operational Amplifiers

- An operational amplifier is a multi-stage amplifier that provides:
 - Very large intrinsic gain
 - Very high input impedance
 - Very low output impedance
- Easily configured into a wide range of analog circuits using discrete components

Operational Amplifiers

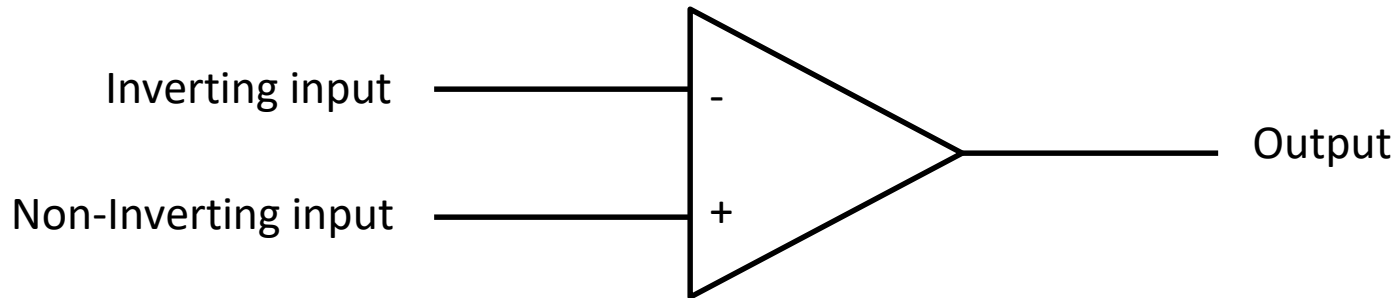

- Connections to the power supply are often not shown.
- Open loop gain:
$$v_{out} = A_0(v_+ - v_-)$$
- The parameter A_0 is usually very large (10^5 - 10^6)

Operational Amplifiers


- In practice, A_0 depends on frequency:



- Typically, the product of the intrinsic gain and the bandwidth is a constant.
 - And it's called the Gain-Bandwidth product

Operational Amplifiers

- So what good is this?

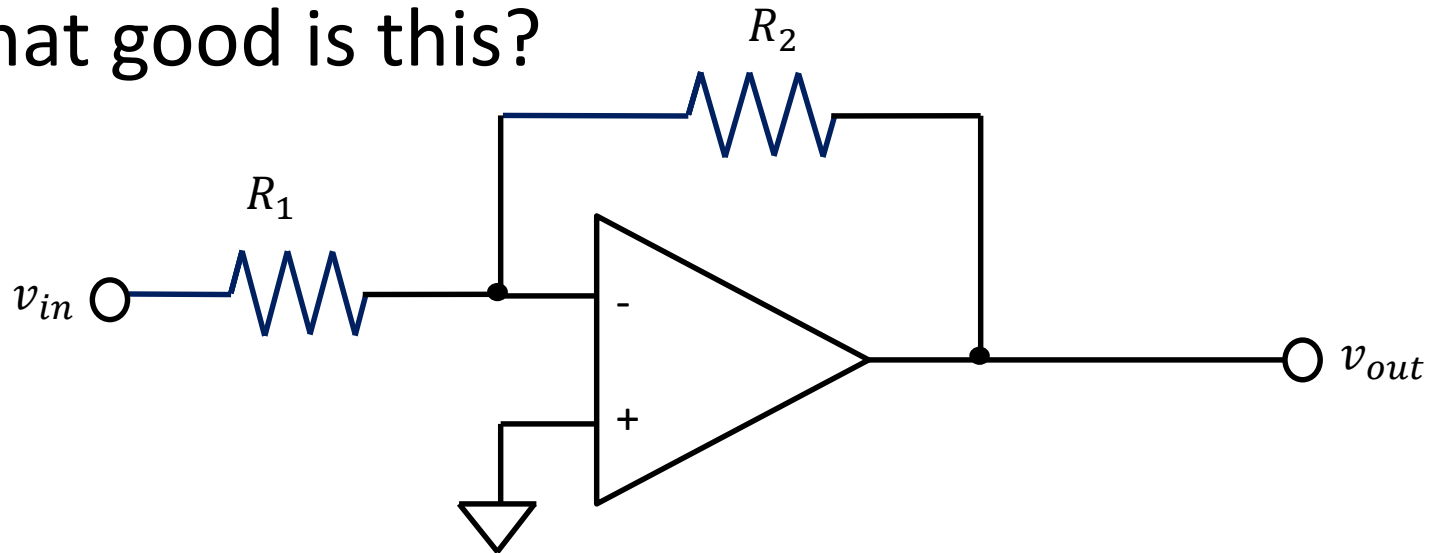

$$v_+ = 0 \text{ V (connected to ground)}$$

$$v_- = \frac{v_{in}R_2 + v_{out}R_1}{R_1 + R_2}$$

$$v_{out} = A_0(v_+ - v_-) = -A_0v_-$$

Operational Amplifiers

- After a little bit of algebra...

$$v_{out} \left(\frac{1}{A_0} + \frac{R_1}{R_1 + R_2} \right) = - \frac{v_{in} R_2}{R_1 + R_2}$$


- But $A_0 \gg 1$ so this becomes

$$v_{out} = -v_{in} \frac{R_2}{R_1}$$

- This configuration is called an inverting amplifier

Operational Amplifiers

- Another example:

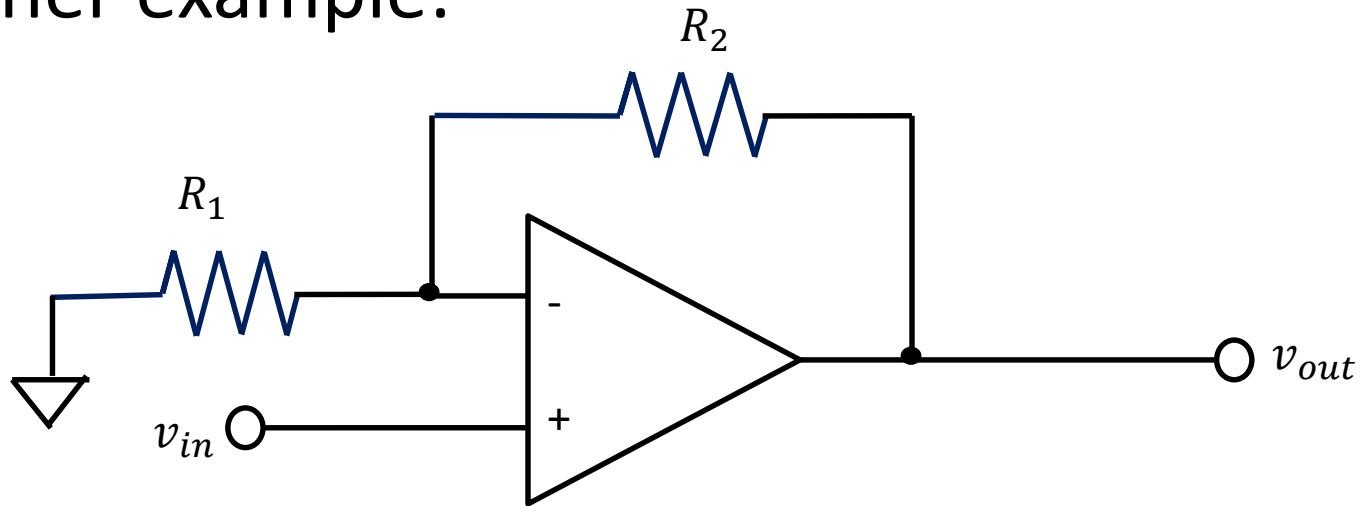

$$v_+ = v_{in}$$

$$v_- = \frac{v_{out} R_1}{R_1 + R_2}$$

$$v_{out} = A_0(v_+ - v_-)$$

Operational Amplifiers

$$v_{out} = \left(v_{in} - \frac{v_{out} R_1}{R_1 + R_2} \right)$$
$$v_{out} \left(\frac{1}{A_0} + \frac{R_1}{R_1 + R_2} \right) = v_{in}$$

- But yet again, $A_0 \gg 1$...

$$v_{out} = v_{in} \left(1 + \frac{R_2}{R_1} \right)$$

- This is called a non-inverting amplifier.

Operational Amplifiers

- There are some simple rules for designing circuits using operational amplifiers:
 1. The inputs draw negligible current
 2. The output will produce whatever voltage is needed to equalize v_+ and v_- (op-amp magic)
- Example: inverting amplifier

$$\begin{aligned}v_+ &= 0 \\v_- &= \frac{v_{in}R_2 + v_{out}R_1}{R_1 + R_2} = 0 \\v_{out} &= -\frac{v_{in}R_2}{R_1}\end{aligned}$$

Operational Amplifiers

- Another example: non-inverting amplifier

$$\begin{aligned}v_+ &= v_{in} \\v_- &= \frac{R_1 v_{out}}{R_1 + R_2} = v_{in} \\v_{out} &= v_{in} \left(\frac{R_1 + R_2}{R_1} \right) = v_{in} \left(1 + \frac{R_2}{R_1} \right)\end{aligned}$$