

Physics 53600


Electronics Techniques for Research

Now in PowerPoint!

Spring 2020 Semester

Prof. Matthew Jones


Operational Amplifiers

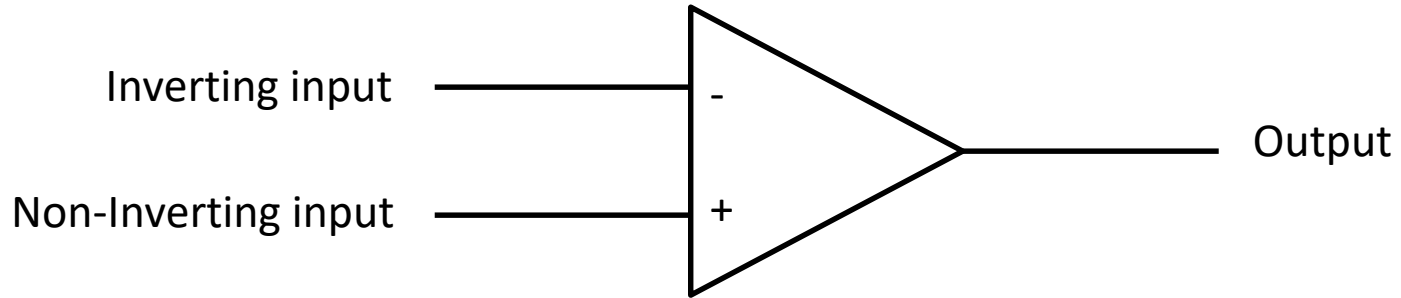


- Basic equation: $v_{out} = A_0(v_+ - v_-)$, $A_0 \gg 1$
- Simplified design rules:
 1. Inputs draw negligible current
 2. Output produces whatever voltage will make $v_+ = v_-$
- Negative feedback:
 - Reduces intrinsic gain
 - Increases bandwidth

Operational Amplifiers


- Inverting amplifier:

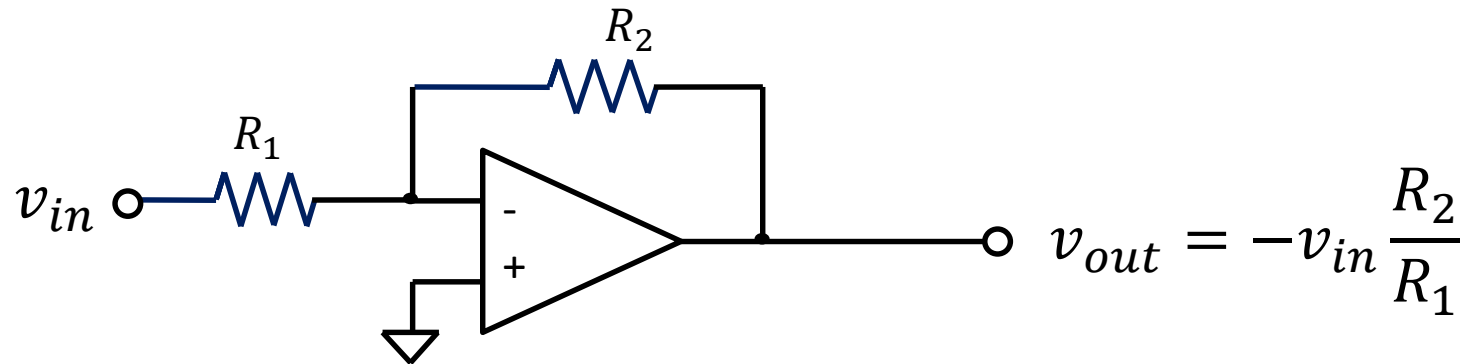

- Non-inverting amplifier:

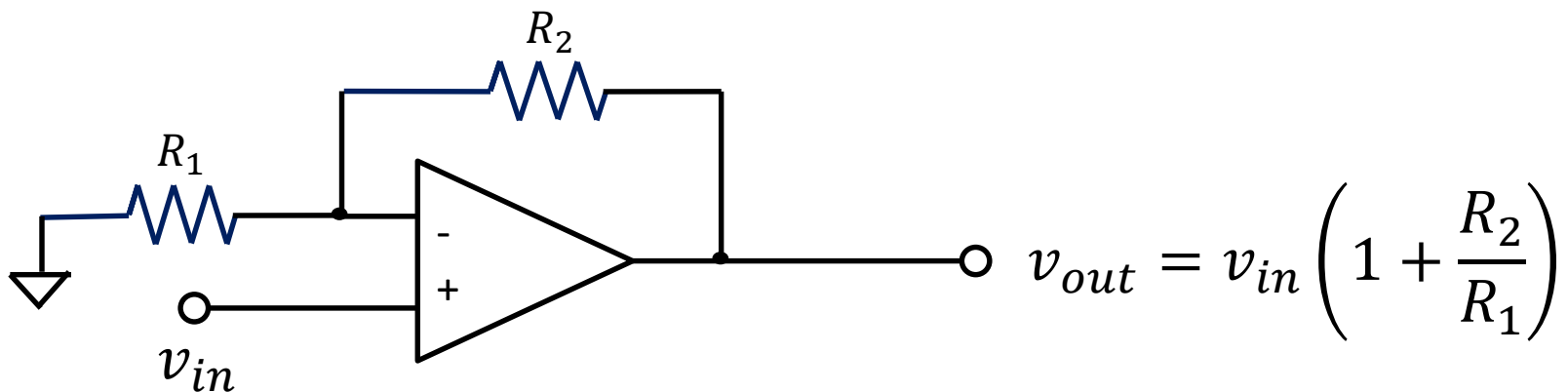

Operational Amplifiers

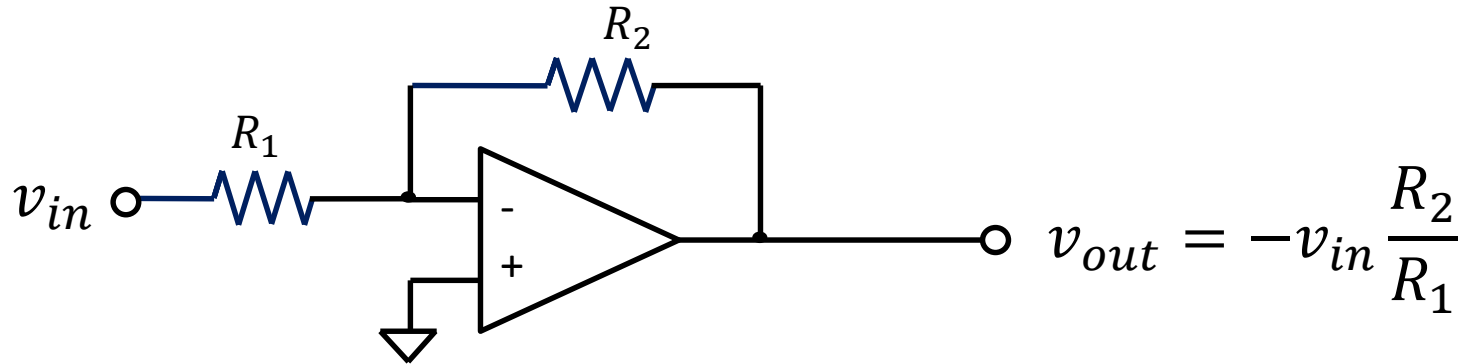

- Input impedance:

$$v_- = 0 \text{ so } i_{R_1} = v_{in}/R_1$$

Input impedance is just R_1


- Output impedance depends on the device in question. It also depends on the gain and the frequency.

Operational Amplifiers

- For low frequencies,


$$R_{out} \lesssim 100 \, \Omega$$

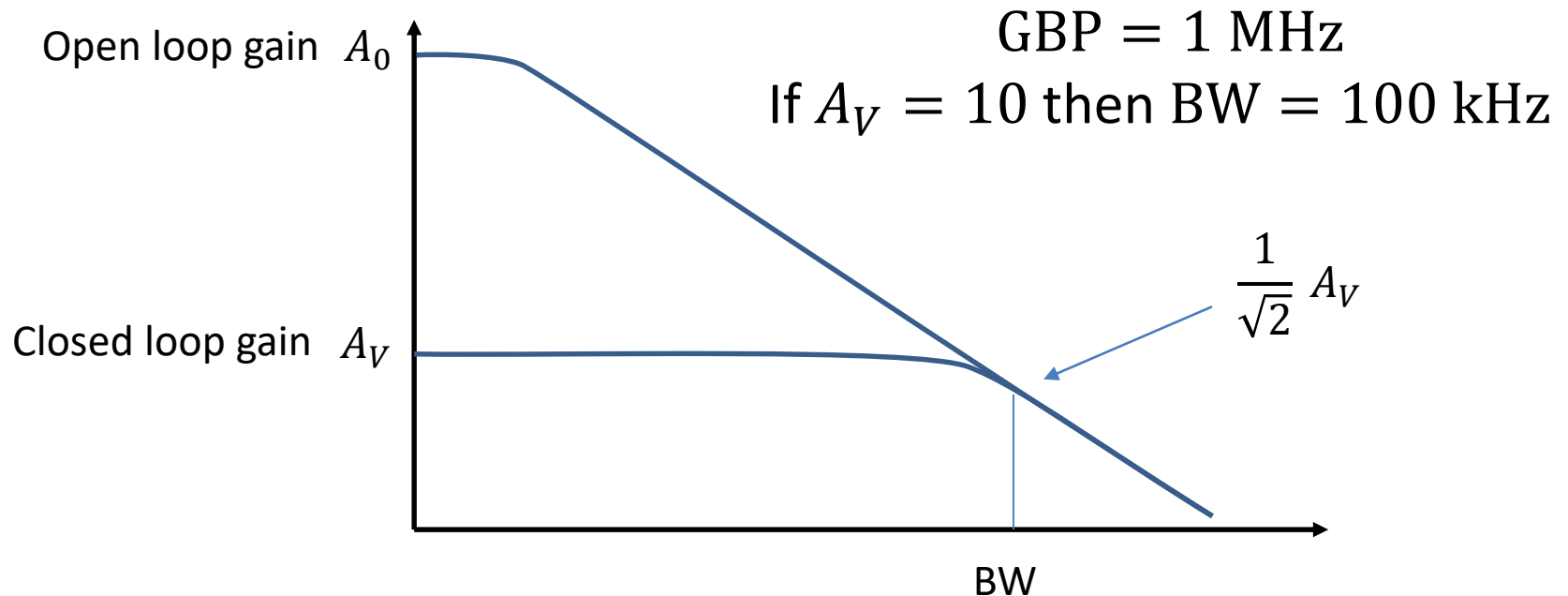- This is dynamically adjusted by the feedback loop
- Frequency response:



Operational Amplifiers

- Summing amplifier:

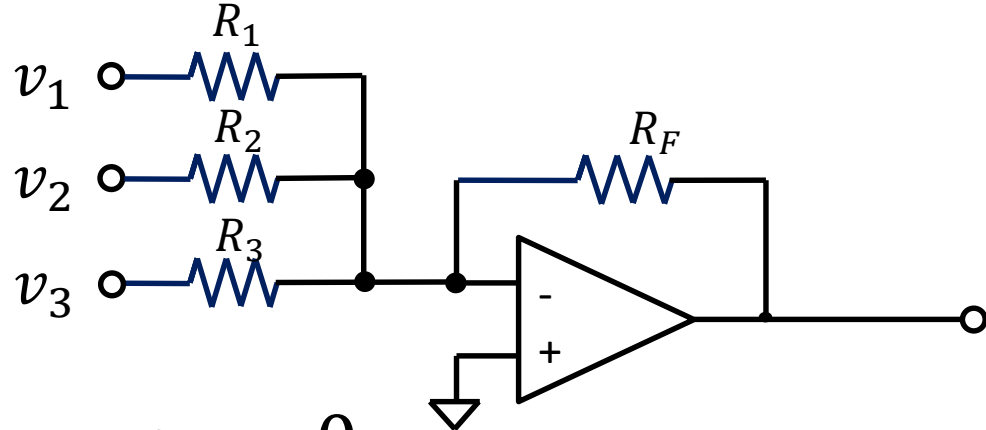

$$v_+ = 0$$

$$v_- = 0$$

- No current flows into the inverting input.

$$\begin{aligned} v_{out} &= -(i_1 + i_2 + i_3)R_F \\ &= -R_F \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} \right) \end{aligned}$$

Operational Amplifiers


- If $R_1 = R_2 = R_3 \equiv R$ then

$$v_{out} = -\frac{R_F}{R} (v_1 + v_2 + v_3)$$

- If R_1, R_2, R_3 are large compared with the output impedance of any non-ideal voltage sources attached to v_1, v_2, v_3 then this will be a good approximation.

Subtracting Amplifier

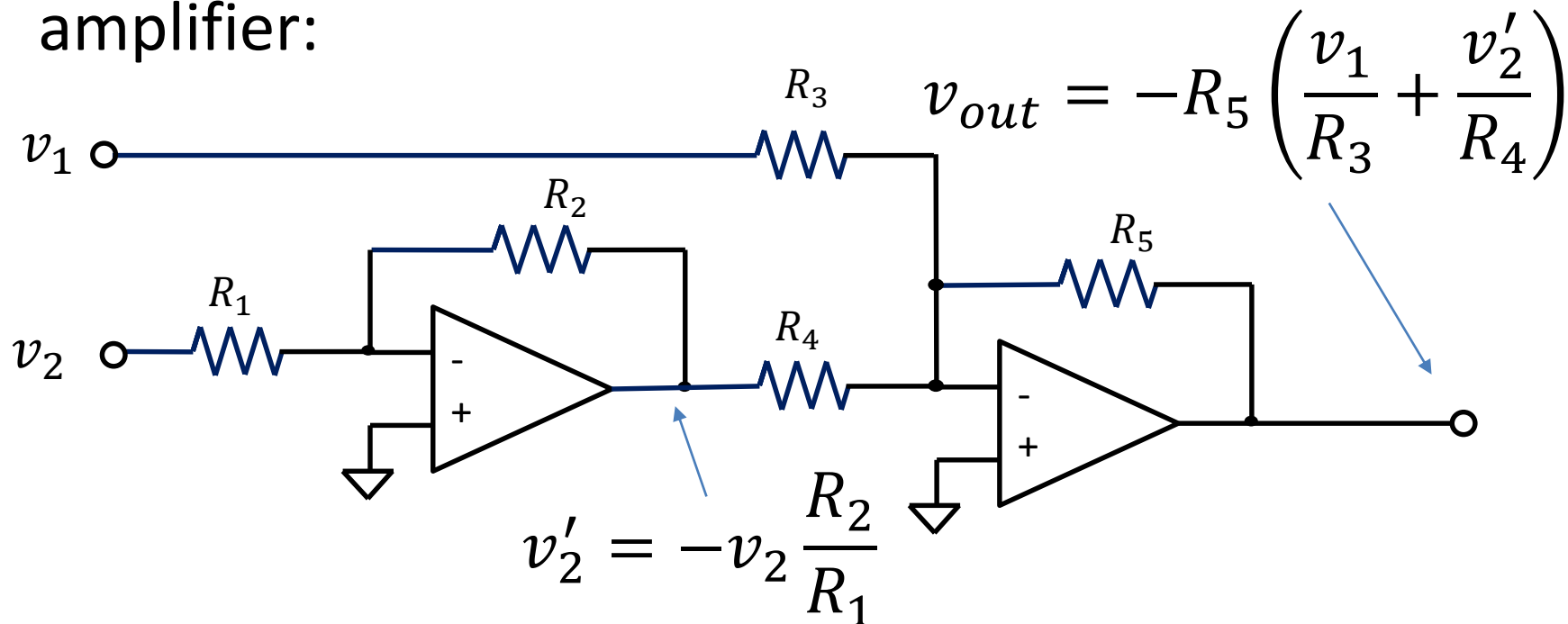
- Connect an inverting amplifier to a summing amplifier:



- If $R_1 = R_2$ and $R_3 = R_4$ then

$$v_{out} = -\frac{R_5}{R_3} (v_1 - v_2)$$

Non-inverting Summing Amplifier

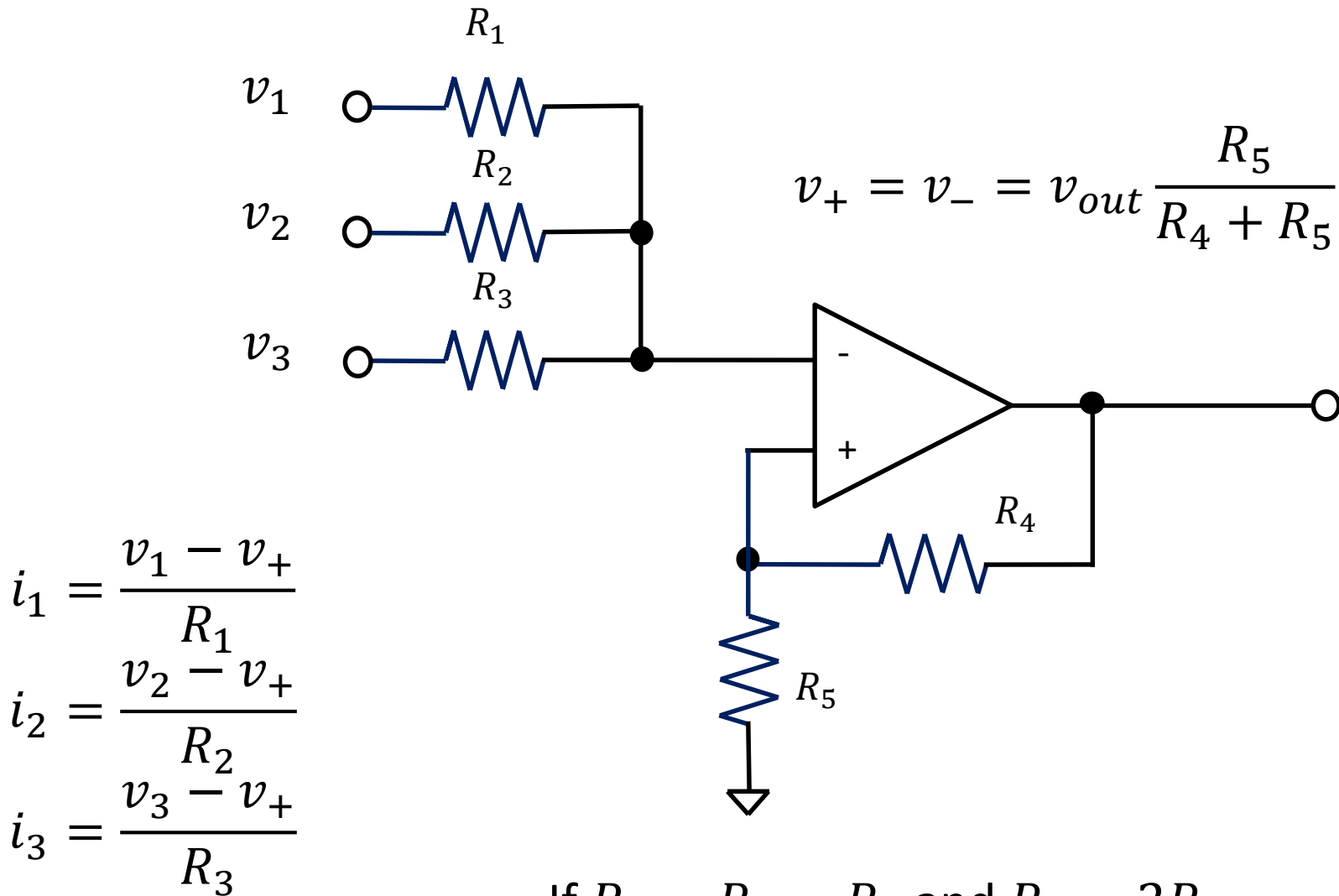


$$i_1 + i_2 + i_3 = 0$$


If $R_1 = R_2 = R_3$ and $R_4 = 2R_5$
 then $v_{out} = v_1 + v_2 + v_3$

Sensitivity Analysis

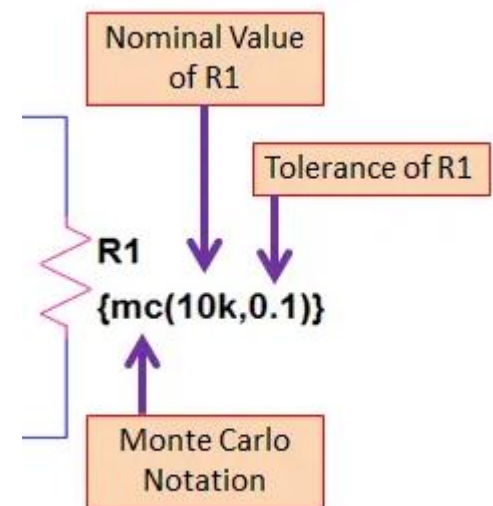
- Remember that resistors have finite tolerance (eg, 5%, 1%, 0.1%)
- How sensitive is the output to their values?
- Repeat the DC operating point analysis with randomly sampled resistor values
- In LTspice, one can specify the random tolerance of resistors using {mc(R,tolerance)}:
- Spice directive:
 .step param run 1 100 1
 (runs 100 iterations)



Sensitivity Analysis

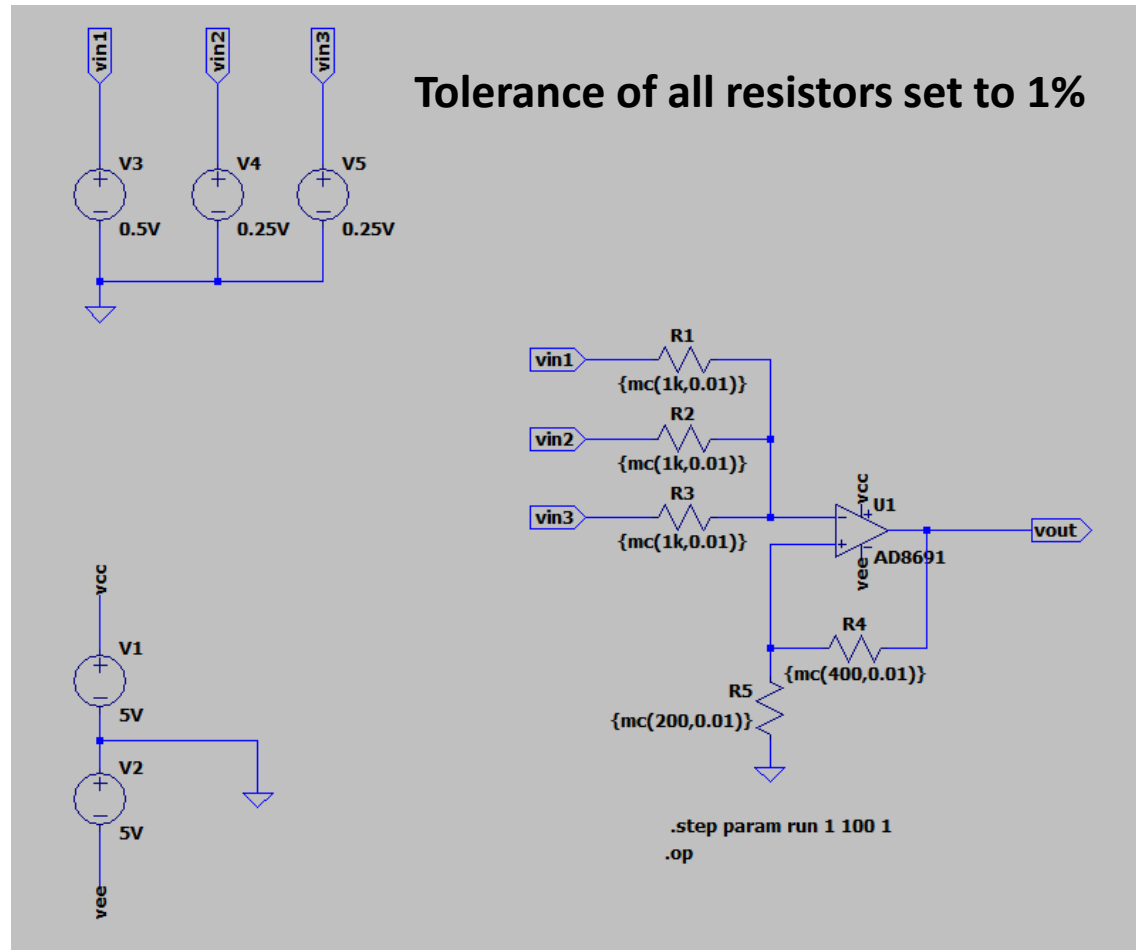


Sensitivity Analysis

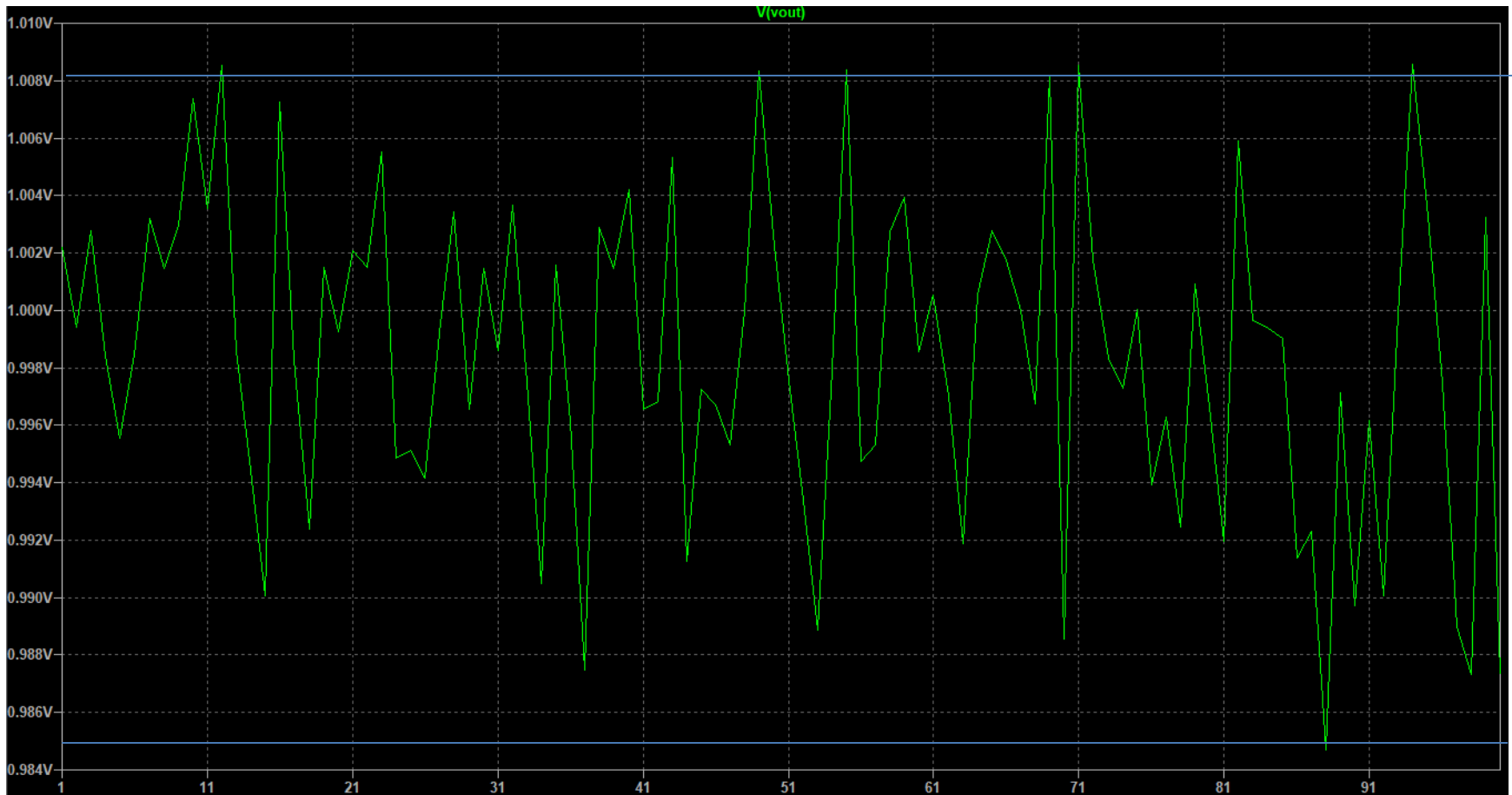

Worst case scenarios: $0.985\text{ V} < v_{out} < 1.008\text{ V}$ (2.3% variation)

More Op-Amp Circuits

- Differentiator:

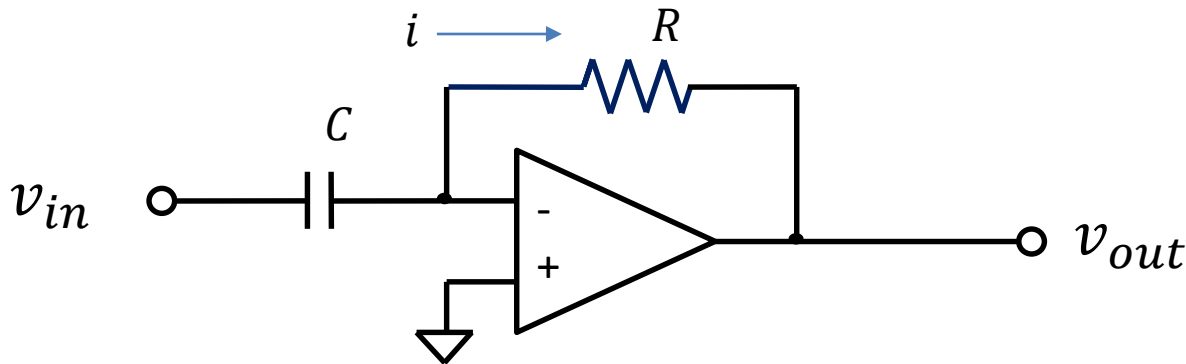

$$v_+ = 0$$

$$v_- = 0$$

- But $v_{out} = -iR$ where i is the current that flows through the capacitor.

Differentiator

$$v_{in} = -\frac{1}{C} \left(Q_0 + \int_0^t i(t) dt \right) = 0$$


$$v_{in} = -\frac{1}{C} \left(Q_0 - \frac{1}{R} \int_0^t v_{out}(t) dt \right) = 0$$

$$\frac{dv_{in}}{dt} + \frac{1}{RC} v_{out}(t) = 0$$

$$v_{out}(t) = -RC \frac{dv_{in}}{dt}$$

More Op-Amp Circuits

- Integrator:

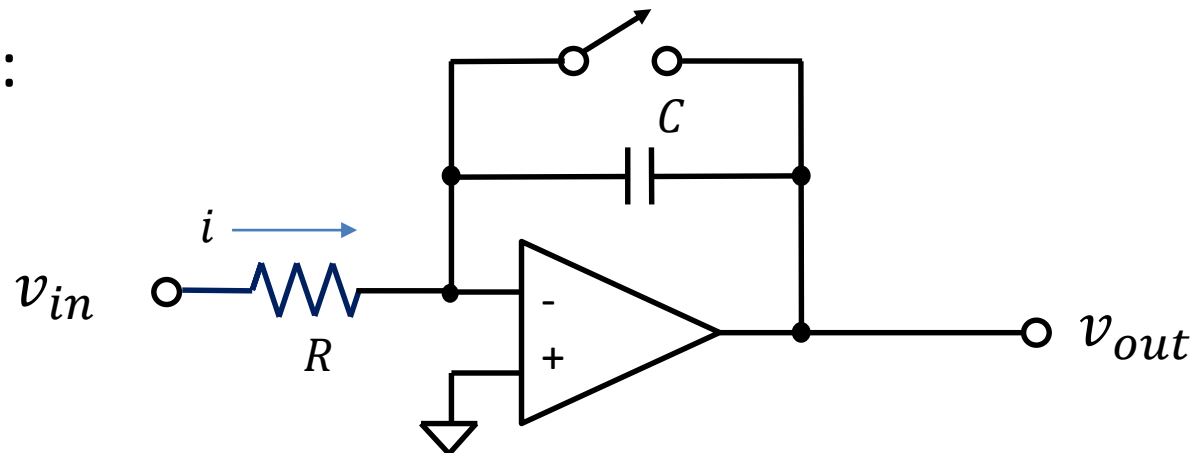

- Open switch at $t = 0$ so that $Q_0 = 0$



$$v_+ = v_- = 0$$

$$i(t) = \frac{v_{in}(t)}{R}$$

$$-\frac{1}{C} \int_0^t i(t) dt = v_{out}$$


$$v_{out}(t) = -\frac{1}{RC} \int_0^t v_{in}(t) dt$$

Example

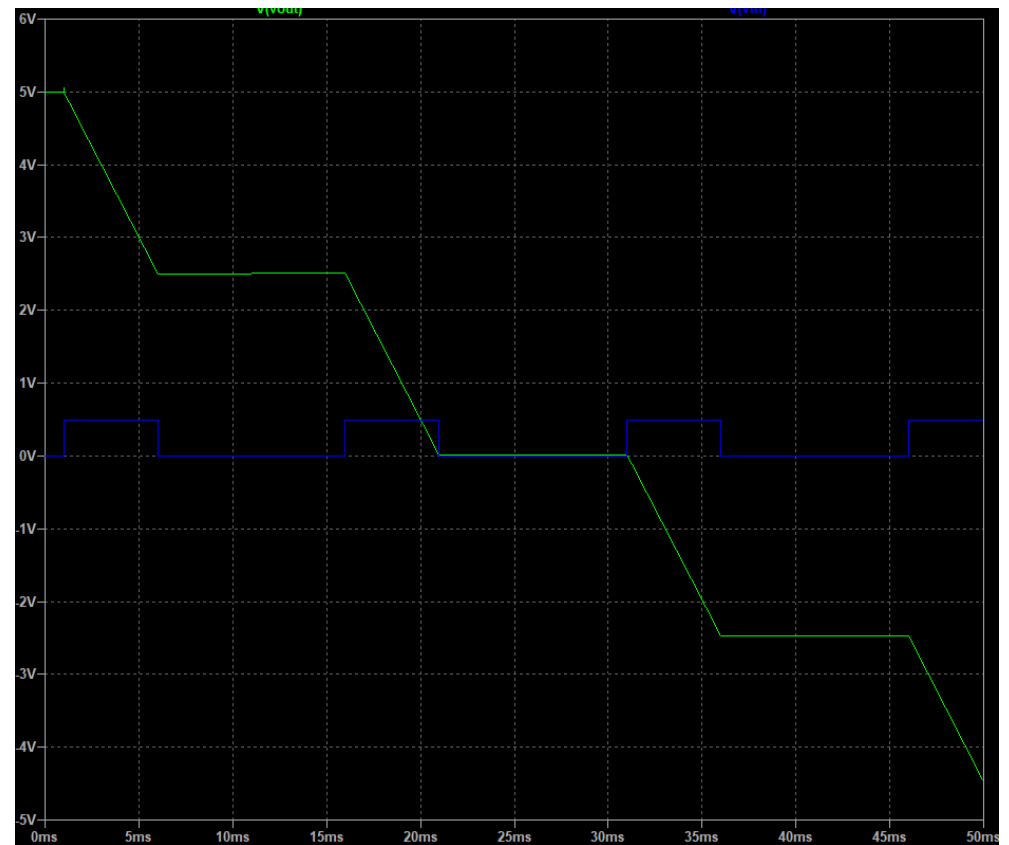
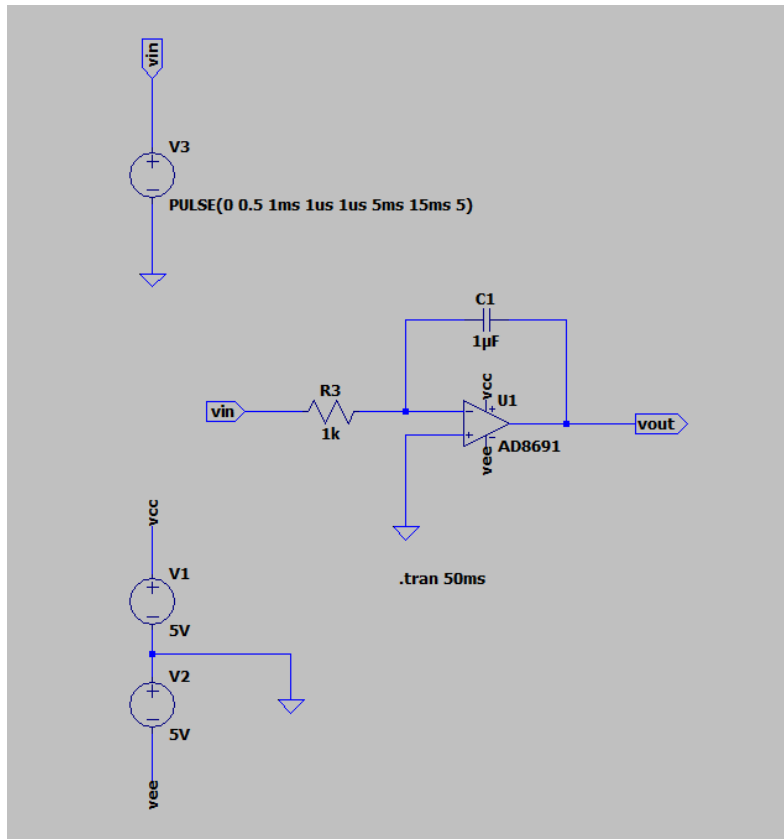


Integrator

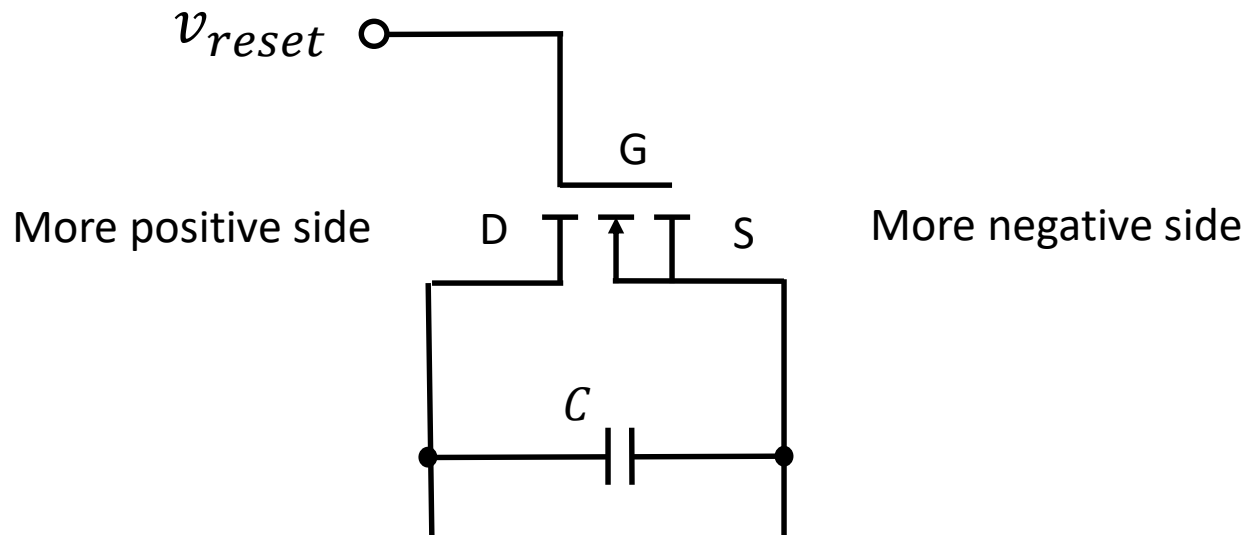- A problem with an integrator is that a mechanical switch can be impractical
- Instead, one can use an n-channel MOSFET




Integrator

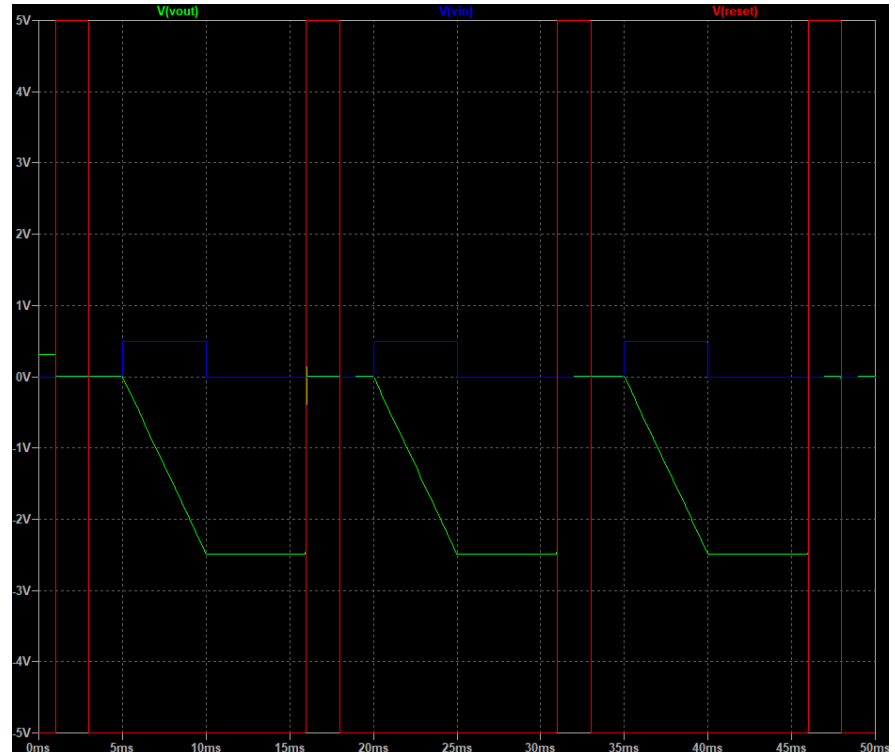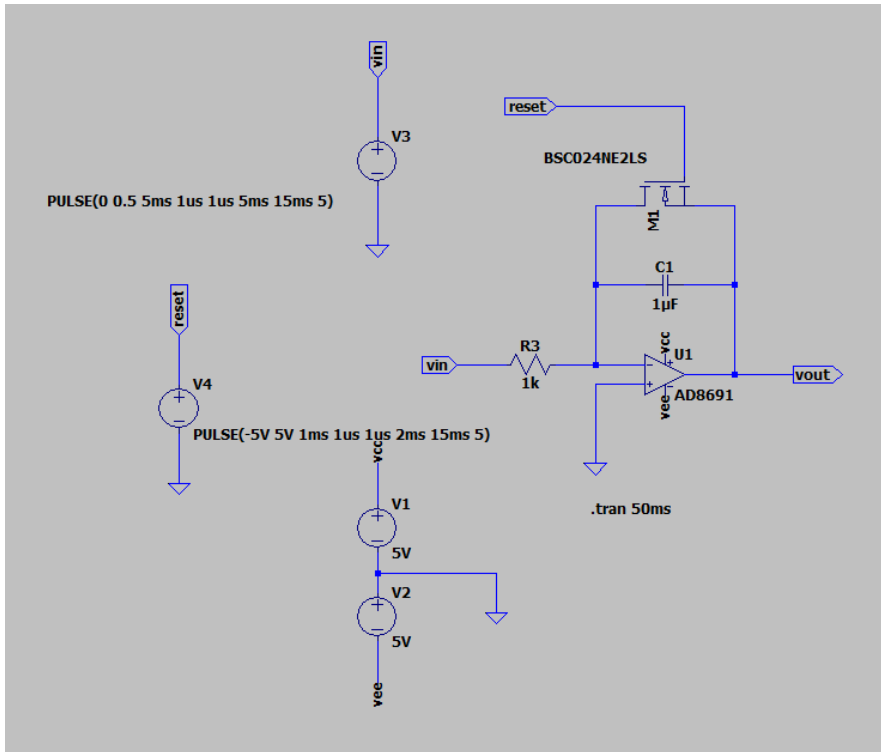

One annoying feature about MOSFET's is that the gate voltage is not compatible with most digital interfaces which range from 0 to 2.5, 3.3V or 5V.

Other Clever Circuits

- Logarithmic amplifier:

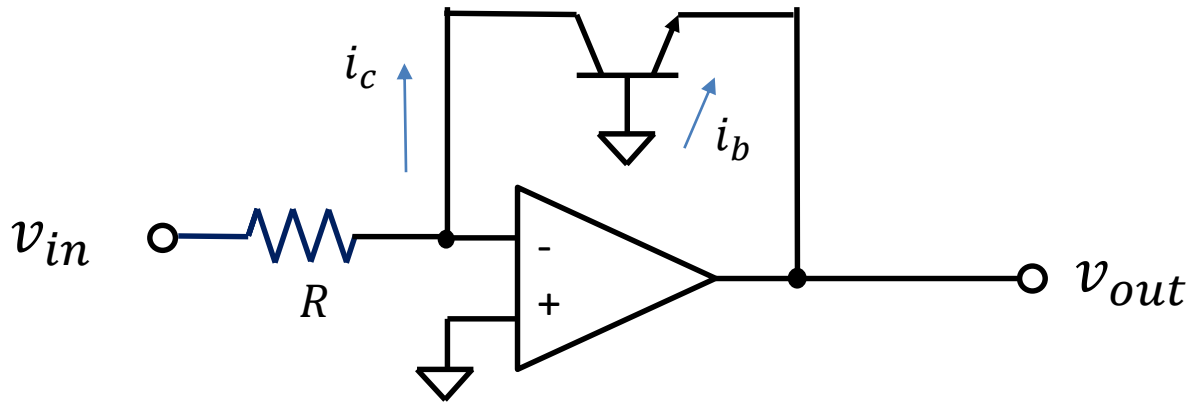

- Shockley equation:

$$i_b = I_0 \left(e^{eV_{be}/kT} - 1 \right)$$

$$i_c = \frac{\beta}{\beta + 1} i_b = \alpha i_b$$

Logarithmic Amplifier

$$i_b = I_0(e^{eV_{be}/kT} - 1) \approx I_0 e^{eV_{be}/kT}$$



$$i_c = \frac{\beta}{\beta + 1} i_b = \alpha i_b$$

- But $V_{be} = v_{out}$
- All the collector current must flow through the resistor

$$\frac{v_{in}}{R} = \alpha I_0 e^{ev_{out}/kT}$$

$$v_{out} = -\frac{kT}{e} \log \left(\frac{v_{in}}{\alpha I_0 R} \right)$$

Logarithmic Amplifier

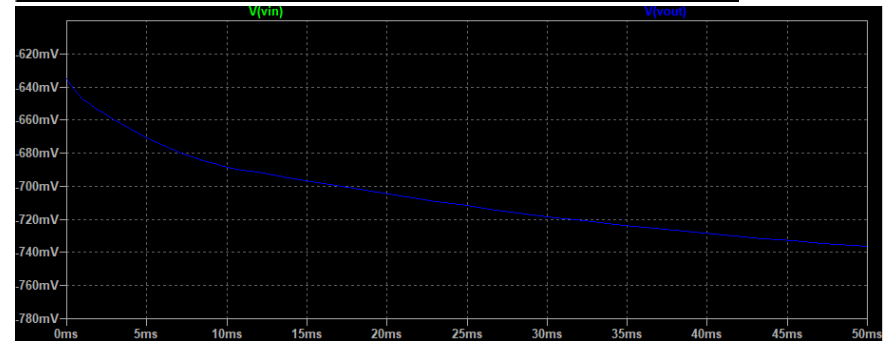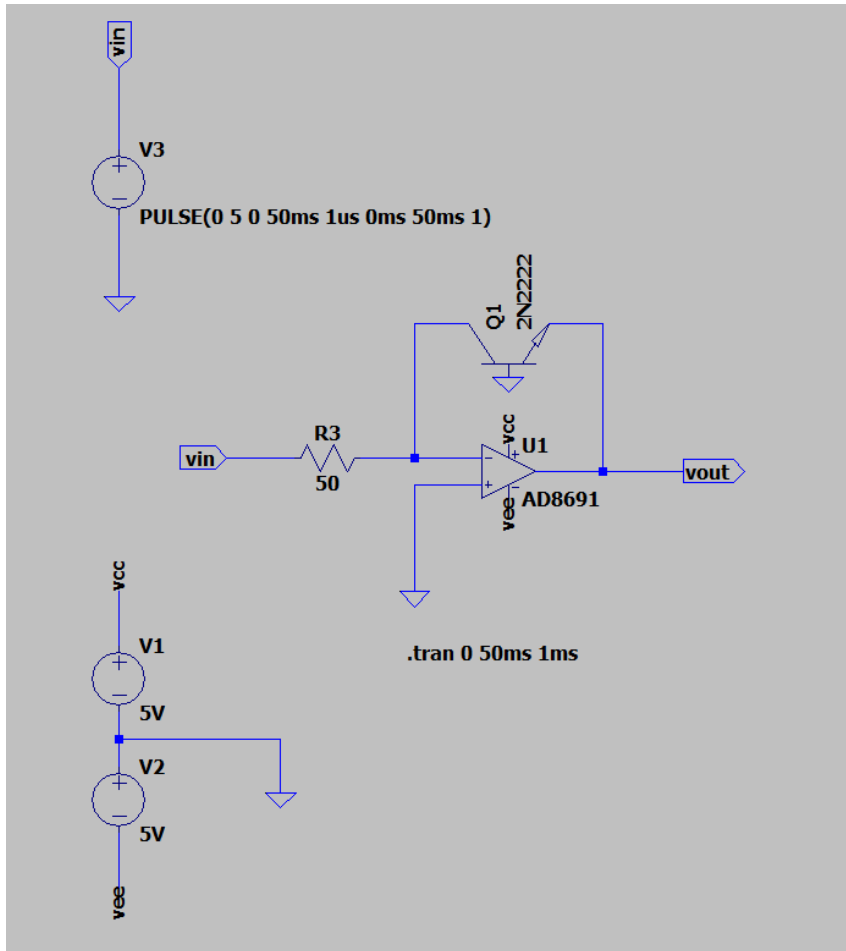

The dynamic range is somewhat limited and there is a significant voltage offset. These can be addressed by adding a summing amplifier as a second stage.