

Physics 53600
**Electronics Techniques for
Research**


Now in PowerPoint!

Spring 2020 Semester

Prof. Matthew Jones

Introduction to Active Filters

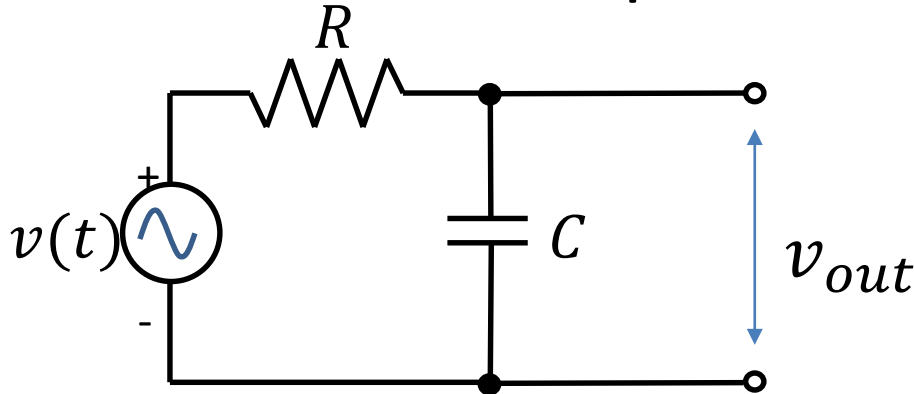- First consider a passive low-pass filter circuit:




$$Z = R - \frac{j}{\omega C}$$

- Voltage gain: $A = \frac{|v_{out}|}{|v_{in}|} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$
- When $\omega \gg RC$, $A \rightarrow \frac{1}{\omega RC}$
- $G = 20 \log_{10} A = -20 \log_{10} \omega + \text{const.}$
- Gain falls off at 20 dB per decade.

Introduction to Active Filters

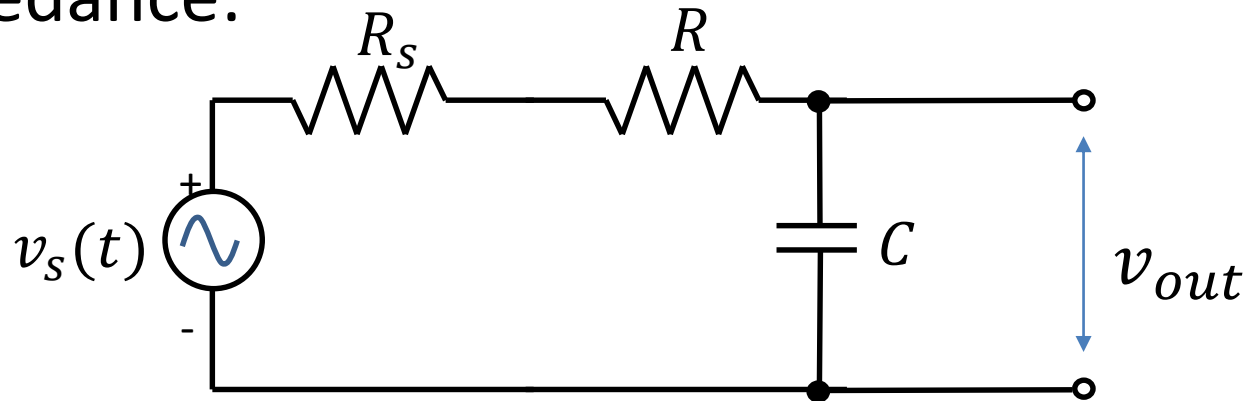
- Even at low frequencies, the circuit attenuates signals from voltage sources with finite output impedance:



- As $\omega \rightarrow 0$, the output impedance of the filter circuit is $R_s + Z$. Increasing the number of filter stages also increases the output impedance.

Active Filters

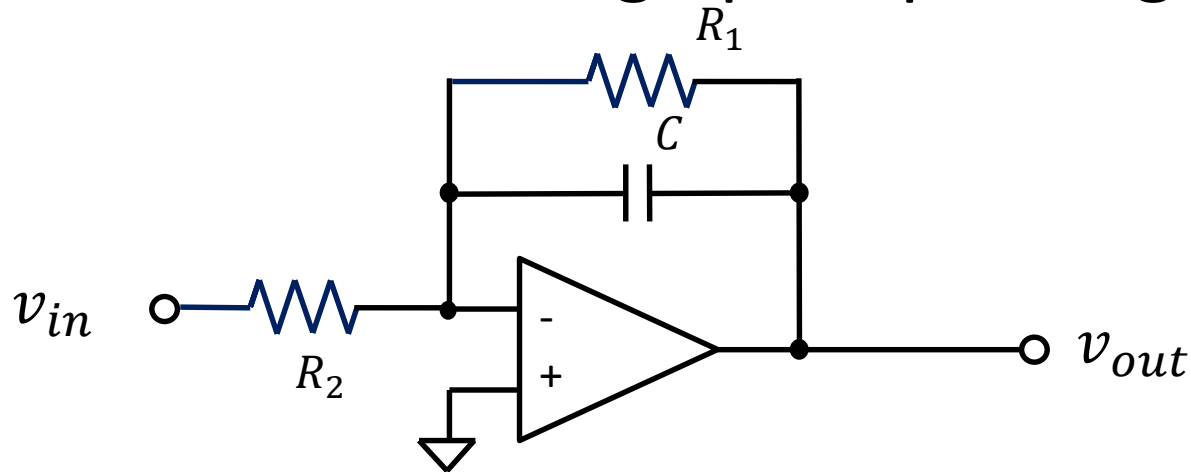- Consider the following op-amp configuration:



$$v_- = v_+ = 0$$

- Input impedance is R_2 . This determines how much current will be drawn from the source.

Active Filters

- Analysis:

$$v_{out}(t) = -i(t)Z$$
$$V_{out} = -\frac{IR_1}{1 + i\omega R_1 C} = -\frac{V_{in}R_1/R_2}{1 + i\omega R_1 C}$$
$$A = \frac{|V_{out}|}{|V_{in}|} = \frac{R_1}{R_2} \frac{1}{\sqrt{1 + \omega^2 R_1^2 C^2}}$$

- As $\omega \gg 1/R_1 C$, $A \rightarrow \frac{1}{\omega R_2 C}$
- As $\omega \rightarrow 0$, $A \rightarrow R_1/R_2$ and $\phi \rightarrow \pi$
- The output impedance is essentially determined by the non-ideal op-amp properties. Adding a load resistance doesn't change the analysis.

Example: AD8047



250 MHz, General Purpose
Voltage Feedback Op Amps

AD8047/AD8048

FEATURES

| | | |
|------------------------|----------------|----------------|
| Wide Bandwidth | AD8047, G = +1 | AD8048, G = +2 |
| Small Signal | 250 MHz | 260 MHz |
| Large Signal (2 V p-p) | 130 MHz | 160 MHz |

5.8 mA Typical Supply Current

Low Distortion, (SFDR) Low Noise

–66 dBc Typ @ 5 MHz

–54 dBc Typ @ 20 MHz

5.2 nV/ $\sqrt{\text{Hz}}$ (AD8047), 3.8 nV/ $\sqrt{\text{Hz}}$ (AD8048) Noise

Drives 50 pF Capacitive Load

High Speed

Slew Rate 750 V/ μs (AD8047), 1000 V/ μs (AD8048)

Settling 30 ns to 0.01%, 2 V Step

± 3 V to ± 6 V Supply Operation

APPLICATIONS

Low Power ADC Input Driver

Differential Amplifiers

IF/RF Amplifiers

Pulse Amplifiers

Professional Video

DAC Current to Voltage Conversion

Baseband and Video Communications


Pin Diode Receivers

Active Filters/Integrators

FUNCTIONAL BLOCK DIAGRAM

8-Pin Plastic PDIP (N)



and SOIC (R) Packages

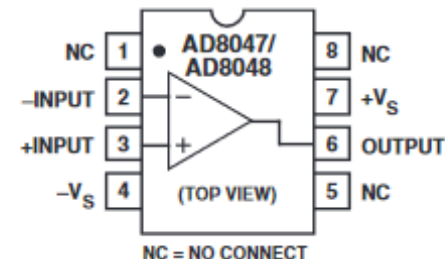

The AD8047 and AD8048's low distortion and cap load drive make the AD8047/AD8048 ideal for buffering high speed ADCs. They are suitable for 12-bit/10 MSPS or 8-bit/60 MSPS ADCs. Additionally, the balanced high impedance inputs of the voltage feedback architecture allow maximum flexibility when designing active filters.

The AD8047 and AD8048 are offered in industrial (-40°C to $+85^{\circ}\text{C}$) temperature ranges and are available in 8-lead PDIP and SOIC packages.

Example

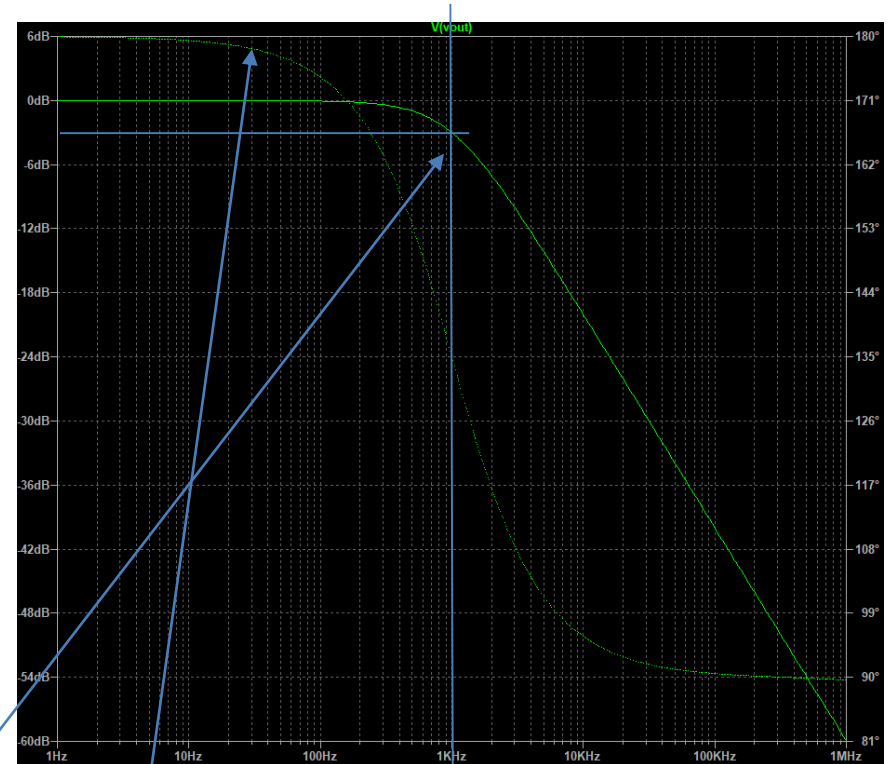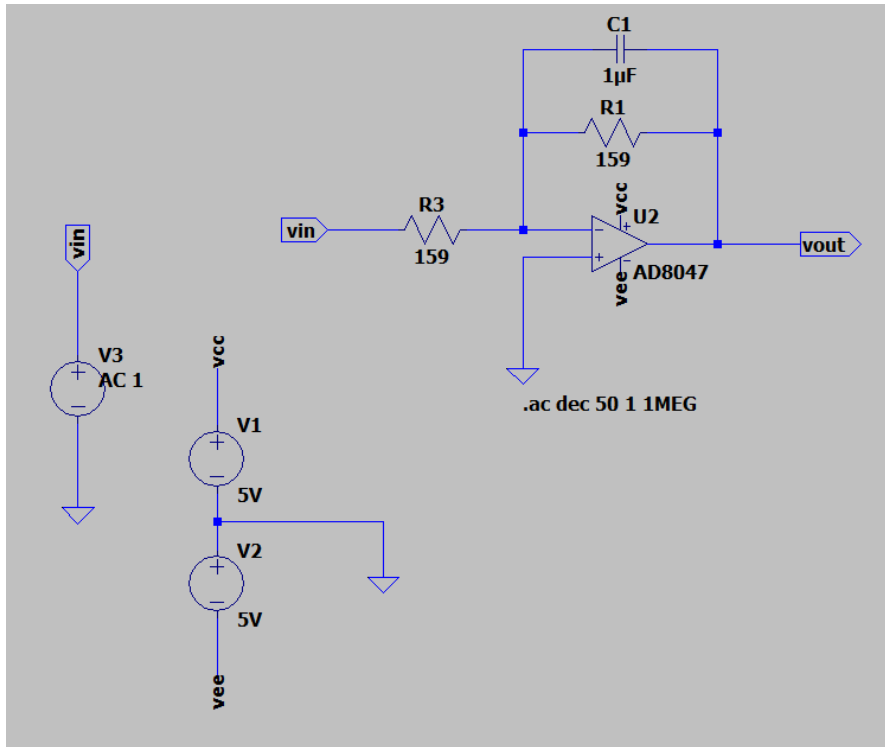


$$R_1 = R_2 = 159 \, \Omega$$
$$(1 \, k\Omega / 2\pi)$$
$$C = 1 \, \mu F$$

-3 dB cutoff frequency = 1 kHz

Phase at low frequencies is 180°

Active Filters

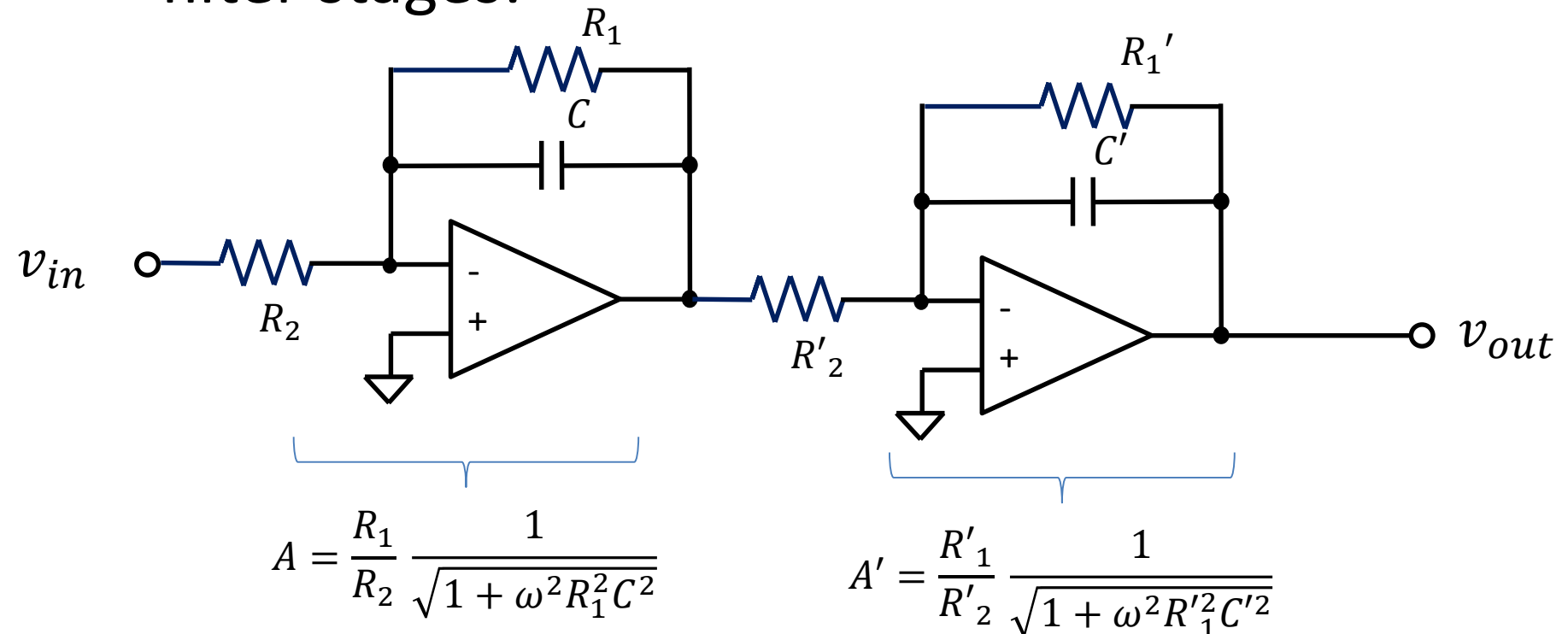- The property of having a low output impedance and an output that is isolated from the input makes it easy to analyze additional filter stages:



Active Filters

- The voltage gains of each stage just multiply:



$$\begin{aligned} A_{total} &= A A' \\ &= \frac{R_1}{R_2} \cdot \frac{R'_1}{R'_2} \cdot \frac{1}{\sqrt{(1 + \omega^2 R_1^2 C^2)(1 + \omega^2 R_1'^2 C'^2)}} \end{aligned}$$

- If $R_1 = R_2 = R'_1 = R'_2 \equiv R$, and $C' = C$ then

$$A = \frac{1}{1 + \omega^2 R^2 C^2}$$

- Unity gain at low frequencies,
- Gain falls off at 40 dB per decade for $\omega \gg 1/RC$

Active Band-Pass Filter

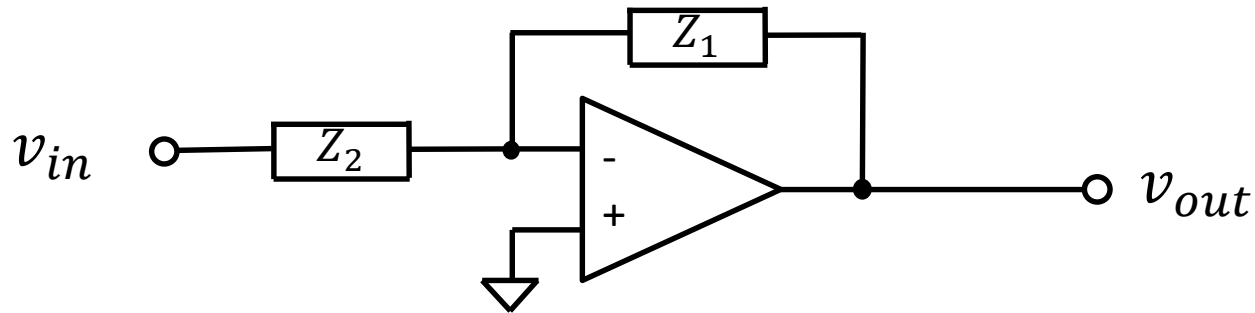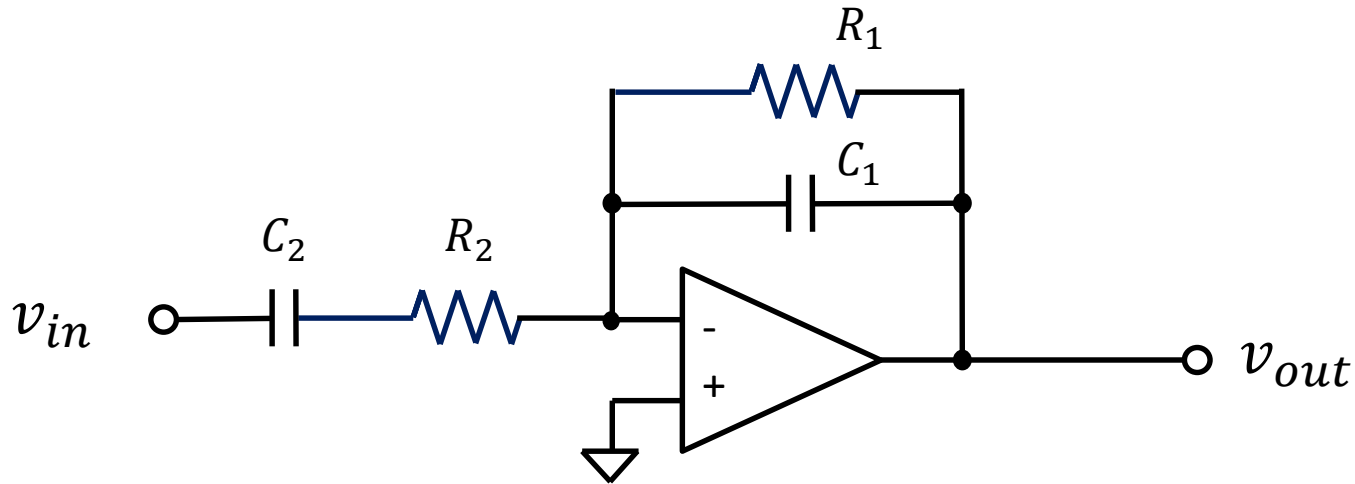

$$v_- = v_+ = 0$$

$$i_{in} = \frac{v_{in}}{Z_2}$$

$$v_{out} = -i_{in}Z_1 = -v_{in} \frac{Z_1}{Z_2}$$

Active Band-Pass Filter

$$Z_1 = \frac{R_1}{1 + i\omega R_1 C_1} \quad (\text{parallel R and C})$$



$$Z_2 = R_2 - \frac{i}{\omega C_2} \quad (\text{series R and C})$$

- From analogy with only resistors, the gain will be

$$A = \left| \frac{Z_1}{Z_2} \right| = \frac{R_1}{R_2} \frac{1}{\sqrt{\left(1 + \frac{R_1 C_1}{R_2 C_2}\right)^2 + \left(\omega R_1 C_1 - \frac{1}{\omega R_2 C_2}\right)^2}}$$

- Cutoff frequencies ($A = 1/\sqrt{2}$):
 - Low frequency: $\omega_- = 1/R_2 C_2$
 - High frequency: $\omega_+ = 1/R_1 C_1$



Example

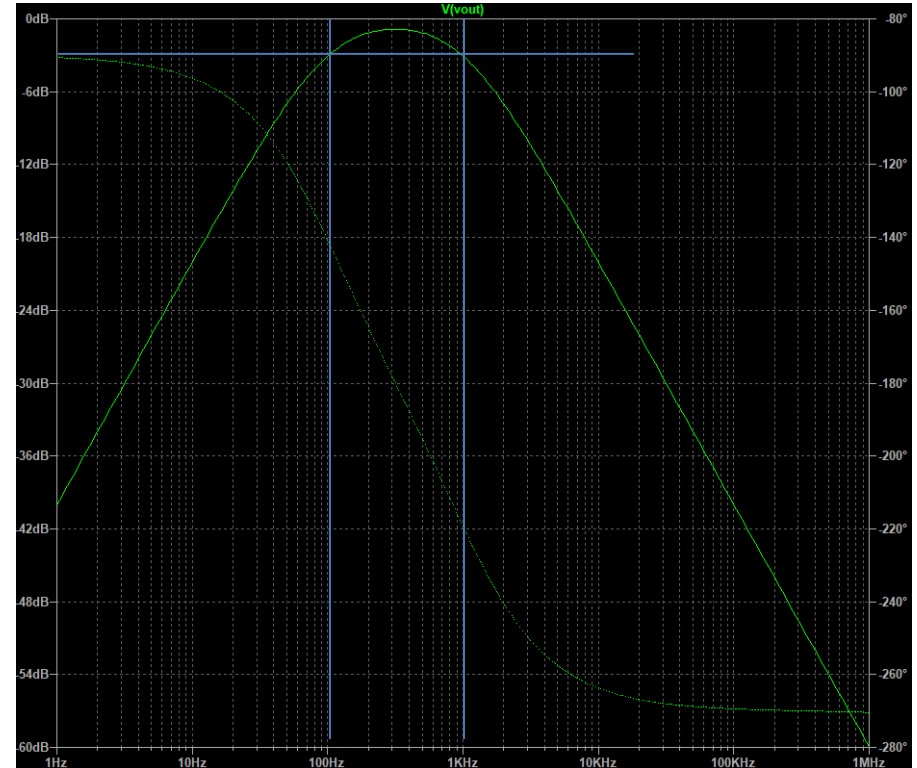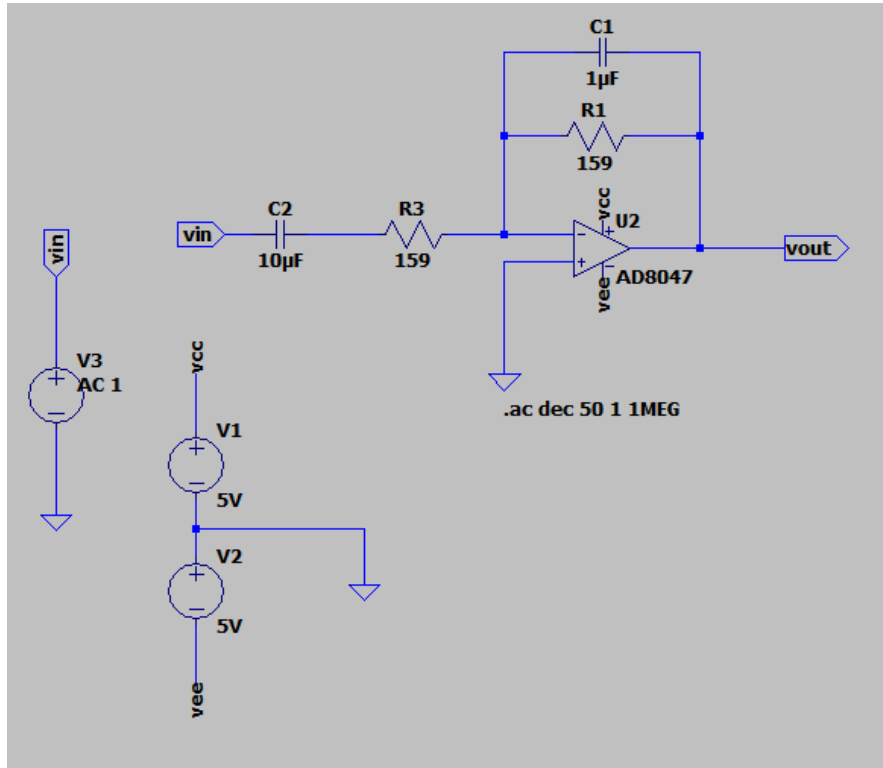

$$\omega_- = \frac{1}{R_2 C_2} = 628.9 \text{ s}^{-1} \rightarrow f_- = 100 \text{ Hz}$$

$$\omega_+ = \frac{1}{R_1 C_1} = 6289 \text{ s}^{-1} \rightarrow f_+ = 1000 \text{ Hz}$$


Example

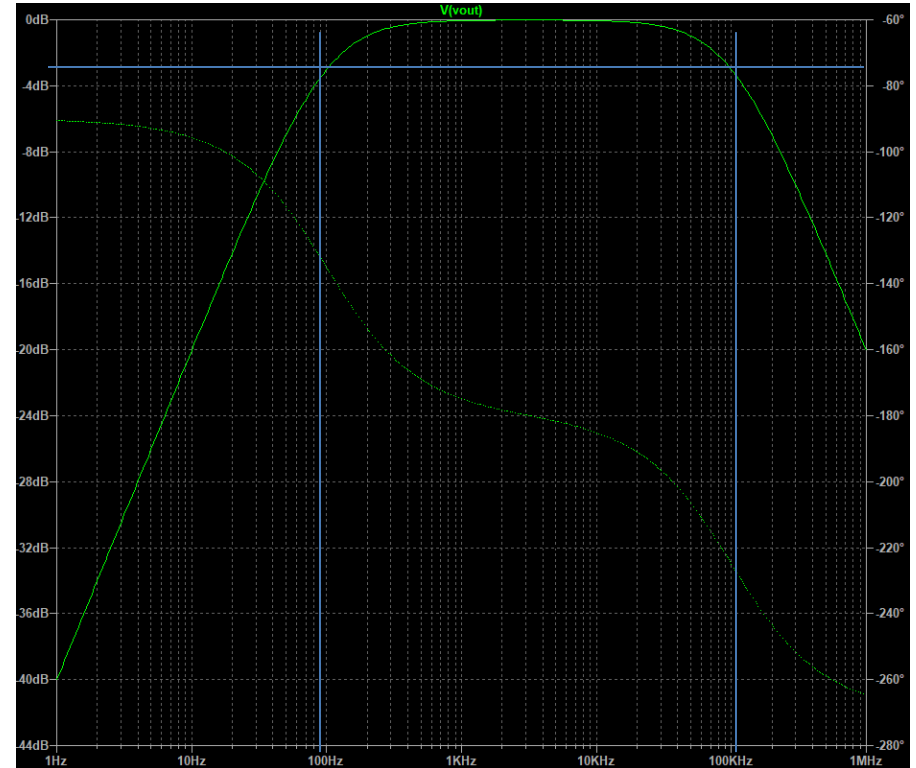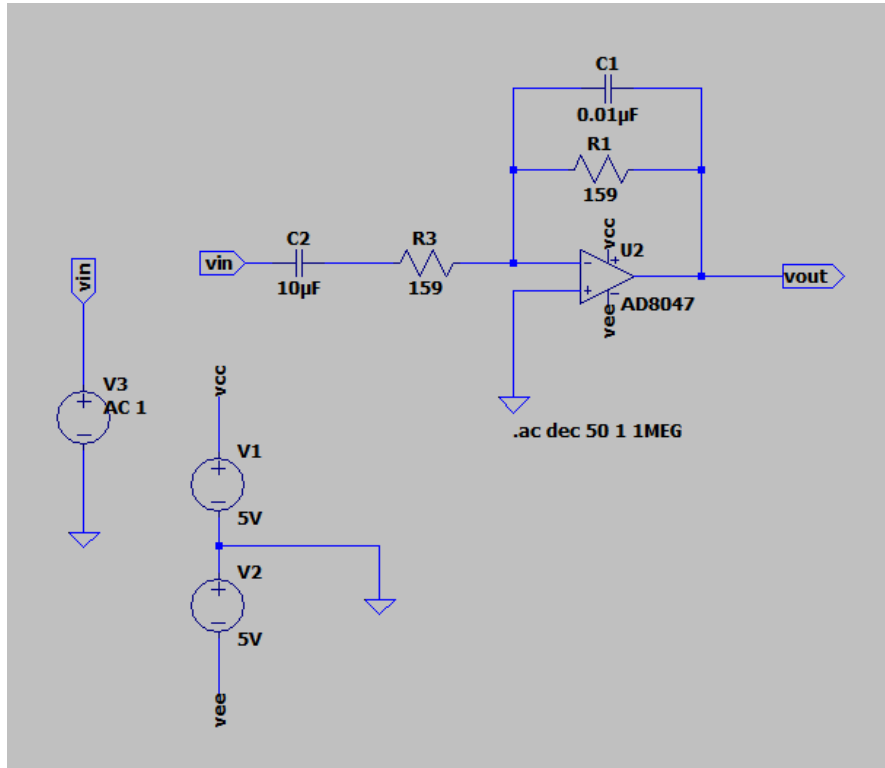

$$\omega_- = \frac{1}{R_2 C_2} = 628.9 \text{ s}^{-1} \rightarrow f_- = 100 \text{ Hz}$$

$$\omega_+ = \frac{1}{R_1 C_1} = 628900 \text{ s}^{-1} \rightarrow f_+ = 100 \text{ kHz}$$

Oscillators

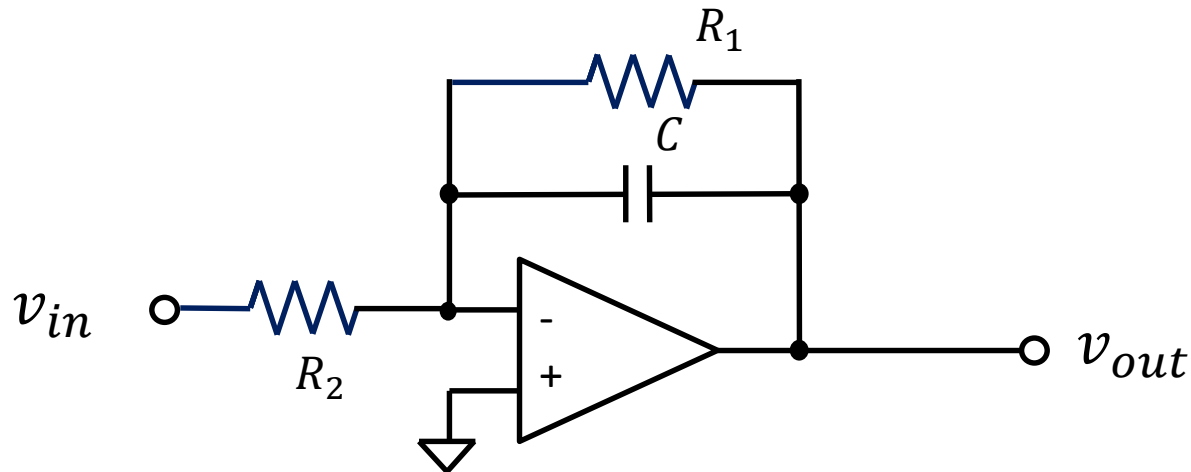


$$V_{out} = -V_{in} \frac{R_1}{R_2} \frac{1}{1 + i\omega R_1 C}$$

$$A = \frac{R_1}{R_2} \frac{1}{\sqrt{1 + \omega^2 R_1^2 C^2}}$$


$$\tan \phi = -\omega R_1 C$$

Oscillators

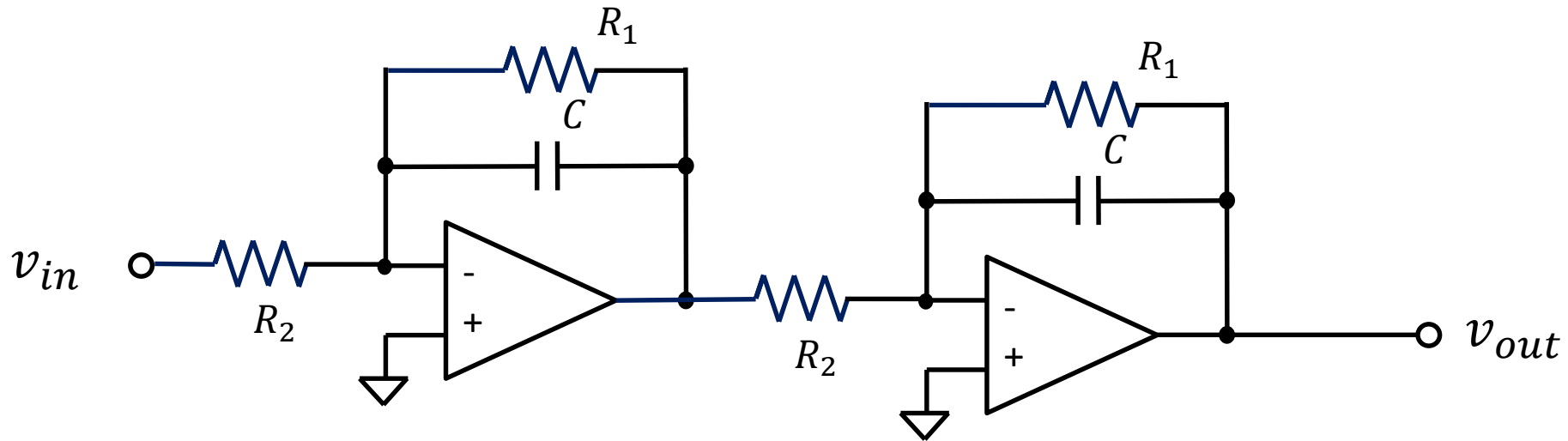

$$A = \left(\frac{R_1}{R_2} \right)^2 \frac{1}{1 + \omega^2 R_1^2 C^2}$$
$$\tan \phi \approx -2\omega R_1 C$$

Oscillators

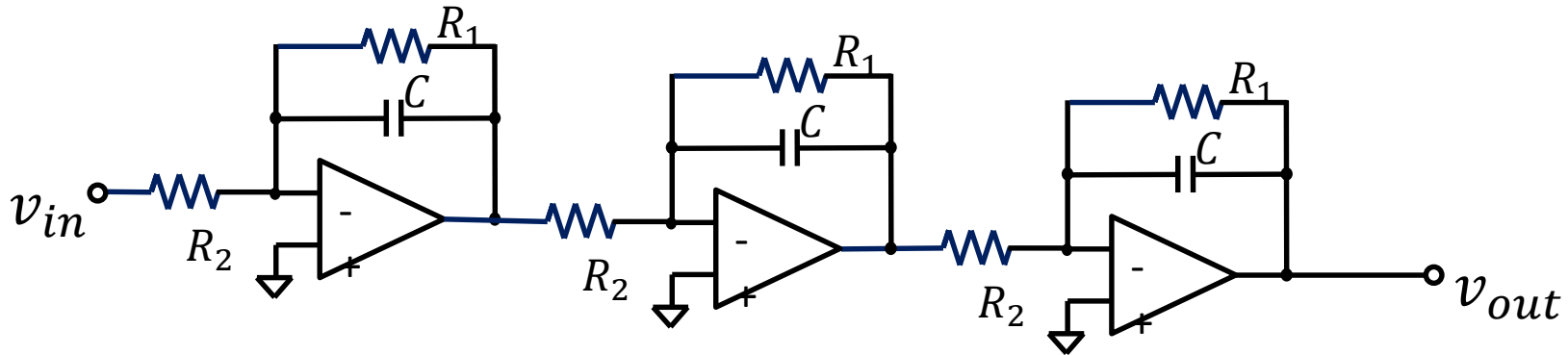


$$A = \left(\frac{R_1}{R_2} \frac{1}{\sqrt{1 + \omega^2 R_1^2 C^2}} \right)^3$$

$$\tan \phi \approx -3\omega R_1 C$$

Oscillators

- Now connect the output to the input:

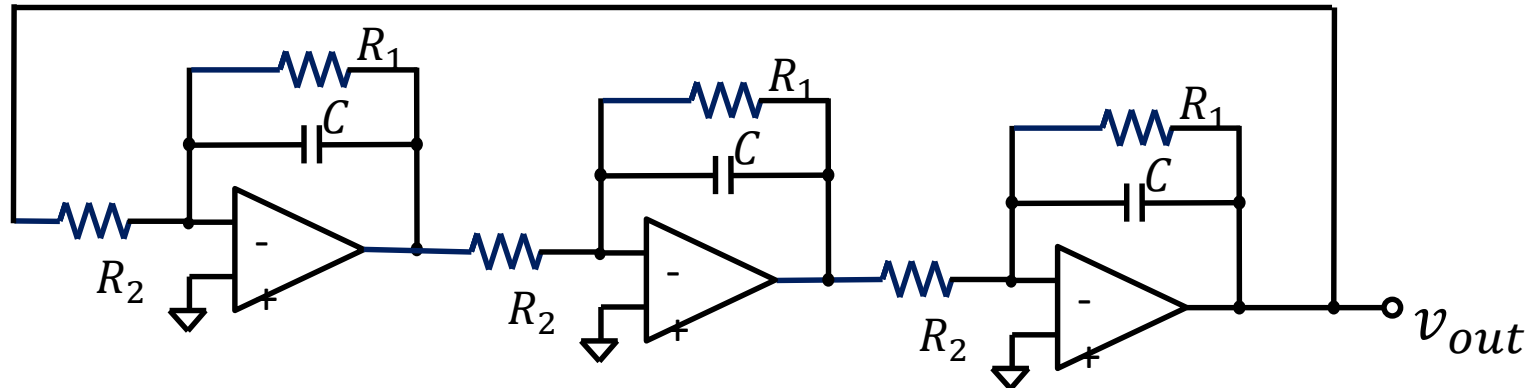

- Total phase shift:

$$\phi = 2n\pi$$

- Individual phase shift:

$$\tan \frac{2\pi}{3} = -\omega R_1 C = -\sqrt{3}$$

- Oscillation frequency is $\omega = \frac{\sqrt{3}}{R_1 C}$