

Physics 53600  
**Electronics Techniques for  
Research**

*Now in PowerPoint!*

Spring 2020 Semester



Prof. Matthew Jones

# More Information

- Course web page, whereat can be found the syllabus:  
[http://www.physics.purdue.edu/~mjones/phys53600\\_Spring2020](http://www.physics.purdue.edu/~mjones/phys53600_Spring2020)
- Information about the lab will be posted before next Tuesday. Check the web page before you attend the lab.
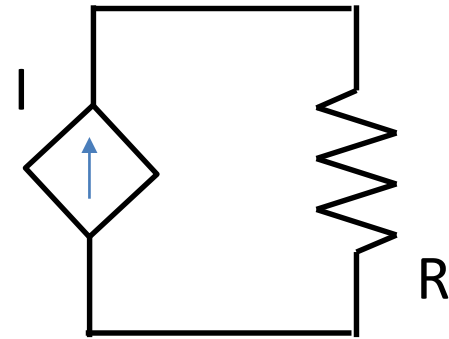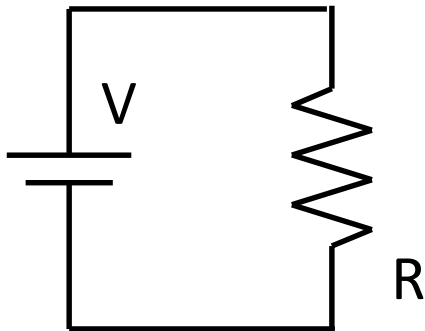
# Circuits

- In general, electrical circuits require
  - A source of energy (electric potential)
  - A path through which current will flow




- What do we want to learn?
  - Current given voltage? Voltage given current?
  - Power dissipated by resistor?

# Modeling Physical Systems

- Another common problem is to describe a physical system in terms of ideal circuit elements.
  - We construct a model of the electrical properties of the physical system
  - If the model is reasonably accurate, then we can use it to predict what the system will do under various conditions

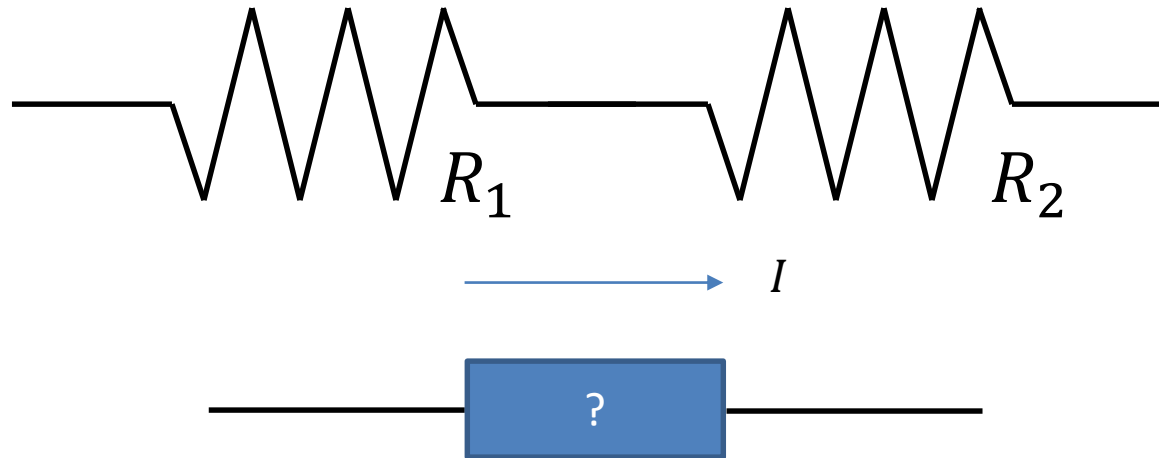
# Example

- Construct a model for a system that consists of two resistors in series:



- The current through each system will be the same
- The potential difference across each system should be the same.

# Example

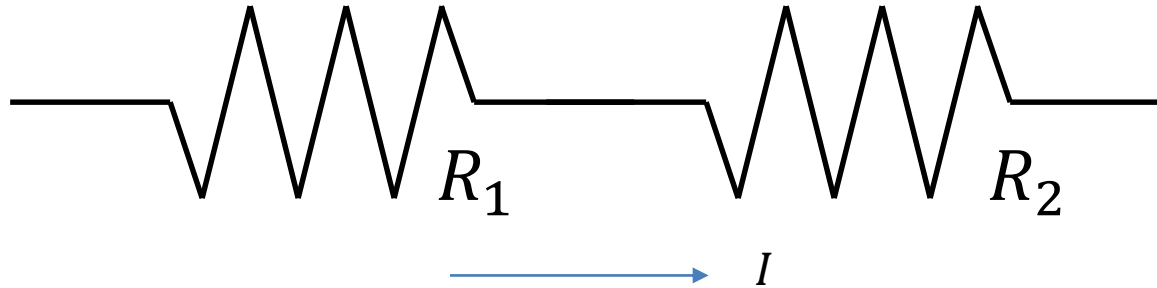

- Potential difference across each resistor:

$$\Delta V_{R_1} = IR_1$$


$$\Delta V_{R_2} = IR_2$$

- Total potential difference:

$$\Delta V = I(R_1 + R_2)$$


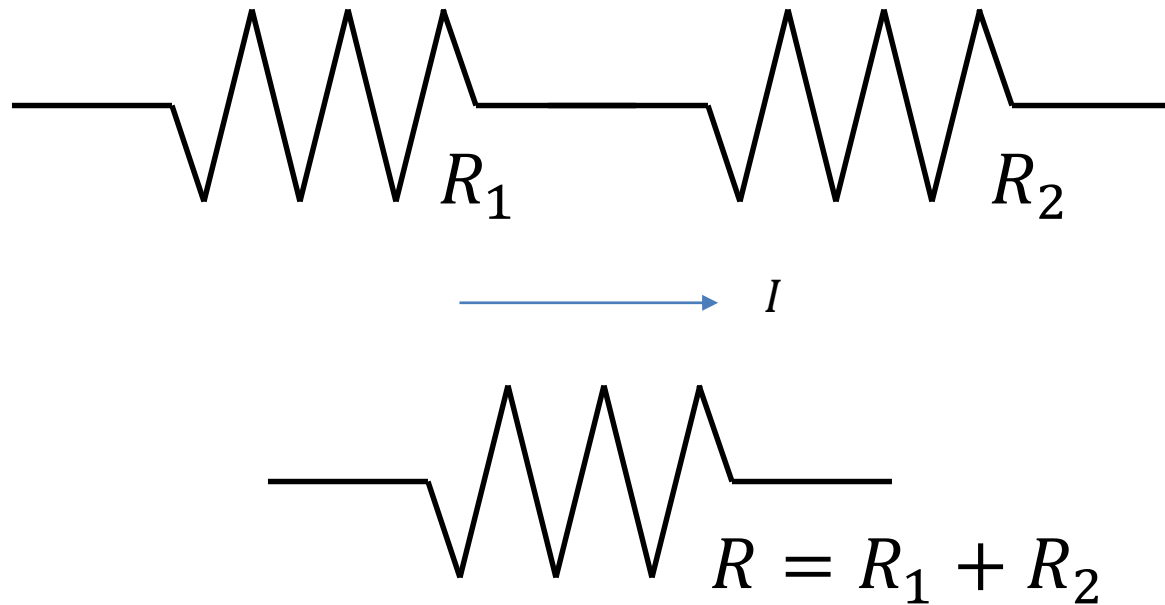
# Example

- The equivalent system can be described using one resistor:



- Both systems behave the same in a circuit.

# Another Example

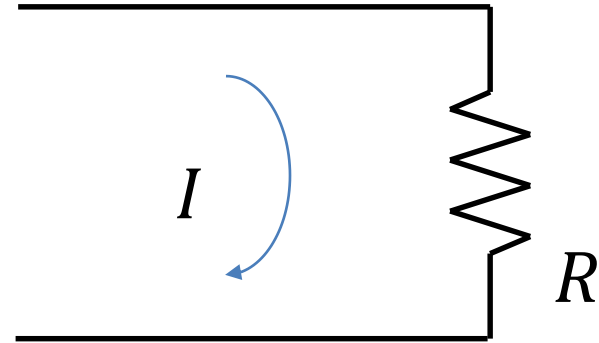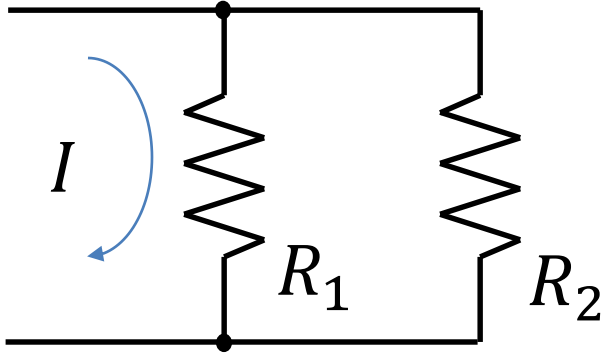


- Equivalent resistance:

$$R = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$

- Both systems behave the same in a circuit.



# Real Resistors

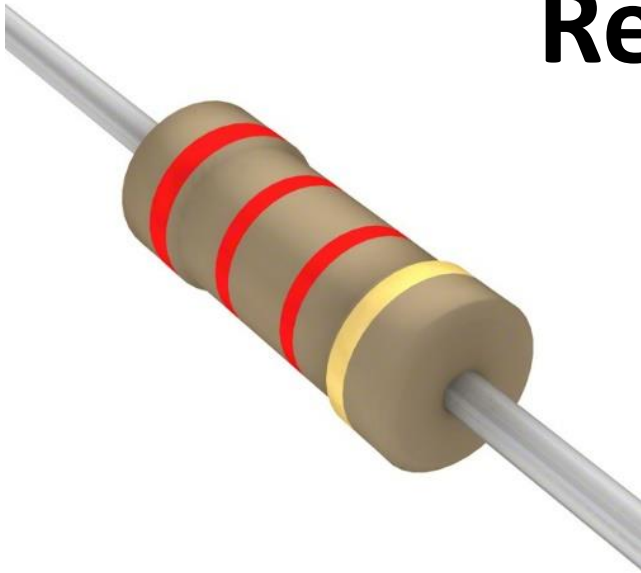











## Product Attributes

TYPE	DESCRIPTION
Categories	<a href="#">Resistors</a> <a href="#">Through Hole Resistors</a>
Manufacturer	Stackpole Electronics Inc
Series	CF
Packaging	Cut Tape (CT) <a href="#">?</a>
Part Status	Active
Resistance	2.2 kOhms
Tolerance	±5%
Power (Watts)	0.25W, 1/4W
Composition	Carbon Film
Features	Flame Retardant Coating, Safety
Temperature Coefficient	0/-400ppm/°C
Operating Temperature	-55°C ~ 155°C
Package / Case	Axial
Supplier Device Package	Axial
Size / Dimension	0.091" Dia x 0.236" L (2.30mm x 6.00mm)

PRICE BREAK	UNIT PRICE	EXTENDED PRICE
1	0.10000	\$0.10
10	0.04000	\$0.40
25	0.02880	\$0.72
50	0.02200	\$1.10
100	0.01620	\$1.62
250	0.01236	\$3.09
500	0.00990	\$4.95
1,000	0.00729	\$7.29

# Real Resistors


Digi-Key Part Number	<a href="#">CF14JT2K20CT-ND</a> 	<a href="#">S2.2KCACT-ND</a> 	<a href="#">2.2KADCT-ND</a> 
Manufacturer Part Number	CF14JT2K20	RNMF14FTC2K20	MFP-25BRD52-2K2
Manufacturer	<a href="#">Stackpole Electronics Inc</a>	<a href="#">Stackpole Electronics Inc</a>	<a href="#">Yageo</a>
Image			
Description	RES 2.2K OHM 1/4W 5% AXIAL	RES 2.2K OHM 1/4W 1% AXIAL	RES 2.2K OHM 1/4W 0.1% AXIAL
Quantity Available 	46,521 - Immediate	83,615 - Immediate	3,122 - Immediate
Unit Price USD	\$0.10000	\$0.10000	\$0.64000
Minimum Quantity	1	1	1
Series	<a href="#">CF</a>	<a href="#">RNMF (Mini)</a>	<a href="#">MFP</a>
Packaging	Cut Tape (CT)  <a href="#">Alternate Packaging</a>	Cut Tape (CT)  <a href="#">Alternate Packaging</a>	Cut Tape (CT)  <a href="#">Alternate Packaging</a>
Part Status	Active	Active	Active
Resistance	2.2 kOhms	2.2 kOhms	2.2 kOhms
Tolerance	±5%	±1%	±0.1%
Power (Watts)	0.25W, 1/4W	0.25W, 1/4W	0.25W, 1/4W
Composition	Carbon Film	Metal Film	Metal Film
Features	Flame Retardant Coating, Safety	Flame Retardant Coating, Safety	-
Temperature Coefficient	0/-400ppm/°C	±50ppm/°C	±25ppm/°C
Operating Temperature	-55°C ~ 155°C	-55°C ~ 155°C	-55°C ~ 155°C
Package / Case	Axial	Axial	Axial
Supplier Device Package	Axial	Axial	Axial
Size / Dimension	0.091" Dia x 0.236" L (2.30mm x 6.00mm)	0.070" Dia x 0.130" L (1.78mm x 3.30mm)	0.094" Dia x 0.248" L (2.40mm x 6.30mm)

# Real Resistors

Electrical Specifications - CF							
Type/Code	Power Rating (Watts) @ 70°C	Maximum Working Voltage <sup>(1)</sup>	Maximum Overload Voltage	Dielectric Withstanding Voltage	Resistance Temperature Coefficient per Ohmic Range	Ohmic Range (Ω) and Tolerance	
						2%	5%
CF18	0.125 W	250 V	500 V	350 V	< 10 Ω = ±400 ppm/°C 10 Ω to 9.99 K Ω = 0 ~ -400 ppm/°C 10 K Ω to 99 K Ω = 0 ~ -500 ppm/°C 100 K Ω to 999 K Ω = 0 ~ -850 ppm/°C 1 M Ω and above = 0 ~ -1500 ppm/°C	10 - 1 M	1 - 22 M
CF14	0.25 W	350 V	600 V	350 V		1 - 1 M	1 - 22 M
CF12	0.5 W	350 V	700 V	600 V		10 - 1 M	1 - 22 M
CF1	1 W	500 V	1,000 V	600 V		1 - 1 M	1 - 10 M
CF2	2 W	500 V	1,000 V	600 V		1 - 1 M	1 - 10 M

- Temperature coefficient:

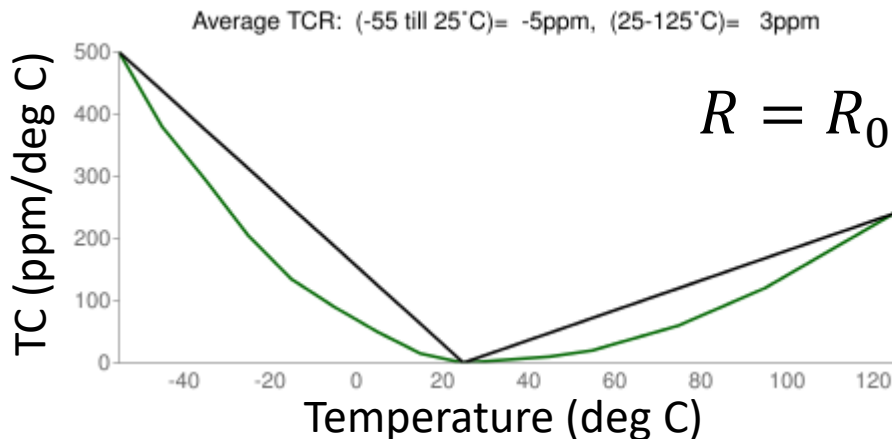
$$TC = \frac{1}{R} \frac{\Delta R}{\Delta T}$$



$$R = R_0(1 + \alpha(T - T_0) + \beta(T - T_0)^2)$$
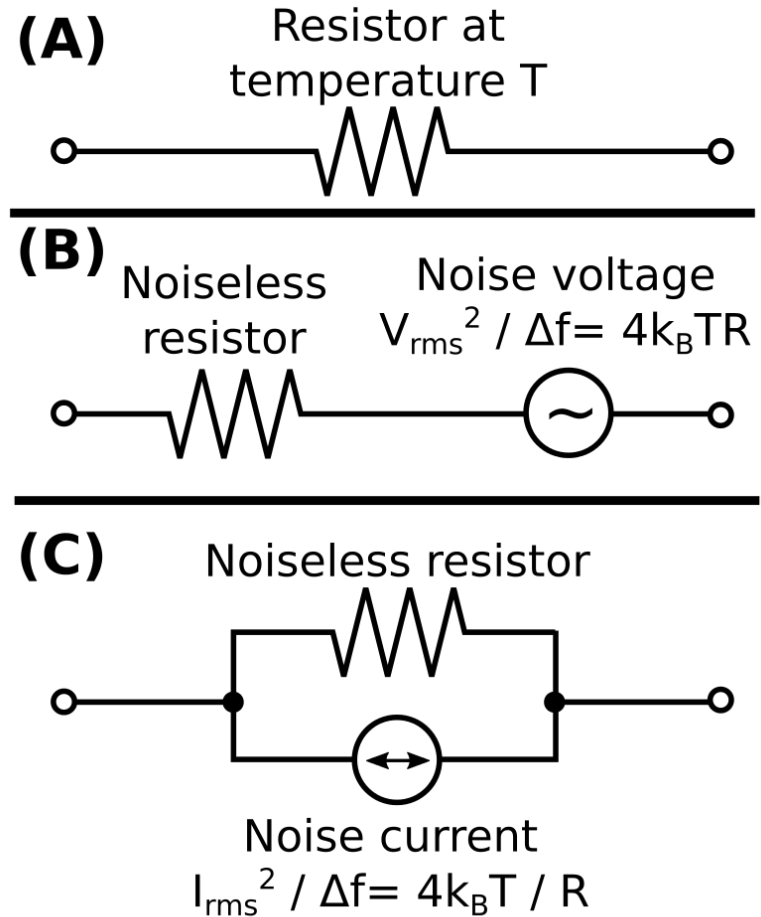
# Real Resistors

- Real resistors are (small) sources of random noise
- Random thermal motion of charge carriers produces (small) voltage/current fluctuations
- Approximately white noise – power spectral density is approximately constant over a wide frequency range





Example:  $R = 50 \Omega$ ,  $\Delta f = 1 \text{ Hz}$ ,  $T = 300 \text{ K} \Rightarrow v_{\text{rms}} = 1 \text{ nV}$

# Real Capacitors


- There are many different types of capacitors constructed using various technologies
- Primary considerations:
  - Voltage rating
  - Capacitance range
  - Polarity (!)
  - Frequency response
  - Operating temperature range
  - Temperature coefficient
  - Size
  - Cost

# Real Capacitors

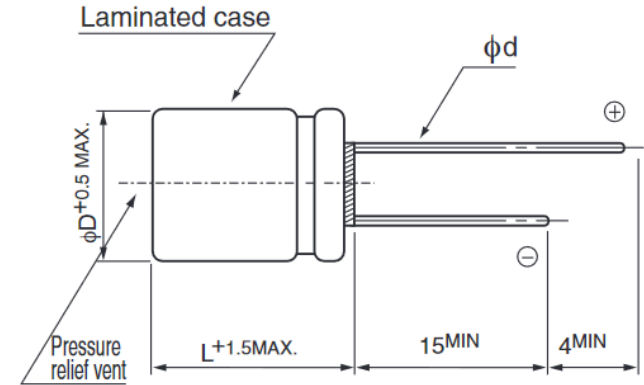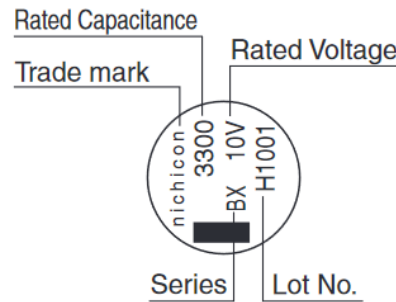
Example: *Aluminum electrolytic capacitor*



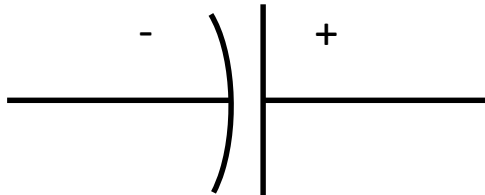Short lead/black mark indicates the cathode (more negative terminal).  
*But be careful:* Sometimes the mark indicates the anode!



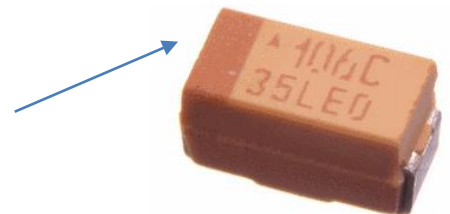Tantalum capacitor with mark labeling the anode.




# Real Capacitors

Axial Leaded Multilayer Ceramic Capacitors

Aximax, 400, Conformally Coated, Z5U Dielectric, 25 – 250 VDC (Commercial Grade)



## Construction

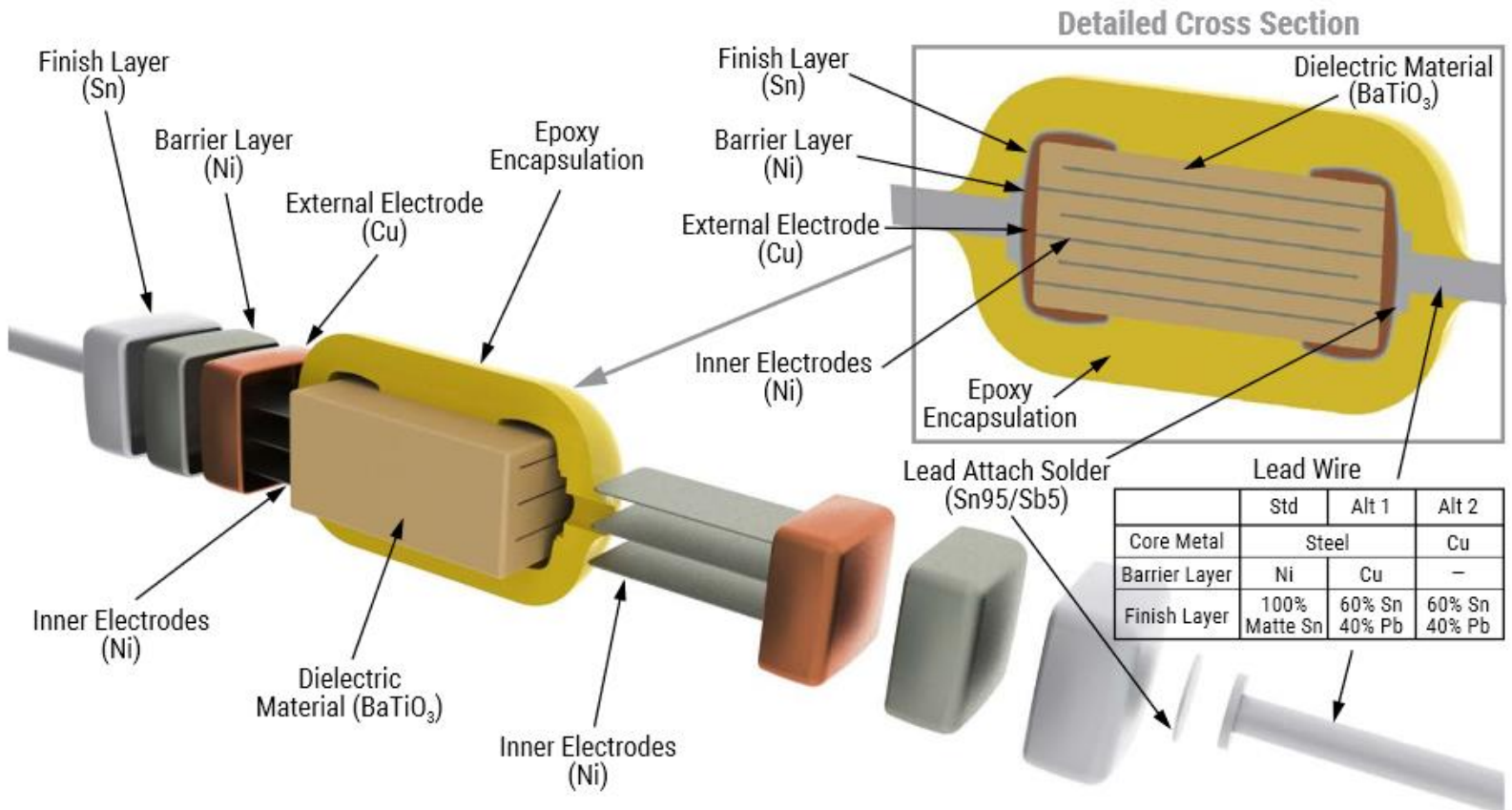

# Real Capacitors

- Ceramic capacitors are not polarized



## Detailed Description

0.22 $\mu$ F  $\pm$ 20% 50V Ceramic Capacitor Z5U Axial


Tolerance

Maximum  
operating  
voltage

Dielectric  
material



# Real Capacitors

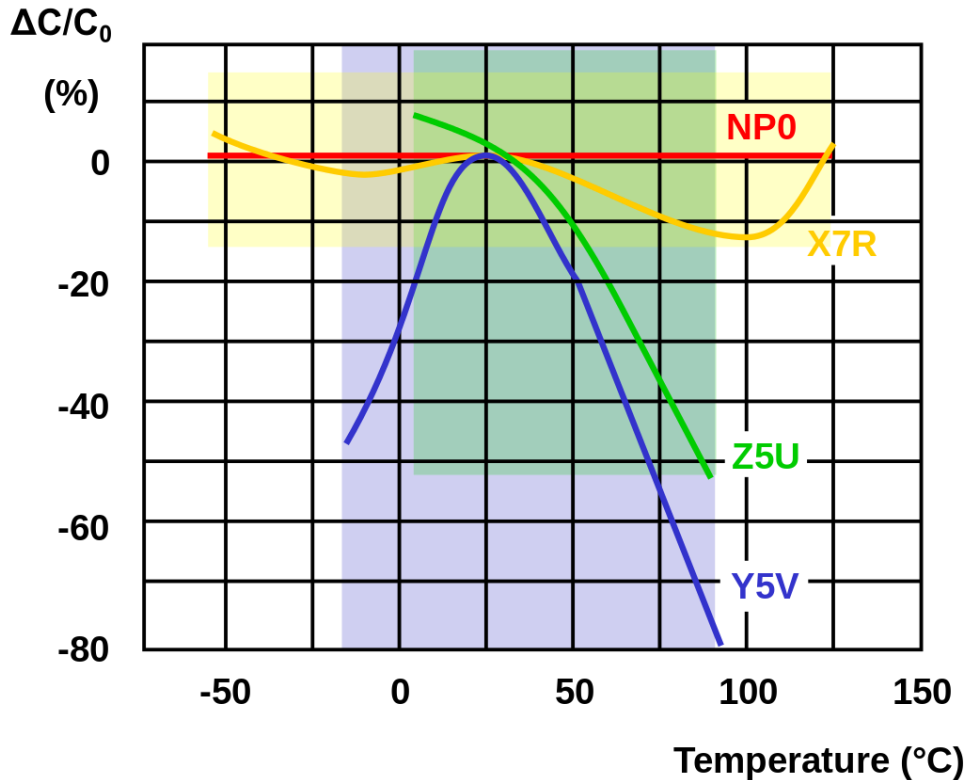

Cost:

**Z5U: \$0.31 each**

**X7R: \$0.51 each**

Model for a real capacitor:

$$C = C_0 \cdot (1 + aV + bV^2) \cdot (1 + \alpha(T - T_0) + \beta(T - T_0)^2)$$

# Real Voltage Sources

- An ideal voltage source produces a constant potential difference, independent of the current through it
- A chemical battery is not an ideal voltage source




## Specifications

Nominal Capacity:	1800 mAh
Nominal Voltage:	3V
Weight:	Approximately 18g
Operating Temperature:	-40°C - +85°C

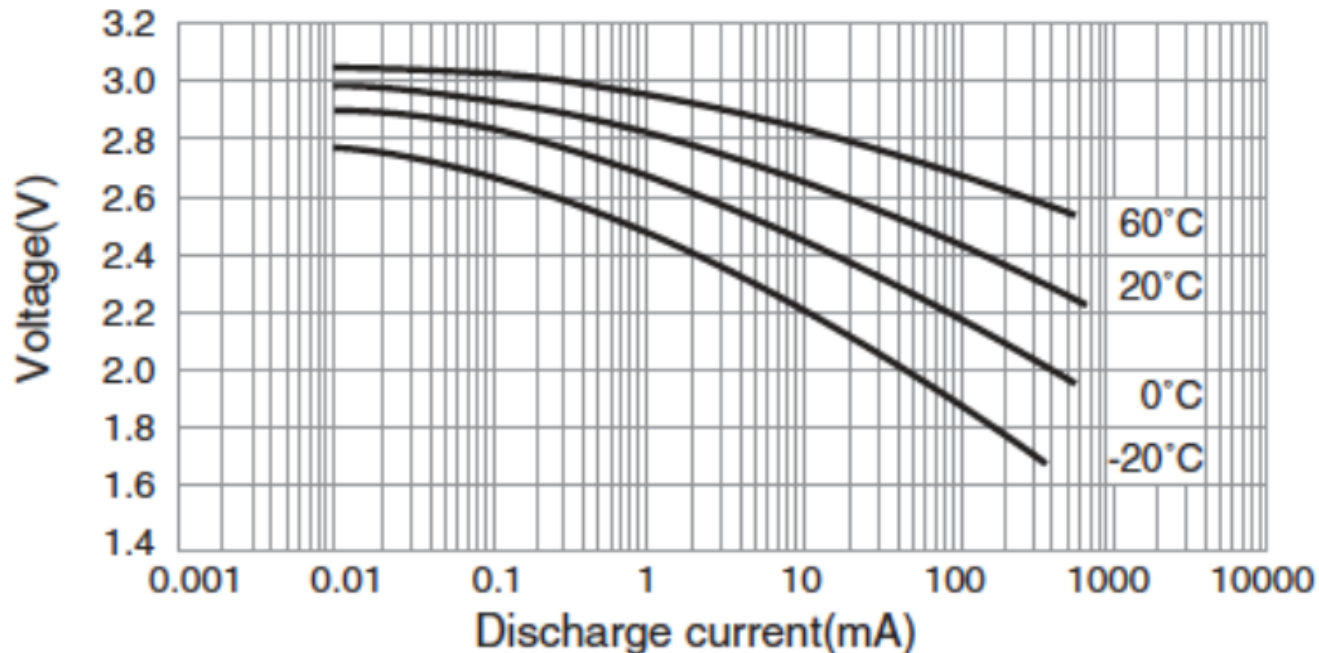
# Real Voltage Sources

- The operating voltage is not constant:


**Operating Voltage vs. Discharge Current  
(voltage at 50% discharge depth)**



# Real Voltage Sources

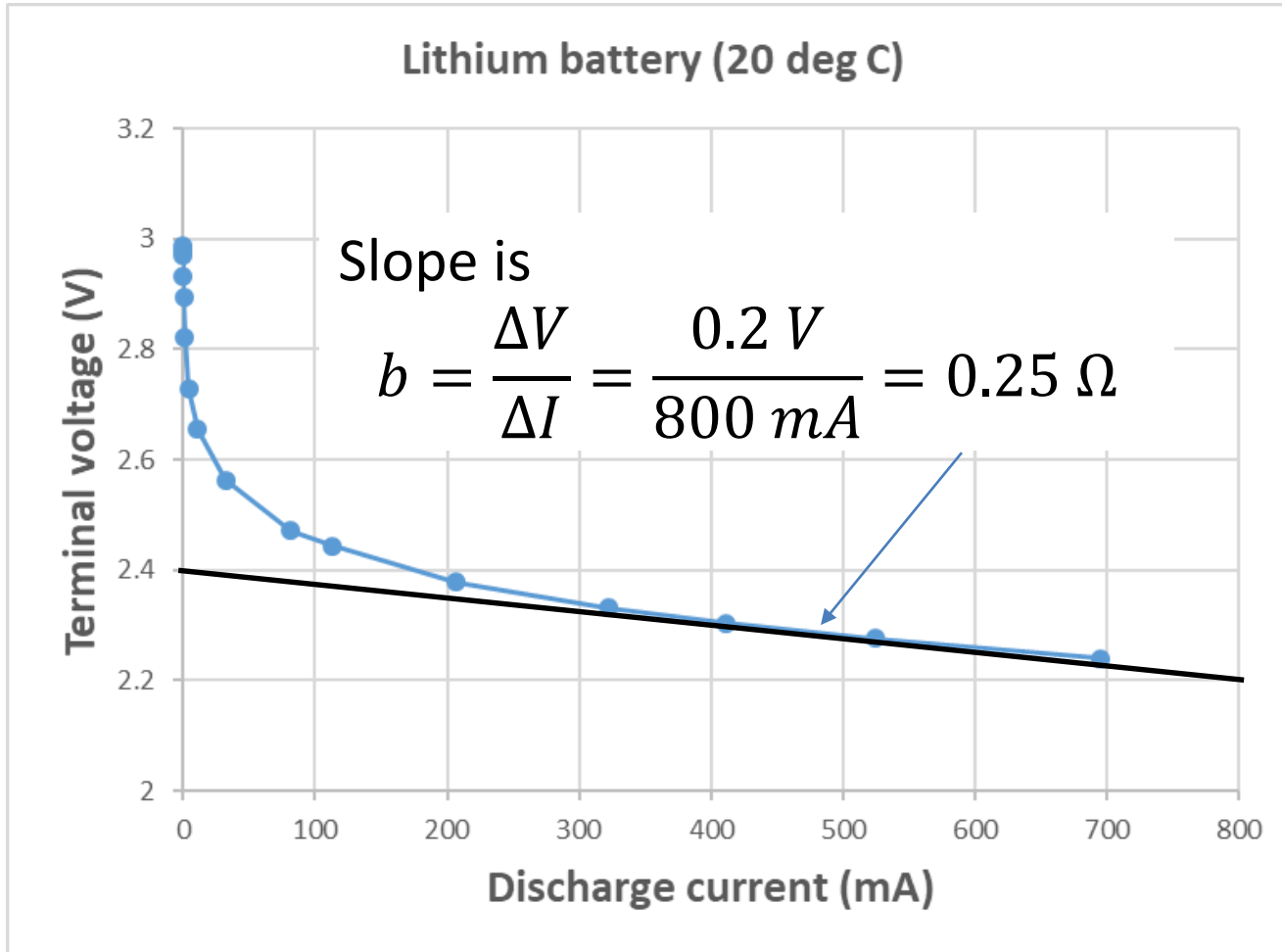

# Model for a Real Voltage Source

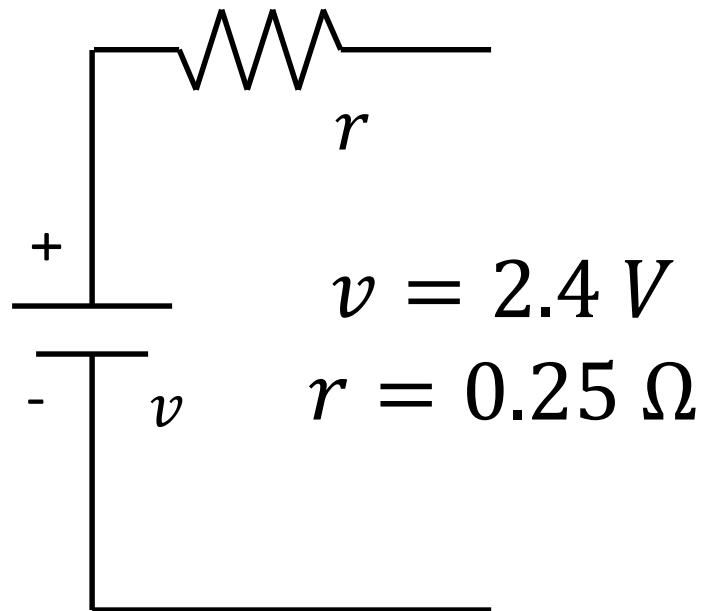

The model is only valid for a specific range of discharge currents, in this case maybe between 300 and 700 mA, and only when the temperature is 20 °C.


# Common DC Voltage Sources

- Frequently, only a limited number of DC voltage sources are present in a circuit:

Voltage (V)	Application
1.2 V	Integrated circuit core voltage
1.8 V	Low voltage digital circuits
2.5 V	Digital I/O logic
3.3 V	Digital logic
5 V	Analog/digital logic
12 V	Power distribution, industrial applications
24 V	Avionics and defense applications
48 V	Power distribution
> 50 V	Safety precautions required!

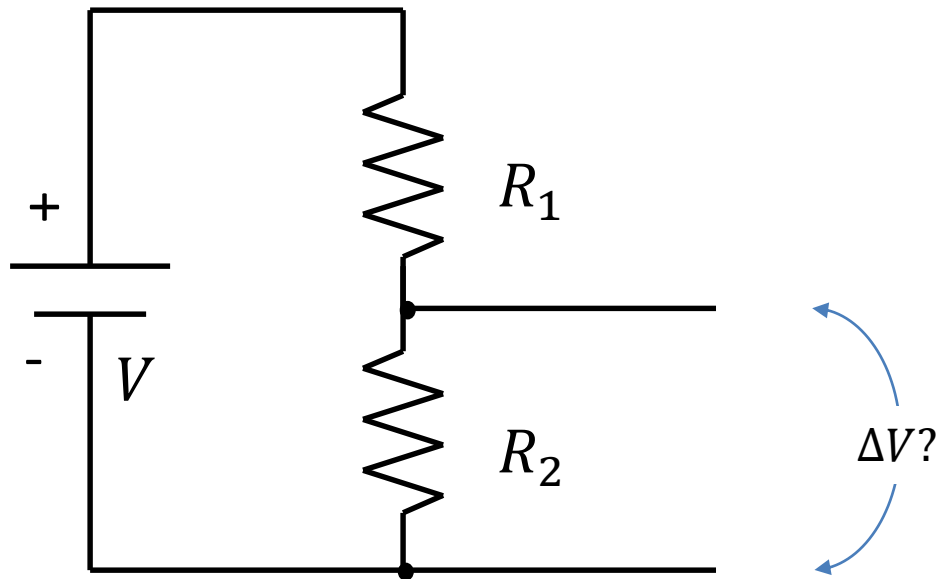
# Voltage Divider Circuit

- A common technique for generating other voltages is with a voltage divider:


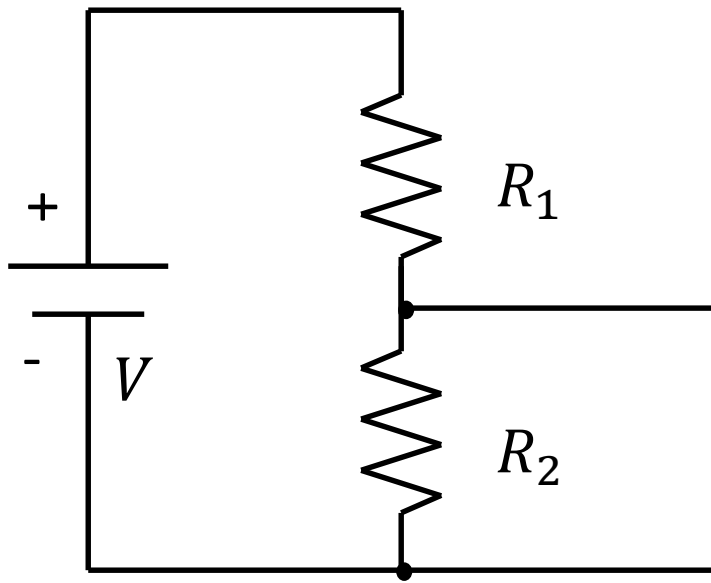
# Voltage Divider Circuit

- A common technique for generating other voltages is with a voltage divider:




With no load applied, the current through  $R_1$  and  $R_2$  will be

$$I = \frac{V}{R_1 + R_2}$$

Then,
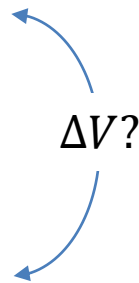
$$\Delta V = IR_2 = \frac{VR_2}{R_1 + R_2}$$




*But this is not enough information to solve for  $R_1$  and  $R_2$  uniquely.*



# Voltage Divider Circuit

- Equivalent circuit:

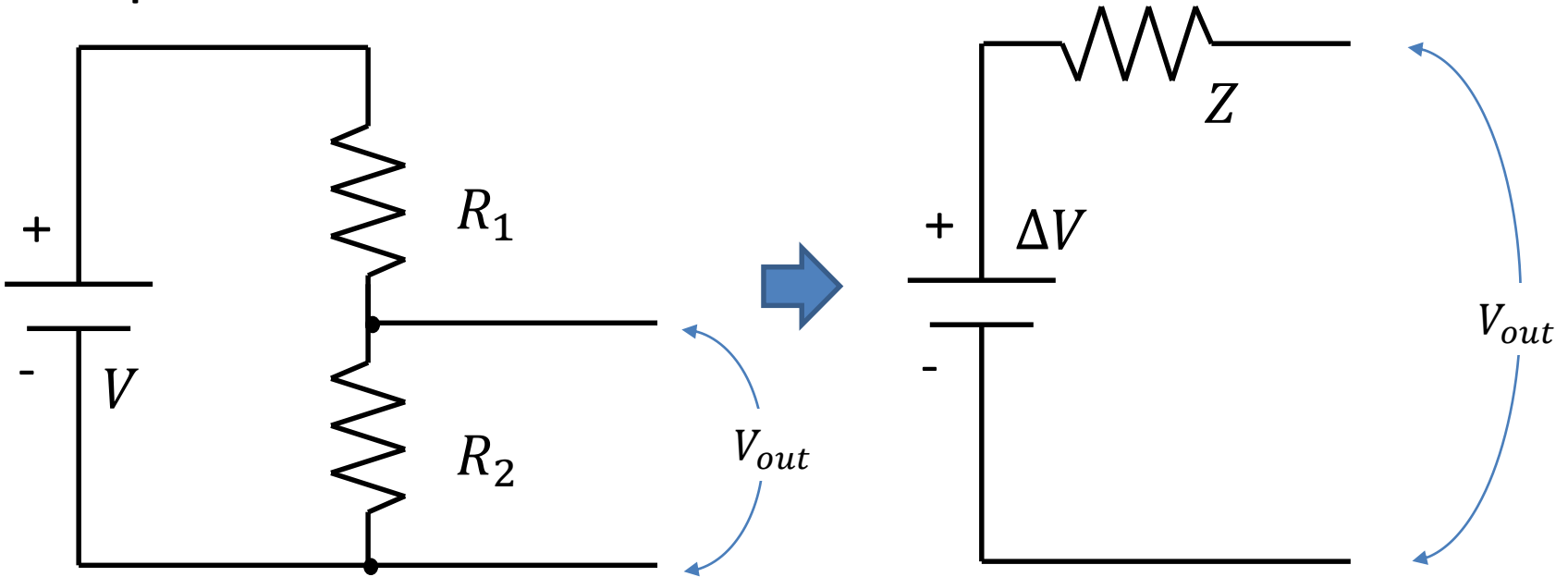

$$\Delta V = \frac{VR_2}{R_1 + R_2} \quad Z = \frac{R_1 R_2}{R_1 + R_2}$$

This is a very good assignment question!


# What about more Complicated Circuits?

- We need a systematic way of analyzing arbitrarily complex circuits
- Calculate the currents that flow in an electric circuit composed of various circuit elements connected by wires.
- The currents will be solutions to a system of (differential) equations
- If the problem is too complicated to solve algebraically, get a computer to solve it numerically

# Kirchhoff Loop Rule

- Recall that work done to move a charge  $q$  from point  $a$  to point  $b$  is  $W = -q \int_a^b \vec{E} \cdot d\vec{\ell}$
- If  $a$  and  $b$  are the same point then  $W = 0$


$$\oint \vec{E} \cdot d\vec{\ell} = 0$$

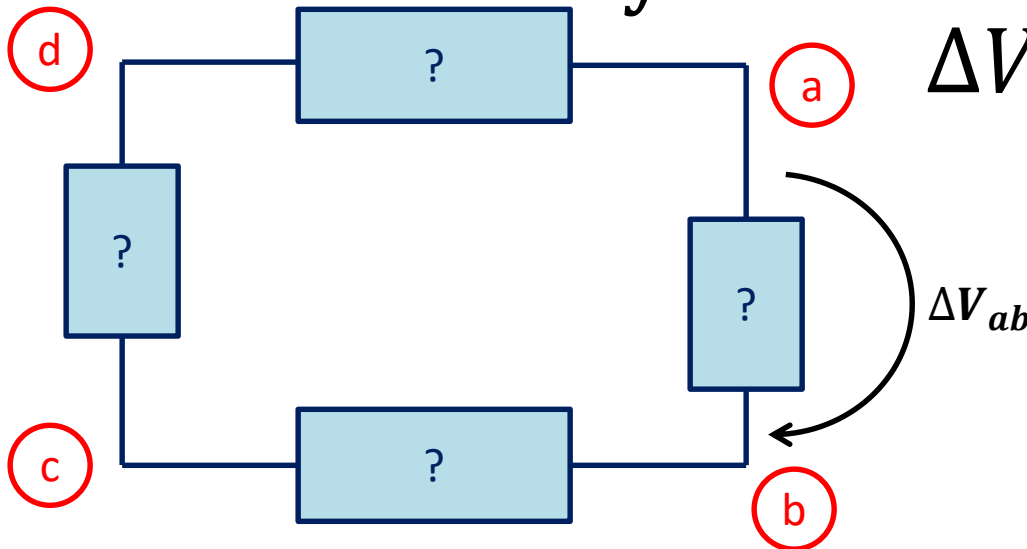


$$\Delta V_{ab} + \Delta V_{bc} + \Delta V_{cd} + \Delta V_{da} = 0$$
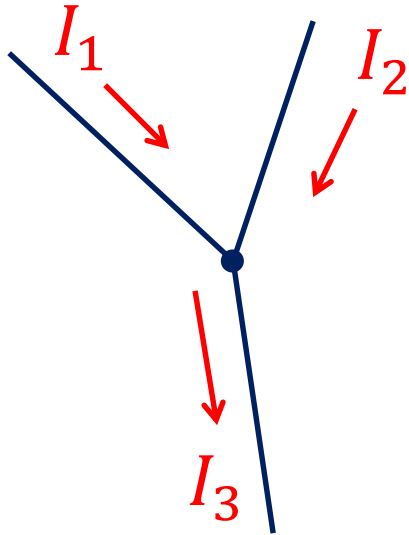
# Kirchhoff's Node Rule

- The sum of the currents entering a node must equal the sum of the currents leaving.



$$I_1 + I_2 = I_3$$

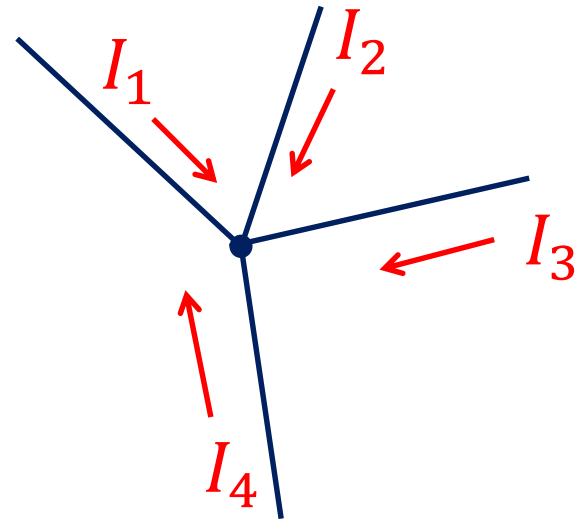


$$I_1 + I_2 + I_3 + I_4 = 0$$


(at least one of these must be negative)

# Circuit Elements

- Voltage sources (like batteries):

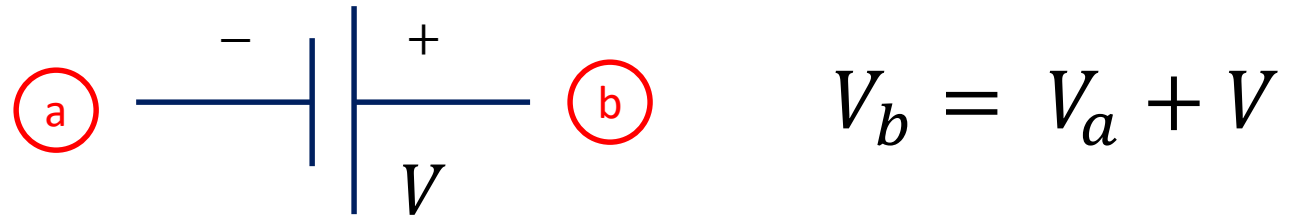


- Make sure you get the sign right!

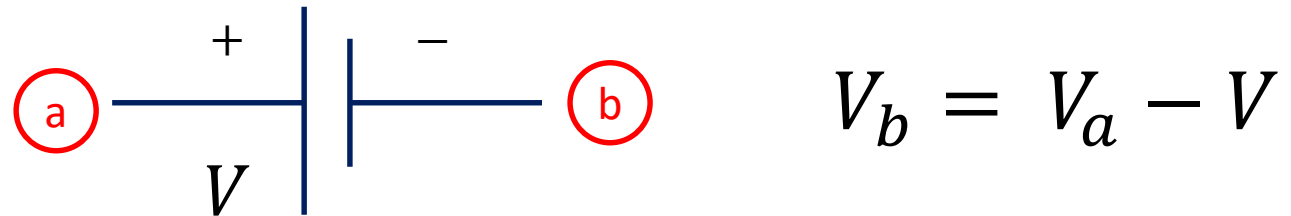
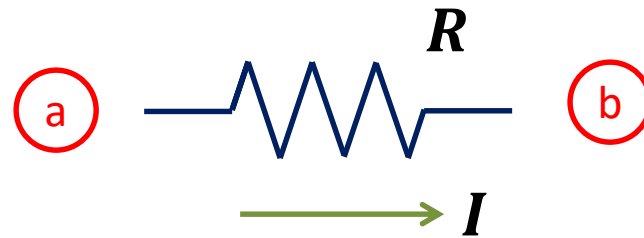
# Circuit Elements


- Resistors:

The charges lose energy as they are pushed through the resistor.



$$V_b = V_a - IR$$


- Make sure you get the sign right!

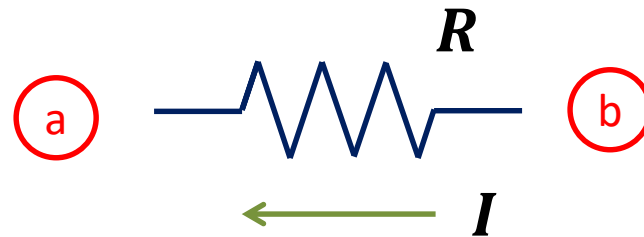

$$V_b = V_a + IR$$

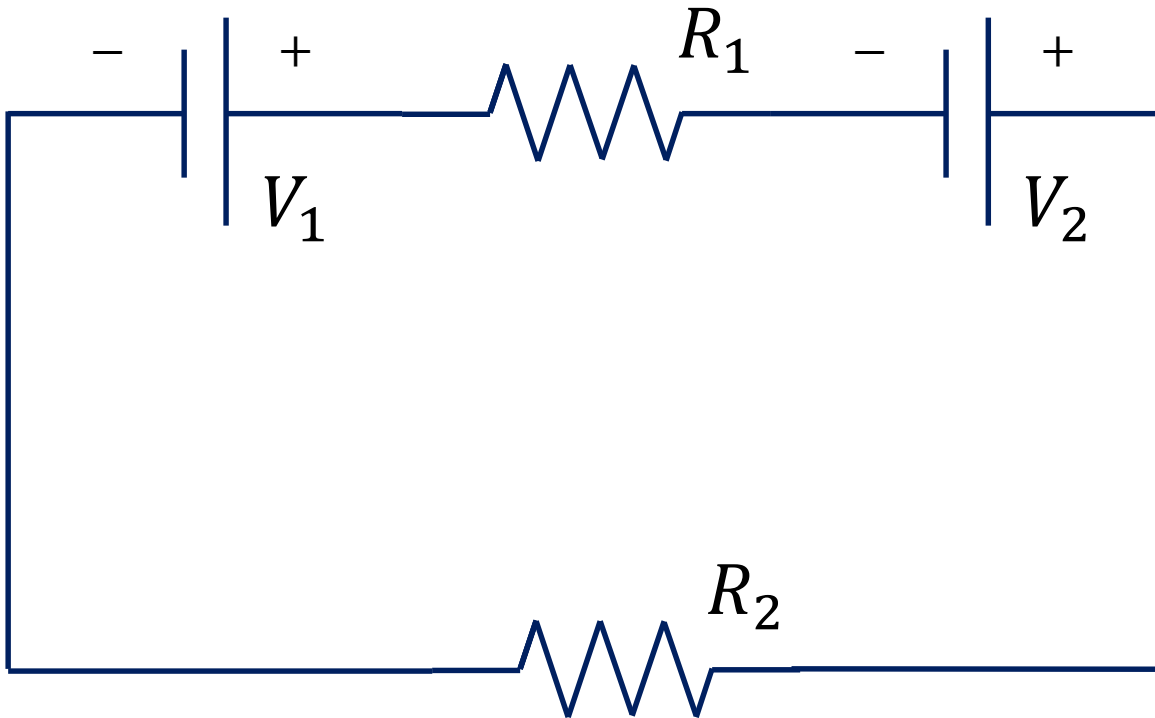
# Circuit Analysis

- Find the current in the following circuit:


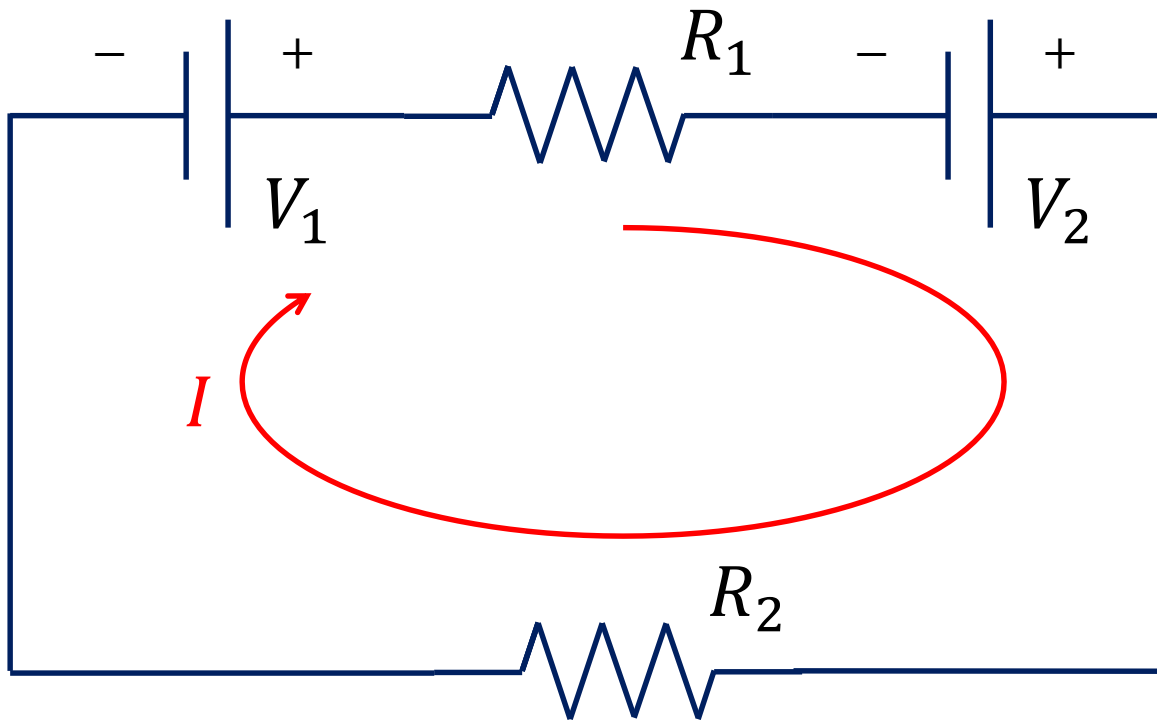
# Circuit Analysis

- Step 1: Draw a loop to represent the current.




Which direction? It doesn't matter, but let's ALWAYS pick clockwise to avoid confusion.



# Circuit Analysis


- Step 2: Apply Kirchhoff's Loop Rule...

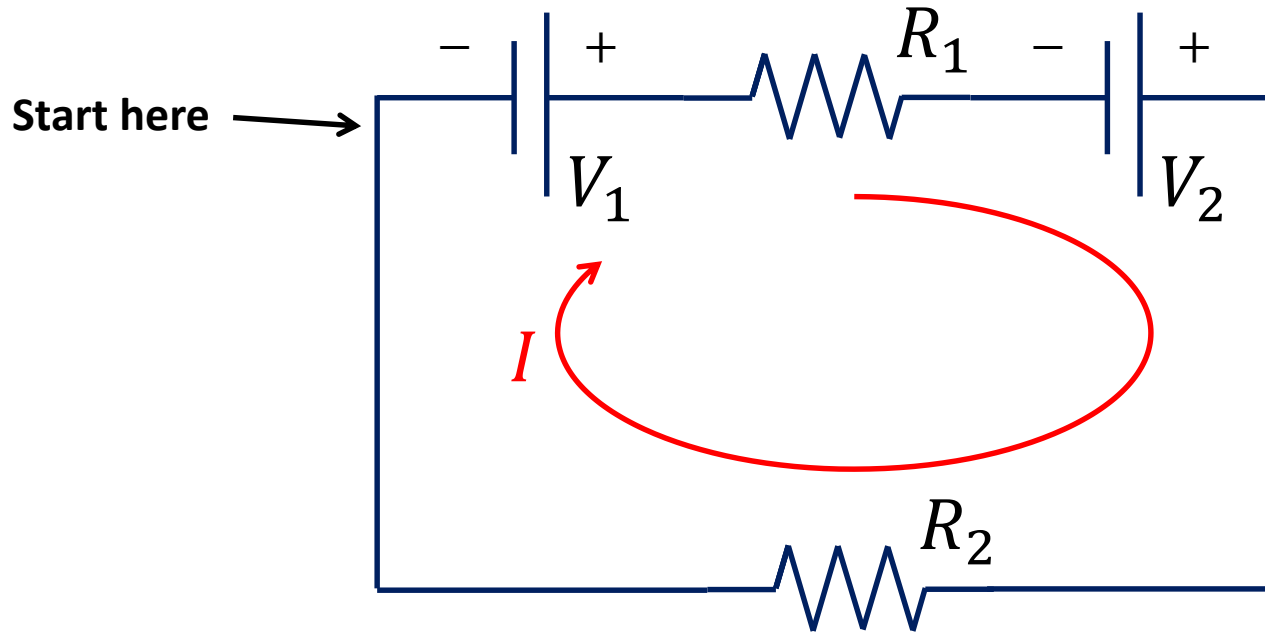

$V_1$

# Circuit Analysis

- Step 3: Solve for  $I$ ...

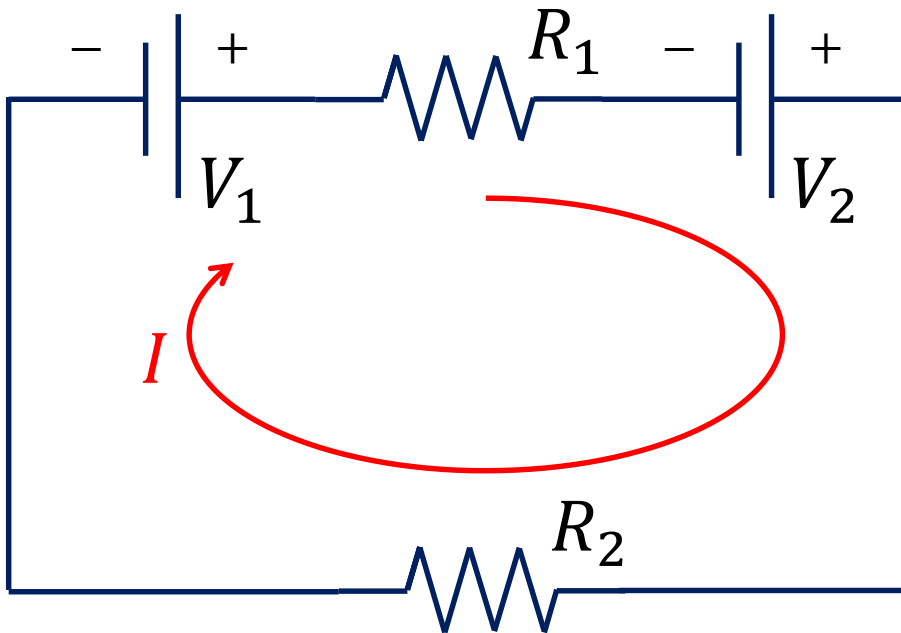


$$I = \frac{V_1 + V_2}{R_1 + R_2}$$

What if  $I$  is negative? Then it means the current flows in the opposite direction.


# Two Loops

- Step 1: Assign currents to each loop

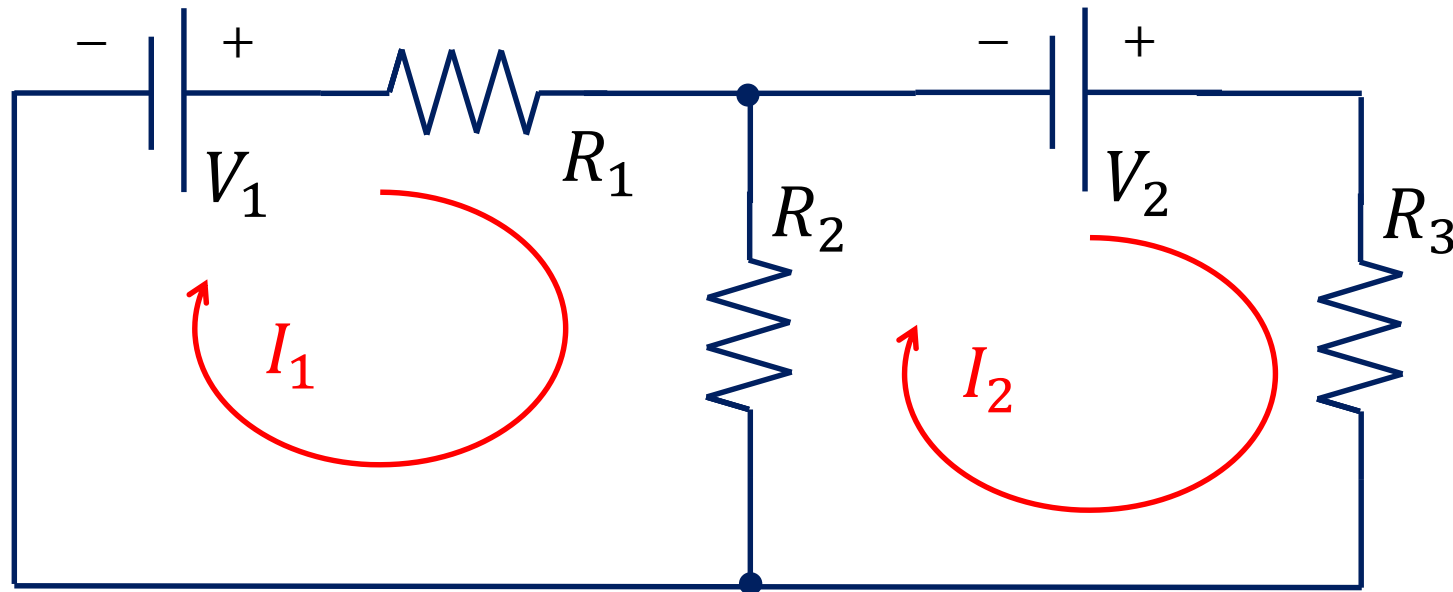

# Two Loops

- Step 2: Apply Kirchhoff's Loop rule

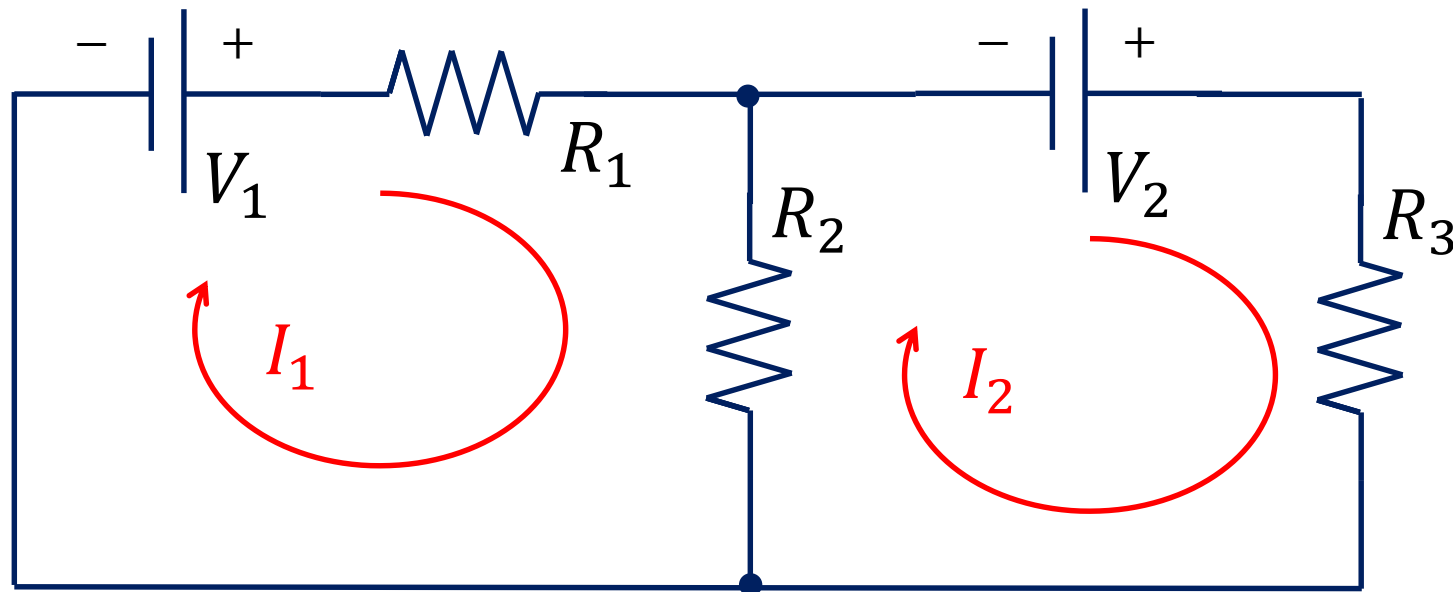

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$V_2 - I_2 R_3 - (I_2 - I_1) R_2 = 0$$

# Two Loops

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$V_2 - I_2 R_3 - (I_2 - I_1) R_2 = 0$$

This is a system of linear equations... write them as a matrix equation:

$$\begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

This should *always* be a symmetric matrix.

# Kramer's Rule

- This is the “formula” that gives you the solution to a system of linear equations:

$$\begin{aligned} a_1x + b_1y &= c_1 \\ a_2x + b_2y &= c_2 \end{aligned}$$
$$x = \frac{\begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}} = \frac{c_1b_2 - c_2b_1}{a_1b_2 - a_2b_1}$$
$$y = \frac{\begin{vmatrix} a_1 & c_1 \\ a_2 & c_2 \end{vmatrix}}{\begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix}} = \frac{a_1c_2 - a_2c_1}{a_1b_2 - a_2b_1}$$

# Two Loops

$$\begin{pmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

$$I_1 = \frac{\begin{vmatrix} V_1 & -R_2 \\ V_2 & R_2 + R_3 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}} = \frac{V_1(R_2 + R_3) + V_2 R_2}{(R_1 + R_2)(R_2 + R_3) - (R_2)^2}$$

$$I_2 = \frac{\begin{vmatrix} R_1 + R_2 & V_1 \\ -R_2 & V_2 \end{vmatrix}}{\begin{vmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{vmatrix}} = \frac{V_2(R_1 + R_2) + V_1 R_2}{(R_1 + R_2)(R_2 + R_3) - (R_2)^2}$$