

Physics 53600

Electronics Techniques for Research

Now in PowerPoint!

Spring 2020 Semester

Prof. Matthew Jones

Simulating Circuits using SPICE


- After the invention of planar integrated circuits, analog designs became increasingly complex
- The time required to fabricate a design became much longer
- It was no longer possible to adjust component values to optimize circuit performance
- There was a need to accurately model analog electronic circuits in the design process

SPICE

- **Simulation Program with Integrated Circuit Emphasis**
 - Initial concept developed in the 1960's
 - SPICE 1 released into public domain May 1972
 - SPICE 2 released in 1975
 - SPICE 3 released in March 1985
 - SPICE 3f.5 released in 1993
- **Commercial versions**
 - PSPICE (Cadence Design Systems)
 - HSPICE (Synopsys)
- **Free spinoffs:**
 - ADICE (Analog Devices)
 - LTspice (Liner Technologies → Analog Devices)
 - A few others

Defining Circuits

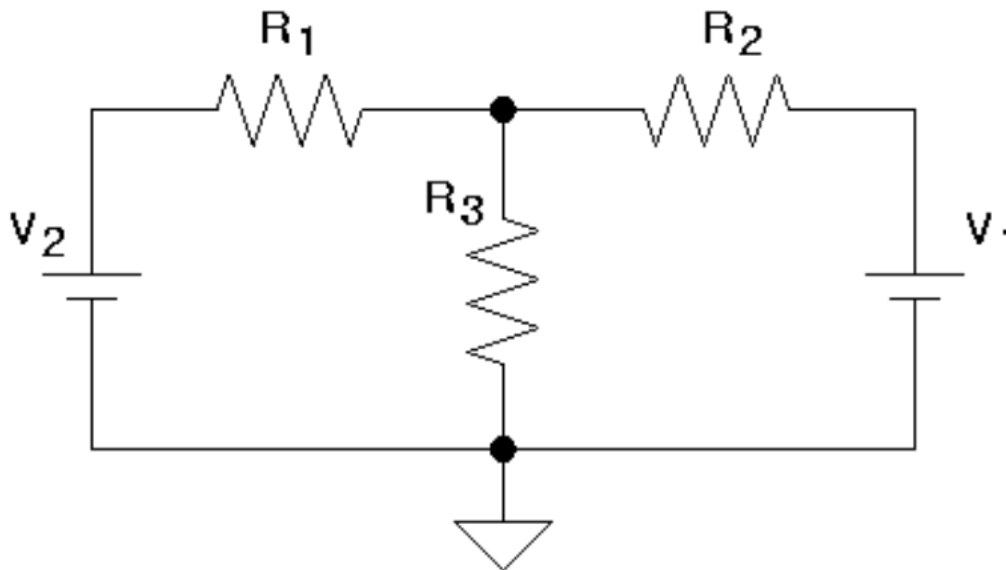- SPICE performs numerical simulation of circuits
 - All components must have numerical values



Component Value


V_1	5 V
V_2	10 V
R_1	10 Ω
R_2	20 Ω
R_3	5 Ω

Defining Circuits

- Simulation of the circuit requires translating the schematic into a representation that can be interpreted by SPICE.
- This representation is called the *netlist*
- First, assign labels to each node in the circuit
- Then specify which components are connected to the nodes

Defining Circuits

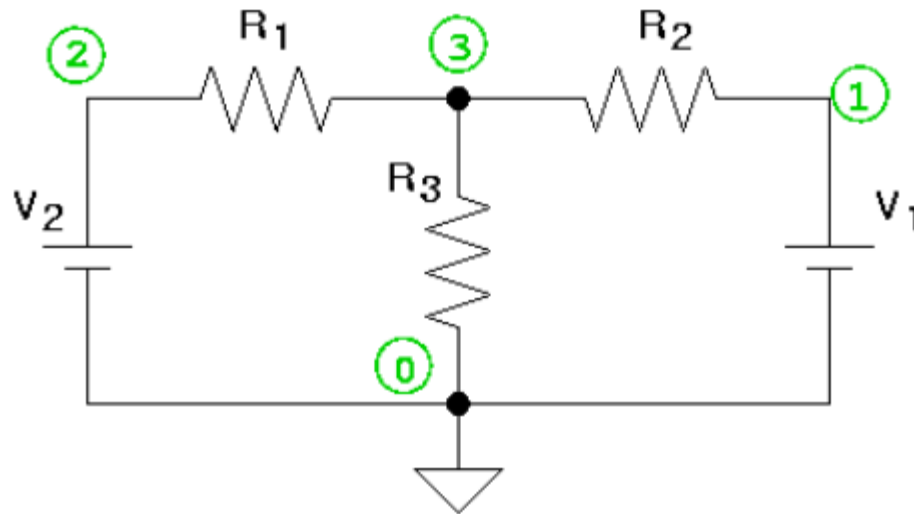- It is necessary to assign a ground node “0” in each disconnected part of the circuit
- Other nodes can have arbitrary labels



Defining Circuits

- The netlist consists of a list of all components and the nodes to which they are connected
 - Resistors: `Rxxxxxxx N1 N2 <VALUE>`
 - Voltage sources: `Vxxxxxxx N+ N- DC <VALUE>`
- This is the complete netlist:

```
V1 1 0 DC 5V
V2 2 0 DC 10V
R1 2 3 10
R2 1 3 20
R3 3 0 5
```

} Assumes ohms

Defining Circuits

- Some minor additions are needed
 - A title for the circuit
 - What type of numerical analysis to perform?
 - The end

```
PHYSICS 536 EXAMPLE CIRCUIT
```

```
V1 1 0 DC 5V
```

```
V2 2 0 DC 10V
```

```
R1 2 3 10
```

```
R2 1 3 20
```

```
R3 3 0 5
```

```
.OP
```

```
.END
```



DC operating point analysis

SPICE Output

Operating point information:

Node	Voltage
----	-----
V(3)	3.571429e+00
V(2)	1.000000e+01
V(1)	5.000000e+00

Voltages of each node
(electric potential with respect to ground)

Source	Current
-----	-----

v1#branch	-7.14286e-02
v2#branch	-6.42857e-01

Current through each voltage source

Resistor models (Simple linear resistor)
model R

rsh	0
narrow	0
tc1	0
tc2	0
defw	1e-05

Resistor models
(with temperature coefficients)

Resistor: Simple linear resistor

device	r3	r2	r1
model	R	R	R
resistance	5	20	10
i	0.714	0.0714	0.643
p	2.55	0.102	4.13

Current and power for each resistor

Vsource: Independent voltage source


device	v2	v1
dc	10	5
acmag	0	0
i	-0.643	-0.0714
p	6.43	0.357

Current and power for each voltage source

CPU time since last call: 0.006 seconds.

Total CPU time: 0.006 seconds.

SPICE Output

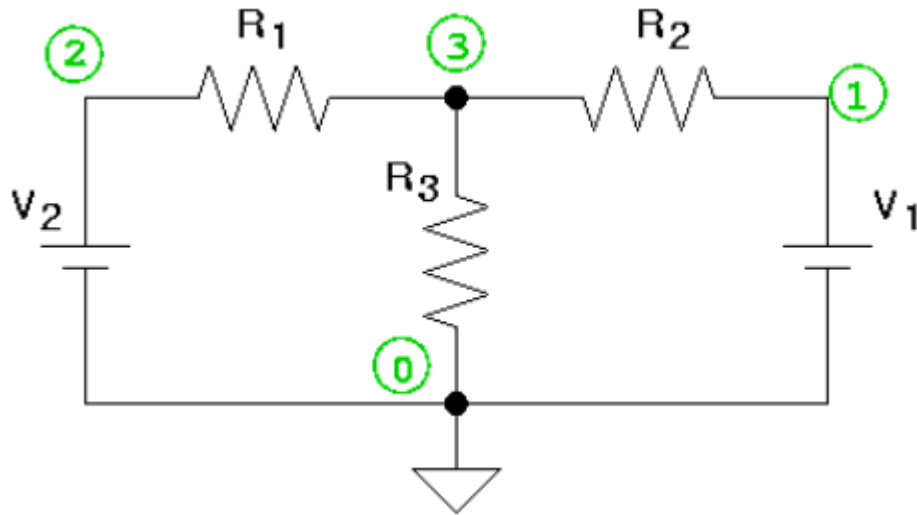

Component Value Current


V ₁	5 V	71.4 mA
V ₂	10 V	643 mA
R ₁	10 Ω	643 mA
R ₂	20 Ω	71.4 mA
R ₃	5 Ω	714 mA

- All the current flowing from V1 must pass through R2
- All the current flowing from V2 must flow through R1
- Current flowing through R3 must be the sum of these currents
- SPICE reports the current flowing *into* the positive node of voltage sources.

Source	Current
-----	-----

v1#branch	-7.14286e-02
v2#branch	-6.42857e-01

Transient Analysis

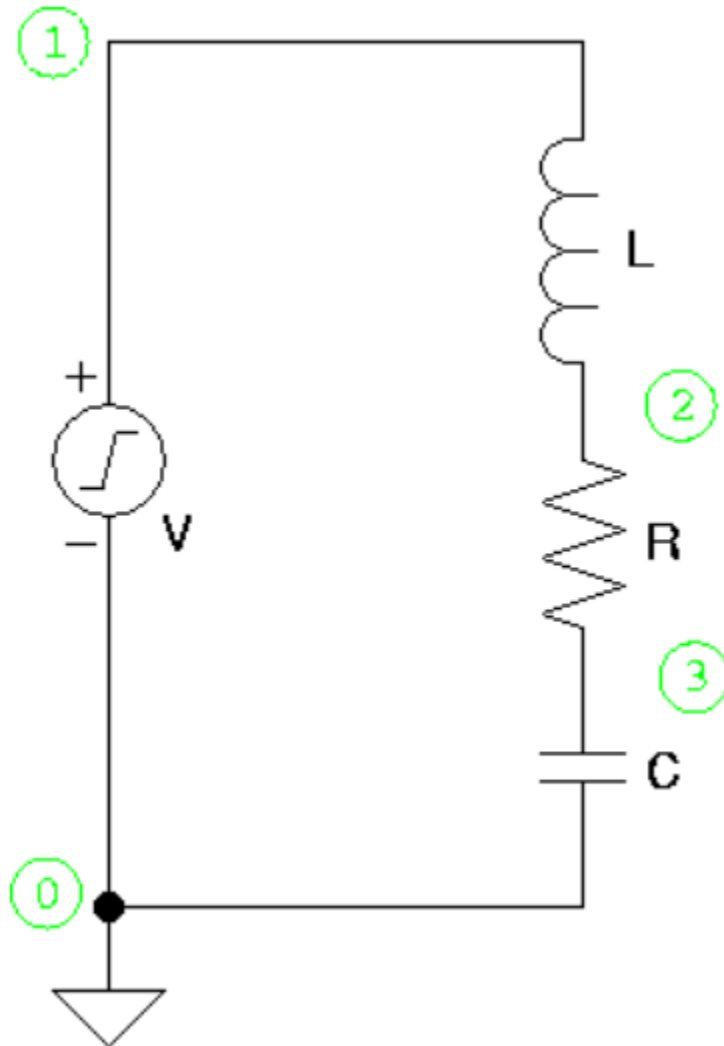

Component

Value

V_1 0 V for $t < 0$, 10 V for $t > 0$

L_1 470 μH

C_1 5.4 nF

R_1 100 Ω

Netlist:

```
RLC CIRCUIT
V1 1 0 PULSE(0 10)
L1 1 2 470UH
C1 3 0 5.4NF
R1 2 3 100
.PRINT TRAN I(V1)
.TRAN 1US 100US
.END
```

Transient Analysis


- What range of resistances will produce oscillations?

$$\frac{R^2}{4L^2} < \frac{1}{LC}$$


- Expect oscillations for $R < 590 \, \Omega$
- Oscillation frequency is $f = \frac{\omega}{2\pi} = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$
- When $R = 100 \, \Omega$, $f = 101 \, kHz$

Transient Response

$R = 100\ \Omega$

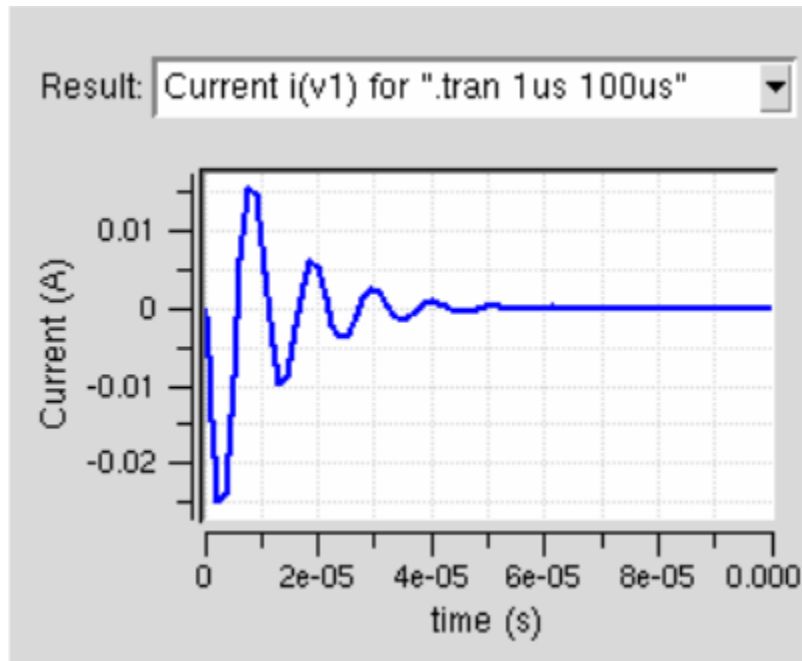


$R = 600\ \Omega$

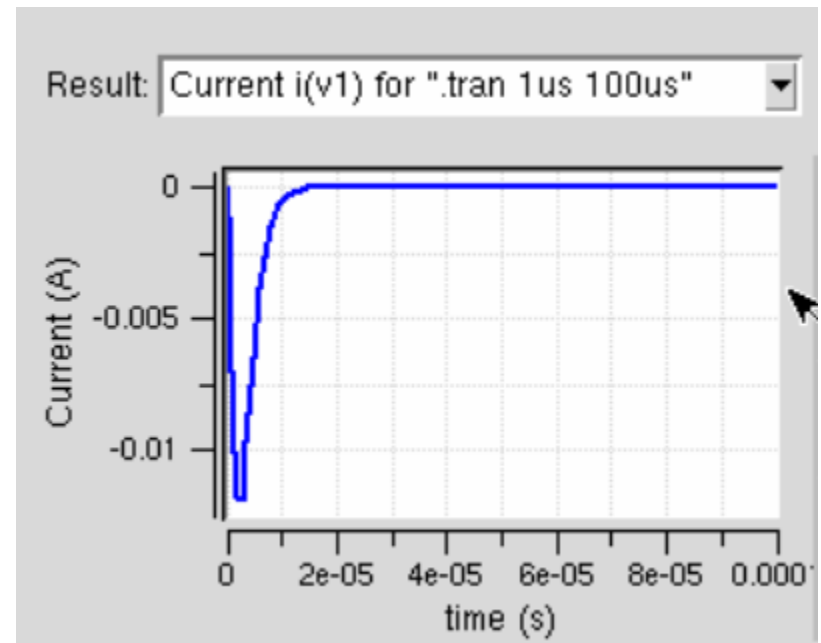

Remember that the current is measured flowing INTO the positive node of the voltage source

A Low-Pass Filter Example

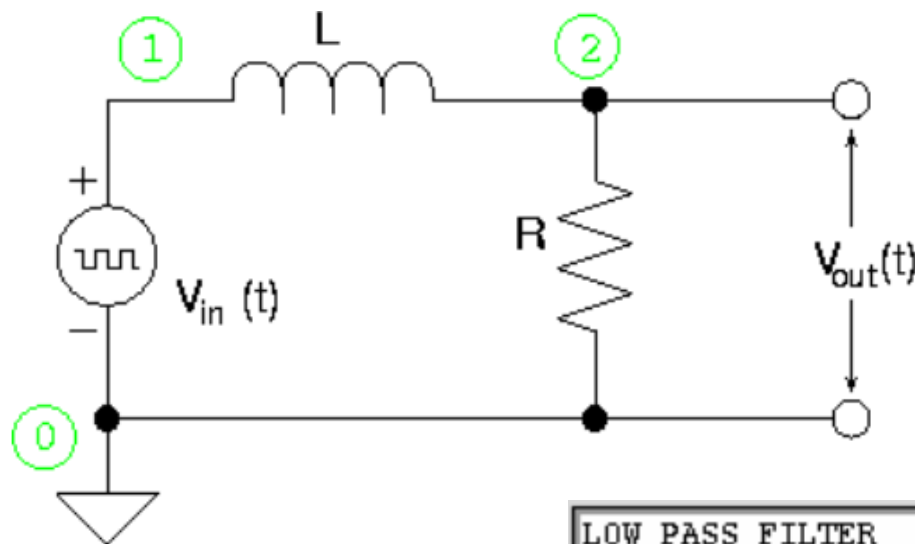- Inductors pass low frequencies (just a wire for DC)
- Capacitors pass high frequencies



Component	Value
$V_{in}(t)$	+ - 1 V square wave, $f=250$ kHz
L	$10 \mu\text{H}$
R	63Ω

```
LOW PASS FILTER
VIN 1 0 PULSE(-1 1 0.0 1NS 1NS 2US 4US)
L1 1 2 10UH
R1 2 0 63
.PRINT TRAN V(2) V(1)
.TRAN 10NS 8US
.END
```

A Low-Pass Filter Example

- Voltage source defined using

```
VIN <N+> <N-> PULSE(V1 V2 TD TR TF PW PER)
```

V1 initial voltage (volts)

V2 pulsed voltage (volts)

TD delay time (seconds)


TR rise time (seconds)

TF fall time (seconds)

PW pulse width (seconds)

PER period of waveform (seconds)

A Low-Pass Filter Example

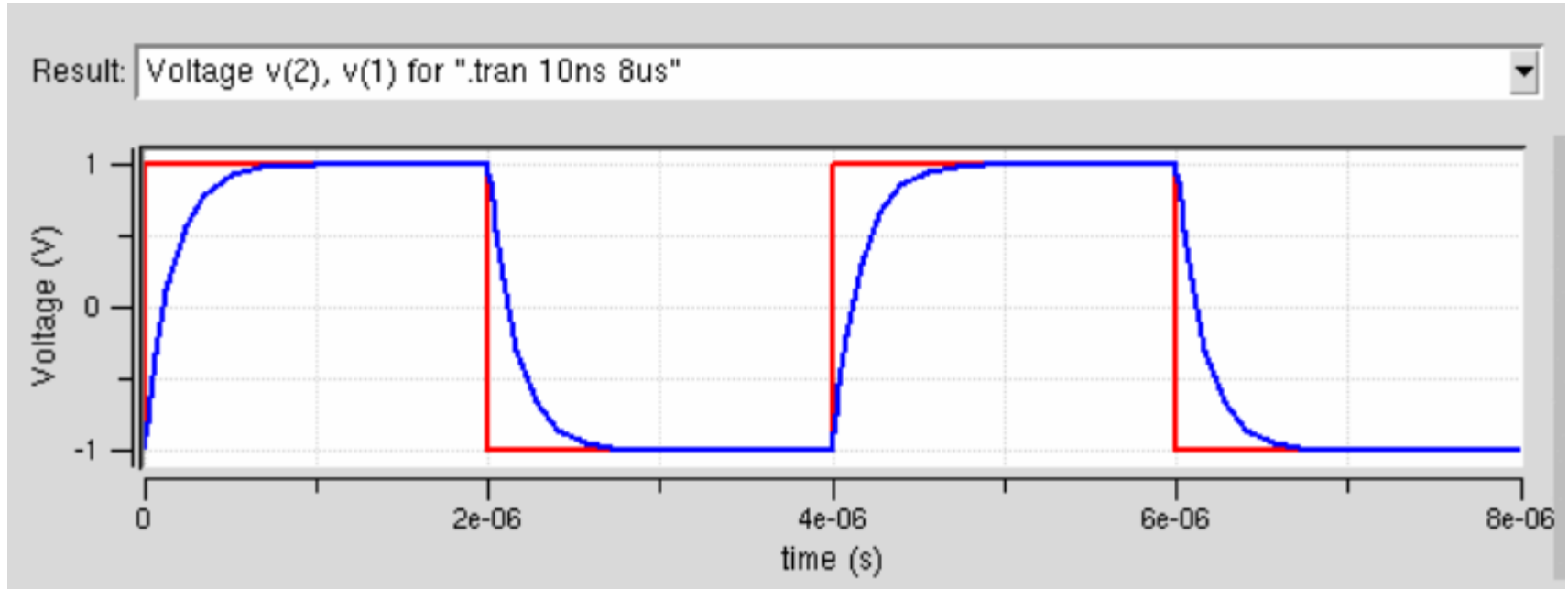

- The inductor blocks the high frequency components and rounds off the sharp corners.

Using LTspice

- LTspice was developed by Linear Technologies and was used in-house for IC and power supply circuit design
- In addition to circuit simulation, it provides a graphical schematic entry interface
- In July 2016, Analog Devices acquired Linear Technologies (amicably) for \$14.8 billion in cash and stock
- <https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

Using LTspice

- Please locate and install LTspice



Download LTspice

Download our LTspice simulation software for the following operating systems:


[Download for Windows 7, 8 and 10](#) Updated on Jan 23 2020 *

[Download for Mac OS X 10.7+](#) Updated on Nov 7 2019 *


It should be installed on the computers in the lab.

Using LTspice

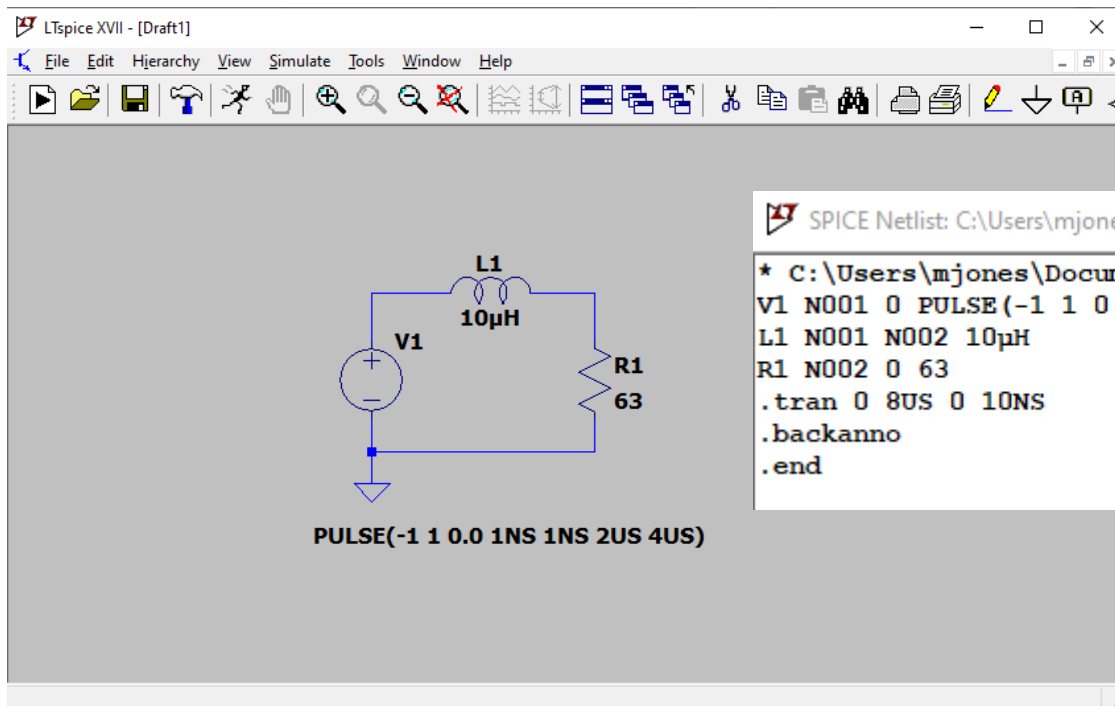
- There is lots of documentation and tutorial videos. Just ask señor google...



Using LTspice

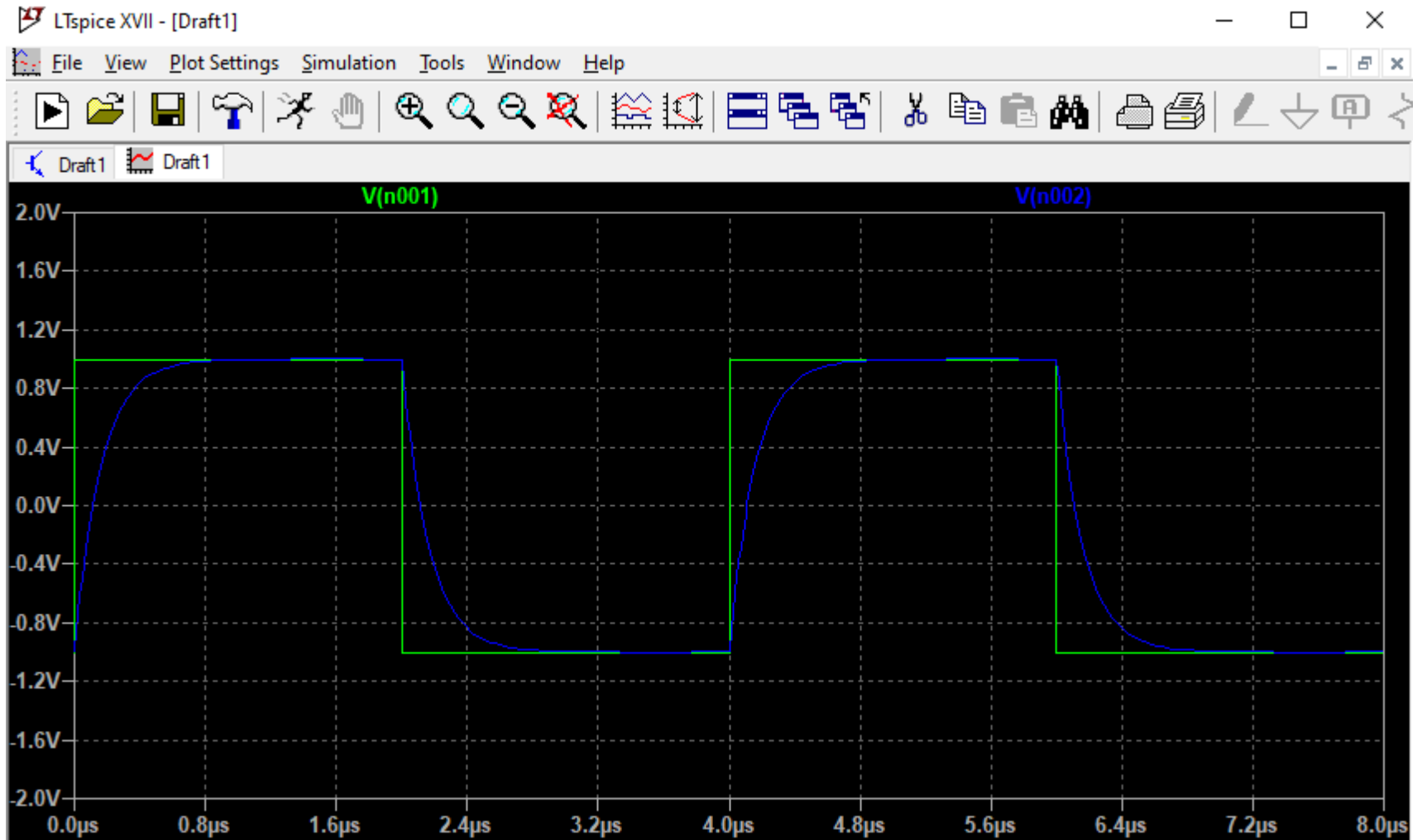


Frequency Analysis

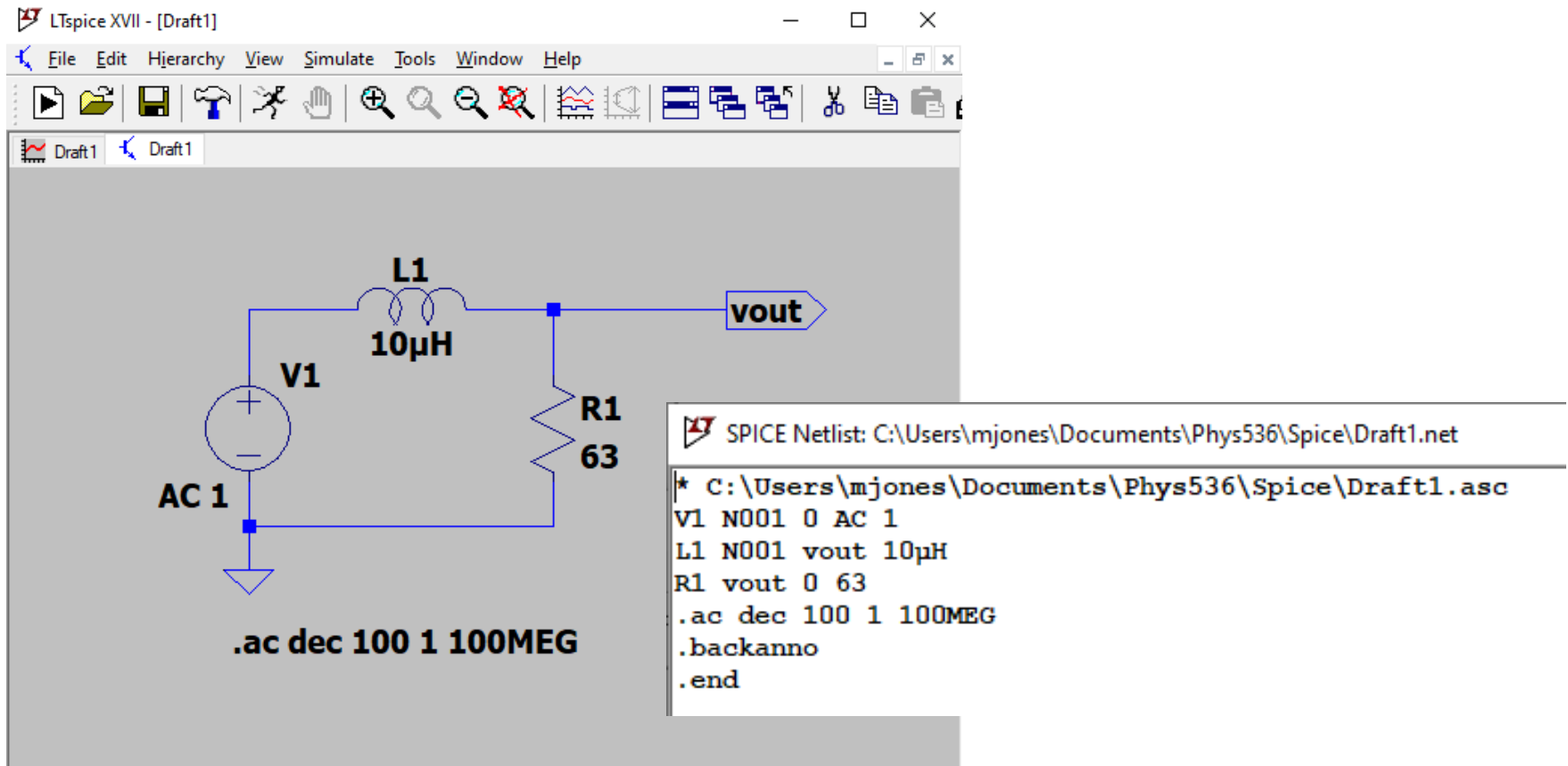

The AC analysis will scan the frequency of a voltage source and plot the ratio voltages and the relative phase

Frequency Analysis

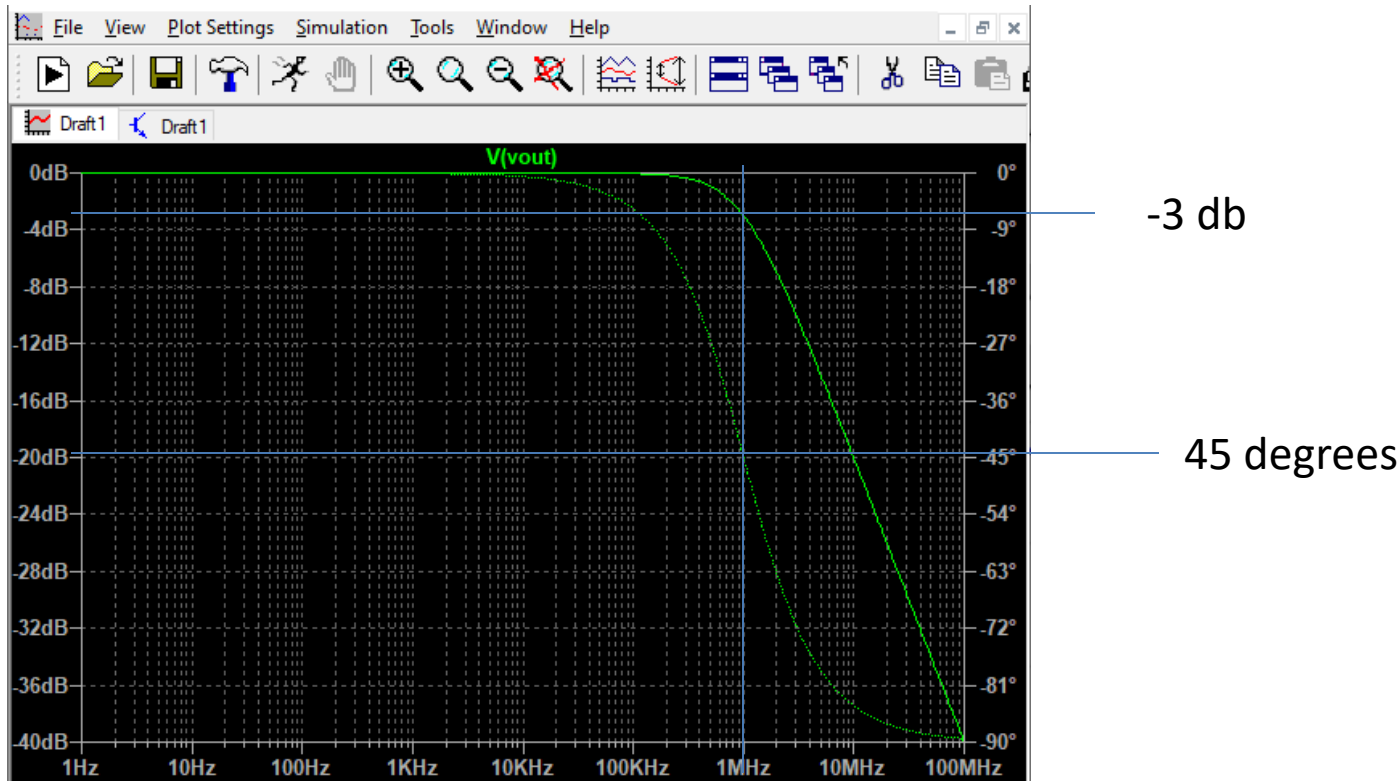


Expected cutoff frequency,

$$f_{-3 \text{ db}} = \frac{R}{2\pi L} = 1 \text{ MHz}$$

Transformers

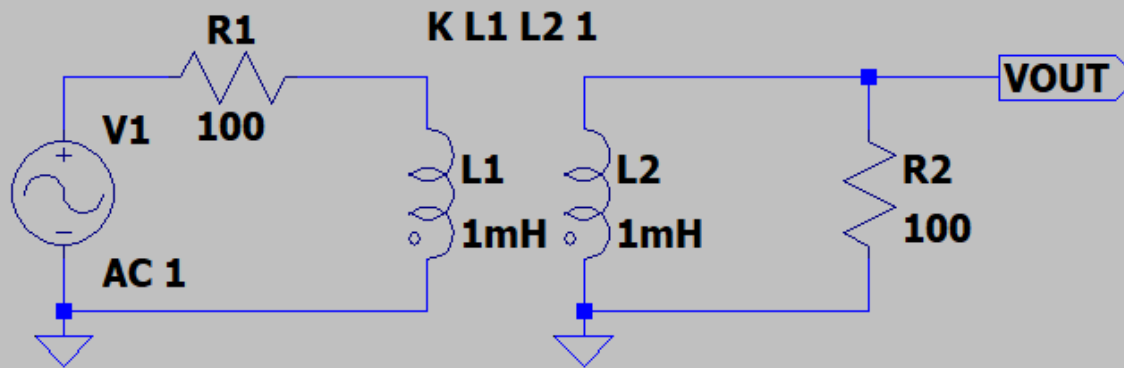
- Transformers are described by individual inductors with a specified coupling



.ac dec 100 1 100MEG

```
* C:\Users\mjones\Documents\Phys536\Spice\Lecture5.asc
R1 N002 N001 100
V1 N001 0 AC 1
L1 N002 0 1mH
L2 VOUT 0 1mH
R2 VOUT 0 100
K L1 L2 1
.ac dec 100 1 100MEG
.backanno
.end
```

Transformers

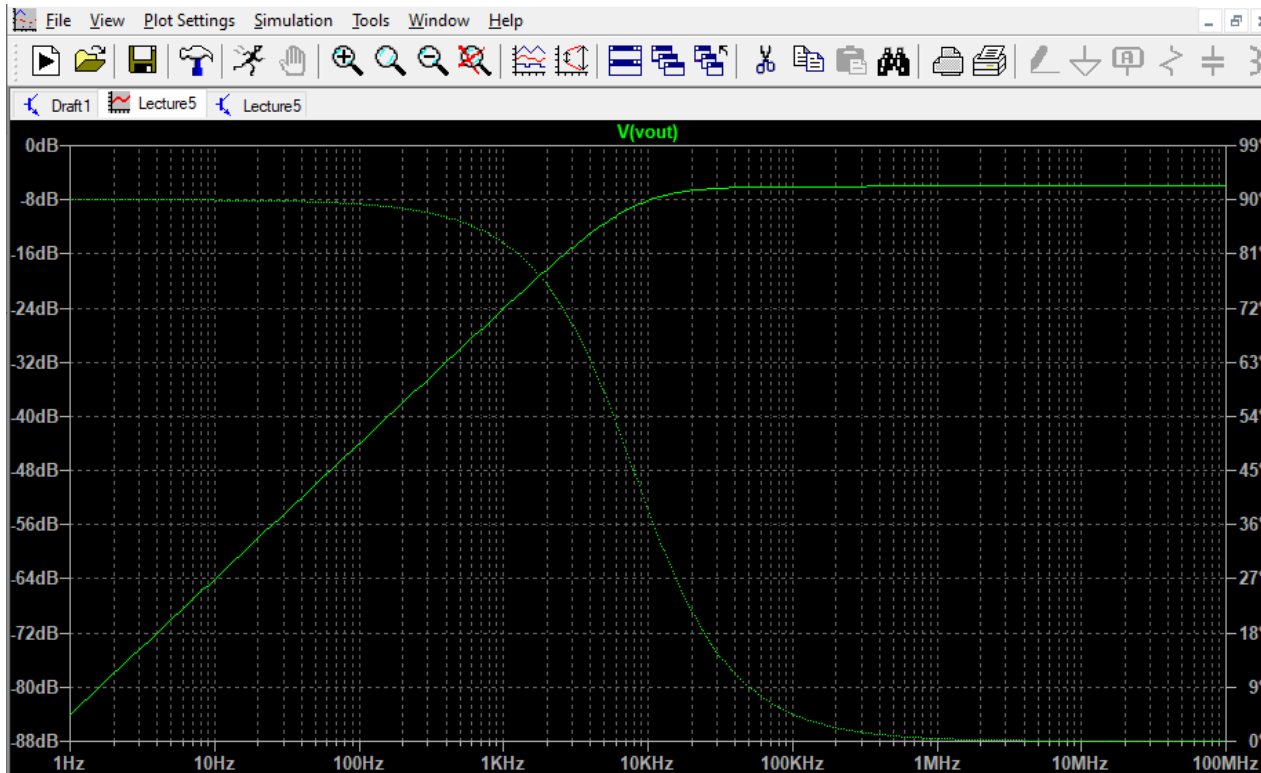

Notes:

- Make sure to define ground on BOTH sides of the transformer
- Alternatively connect both sides by a LARGE resistor