


Physics 53600
**Electronics Techniques for
Research**

Now in PowerPoint!

Spring 2020 Semester

Prof. Matthew Jones

Transmission Lines

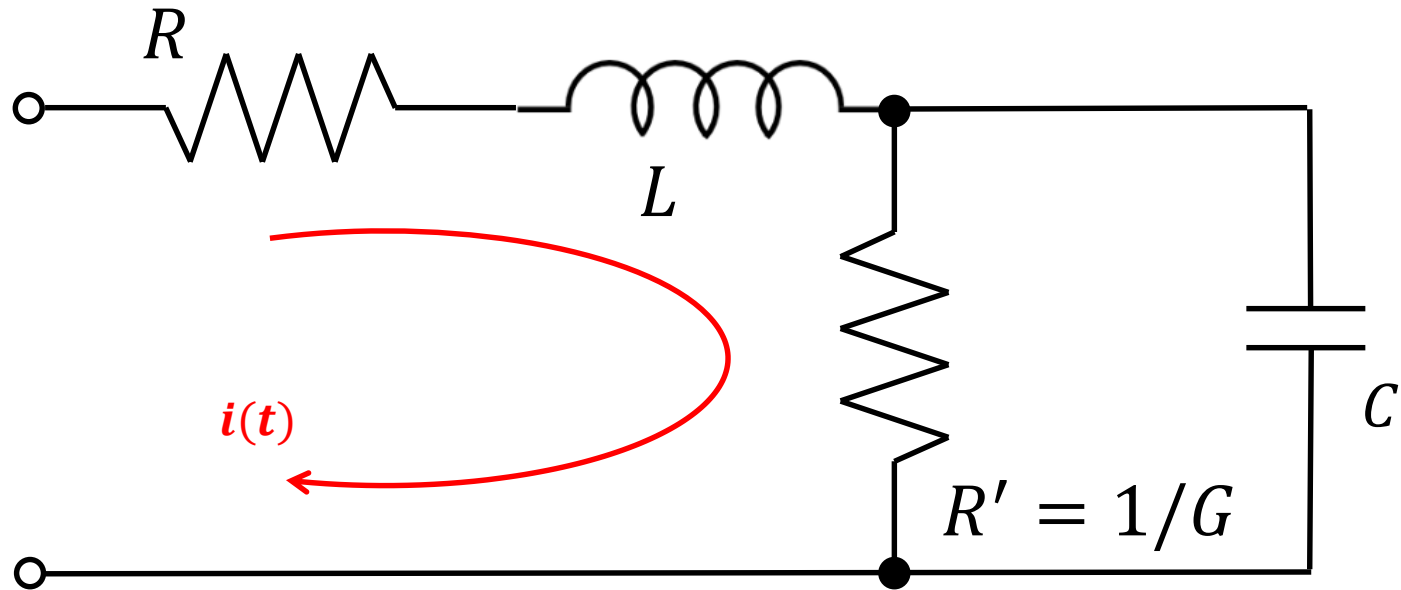

- Total equivalent impedance:

$$Z = R + j\omega L + (G + j\omega C)^{-1}$$

$$= x + \frac{1}{y}$$

$$x = R + j\omega L$$

$$y = G + j\omega C$$

Transmission Lines

- Suppose we had an infinite chain of these lumped circuit elements.
- If we add one more lump, the impedance should not change:

$$Z = R + j\omega L + \left(G + j\omega C + \frac{1}{Z} \right)^{-1}$$

$$= x + \left(y + \frac{1}{Z} \right)^{-1}$$

$$Z = x + \sqrt{\frac{x^2}{4} + \frac{x}{y}}$$

Transmission Lines

- Now suppose that each lump was split into n smaller lumps

$$\left. \begin{array}{l} R \rightarrow R/n \\ L \rightarrow L/n \end{array} \right\} x \rightarrow x/n$$
$$\left. \begin{array}{l} G \rightarrow G/n \\ C \rightarrow C/n \end{array} \right\} y \rightarrow y/n$$

$$Z = \frac{x}{n} + \sqrt{\frac{x^2}{4n^2} + \frac{x/n}{y/n}}$$

$$\lim_{n \rightarrow \infty} Z = \sqrt{\frac{x}{y}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$


Transmission Lines

- At high frequencies, $\omega L \gg R$ and $\omega C \gg G$

$$Z \rightarrow \sqrt{\frac{L'}{C'}}$$

- Inductance per unit length: L'
- Capacitance per unit length: C'
- Resistance per unit length: R'
- Conductance per unit length: $G' \approx 0$

Transmission Lines

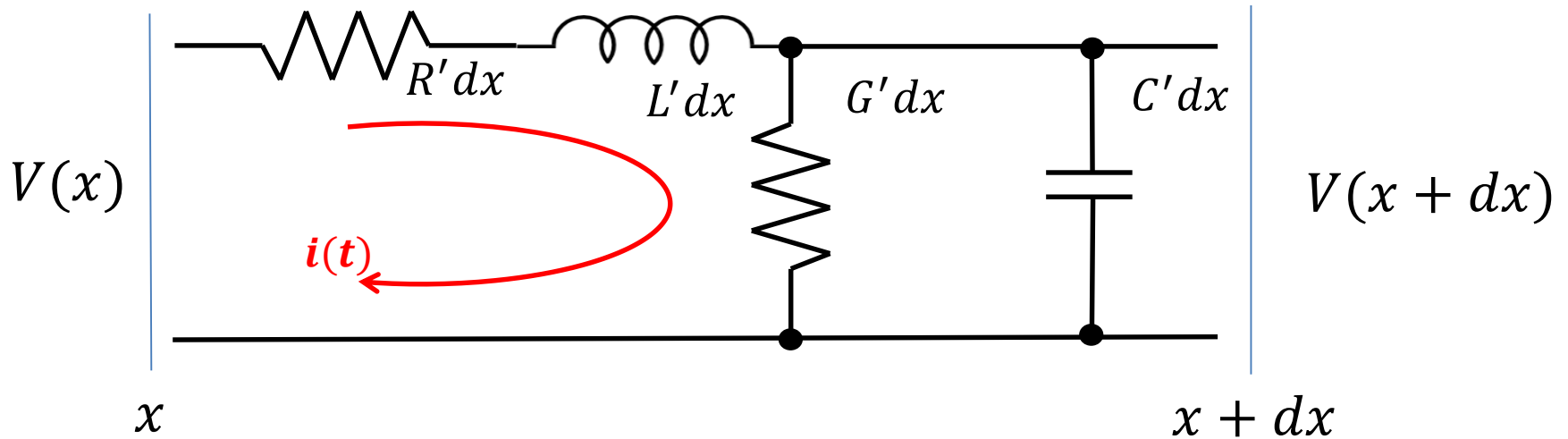


$$I(x+dx) = I(x) - V(x)Y(x)$$

where

$$Y(x) = (G' + j\omega C')dx$$

$$\frac{\partial I}{\partial x} = \frac{I(x+dx) - I(x)}{dx} = -(G' + j\omega C')V(x)$$

Transmission Lines

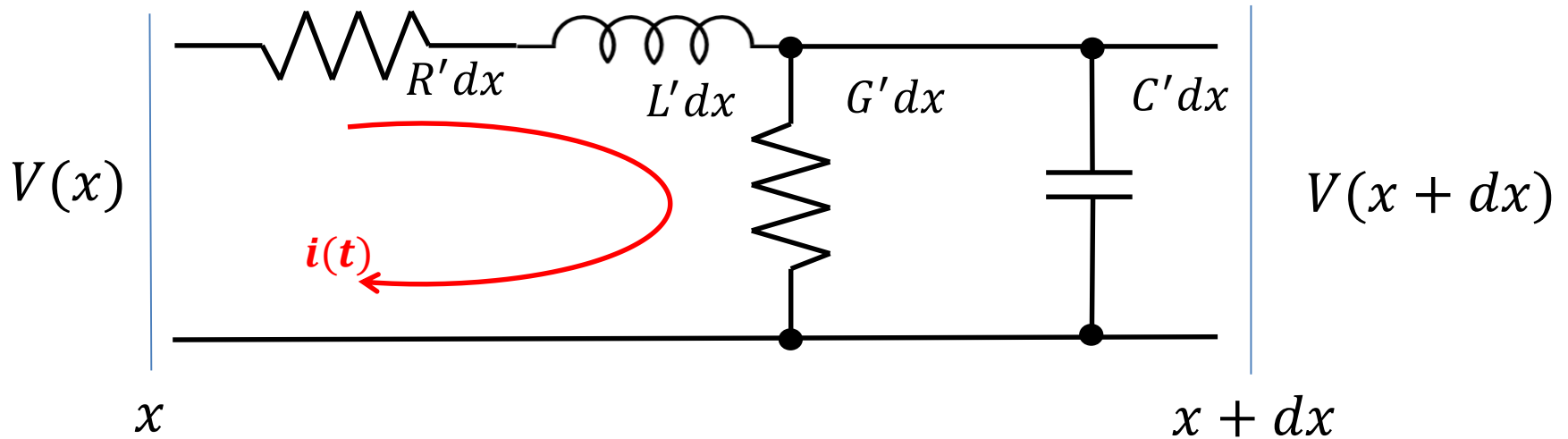

$$V(x + dx) = V(x) - I(x)X(x)$$

where

$$X(x) = (R' + j\omega L')dx$$

$$\frac{\partial V}{\partial x} = \frac{V(x + dx) - V(x)}{dx} = -(R' + j\omega L')I(x)$$

Transmission Lines

$$\frac{\partial^2 V}{\partial x^2} - \gamma^2 V(x) = 0$$

$$\begin{aligned}\gamma &= \sqrt{(R' + j\omega L')(G' + j\omega C')} \\ &= \alpha + j\beta \\ \beta &\approx \omega\sqrt{L'C'}\end{aligned}$$

$$V(x) = V_1 e^{\gamma x} + V_2 e^{-\gamma x}$$

Transmission Lines

- Time dependence:

$$V(x, t) = V_1 e^{\alpha x} e^{j(\omega t + \beta x)} + V_2 e^{-\alpha x} e^{j(\omega t - \beta x)}$$


- Speed of wave propagation:

$$\omega t - \beta x = \text{const.}$$

$$\omega - \beta \frac{dx}{dt} = 0$$

$$\frac{dx}{dt} = v = \frac{\omega}{\beta} \approx \frac{1}{\sqrt{L' C'}}$$

What are L' and C' in practice?

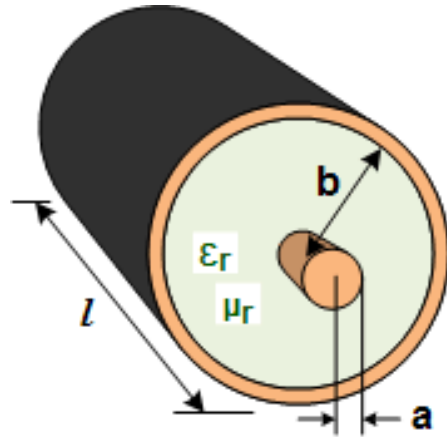

Maxwell's equation:

$$\nabla \cdot \mathbf{E} = \frac{\rho}{\epsilon_0}$$
$$\oint_S \mathbf{E} \cdot d\mathbf{a} = \frac{Q}{\epsilon_0}$$
$$E(r) = \frac{Q}{2\pi\epsilon_0 l} \cdot \frac{1}{r}$$

What are L' and C' in practice?

$$V(r) = \int_a^b \mathbf{E} \cdot d\mathbf{r} = \frac{Q}{2\pi\epsilon_0 l} \log \frac{b}{a}$$

The charge is determined by the capacitance:

$$Q = CV$$
$$C = \frac{2\pi\epsilon_0 l}{\log b/a}$$

If the space between the conductors was filled with a dielectric material then $\epsilon_0 \rightarrow \epsilon = \epsilon_0\epsilon_r$

Capacitance per unit length:

$$C' = \frac{2\pi\epsilon_0\epsilon_r}{\log b/a}$$

What are L' and C' in practice?

- Similarly, the inductance per unit length is

$$L' = \frac{\mu_0}{2\pi} \log \frac{b}{a}$$

- Characteristic impedance of a coaxial cable:

$$\begin{aligned} Z_0 &= \sqrt{\frac{L'}{C'}} = \frac{1}{2\pi} \sqrt{\frac{\mu_0}{\epsilon_0} \frac{\log b/a}{\sqrt{\epsilon_r}}} \\ &= (59.97 \, \Omega) \frac{\log b/a}{\sqrt{\epsilon_r}} \end{aligned}$$

What are L' and C' in practice?

- Speed of signal propagation:

$$v = \frac{1}{\sqrt{L'C'}} = \frac{1}{\sqrt{\epsilon_0\mu_0}} = c$$

- If a dielectric is used, then


$$v = \frac{c}{\sqrt{\epsilon_r}} < c$$

- A common dielectric material is polyethylene (P.E.) which has $\epsilon_r = 2.25 \Rightarrow v \approx \frac{2}{3}c = 20 \text{ cm/ns}$
- Printed circuit boards use FR4/epoxy which has $\epsilon_r \approx 4.2 - 4.5 \Rightarrow v \approx \frac{1}{2}c = 15 \text{ cm/ns}$

Coaxial Cables

25 ¢/Foot

20 ¢/Foot

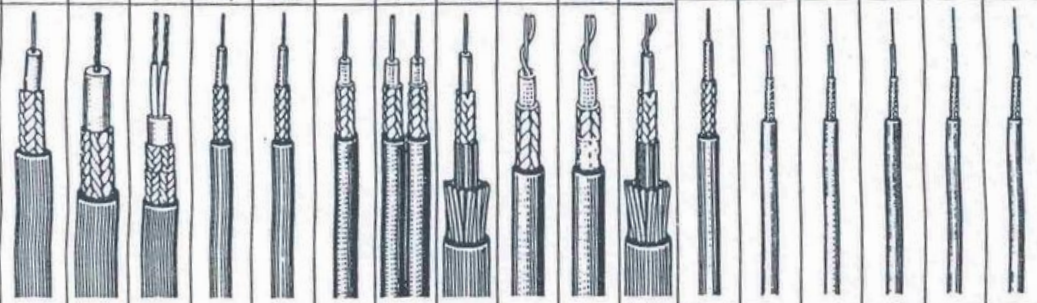TRANSRADIO PART NO.	Q 98100	Q 98101	Q 98102	Q 98103	Q 98104	Q 98105	Q 98137	Q 98139	Q 98106	Q 98107	Q 98141	Q 98111	Q 98112	Q 98113	Q 98114	Q 98115	Q 98116	
RG TYPE	6A/U	11A/U	22B/U	58 C/U Grey	58 C/U Black	59B/U	59 B/U Twin	59 B/U Armoured	62 A/U	62 A/U Outdoor	62A/U Armoured	142B/U	174U	178B/U	179B/U	180B/U	188A/U	
																		
NOM. IMPEDANCE OHMS	75	75	93	50	50	75	75	75	93	93	93	50	50	50	75	95	50	
NOM. CAPACITANCE pF/m	67.5	67.5	52	101	101	67.6	67.6	67.6	44.3	44.3	44.3	96.4	101.0	96.4	50.5	50.5	96.4	
ATTENUATION db/100M	10MHZ	3.0	1.8	2.8	5.0	5.0	3.5	3.5	3.5	2.9	2.9	2.9	5.0	10	14	8.5	6.0	12
	50MHZ	7.0	4.5	6.2	12	12	8.0	8.0	8.0	6.5	6.5	6.5	12.0	24	32	20	14	18
	100MHZ	10.0	6.5	9.0	16	16	12	12	12	9.2	9.2	9.2	16	34	46	28	21	37.7
	800MHZ	28	22	—	50	50	34	34	34	26	26	26	48	130	150	94	70	90
CONDUCTOR: Material	Cu W SOLID	TiC 7/0.40	2xCu 7/0.40	Cu 19/0.18	Cu 19/0.18	Cu W SOLID	Cu W SOLID	Cu W SOLID	Cu W SOLID	Cu W SOLID	Cu W SOLID	Si,Cu,W SOLID	Cu,W 7/0.16	Si,Cu,W 7/0.10	Si,Cu,W 7/0.10	Si,Cu,W 7/0.10	Si,Cu,W 7/0.17	
DIA. MM.	0.7	1.2	1.2	0.9	0.9	0.6	0.6	0.6	0.64	0.64	0.64	0.99	0.48	0.305	0.305	0.305	0.50	
DIELECTRIC: Material	P.E.	P.E.	P.E.	P.E.	P.E.	P.E.	P.E.	P.E.	PE+TH	PE+TH	PE+TH	PTFE	PE	PTFE	PTFE	PTFE	PTFE	
O/D(NOM.)	4.6	7.2	7.3	3.0	3.0	3.7	3.7	3.7	3.7	3.7	3.7	3.0	1.5	0.86	1.6	2.6	1.5	
SCREEN: Material	1st	SiCu	Cu	TiC	TiC	TiC	Cu	Cu	Cu	Cu	Cu	Si,Cu	TiC	Si,Cu	Si,Cu	Si,Cu	Si,Cu	
2nd	SiCu	—	TiC	—	—	—	—	—	—	—	—	Si,Cu	—	—	—	—	—	
SHEATH: Material	PVC	PVC	PVC	PVC	PVC	PVC	PVC	PVC	PVC	PE	PVC	FEP	PVC	FEP	FEP	FEP	PTFE	
O/D(NOM.)	8.4	10.3	10.3	4.9	4.9	6.2	6.2	—	6.2	6.2	—	4.9	2.54	1.9	2.54	3.7	2.8	
Weight: Approx KG/KM	119	143	180	43	43	48	96	—	56	57	—	74	11.8	7.4	14.8	28.1	16.2	
MIN. BENDING RADIUS	102	114	51	51	51	51	—	—	51	116	—	51	25.4	25.4	25.4	50.8	25.4	

Coaxial Cable Properties

- For typical coaxial cable, eg. RG-58

$$C' = 26.4 \text{ pF/foot} = 86.6 \text{ pF/m}$$

$$L' = 0.070 \text{ } \mu\text{H/foot} = 0.230 \text{ } \mu\text{H/m}$$

$$R' = 17 \text{ } \Omega/\text{foot} = 0.056 \text{ } \Omega/\text{m}$$

- At what frequency does $|\omega L'| \approx R'$?

$$\omega = \frac{0.056 \text{ } \Omega/\text{m}}{0.230 \text{ } \mu\text{H/m}} \sim 250 \text{ kHz}$$

- At 1 MHz, $\omega L'$ is four times larger than R'
- At 10 MHz, it is reasonable to ignore R'

Coaxial Cable Properties

- Recall that

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')} = \alpha + j\beta$$

- At low frequencies, say 10 kHz,

$$\gamma \approx \sqrt{j\omega R' C'} = (5.5 \times 10^{-4} \text{ m}^{-1}) \frac{(1 + j)}{\sqrt{2}}$$

$$\alpha = 3.89 \times 10^{-4} \text{ m}^{-1}$$

- For example, when $\ell = 100 \text{ m}$, $A' = Ae^{-\alpha\ell}$

$$\begin{aligned} G &= 20 \log_{10} \frac{A'}{A} = 20 \log_{10} e^{-\alpha\ell} \\ &= 20 (-\alpha\ell) \log_{10} e \\ &= 0.34 \text{ dB} \end{aligned}$$

Coaxial Cable Properties

- At medium frequencies, say 100 MHz,

$$\begin{aligned}\gamma &= \sqrt{(j\omega L')(j\omega C')} \\ &= j\omega\sqrt{L'C'}\end{aligned}$$

- Does this mean that $\alpha \rightarrow 0$ as $\omega \rightarrow \infty$?
- Skin effect results in resistive losses
- At high frequencies, the electric and magnetic fields penetrate conductors with an exponential falloff:

$$\begin{aligned}E &= E_0 e^{-x/\delta} \\ \delta &= \sqrt{\frac{2}{\omega\mu_0\sigma}}\end{aligned}$$

Coaxial Cable Properties

- At high frequencies, the resistance is mostly due to the skin effect:

$$R' \sim \frac{1}{p} \sqrt{\frac{\omega}{\sigma}}$$

where p is the perimeter of the conductor.


- Impedance,

$$Z(\omega) \sim \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\lim_{\omega \rightarrow \infty} Z(\omega) = \sqrt{\frac{L'}{C'}}$$

- However, $\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$
$$\lim_{\omega \rightarrow \infty} \gamma(\omega) = j\omega \sqrt{L' C'} + \alpha(\omega)$$
$$\alpha(\omega) \approx \sqrt{\omega}$$


Other Transmission Line Configurations

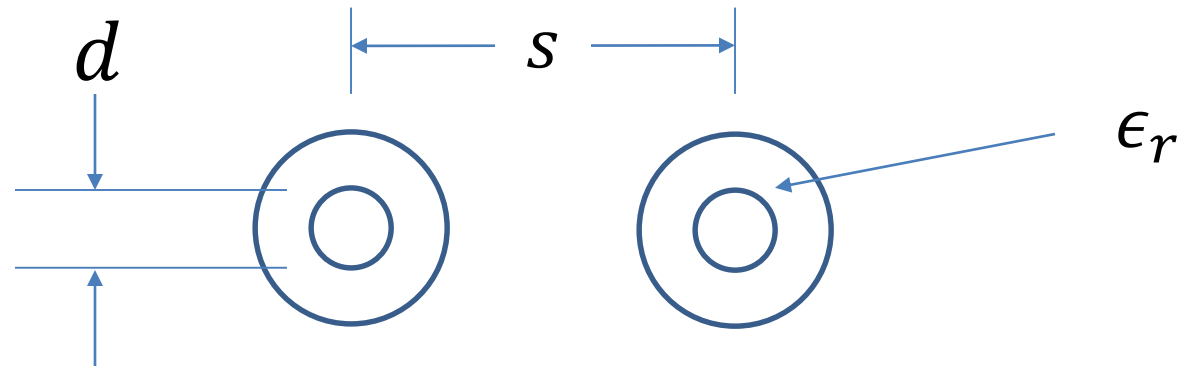

$$Z \approx \frac{120 \, \Omega}{\sqrt{\epsilon_r}} \log \left(\frac{2s}{d} \right)$$

- This is called “twisted pair” cable
eg. CAT4/5 Ethernet cable


Other Transmission Line Configurations

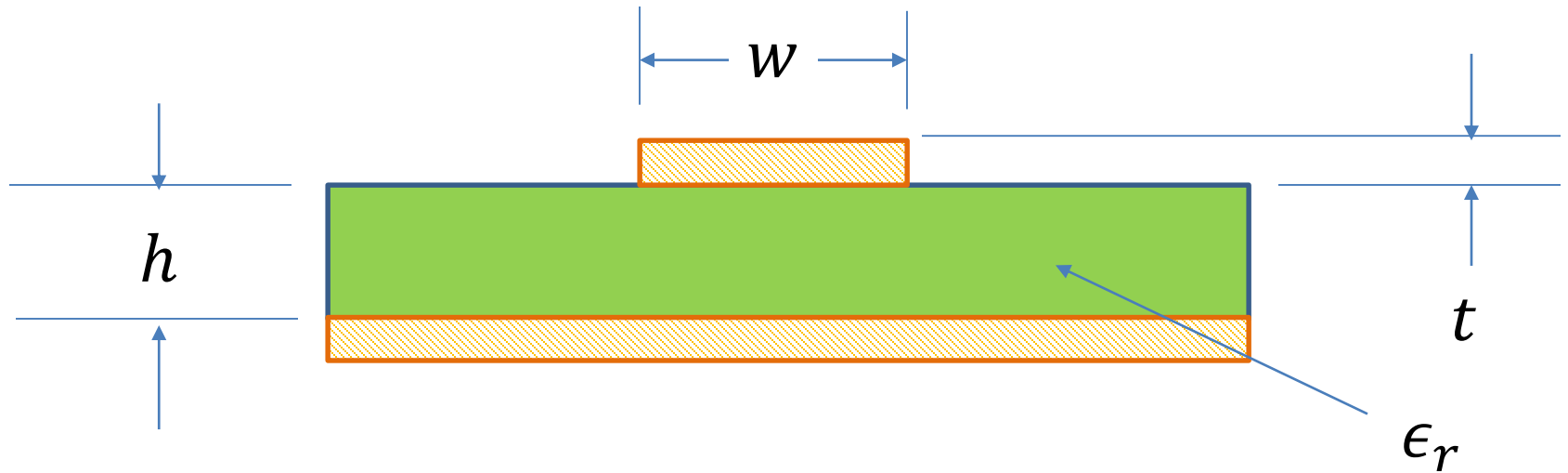

$$Z \approx \frac{87 \, \Omega}{\sqrt{1.41 + \epsilon_r}} \log \left(\frac{5.98 \, h}{t + 0.8 \, w} \right)$$

ϵ_r is typically about 4.2-4.5
“microstrip” transmission line

Other Transmission Line Configurations

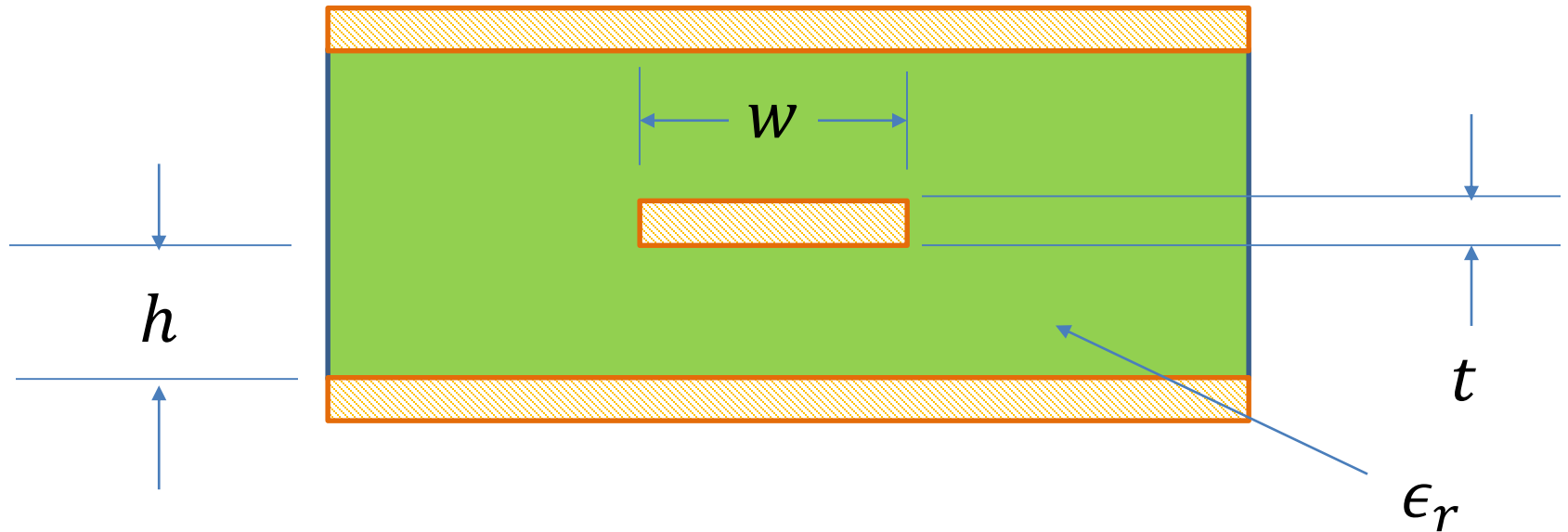

$$Z \approx \frac{60 \, \Omega}{\sqrt{\epsilon_r}} \log \left(1.9 \frac{2h + t}{0.8 w + t} \right)$$

Embedded microstrip

Transmission Lines

- When do we need to think of a conductor as a transmission line and not just a wire?
- Generally, when the wavelength is shorter than the length of the transmission line
- Example:


A signal with a fast rise-time of 200 ps:

$$\lambda = v \Delta t = \frac{c}{\sqrt{\epsilon_r}} \Delta t = 2.8 \text{ cm}$$

A slower signal with $\Delta t \sim 1 \text{ ns}$ over 10 meters of cable:

$$\lambda = v \Delta t = 19 \text{ cm} \ll 10 \text{ m}$$

Transmission Lines in Circuits

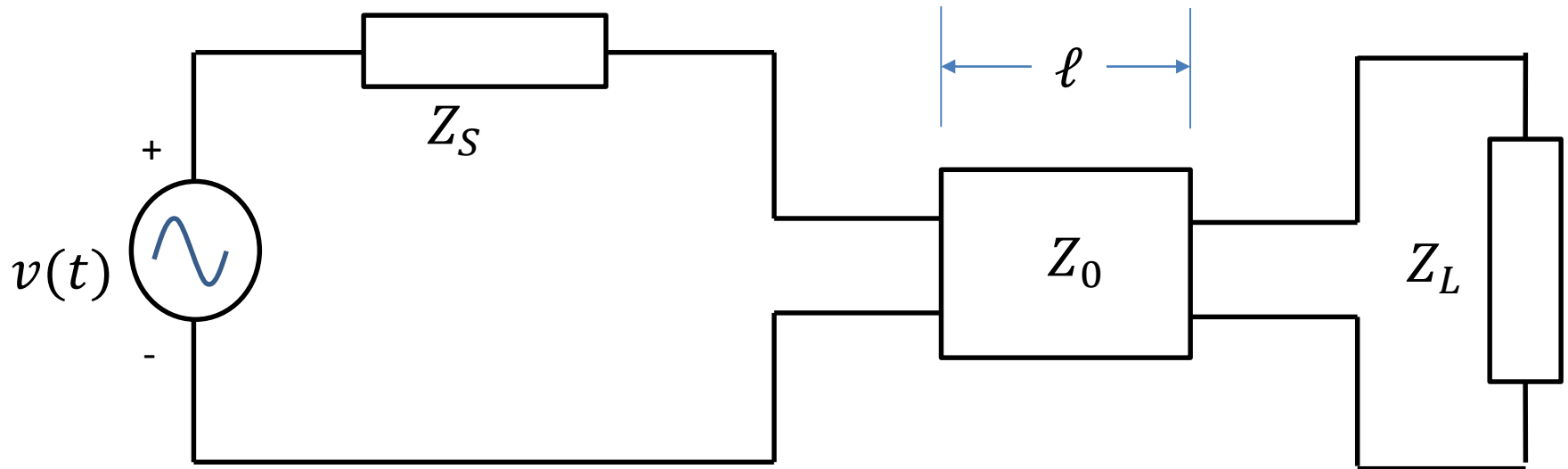

- Ideal voltage source: $v(t) = V_0 e^{j\omega t}$
- Source impedance: Z_S
- Transmission line impedance: Z_0
- Load impedance: Z_L

Transmission Lines in Circuits

- The general solution to the differential equation in the transmission line:

$$I(x) = Ae^{\gamma x} + Be^{-\gamma x}$$

- Voltage and current in the transmission line are related by

$$\begin{aligned} V(x) &= -\frac{1}{G' + j\omega C'} \frac{\partial I}{\partial x} \\ &= -\frac{\gamma}{G' + j\omega C'} (Ae^{\gamma x} - Be^{-\gamma x}) \\ &= -Z_0 (Ae^{\gamma x} - Be^{-\gamma x}) \end{aligned}$$

- The constants A and B must make the solution in the transmission line match the boundary conditions at the ends.

Transmission Lines in Circuits

- At the source end, $x = 0$

$$V_0 - I(0)Z_S - V(0) = 0$$

$$I(0) = A + B$$

$$V(0) = -Z_0(A - B)$$

$$V_0 - Z_S(A + B) + Z_0(A - B) = 0$$

- At the load end, $x = \ell$

$$V(\ell) - I(\ell)Z_L = 0$$

$$-Z_0(Ae^{\gamma\ell} - Be^{-\gamma\ell}) - Z_L(Ae^{\gamma\ell} + Be^{-\gamma\ell}) = 0$$

- Two equations in two unknowns...

Transmission Lines in Circuits

$$A = \frac{V_0 \Gamma_L e^{-2\gamma \ell}}{(Z_S + Z_0)(1 - \Gamma_S \Gamma_L e^{-2\gamma \ell})}$$
$$B = \frac{V_0}{(Z_S + Z_0)(1 - \Gamma_S \Gamma_L e^{-2\gamma \ell})}$$

$$\left. \begin{aligned} \Gamma_S &= \frac{Z_S - Z_0}{Z_S + Z_0} \\ \Gamma_L &= \frac{Z_L - Z_0}{Z_L + Z_0} \end{aligned} \right\} \begin{array}{l} \text{reflection} \\ \text{coefficients} \end{array}$$

Interpretation

- If V_0 produces a wave travelling to the right, the current induced by this wave in the transmission line is

$$I_0 = \frac{V_0}{Z_0 + Z_S}$$

- This wave propagates down to the end of the transmission line.
- At the far end,

$$I'_0 = \frac{V_0}{Z_0 + Z_S} e^{-\gamma \ell}$$

Interpretation

- Some energy is dissipated in the load Z_L but some is reflected back towards the source.
- Reflected component:

$$I'_1 = I'_0 \Gamma_L = \frac{V_0}{Z_0 + Z_S} \Gamma_L e^{-\gamma \ell}$$

- The reflected wave propagates back towards the source.
- When it arrives,

$$I_1 = I'_1 e^{-\gamma \ell} = \frac{V_0}{Z_0 + Z_S} \Gamma_L e^{-2\gamma \ell}$$

Interpretation

- When the reflected wave arrives back at the source, some energy is dissipated in the source impedance, but some is reflected back towards the load.

$$I_2 = I_1 \Gamma_S = \frac{V_0}{Z_0 + Z_S} \Gamma_S \Gamma_L e^{-2\gamma \ell}$$

- This process continues, *ad infinitum*

Interpretation

- Adding up all the components gives:
 - Current flowing in the +x direction:

$$I_+(x) = \frac{V_0}{Z_0 + Z_S} \frac{e^{-\gamma x}}{1 - \Gamma_S \Gamma_L e^{-2\gamma \ell}}$$

- Current flowing in the -x direction:

$$I_-(x) = \frac{V_0}{Z_0 + Z_S} \frac{\Gamma_L e^{-2\gamma \ell} e^{\gamma x}}{1 - \Gamma_S \Gamma_L e^{-2\gamma \ell}}$$

- If $Z_L = Z_0$ then no energy is reflected from the load.
- If $Z_S = Z_0$ then no energy is reflected from the source.