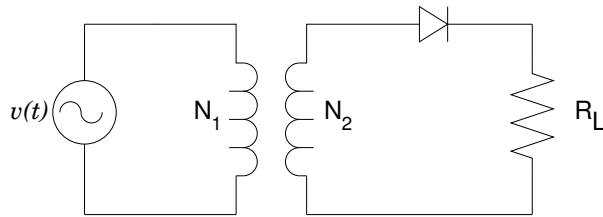


## Physics 536 - Assignment #4


1. In the following, treat the diodes as idealized devices that allow current to flow in one direction only, ignoring any voltage drop across them.

(a) Consider a transformer being driven by an AC voltage source with RMS amplitude  $V_0$ . Calculate the peak amplitude of this voltage source and sketch its waveform.

(b) If the transformer in the circuit shown below has a turns ratio of  $n = N_2/N_1$ , sketch the waveform of the voltage across the load  $R_L$ , comparing it with the waveform in (a). Calculate the RMS voltage,  $V_L$ , across the load.



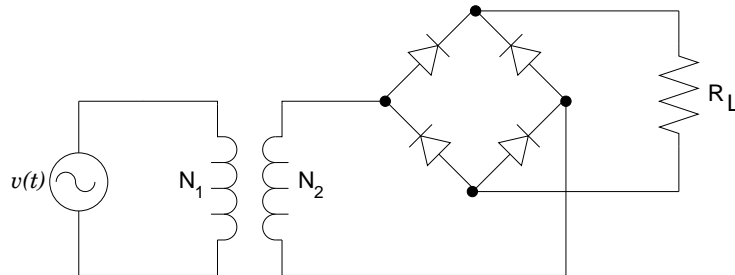(c) The diodes in the circuit shown below are in a configuration referred to as a bridge rectifier. Sketch the waveform of the voltage across the load,  $R_L$ , and calculate the RMS voltage of this waveform.



(d) Suppose the transformer has a center tap that is held at ground potential and is connected in the configuration shown below. Sketch the waveform for the voltage across  $R_L$  in this configuration and calculate RMS voltage.

